

CMOS Inverter


Copyright (c) 2011-2016 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.

Operation Modes

 

nLIN


$$I_{ds} \propto V_{ds}$$

nSAT


$$I_{ds} = \text{const}$$

nOFF


$$I_{ds} = 0$$

 



Operation Modes and Bias Voltages

 


$I_{ds} \propto V_{ds}$
nLIN

 

$I_{ds} = c$
nSAT

  


$I_{ds} = 0$
nOFF

 


$I_{ds} = 0$
nOFF

nMOS Bias

<https://en.wikipedia.org/wiki/CMOS>

 

 
N-channel MOS capacitor: (a) no charge, (b) charged.




N-channel MOSFET (enhancement type): (a) 0 V gate bias, (b) positive gate bias.

pMOS Bias

<https://en.wikipedia.org/wiki/CMOS>

 


 
N-channel MOS capacitor: (a) no charge, (b) charged.





N-channel MOSFET (enhancement type): (a) 0 V gate bias, (b) positive gate bias.

Pinch-Off

<https://en.wikipedia.org/wiki/CMOS>

  




nLIN

  

Most of Vds

To prevent forward
biased junction

Notation

   

Current
Notation

$$V_{in} = V_{GSp} + V_{dd} = V_{GSn}$$

$$V_{out} = V_{DSp} + V_{dd} = V_{DSn}$$


<https://en.wikipedia.org/wiki/CMOS>

Input Voltage


$$V_{GSp} = V_{Gp} - V_{Sp}$$
$$= V_{in} - V_{dd}$$

$$V_{in} = V_{GSp} + V_{dd}$$
$$= V_{GSn}$$
 
$$V_{GSn} = V_{Gn} - V_{Sn}$$
$$= V_{in} - V_{ss}$$





 
$$V_{SGp} = V_{Sp} - V_{Gp}$$
$$= V_{dd} - V_{in}$$



<https://en.wikipedia.org/wiki/CMOS>

Output Voltage

<https://en.wikipedia.org/wiki/CMOS>

   


$$\begin{aligned}V_Q &= V_{DSp} + V_{Sp} \\&= V_{DSp} + V_{dd}\end{aligned}$$

$$\begin{aligned}V_Q &= V_{DSn} + V_s \\&= V_{DSn} + V_{ss} \\&= V_{DSn}\end{aligned}$$

$$V_{out} = V_{DSp} + V_{dd} = V_{DSn}$$


Characteristic Curves

<https://en.wikipedia.org/wiki/CMOS>

 





Flip up pMOS curves

<https://en.wikipedia.org/wiki/CMOS>

 

Shift right pMOS curves

<https://en.wikipedia.org/wiki/CMOS>

  
 
 


Overlay pMOS & nMOS curves





<https://en.wikipedia.org/wiki/CMOS>

$$V_{in} = V_{GSp} + V_{dd} = V_{GSn}$$

$$V_{out} = V_{DSP} + V_{dd} = V_{DSn}$$

   


    [Ids-Vgs], [Ids-Vds] Characteristic Curves




$$V_{in} = V_{GSp} + V_{dd} = V_{GSn} \quad \star$$

$$V_{out} = V_{DSP} + V_{dd} = V_{DSn}$$






 


V_{in}	0	1	2	3	4	5
V_{GSp}	-5	-4	-3	-2	-1	0
V_{GSn}	0	1	2	3	4	5




→

 





Intersect Points

      

  
 
Intersect Points in [Ids-Vgs], [Ids-Vds] Curves







Mode Changes

    


Resistance and Mode Changes

  


Abruptly Changing Region

    


Input Switching $1 \rightarrow 0$

 



Input Switching $0 \rightarrow 1$

 

$[V_{IL}, V_{IH}]$ & $[V_{OL}, V_{OH}]$

 

Noise Margin

  

Simple Transistor Model

<https://en.wikipedia.org/wiki/CMOS>

Cutoff, subthreshold, or weak-inversion mode

When $V_{GS} < V_t$:

$$I_d = 0$$

Triode mode or linear region (the ohmic mode)




When $V_{GS} > V_t$ and $V_{DS} < (V_{GS} - V_t)$

$$I_d = k' \frac{W}{L} \left[(v_{gs} - v_t) v_{ds} - \frac{1}{2} v_{ds}^2 \right]$$

Saturation or active mode

When $V_{GS} > V_t$ and $V_{DS} \geq (V_{GS} - V_t)$
   
$$I_d = \frac{1}{2} k' \frac{W}{L} (v_{gs} - v_t)^2$$




Linear and Saturation Models

<https://en.wikipedia.org/wiki/CMOS>

linear region

When $V_{GS} > V_t$ and $V_{DS} < (V_{GS} - V_t)$

 
$$I_d = k' \frac{W}{L} \left[(v_{gs} - v_t) v_{ds} - \frac{1}{2} v_{ds}^2 \right]$$



Saturation or active mode

When $V_{GS} > V_t$ and $V_{DS} \geq (V_{GS} - V_t)$
 
$$I_d = \frac{1}{2} k' \frac{W}{L} (v_{gs} - v_t)^2$$



Bias Conditions

<https://en.wikipedia.org/wiki/CMOS>

Cutoff

$$V_{GS} < V_t$$

Linear region


$$V_{GS} > V_t$$

$$V_{DS} < (V_{GS} - V_t)$$

Saturation

$$V_{GS} > V_t$$

$$V_{DS} > (V_{GS} - V_t)$$

 

Characteristic Curve

References

- [1] <http://en.wikipedia.org/>
- [2] <http://www.allaboutcircuits.com/>
- [3] W. Wolf, "Modern VLSI Design : Systems on Silicon"
- [4] N. Weste, D. Harris, "CMOS VLSI Design: A Circuits and Systems Perspective"
- [5] J. P. Uyemura, "Introduction to VLSI Circuits and Systems"
- [6] https://en.wikiversity.org/wiki/The_necessities_in_SOC_Design
- [7] https://en.wikiversity.org/wiki/The_necessities_in_Digital_Design
- [8] https://en.wikiversity.org/wiki/The_necessities_in_Computer_Design
- [9] https://en.wikiversity.org/wiki/The_necessities_in_Computer_Architecture
- [10] https://en.wikiversity.org/wiki/The_necessities_in_Computer_Organization
- [11] https://en.wikiversity.org/wiki/Verilog_programming_in_plain_view