

BJT Amplifier

Common Base Amp (H.13)

20170630

Copyright (c) 2016 - 2017 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the
GNU Free Documentation License, Version 1.2 or any later version published by the Free Software
Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of
the license is included in the section entitled "GNU Free Documentation License".

References

Based

[1] Floyd, Electronic Devices 7th ed

[2] Cook,

[2] en.wikipedia.org

Common Base


Common Emitter

Common Collector

Z_{in}	CB : low $r_e \parallel R_E \approx r_e$	CE : med $R_1 \parallel R_2 \parallel \beta r_e$	CC : high $R_1 \parallel R_2 \parallel \beta(r_e + R_E)$
Z_{out}	CB : high R_C	CE : med R_C	CC : low $(r_e + \frac{R_s}{\beta}) \parallel R_E = \frac{R_s}{\beta} \parallel R_E$
A_v	CB : high $\frac{R_C}{r_e}, \frac{R_C \parallel R_L}{r_e}$	CE : med $\frac{R_C}{r_e}, \frac{R_C \parallel R_L}{r_e}$	CC : unity $\frac{R_E}{(r_e + R_E)} \approx 1$
A_i	CB : unity	CE : med	CC : high


VDB

Common Base Configuration

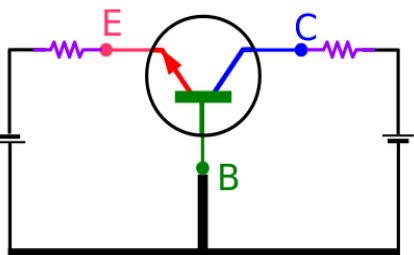


Common Base

DC Bias

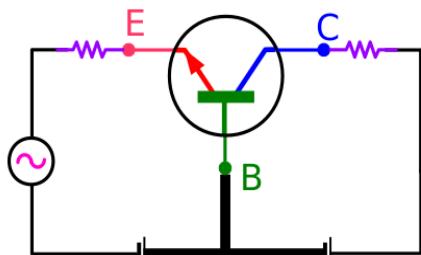




Common Base


DC Bias + AC Signal


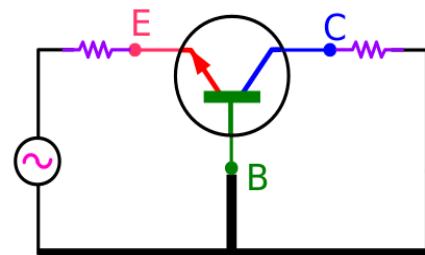


Common Base

AC Signal

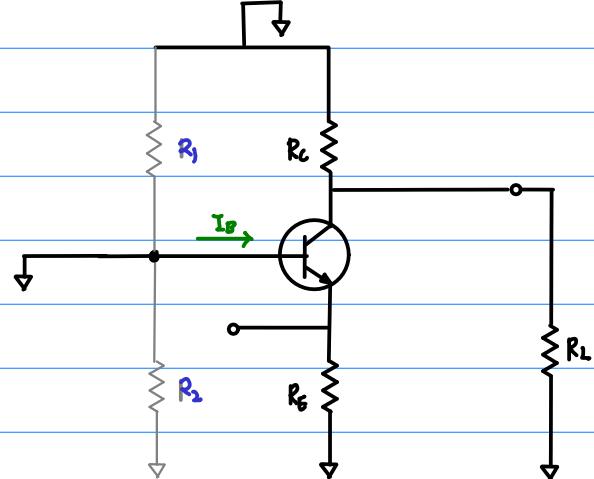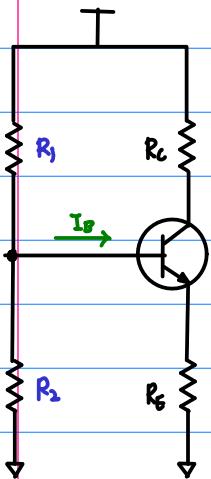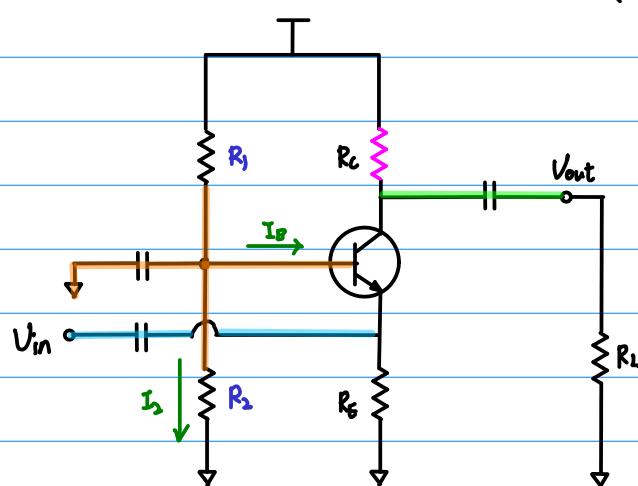

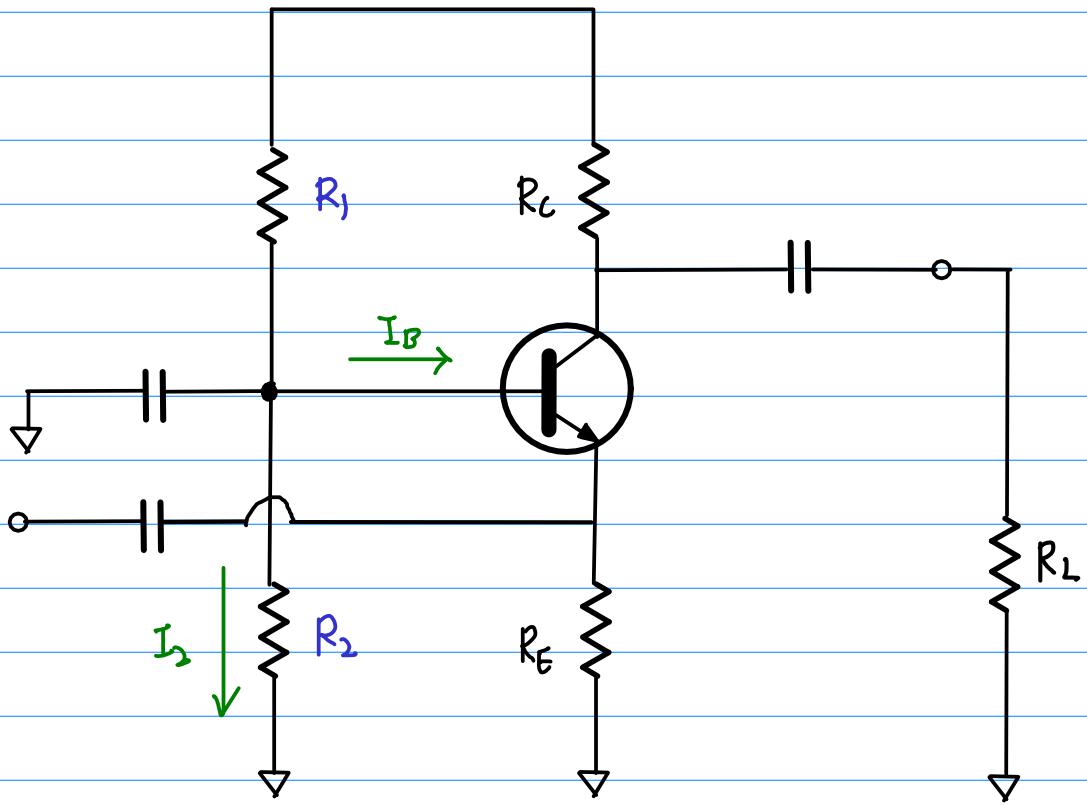

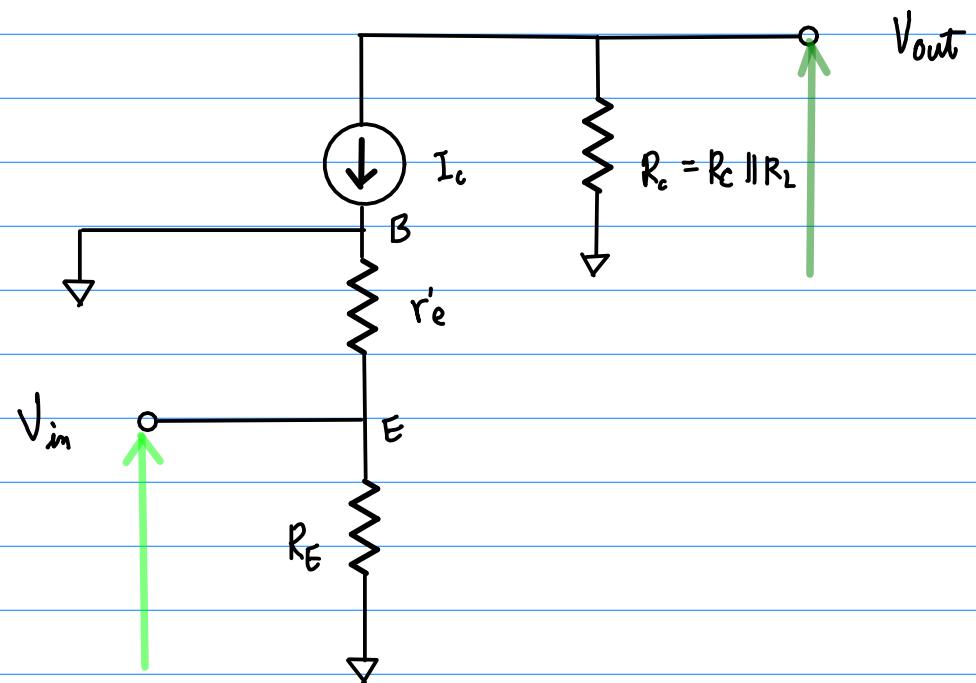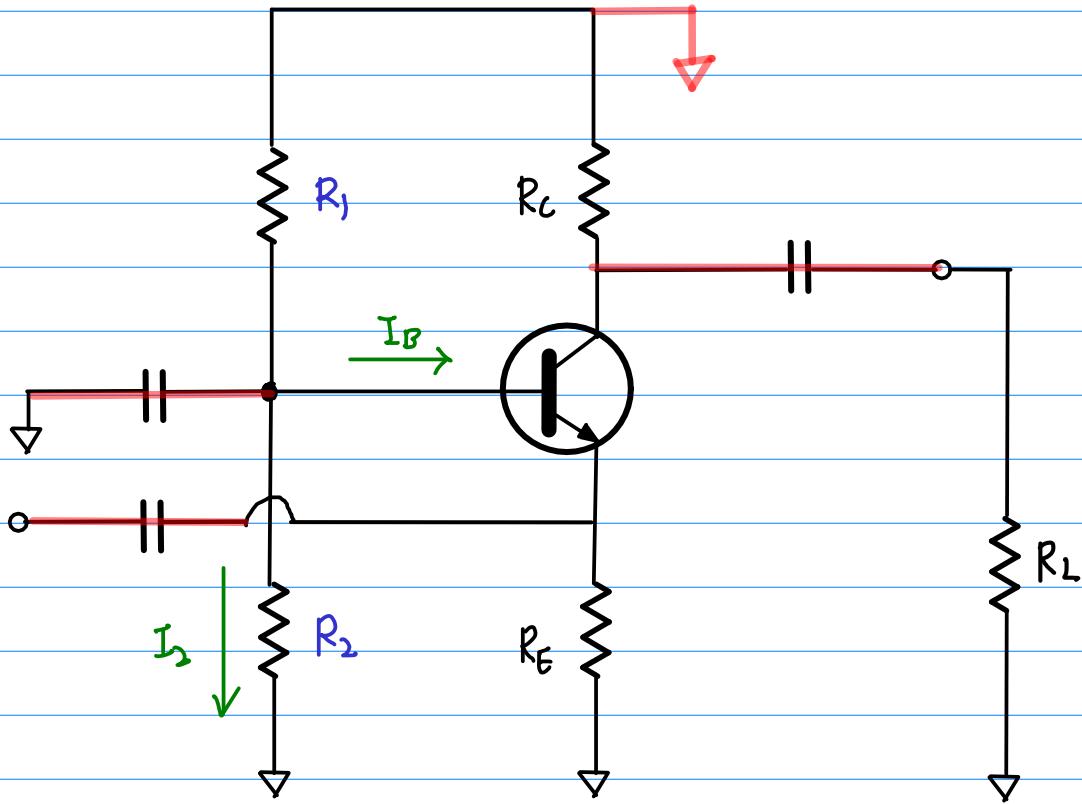

$$A_V = \frac{V_{out}}{V_{in}} = \frac{V_C}{V_E} = \frac{I_C R_C}{I_E (r'_E \parallel R_E)} \approx \frac{I_C R_C}{I_E (r'_E \parallel R_E)}$$

$$R_E \gg r'_E$$

$$A_V = \frac{R_C}{r'_E} \quad R_C = R_C \parallel R_L$$

$$R_{in(emitter)} = \frac{V_{in}}{I_{in}} = \frac{V_E}{I_E} = \frac{I_E (r'_E \parallel R_E)}{I_E}$$

$$R_E \gg r'_E$$

$$R_{in(emitter)} \approx r'_E$$

$$R_{out} \approx R_C \quad r'_C \parallel R_C \quad r'_C \gg R_C$$

$$I_C \approx I_E$$

$$A_i = 1$$

