

# BJT Overview Amplifiers (H.2)

20170420

Copyright (c) 2016 - 2017 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".


# References

Based

[1] Floyd, Electronic Devices 7th ed

[2] Cook,

[2] en.wikipedia.org

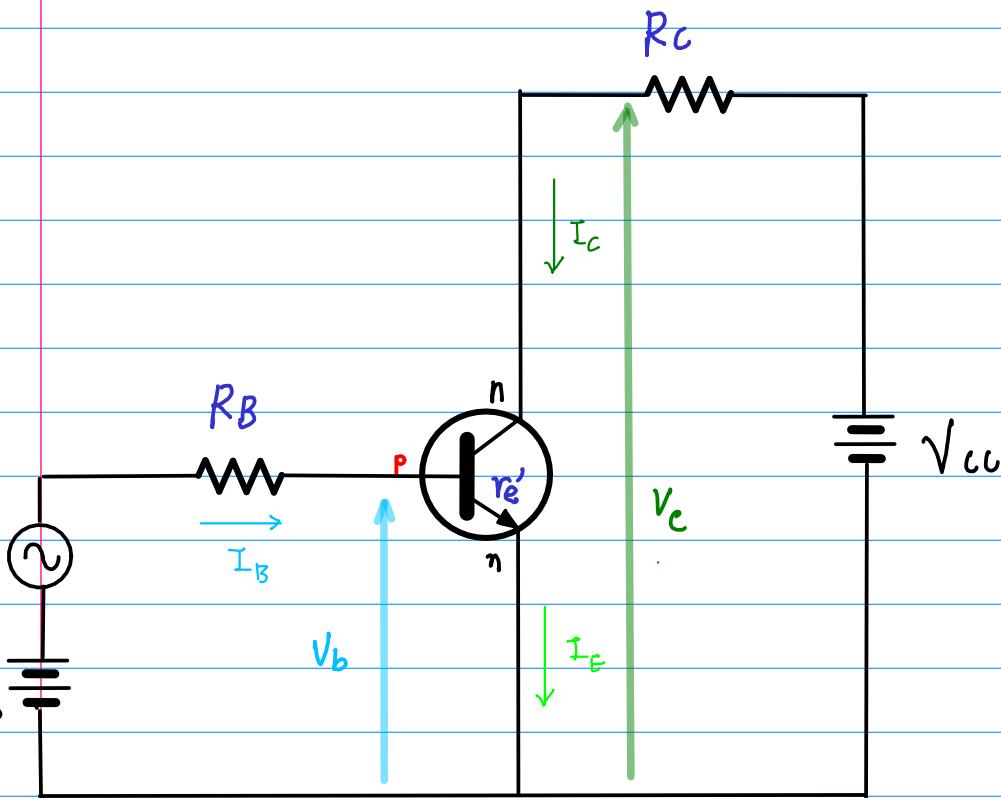


$$I_e \approx I_c = \frac{V_b}{r'_e}$$

$$V_c = I_c R_C \approx V_e$$

$$V_b = V_{in} - I_b R_B$$
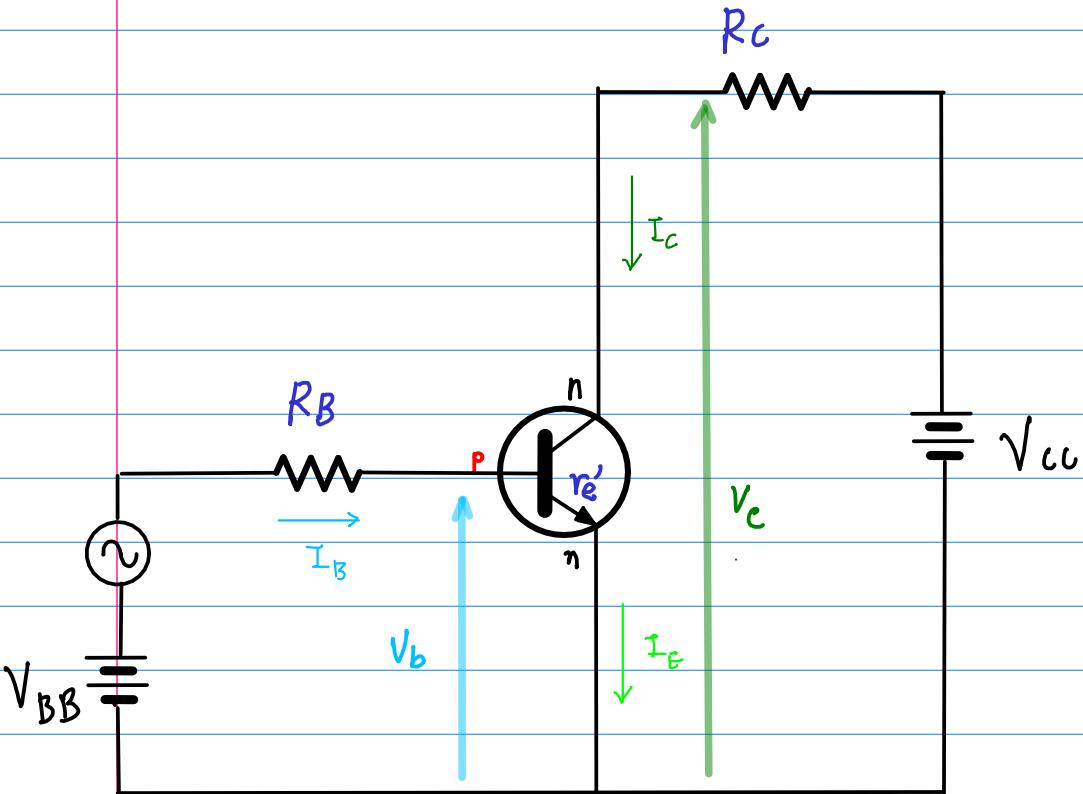
$$A_v = \frac{V_c}{V_b} \approx \frac{I_c R_C}{I_e r'_e} = \frac{R_C}{r'_e}$$



$v_b$  (mA)

$v_{BB}$

→

$v_c$  (mA)

$v_{CC}$

→