


 

 
```
*****
* Based on Technical Report 94-9 Monash University
*
* Being Modified By Young W. Lim
*
* Modified code is to be distributed under the GNU LGPL license.
*****
```



 


• • •

 

Loop Unrolled Arch

Word-Parallel Architecture

 

addsub.vhd

```

addsub : PROCESS(a,b,sel)
  VARIABLE res : VLBIT_VECTOR(n DOWNTO 0);
BEGIN
  result := zero(n DOWNTO 0);    -- needs to be initialised

  IF sel = '1' THEN
    result := add2c(a,b);
  ELSE
    result := sub2c(a,b);
  END IF;

  s <= result(n-1 downto 0);    -- discard cout
END PROCESS;

```

IEEE Standard Packages

```

add2c()
sub2c()
function add2c (v1, v2: vlbit_1d) return vlbit_1d;
function sub2c (v1, v2: vlbit_1d) return vlbit_1d;
-----
```

adder/subtractor structure

```

c(0) <= sel; -- carry in
connect: FOR i IN 0 TO n-1 GENERATE
  invert:      invf101 PORT MAP( b(i), b_bar(i) );
  mux_b_b_bar: muxf201 PORT MAP( b_bar(i), b(i), sel, b_hat(i) );
  addsub:     faf001 PORT MAP( a(i), b_hat(i), c(i), s(i), c(i+1) );
END GENERATE

```

Standard Cell library

Assume the library contains the following 6 components

```

nandf201: 2 input nand with 1x output drive
norf201: 2 input nor with 1x output drive
invf101: 1 input not gate with 1x output drive
xorf201: 2 input xor gate with 1x output drive
xnof201: 2 input xnor gate with 1x output drive
dfbf311: D-Flip Flop with D, Reset, Set, Q, QN, Clk

```

```


invf101
muxf201
faf001
-----
```

addsub

```

SUM <= A1 xor B1 xor CIN2;
CO <= (A1 and B1) or (A1 and CIN2) or (B1 and CIN2);

```

 

```

ARCHITECTURE behaviour OF adder IS
begin
    cell_i : process (xi,xs,yi,ys,zi,ai)
        VARIABLE x_res: vlbit_vector(n downto 0); -- temporary results
        VARIABLE y_res: vlbit_vector(n downto 0);
        VARIABLE z_res: vlbit_vector(k downto 0);

        begin
            x_res := zero(n downto 0); -- initialise, unless comp complains
            y_res := zero(n downto 0);
            z_res := zero(k downto 0);

            if zi(k-1) = '0' then -- z_i is positive
                x_res := add2c (xi, ys);
                y_res := sub2c (yi, xs);
                z_res := sub2c (zi, ai);
            else -- z_i is negative
                x_res := sub2c (xi, ys);
                y_res := add2c (yi, xs);
                z_res := add2c (zi, ai);
            end if;

            xip1 <= x_res (n-1 downto 0);
            yip1 <= y_res (n-1 downto 0);
            zip1 <= z_res (e-1 downto 0);
    end process;
end;

```

```

    end process;
END behavior;

```

The Rounding Unit

Formed by the interconnection of n half adders.

Adding the shifted-out bit.

inc001 components => HA (AND and XOR)

```


c(0) <= cin; -- first carry
connect: for i in 0 to n-1 generate
    addsub: inc001 port map( a(i), c(i), s(i), c(i+1) );
end generate;
-----
```

```
inc001
```

```

rounder : process (a,cin)
    VARIABLE res: vlbit_vector(n downto 0); -- temporary results
begin
    res := zero(n downto 0); -- initialise, unless comp complains
    res := addum(a,cin); -- use addum instead of add2c as it sign
                           -- extends the cin input making it -1 not +1
    s <= res (n-1 downto 0);
end process;
```

```
-----  
addum
```

 


```
shift value is not recognizable inside the generate statement.
```

```
-- Scaled a_i * 2^i values are decimal 45 53 56 57 57 57 57 57  
ai <= X"39_39_39_39_39_38_35_2D";
```

```
sh_x: xis <= shift_all(xi); -- xis, xi width?  
sh_y: yis <= shift_all(yi); -- yis, yi width?  
sh_z: zis <= shift_z(z);
```

i = iteration index

```
FUNCTION shift_all (x : vlbit_vector (n*(k-1)-1 downto 0))  
RETURN vlbit_vector IS  
  VARIABLE x_s : vlbit_vector(n*(k-1)-1 downto 0)  
    := zero(n*(k-1)-1 downto 0);  
BEGIN  
  x_s(1*n-1 downto 0)      := shiftr2c(x( 1*n-1 downto 0),1); -- 2 stage  
  x_s(2*n-1 downto 1*n)    := shiftr2c(x( 2*n-1 downto 1*n),2); -- 3 stage  
  x_s(3*n-1 downto 2*n)    := shiftr2c(x( 3*n-1 downto 2*n),3); -- 4 stage  
  x_s(4*n-1 downto 3*n)    := shiftr2c(x( 4*n-1 downto 3*n),4); -- 5 stage  
  x_s(5*n-1 downto 4*n)    := shiftr2c(x( 5*n-1 downto 4*n),5); -- 6 stage  
  x_s(6*n-1 downto 5*n)    := shiftr2c(x( 6*n-1 downto 5*n),6); -- 7 stage  
  x_s(7*n-1 downto 6*n)    := shiftr2c(x( 7*n-1 downto 6*n),7); -- 8 stage  
  x_s(8*n-1 downto 7*n)    := shiftr2c(x( 8*n-1 downto 7*n),8); -- 9 stage  
  x_s(9*n-1 downto 8*n)    := shiftr2c(x( 9*n-1 downto 8*n),9); -- 10 stage  
  
  return x_s;  
END shift_all;
```

 

Standard Cell library

```
function shiftr2c (v: vlbit_1d; i: integer) return vlbit_1d;
```

```

initial: init port map( xi <= X"00",
                           xs <= x_in,
                           yi <= X"00",
                           ys <= y_in,
                           zi <= z_in,
                           ai <= B"0_0101_1010", -- add/sub 90 degrees
                           xip1 <= xinit, -- xinit = 0 +- yin
                           yip1 <= yinit, -- yinit = 0 +- xin
                           zip1 <= zinit );

```

connect: **for** i in 0 to k-1 **generate** -- k stages

```

ls_unit: if i=0 generate
    first_unit:      adder port map( ... );
end generate ls_unit;

i_unit: if i>0 and i<k-1 generate
    x_round:         round port map ( ... );
    y_round:         round port map ( ... );
    middle_units:   adder port map( ... );
end generate ls_unit;

ms_unit: if i=k-1 generate
    x_round_last:   round port map ( ... );
    y_round_last:   round port map ( ... );
    last_unit:      adder port map( ... );
end generate ms_unit;

end generate connect;

```