

Memory (1A)



Copyright (c) 2011, 2015 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice.

Memory Access Operations

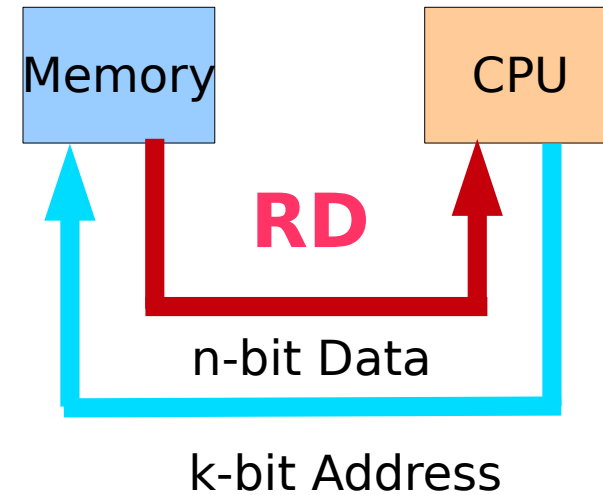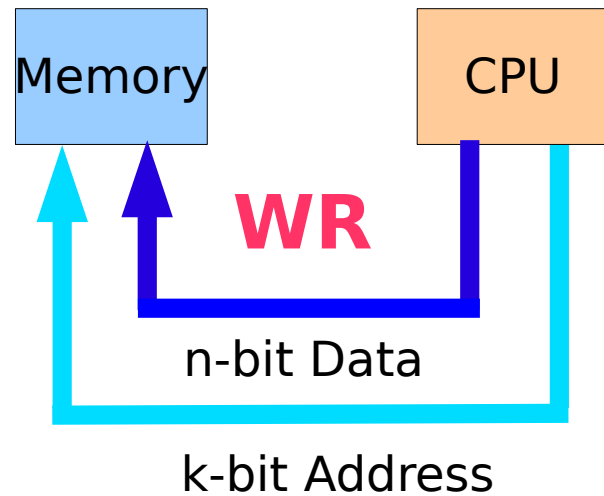


A Memory Write Example

2-bit address	4-bit data
00	0101
01	
10	1100
11	



2-bit address	4-bit data
00	0101
01	0111
10	1100
11	

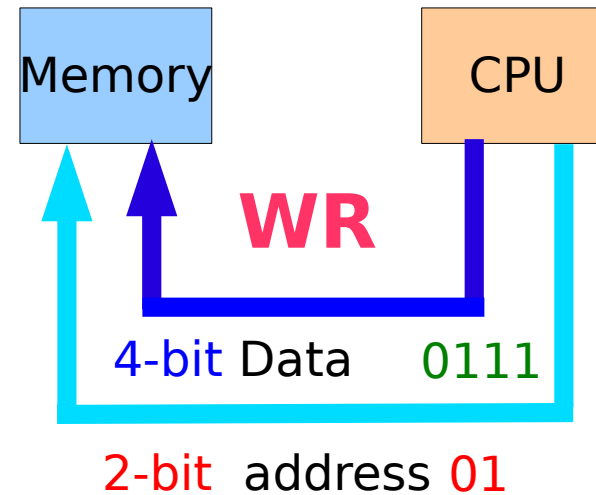


WR

Address: 01

Data: 0111

A Memory Read Example

2-bit address	4-bit data
00	0101
01	0111
10	1100
11	

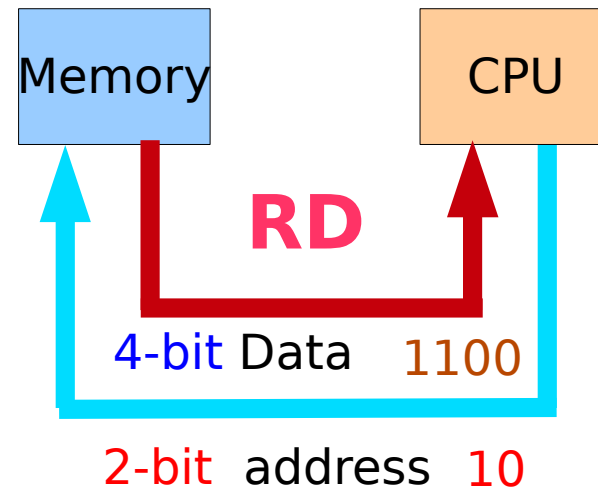


RD


Address: 10

Data: ➡ 1100

A Memory and A Memory Map

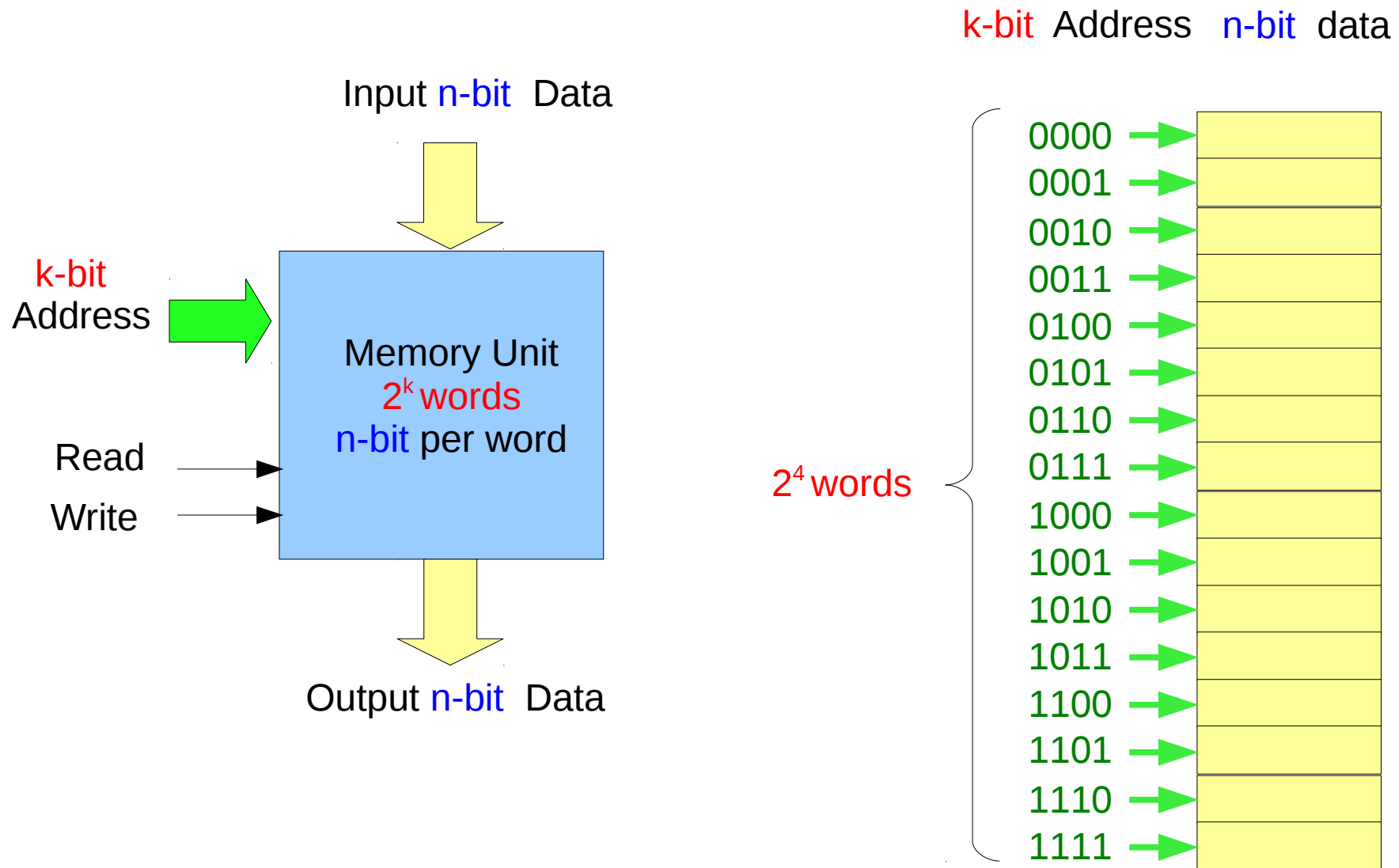

Address Bits and Data Bits

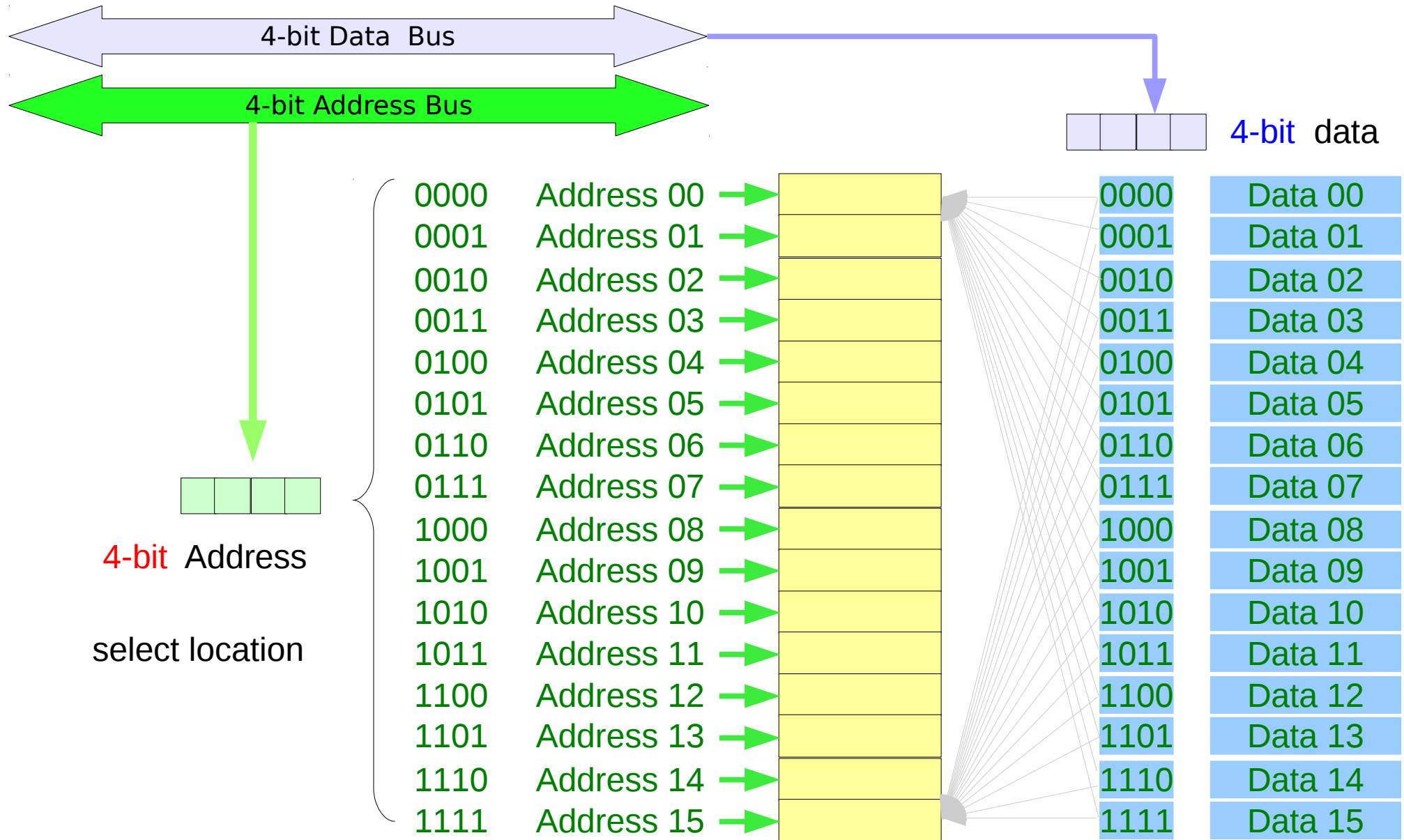

Increasing Memory Locations


5-bit Address

00000	Address 00	→	
00001	Address 01	→	
00010	Address 02	→	
00011	Address 03	→	
00100	Address 04	→	
00101	Address 05	→	
00110	Address 06	→	
00111	Address 07	→	
01000	Address 08	→	
01001	Address 09	→	
01010	Address 10	→	
01011	Address 11	→	
01100	Address 12	→	
01101	Address 13	→	
01110	Address 14	→	
01111	Address 15	→	



5-bit Address

10000	Address 16	→	
10001	Address 17	→	
10010	Address 18	→	
10011	Address 19	→	
10100	Address 20	→	
10101	Address 21	→	
10110	Address 22	→	
10111	Address 23	→	
11000	Address 24	→	
11001	Address 25	→	
11010	Address 26	→	
11011	Address 27	→	
11100	Address 28	→	
11101	Address 29	→	
11110	Address 30	→	
11111	Address 31	→	


Increasing Memory Width

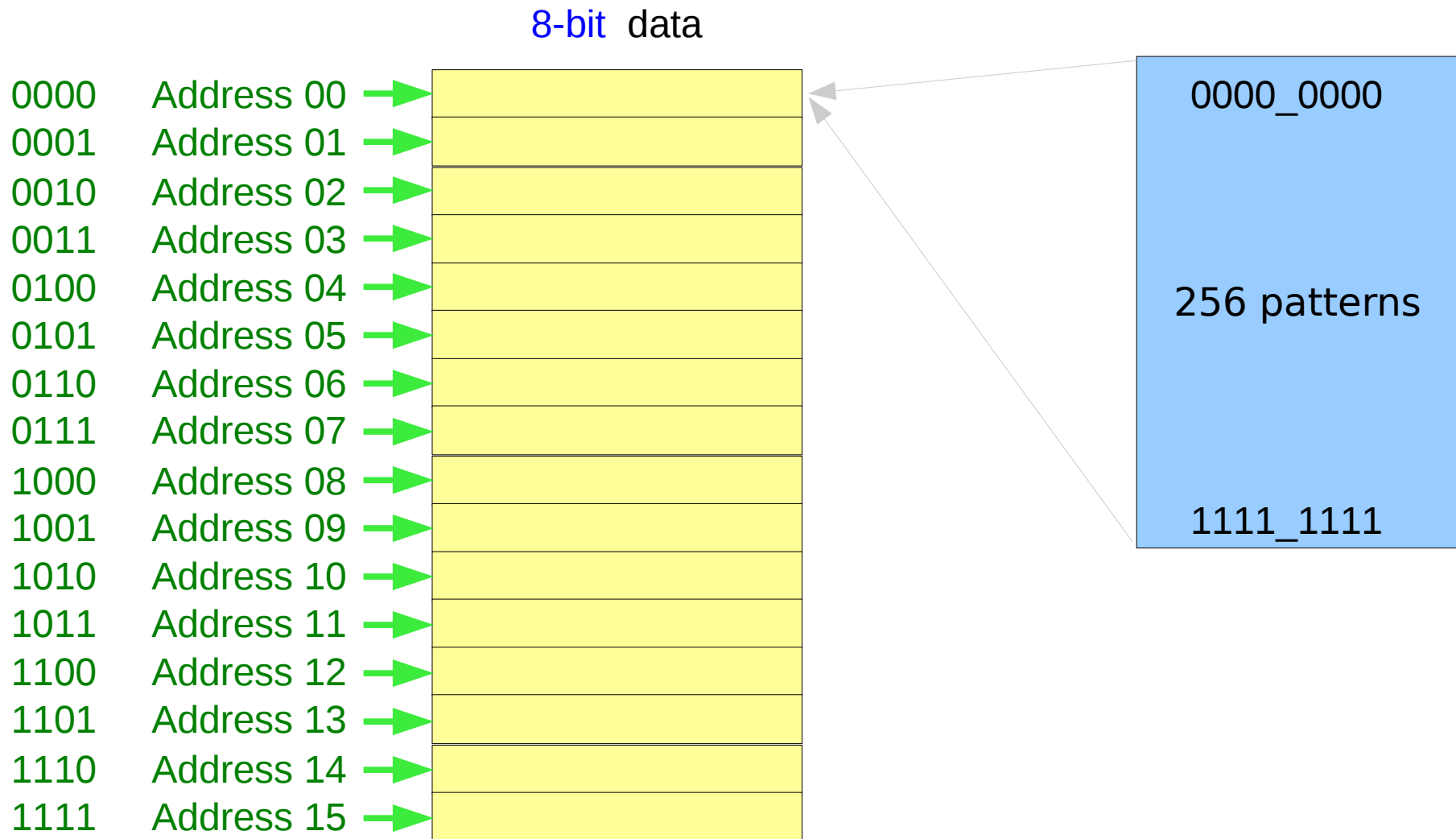

The Inputs and Outputs of a Memory

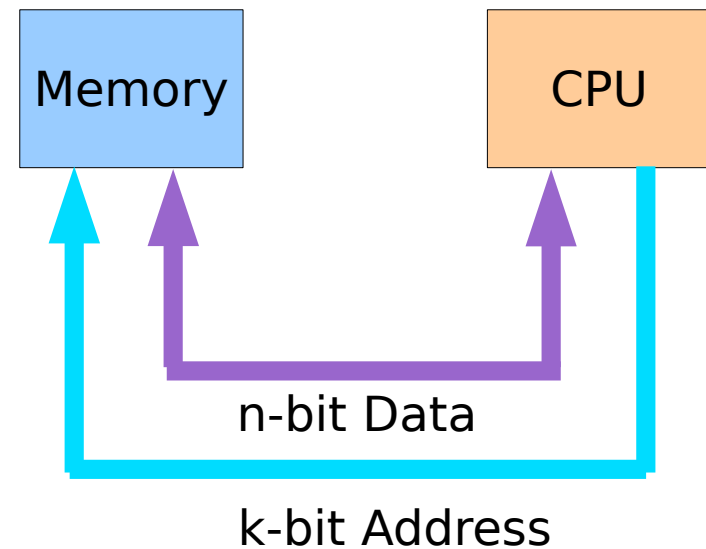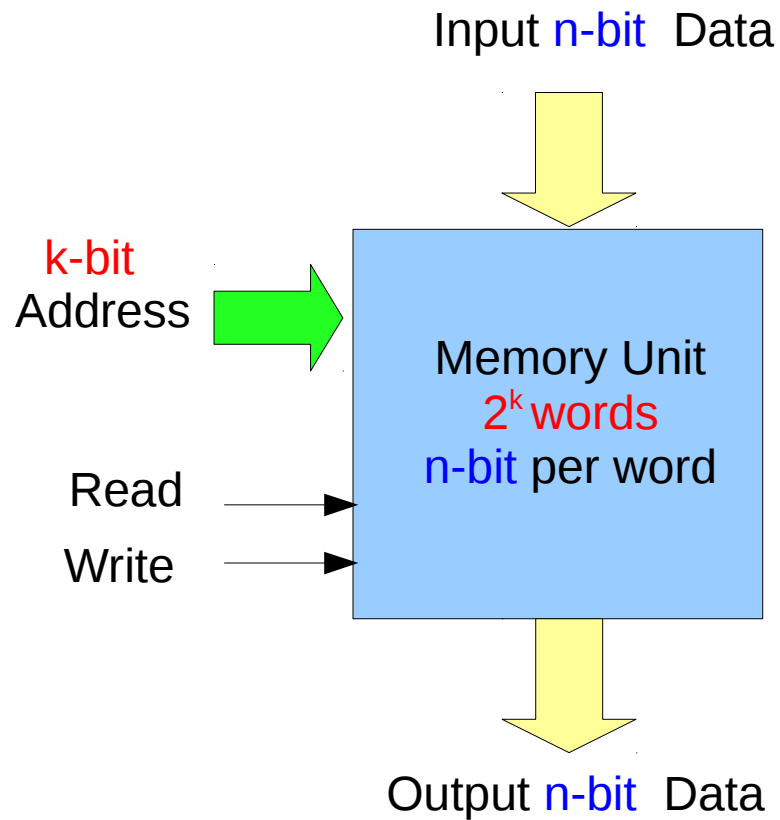


Block Diagram of a Memory Unit

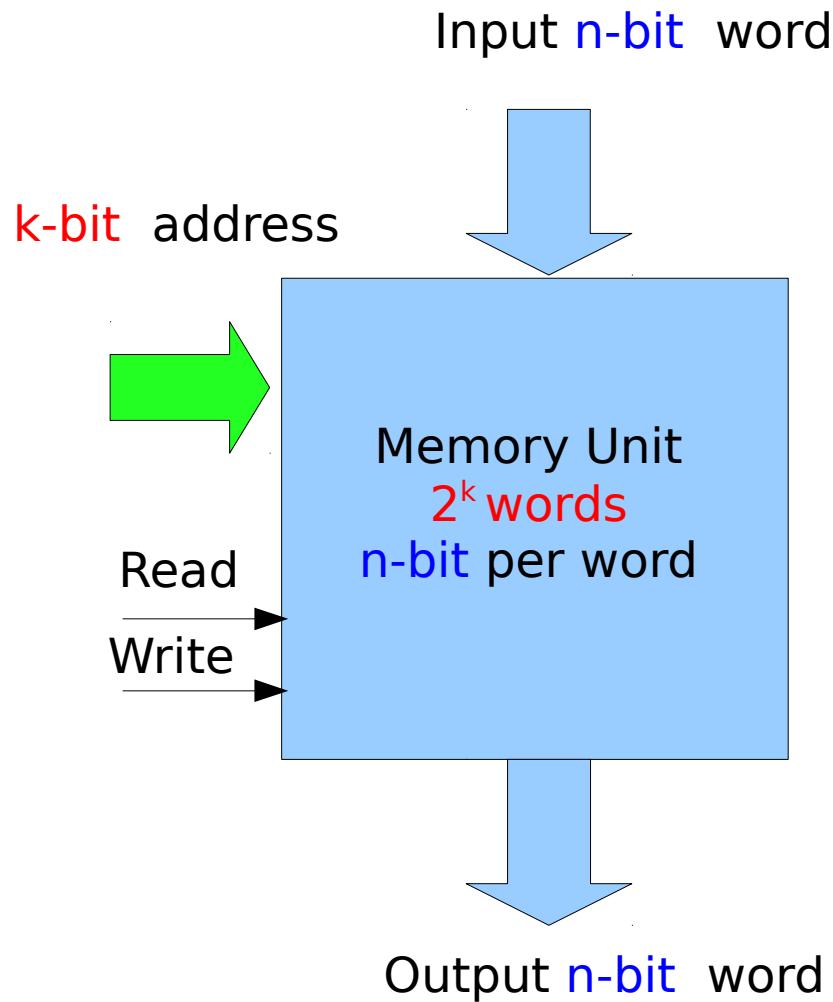



k-bit address n-bit word

 0000
0001
0010
0011
0100
0101
0110
0111
1000
1001
1010
1011
1100
1101
1110
1111




2^4 words




Memory Control Lines

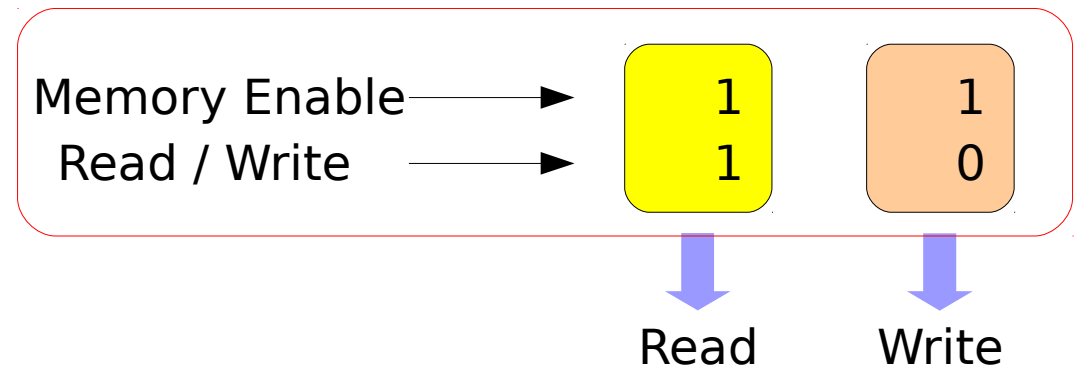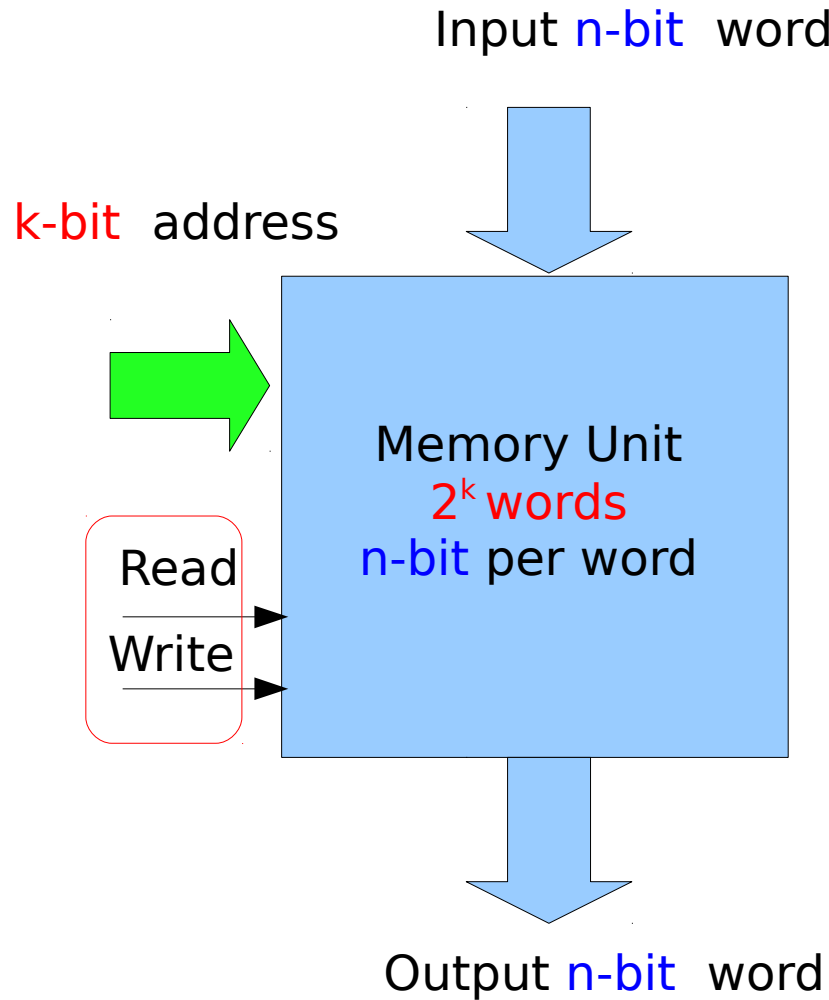




Address & Data Buses

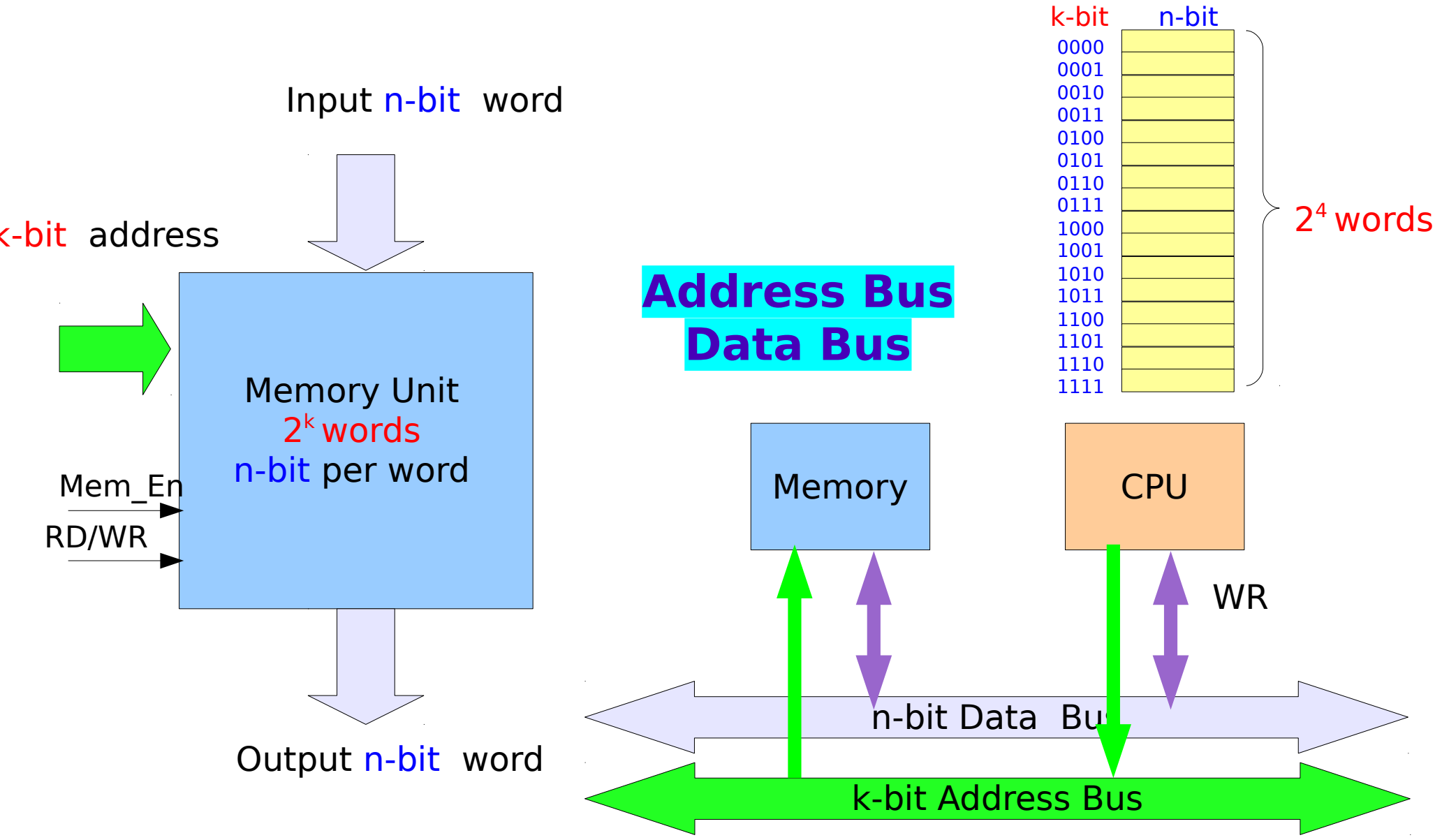


RD & WR Operations

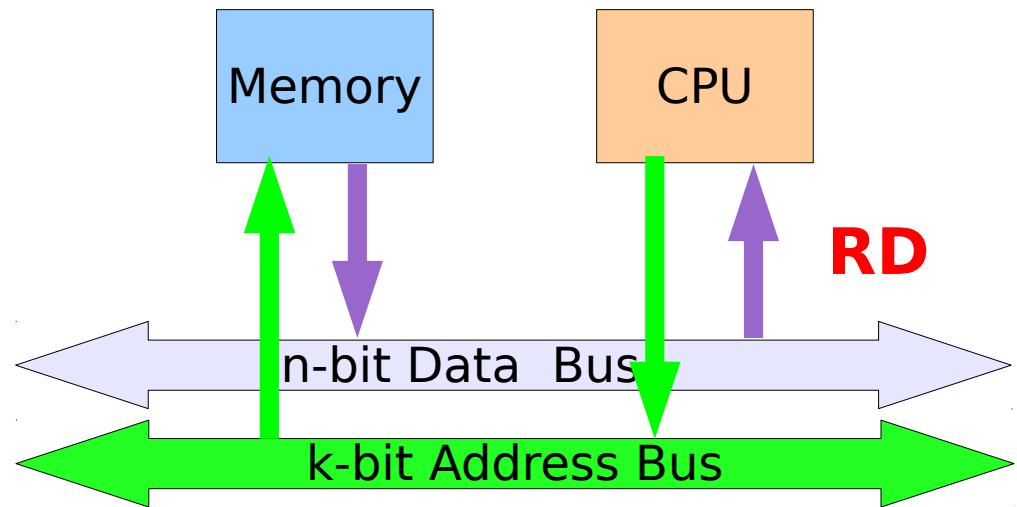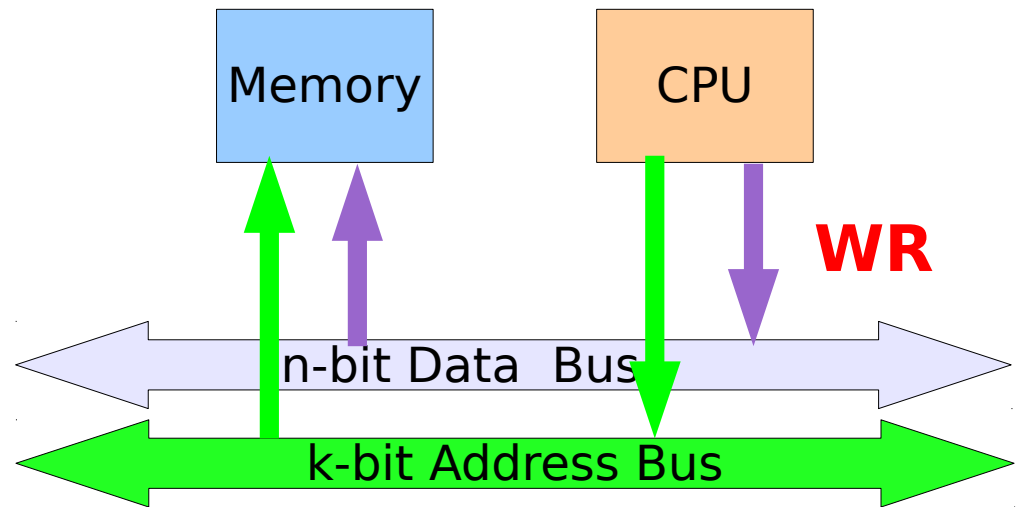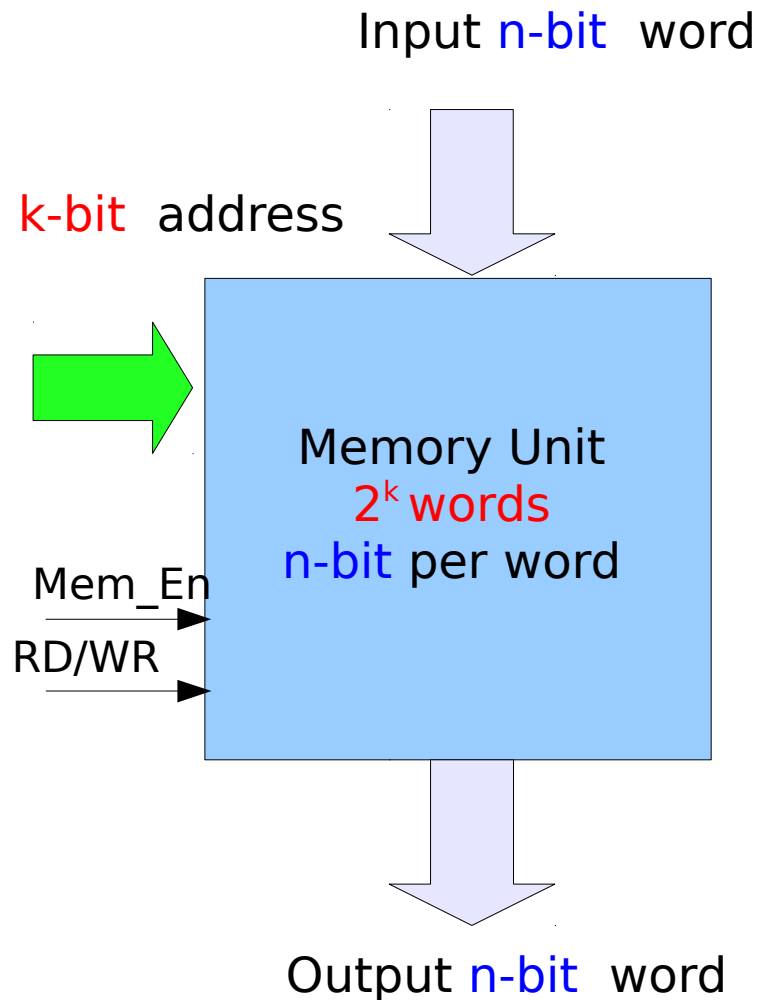




Memory Write Cycle

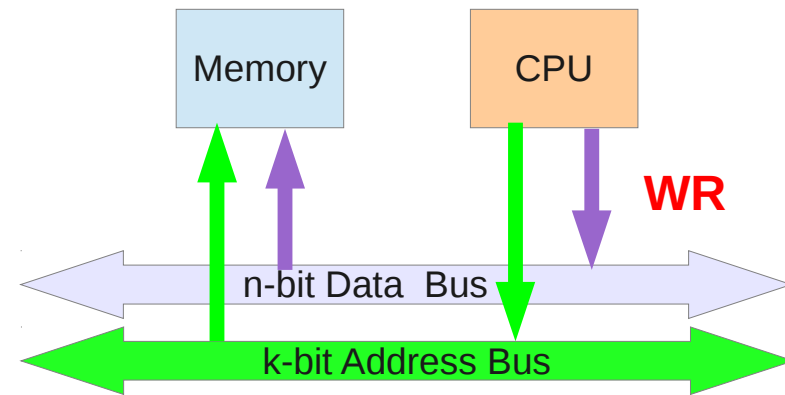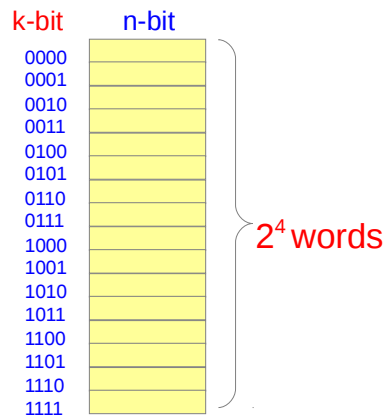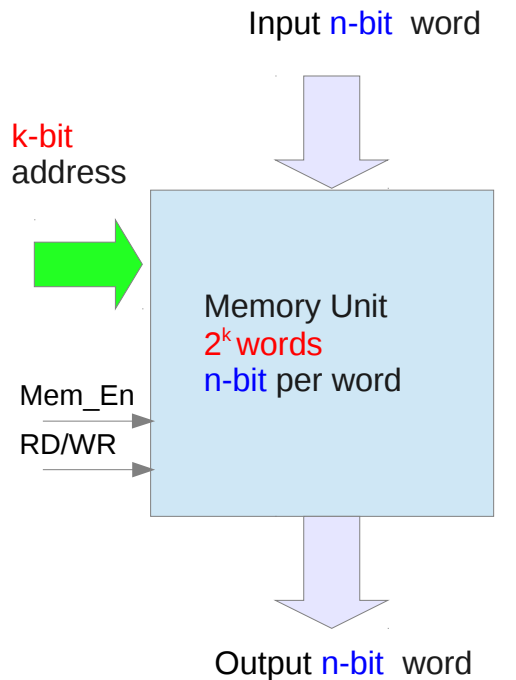

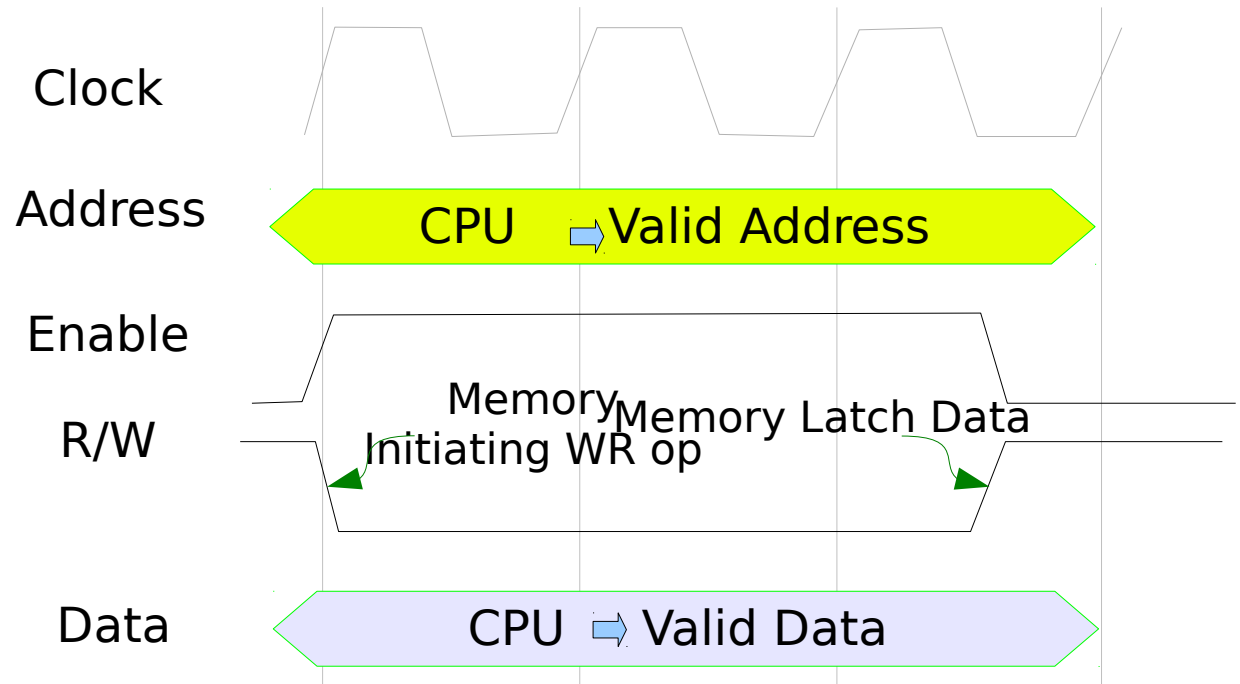
Usually, clock is seldom used. (shown for a reference)






Memory Read Cycle

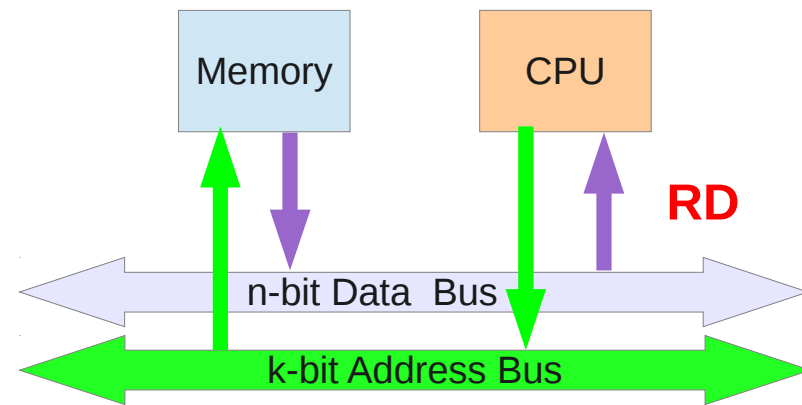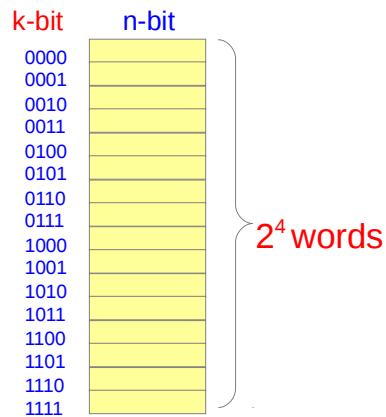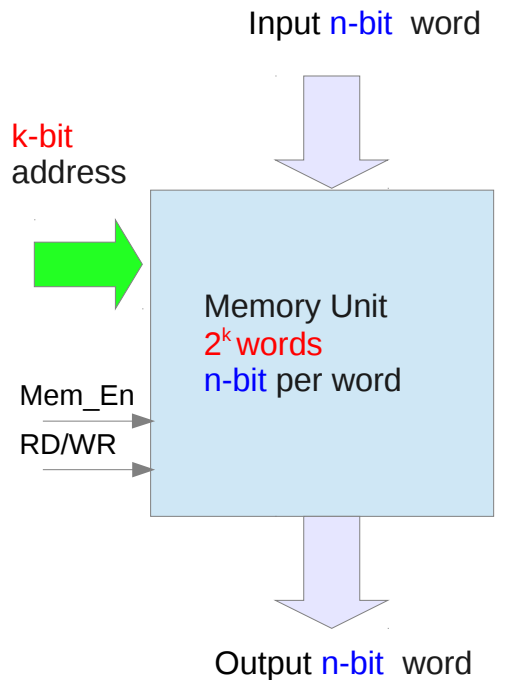

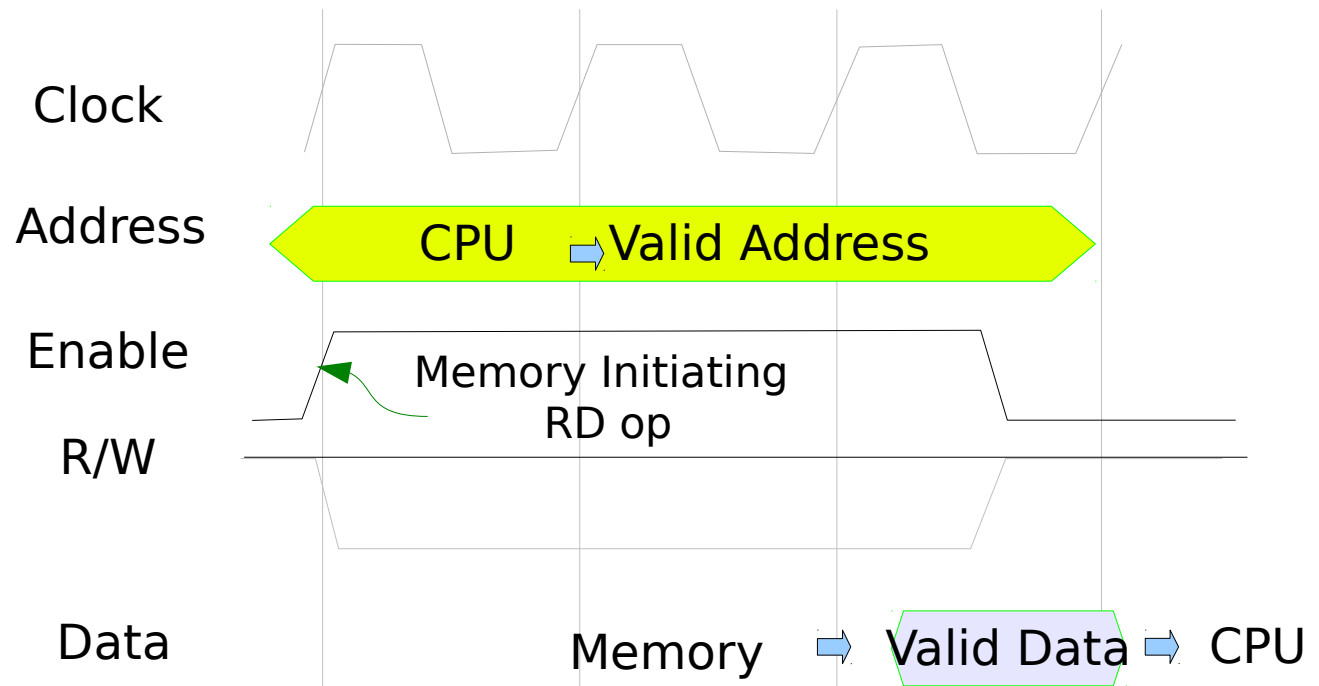
Usually, clock is seldom used. (shown for a reference)



Memory Write Example

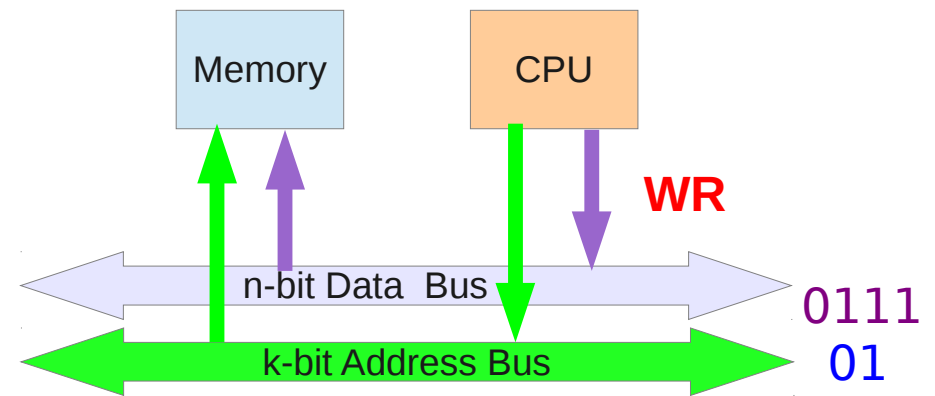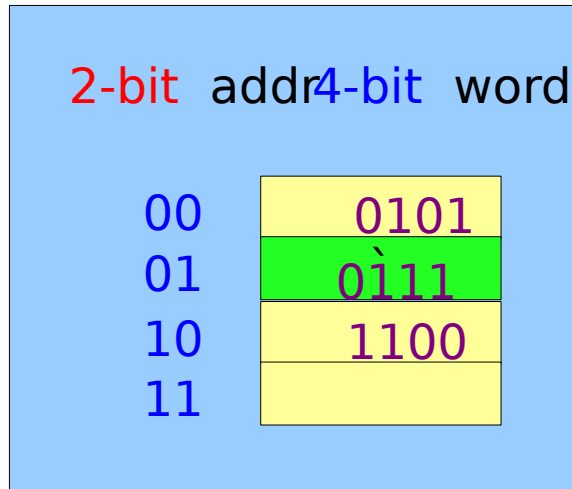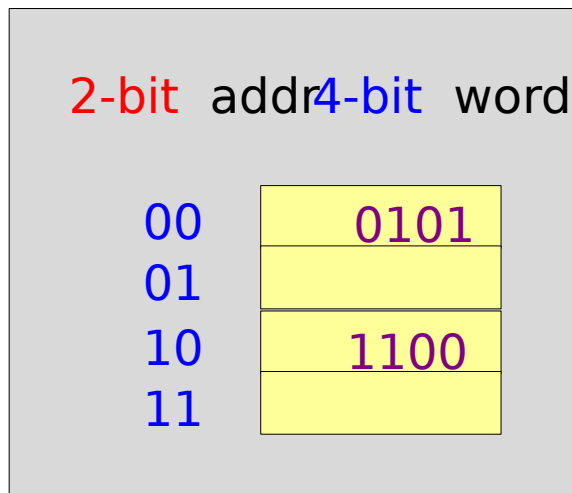


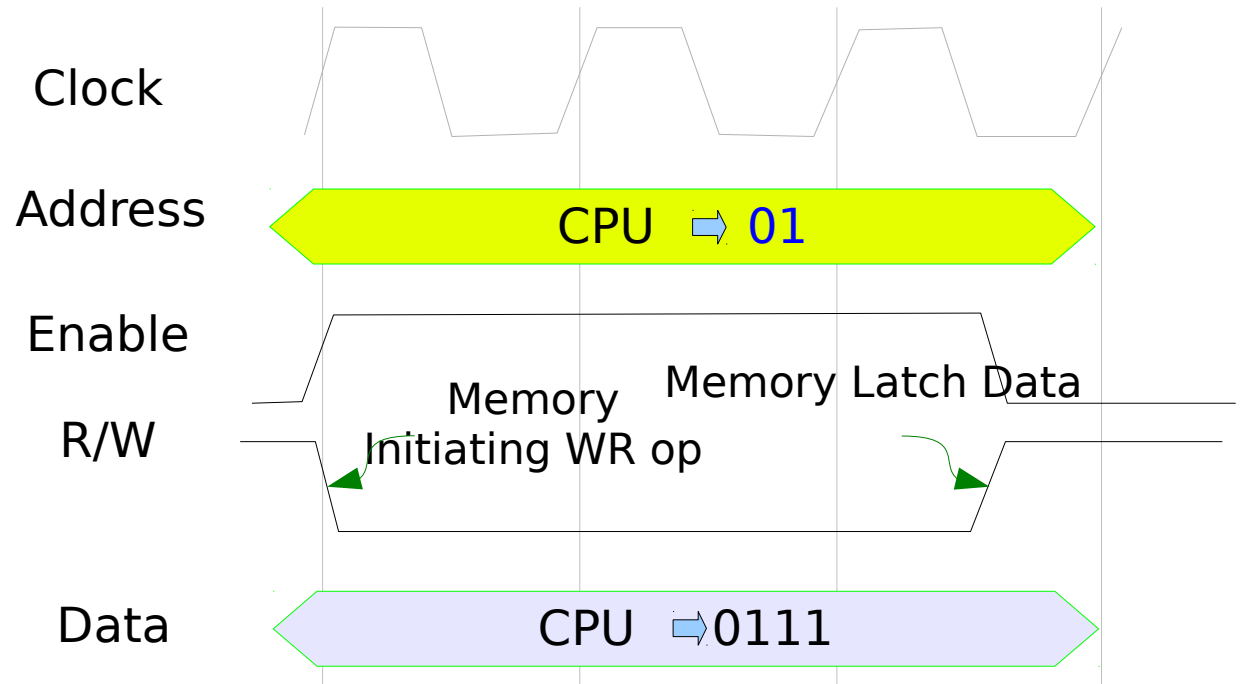Usually, clock is seldom used. (shown for a reference)




Memory Read Example


2-bit addr	4-bit word
00	0101
01	
10	1100
11	

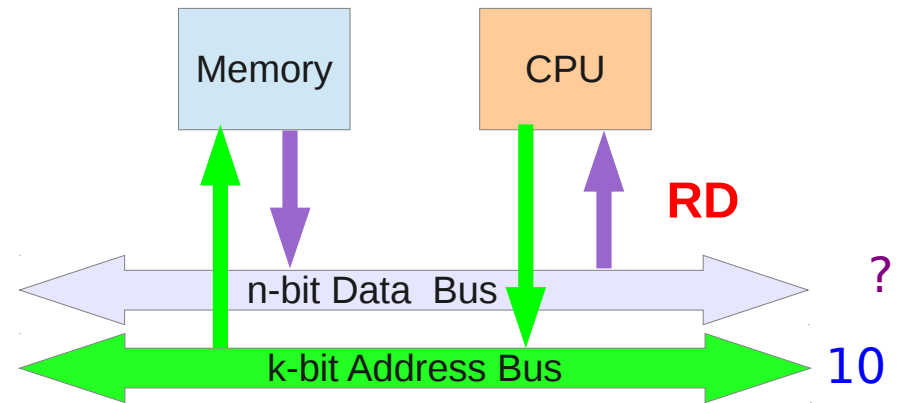


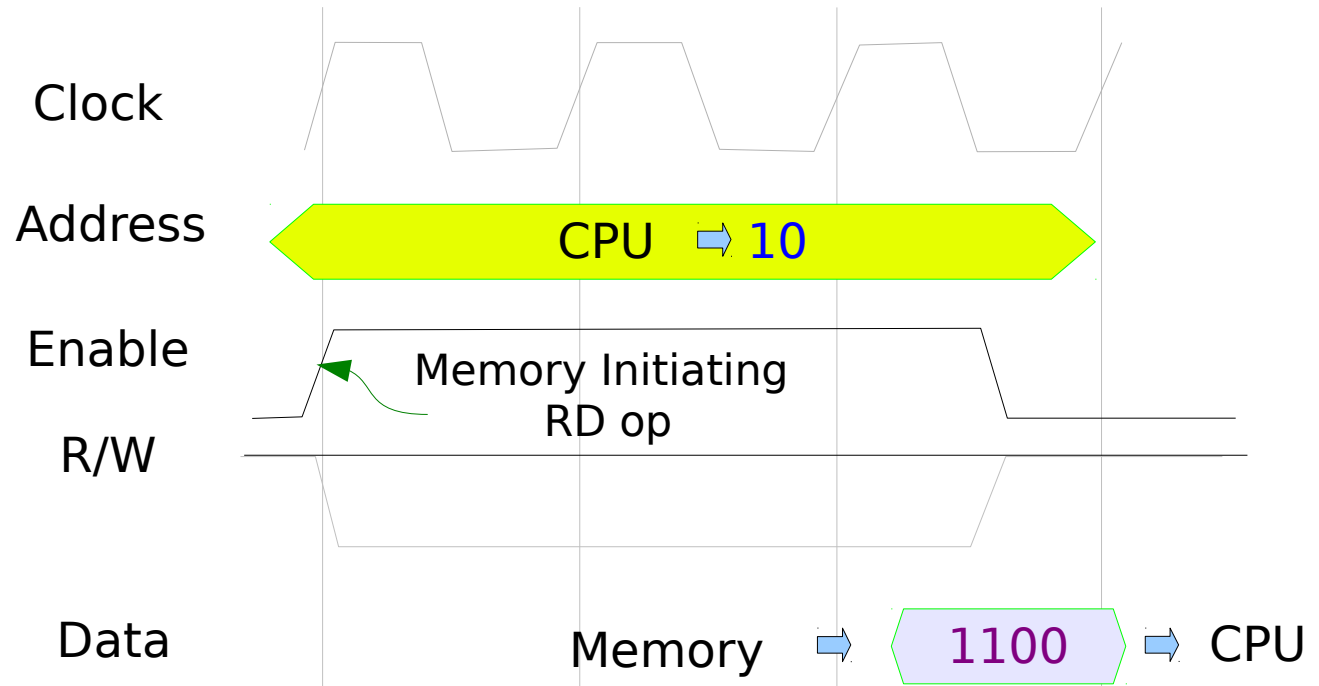
Usually, clock is seldom used. (shown for a reference)




Selecting a Word

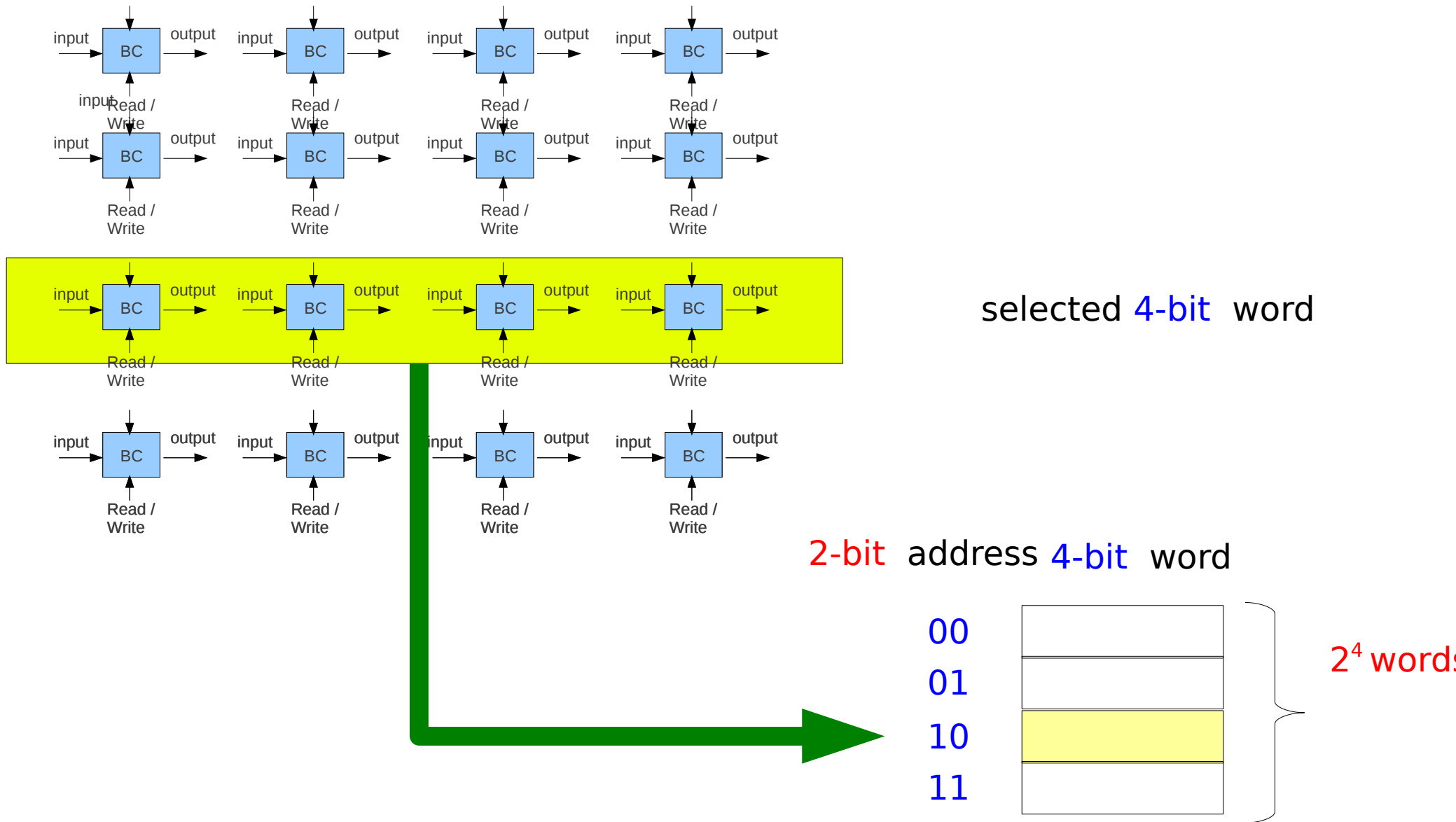

Selecting a Word

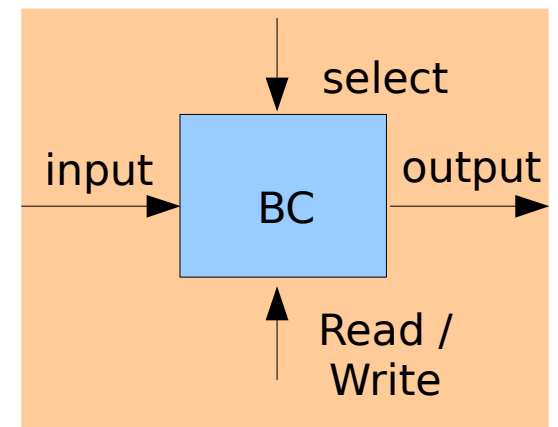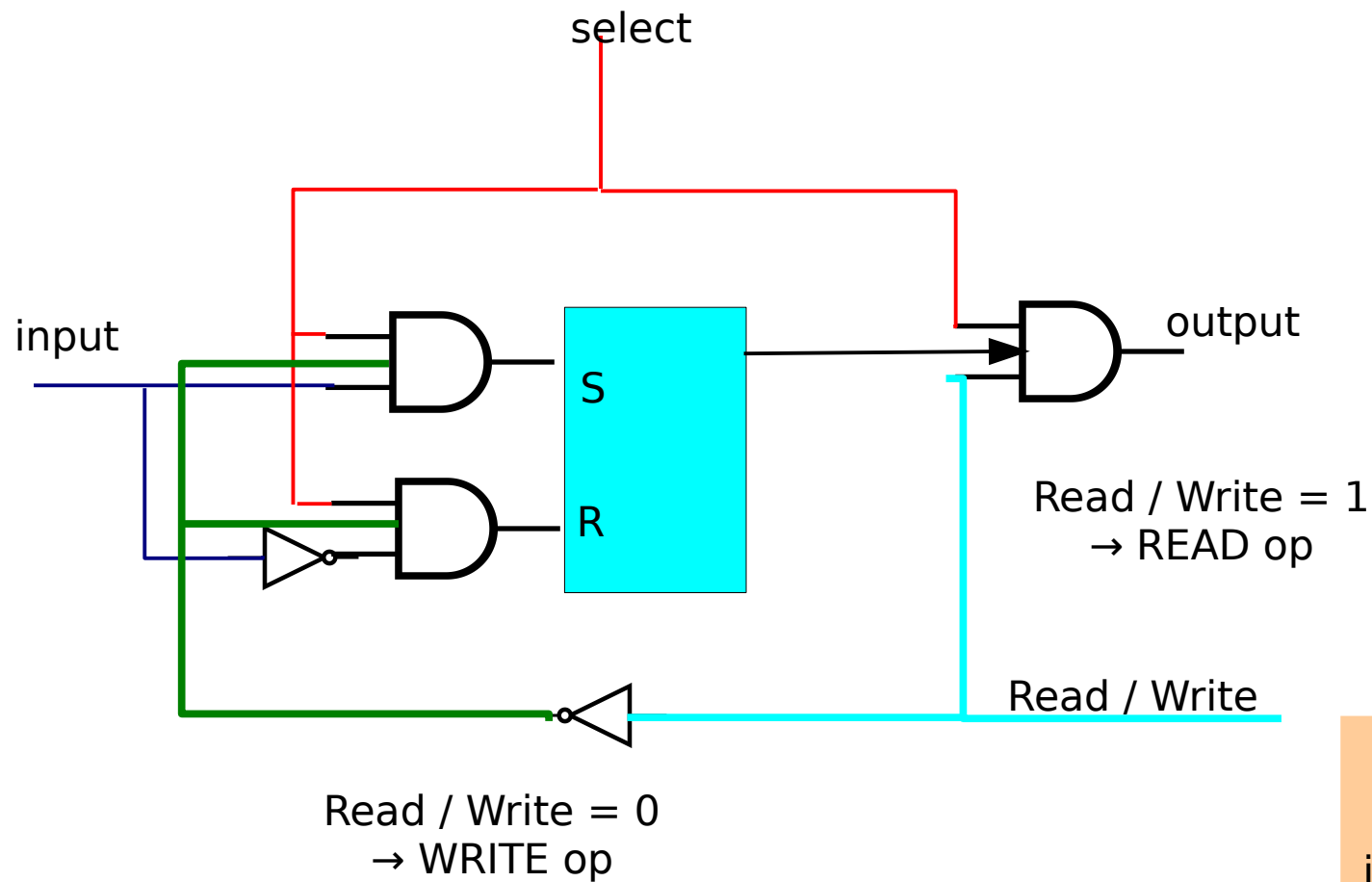

A Memory Map

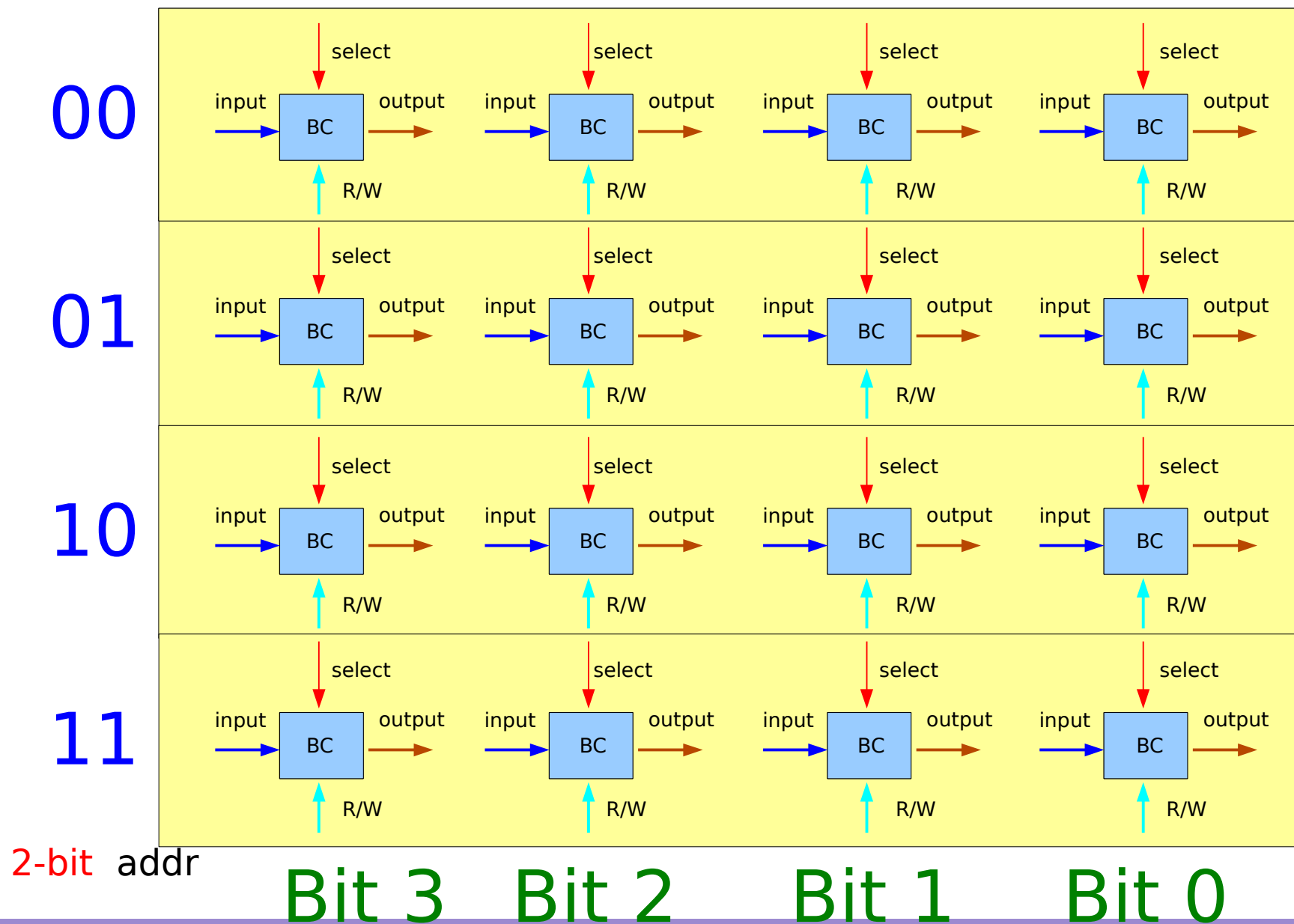

4x4 Memory


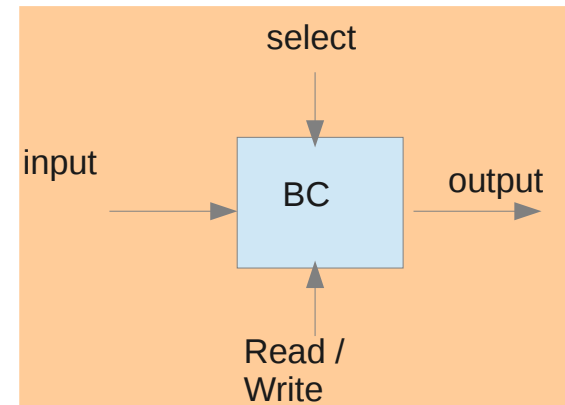
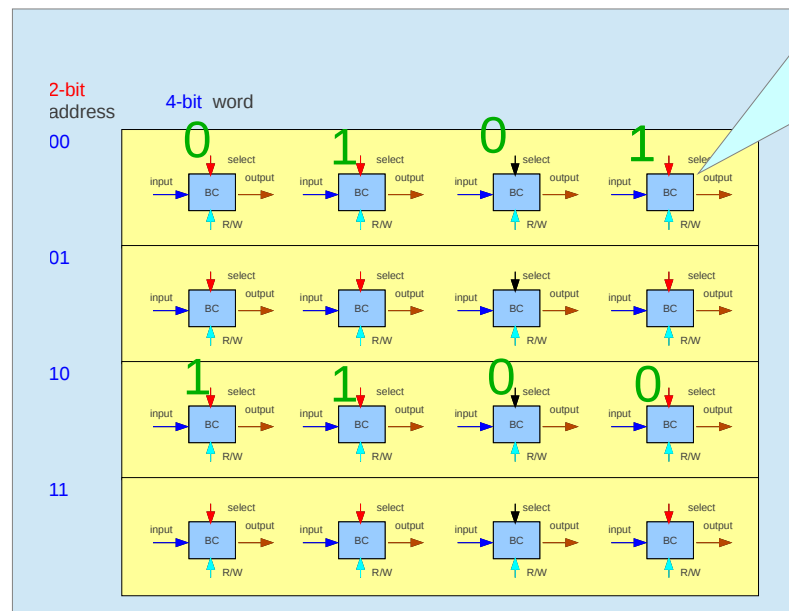
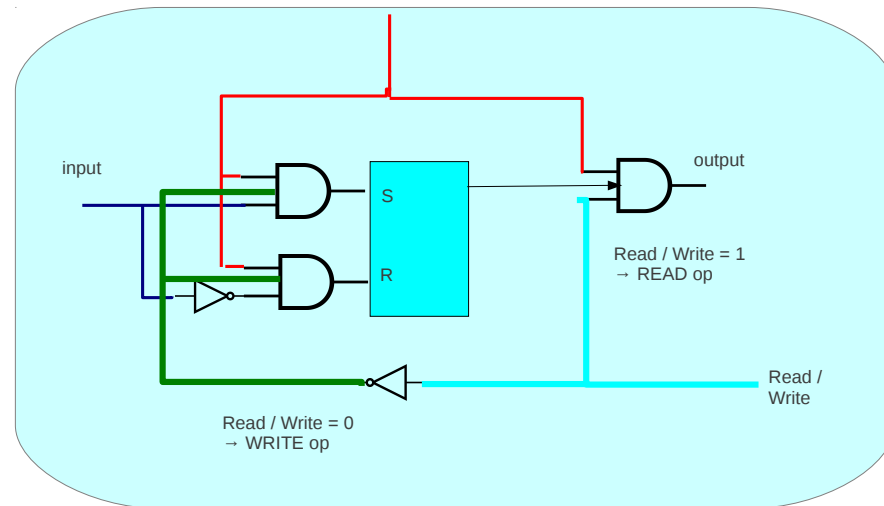
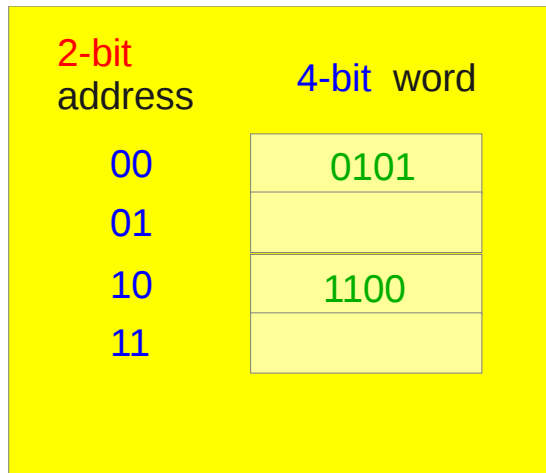



Diagram for a 4x4 Memory

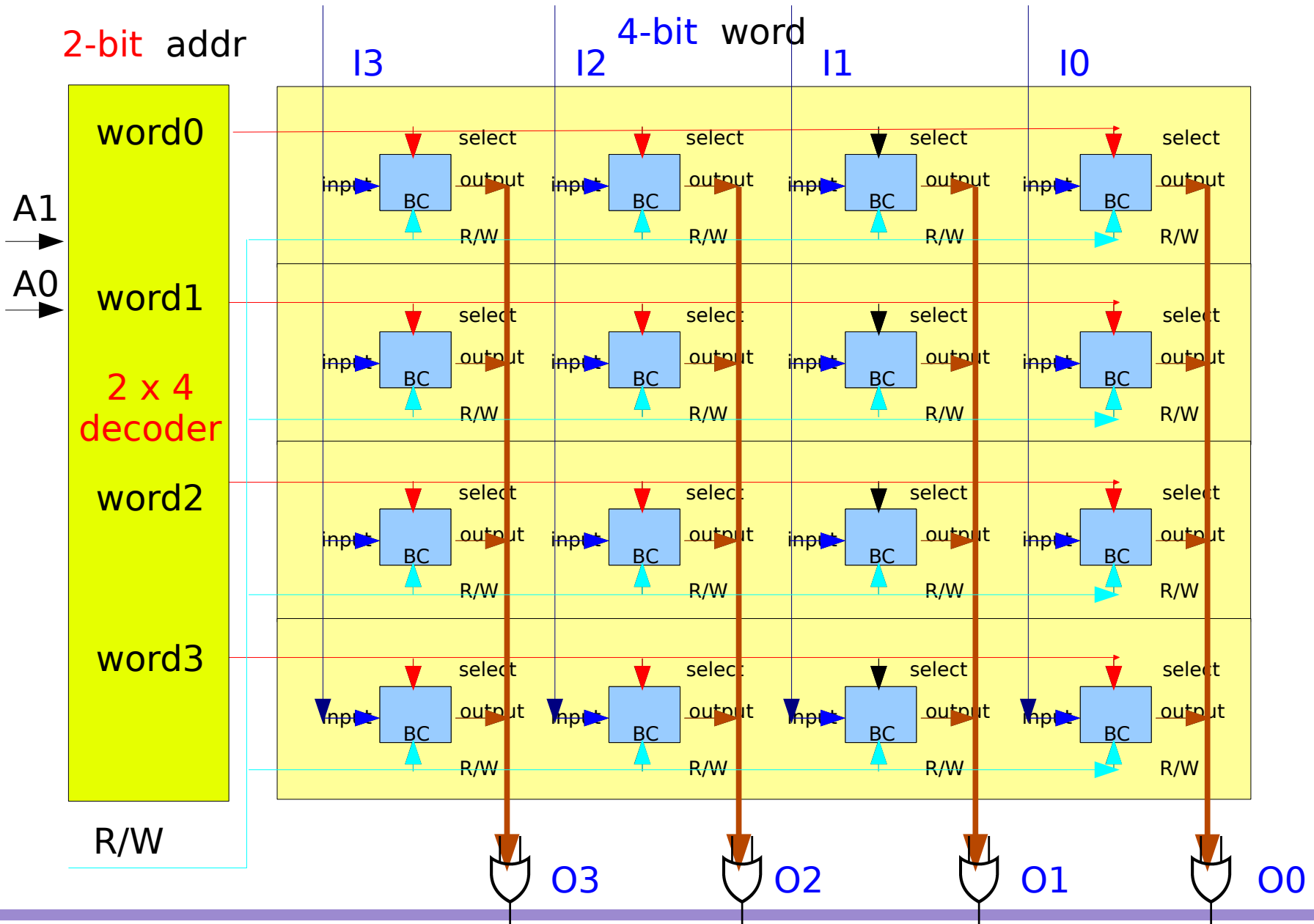


Memory

23


Write Cycle Example for a 4x4 Memory

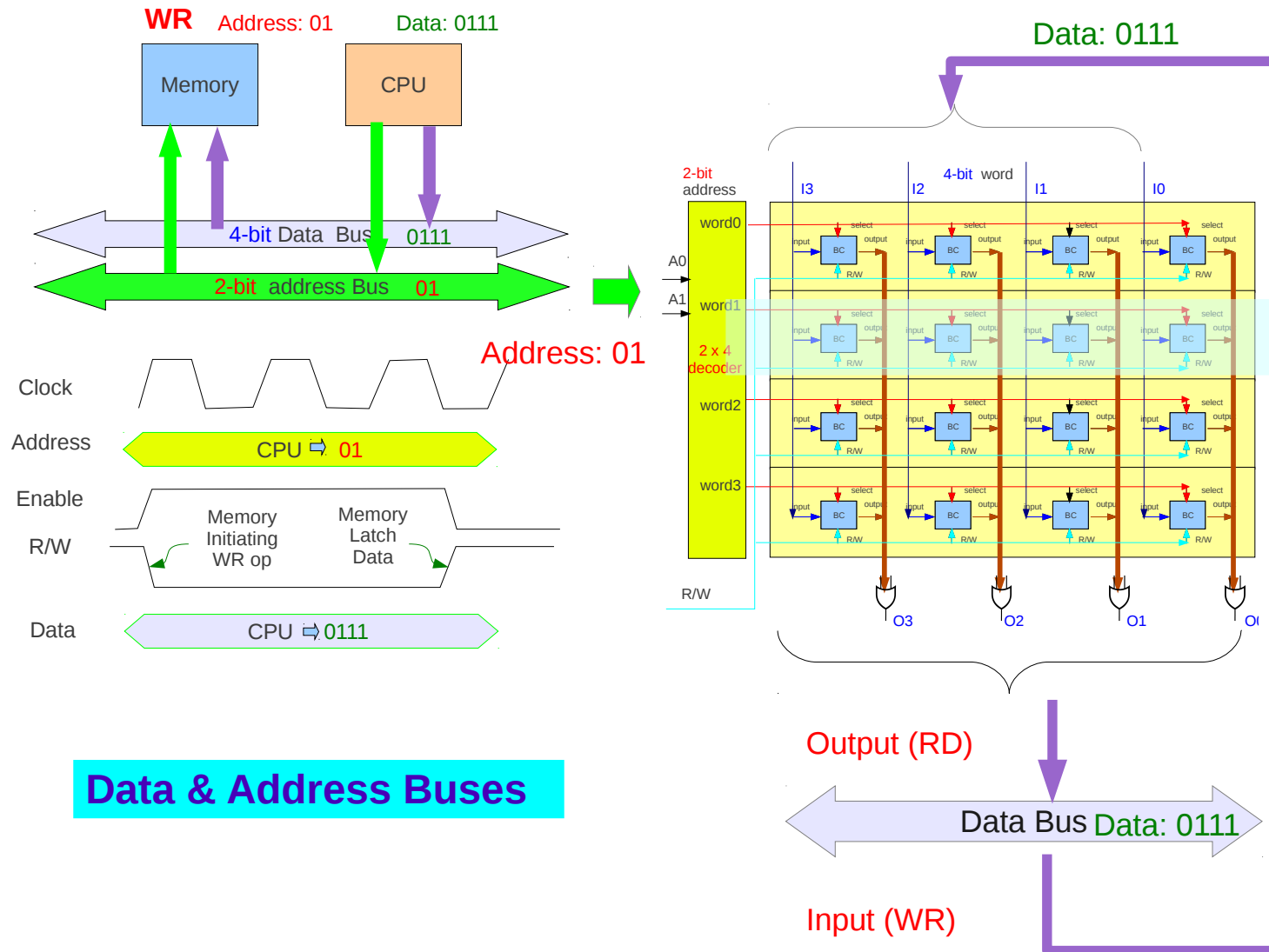


Bi-directional Data Bus

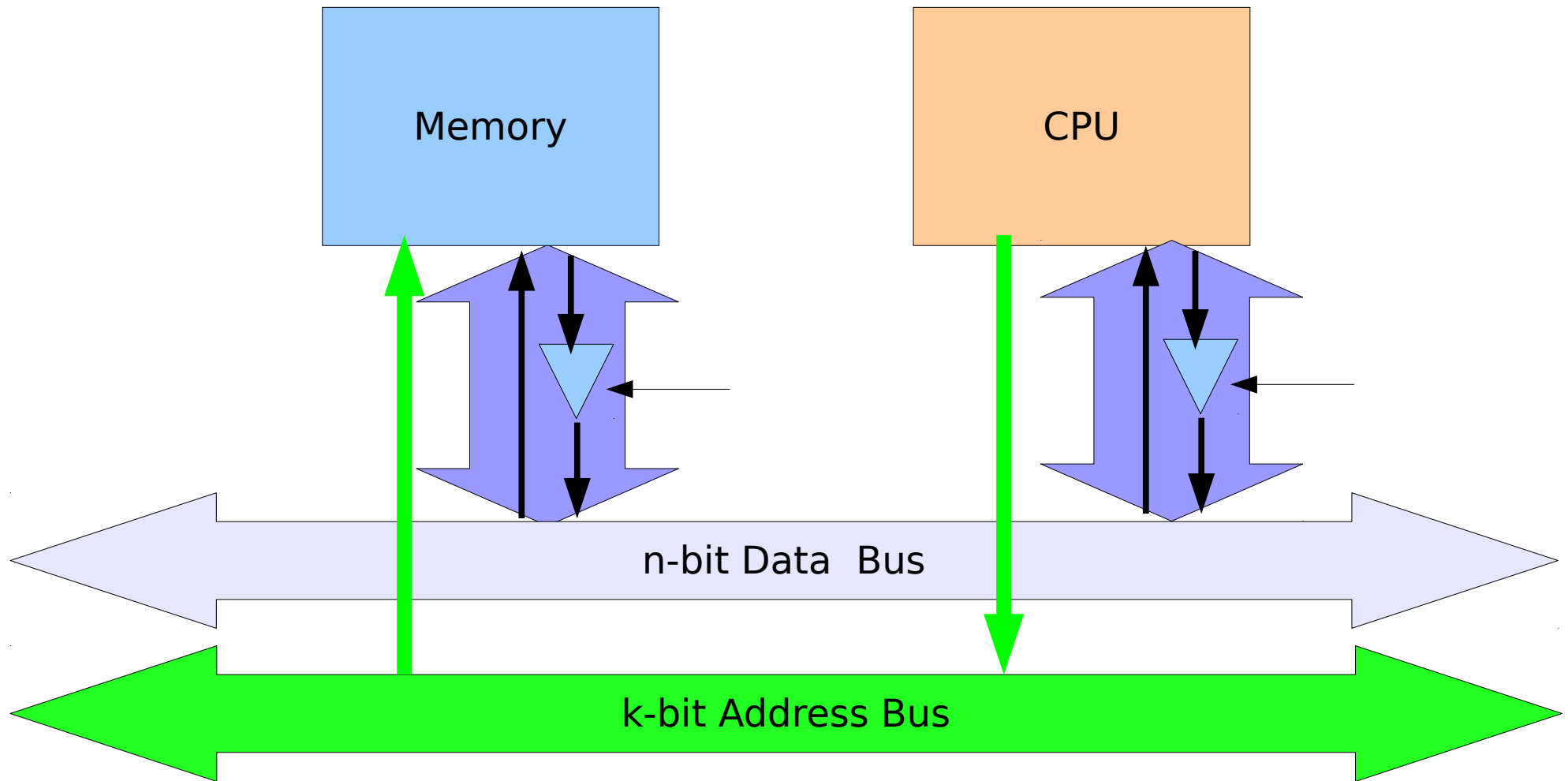


From CPU to Memory

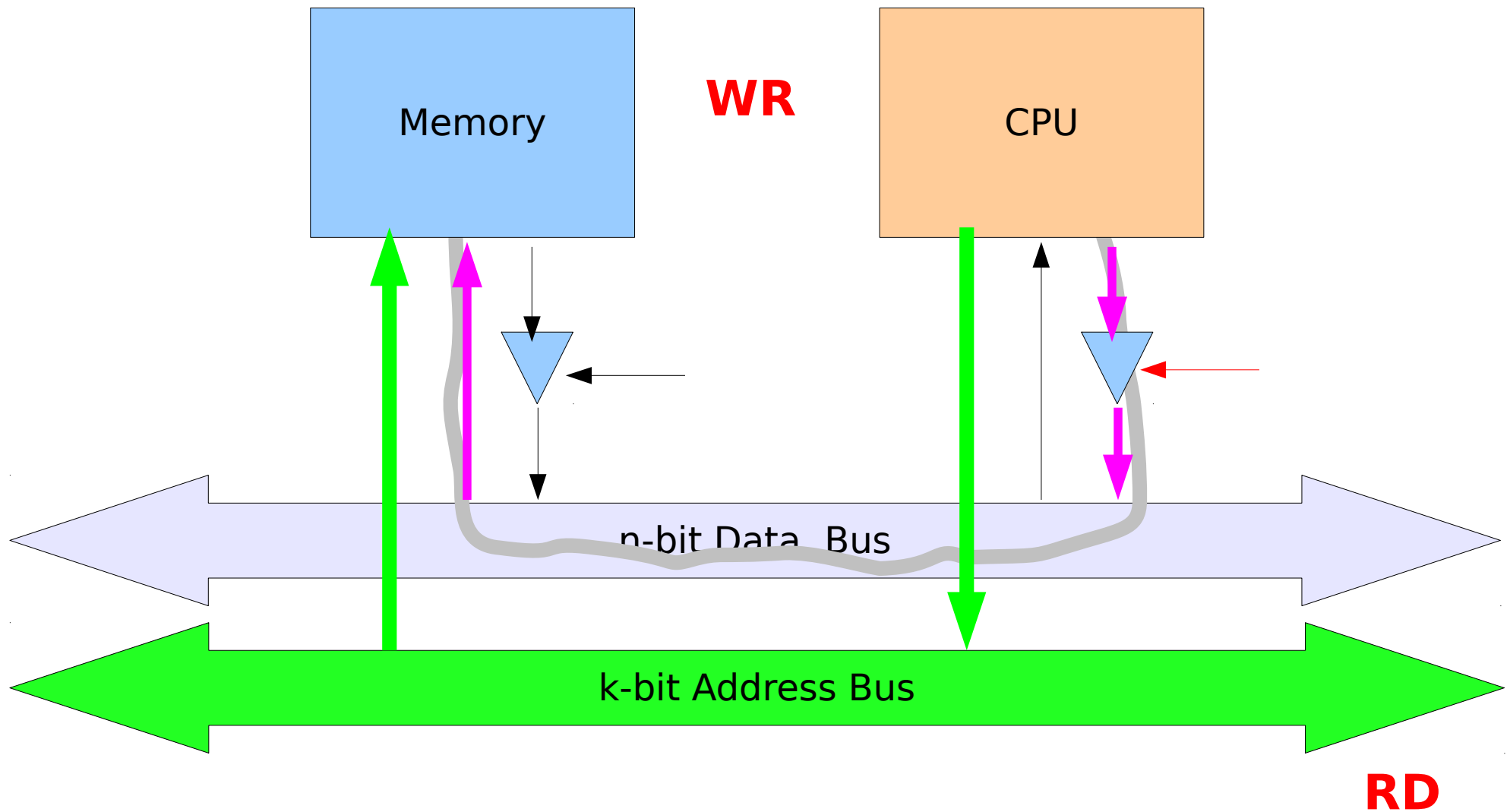

From Memory to CPU

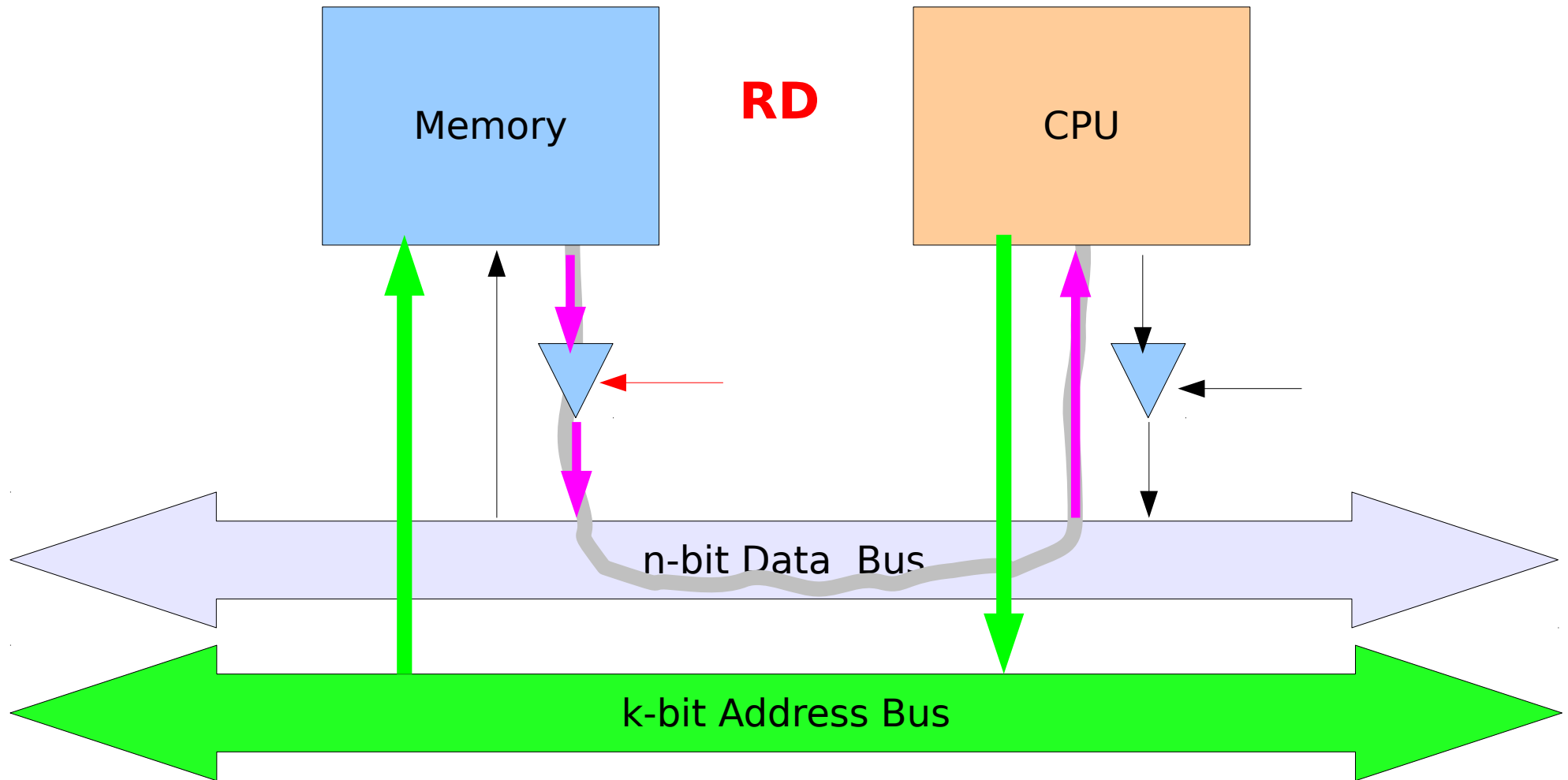


2 to 4 Decoder

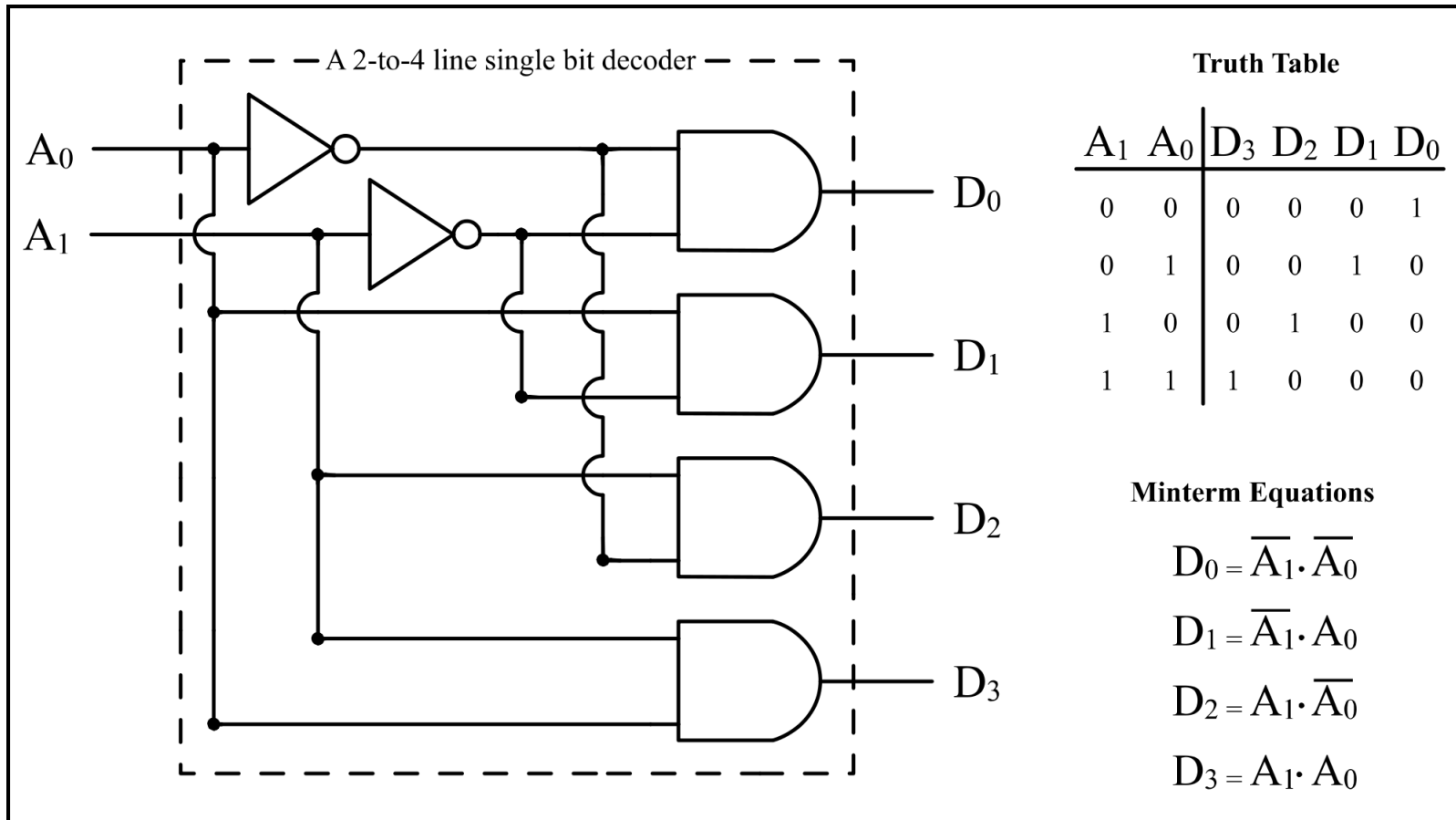


2 x 4 decoder : 4 AND gates
4 x 16 decoder : 16 AND
gates

10 x 1024 decoder : 1024 AND
gates

Coincidence Decoder

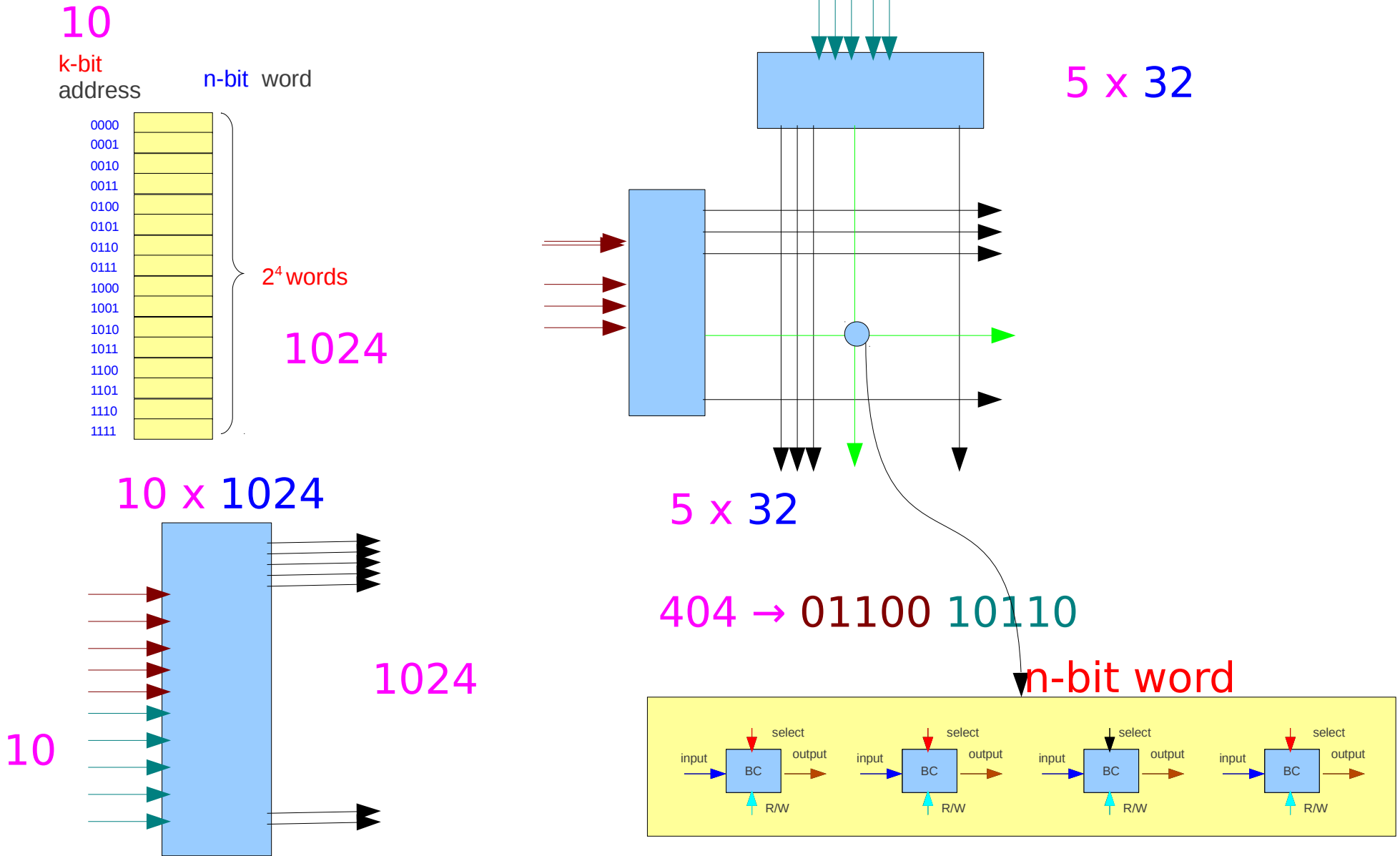

Time Sharing Address Bus

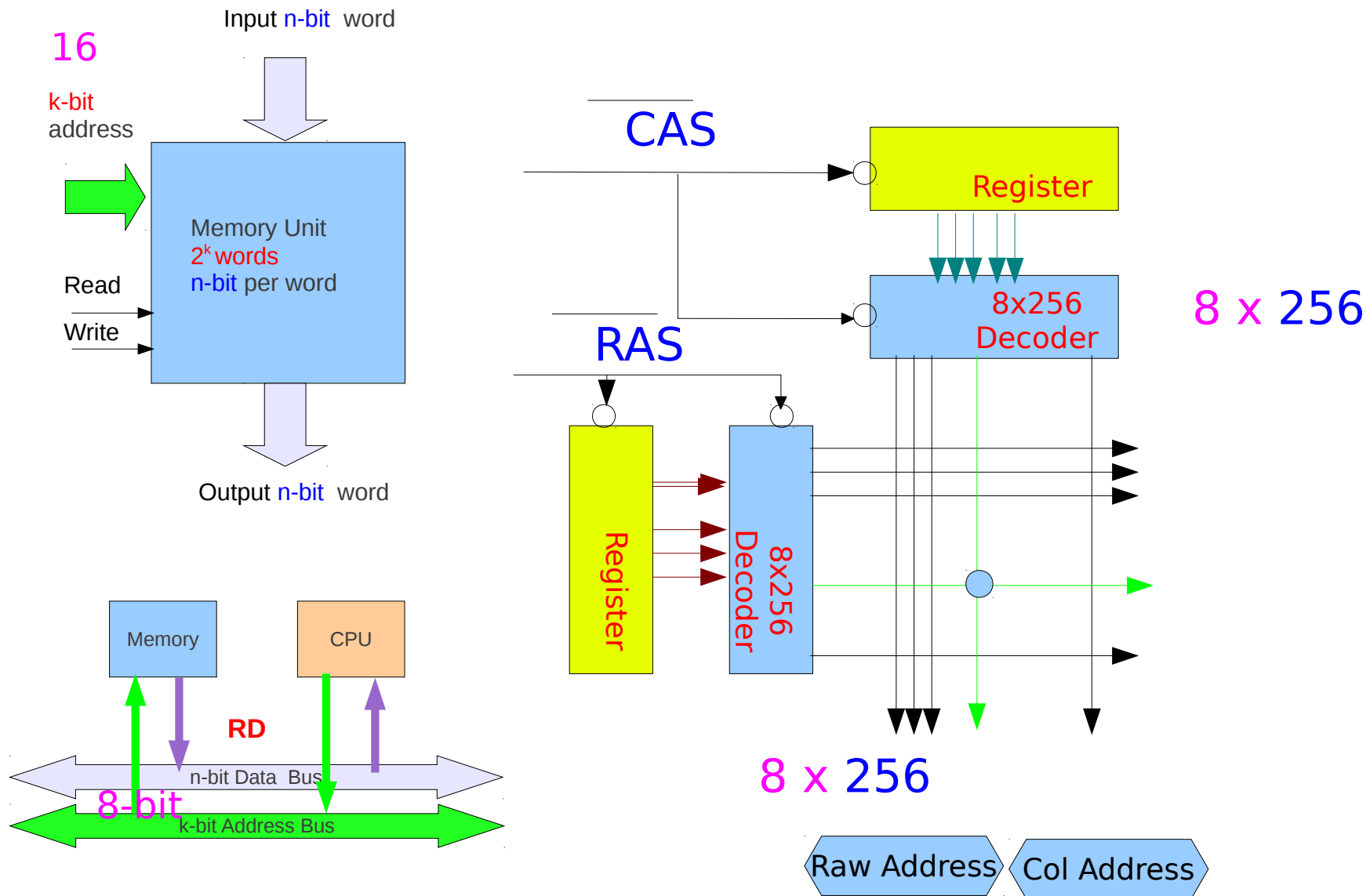

References

- [1] Essential C, Nick Parlante
- [2] Efficient C Programming, Mark A. Weiss
- [3] C A Reference Manual, Samuel P. Harbison & Guy L. Steele Jr.
- [4] C Language Express, I. K. Chun