# Capacitor in a DC circuit

Young Won Lim 06/24/2017 Copyright (c) 2011 – 2017 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.

Young Won Lim 06/24/2017

#### Charge





**Final** No more electrons to leave



crowded electrons prevent other electrons from arriving

Energy stored in Electric Field

$$v_c(\infty) = V_0$$

 $i_c(\infty) = 0$ 



$$i_c = C \cdot \frac{d v_c}{d t}$$

 $v_c(0^-) = v_c(0^+)$ unyielding voltage

 $i_{c}(0^{-}) \neq i_{c}(0^{+})$ 

current jump

**Capacitor – DC** 

## Discharge





$$i_c = C \cdot \frac{d v_c}{d t}$$

 $v_c(0^-) = v_c(0^+)$ 

unyielding voltage  $i_c(0^-) \neq i_c(0^+)$  current jump

4

$$v_c(\infty) = 0$$
  
 $i_c(\infty) = 0$ 

**Capacitor – DC** 

### Charge



## Discharge



Pulse



7

Pulse



#### References

- [1] http://en.wikipedia.org/
- [2] J.H. McClellan, et al., Signal Processing First, Pearson Prentice Hall, 2003