

# CMOS Combi-1 (H.1)

20151118

Copyright (c) 2015 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

# References

Some Figures from the following sites

[1] <http://pages.hmc.edu/harris/cmosvlsi/4e/index.html>

Weste & Harris Book Site

[2] [en.wikipedia.org](http://en.wikipedia.org)



[3] Digital Integrated Circuits : A Design Perspective,

Jan M. Rabaey,



(<http://bwracs.eecs.berkeley.edu/Courses/lcBook/>)

[4] Digital Electronics and Design with VHDL


Pedroni

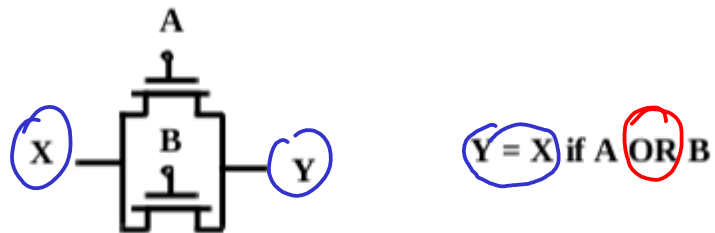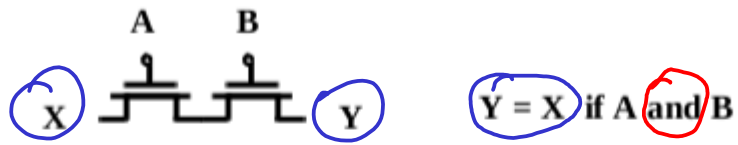

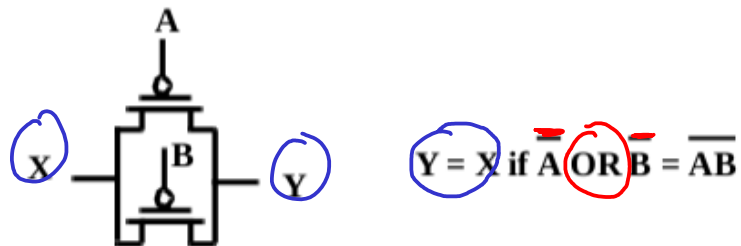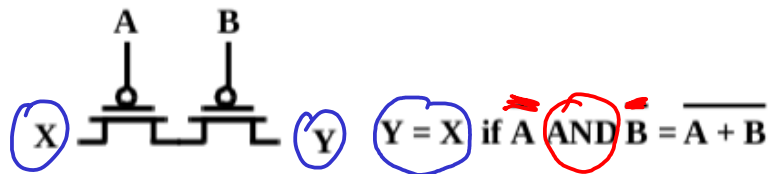NMOS Transistors pass a “strong” 0 but a “weak” 1



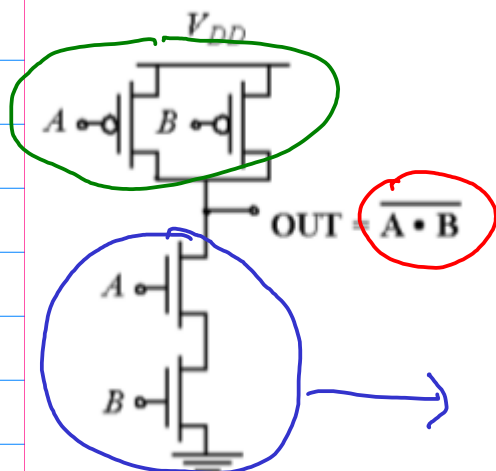PMOS Transistors pass a “strong” 1 but a “weak” 0




if  $\overline{A} + \overline{B}$ , then  $OUT \Rightarrow 1$

$$\overline{A} + \overline{B}$$

if  $A \cdot B$ , then  $OUT \Rightarrow 0$

$\overline{A \cdot B}$  NAND
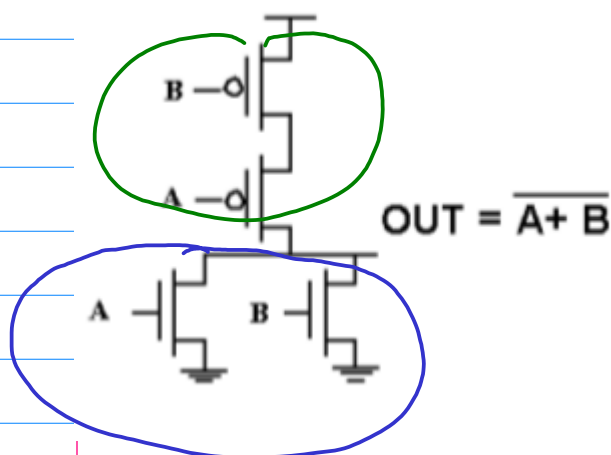
$$\overline{A \cdot B} = \overline{A} + \overline{B}$$



if  $\overline{A} \cdot \overline{B}$ , then  $OUT \Rightarrow 1$

$$\overline{A} \cdot \overline{B}$$

if  $A + B$ , then  $OUT \Rightarrow 0$


$\overline{A + B}$  NOR

$$\overline{A} \cdot \overline{B} = \overline{A + B}$$

NAND

$$\overline{A \cdot B}$$




$$= \bar{A} + \bar{B}$$

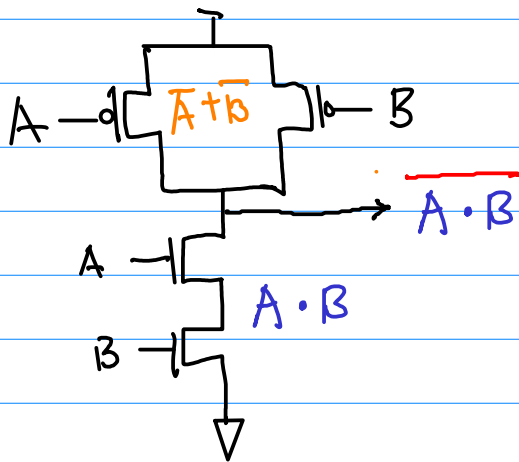


NOR

$$\overline{A + B}$$

$$= \bar{A} \cdot \bar{B}$$

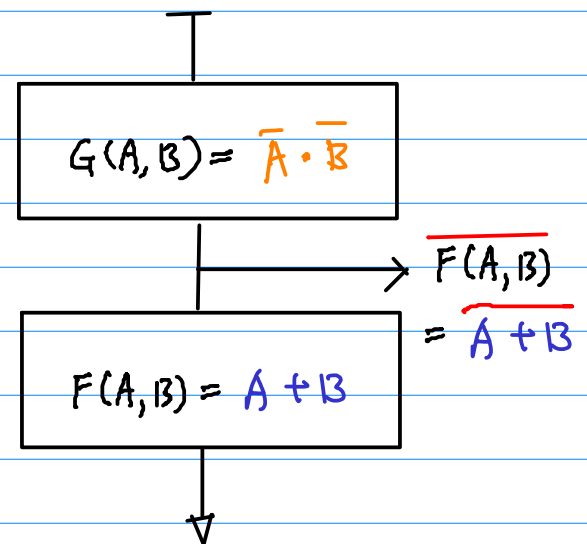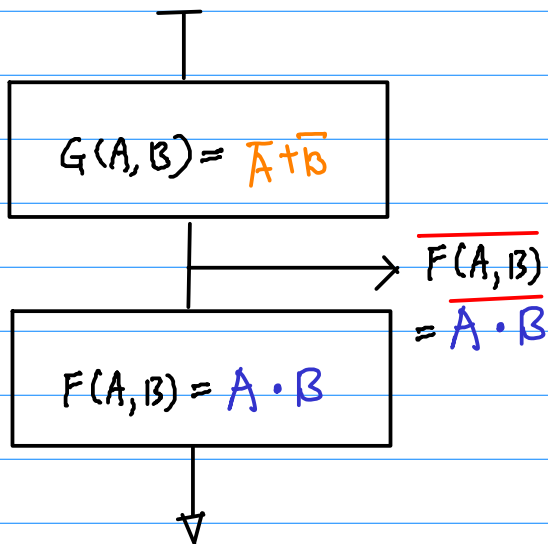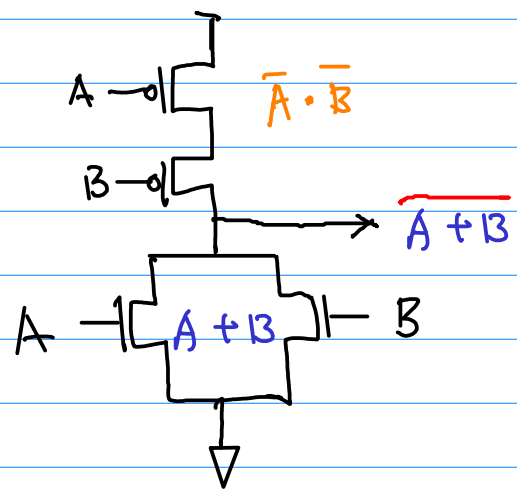

# Logic Function

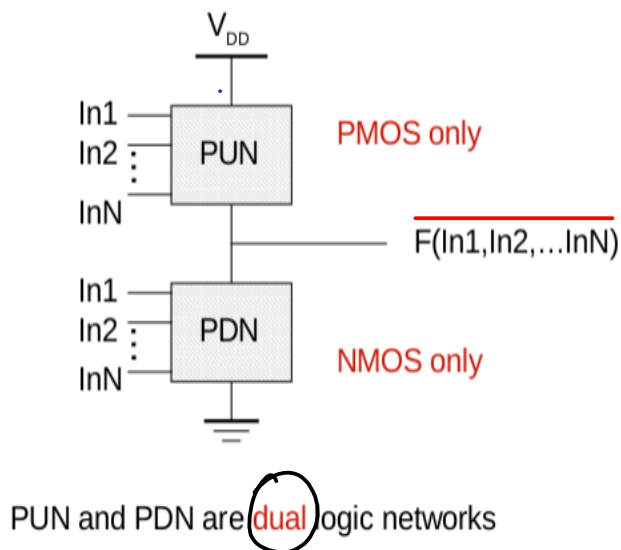


pull up Network — pMOS  
implements  $G$

pull down Network — nMOS  
implements  $\overline{F}$


$$\overline{F(in1, in2, \dots, inN)} = G(\overline{in1}, \overline{in2}, \dots, \overline{inN})$$






$$pMOS: G(\overline{in1}, \overline{in2}, \dots, \overline{inN})$$
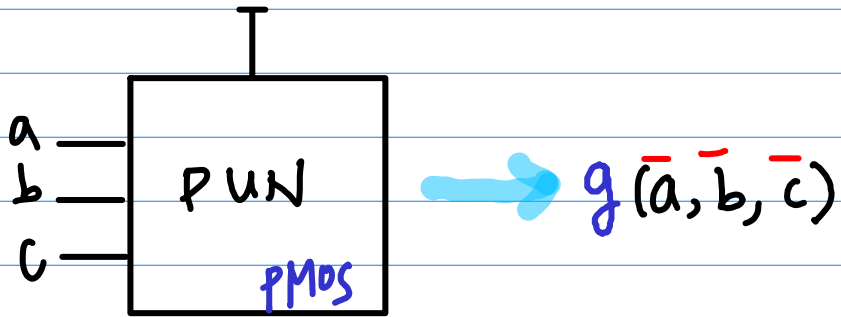
$$nMOS: \overline{F(in1, in2, \dots, inN)}$$




$\overline{f(a, b, c)}$

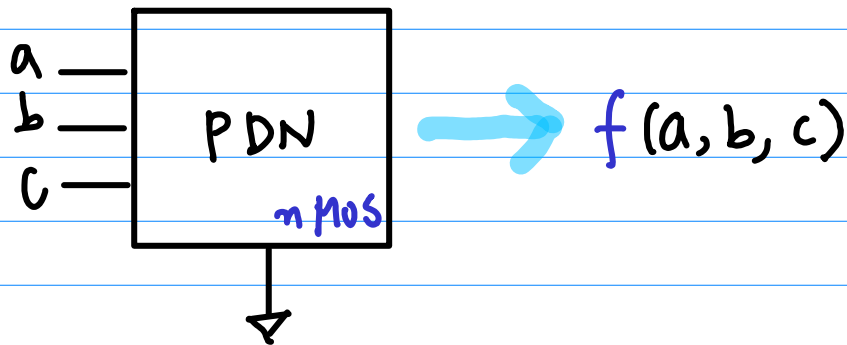

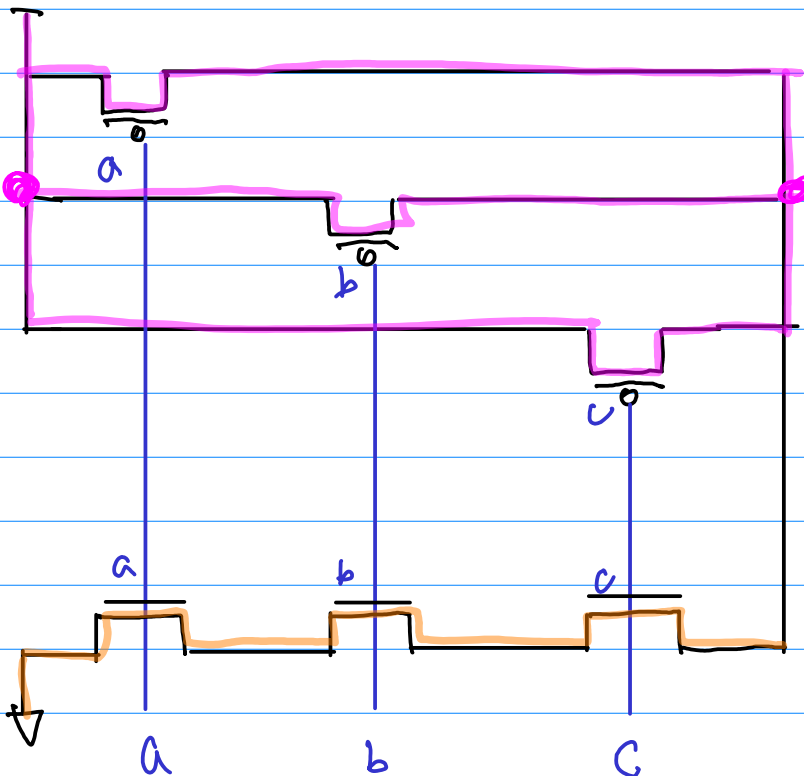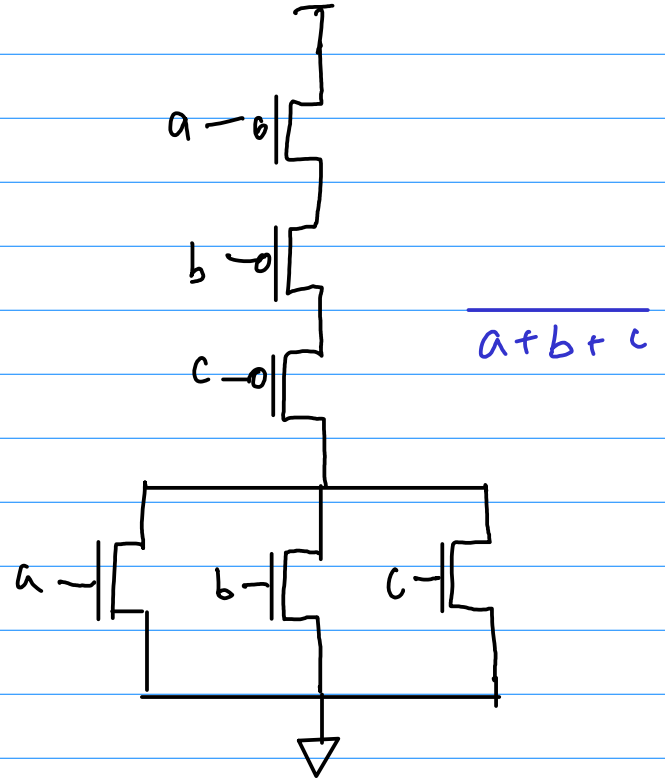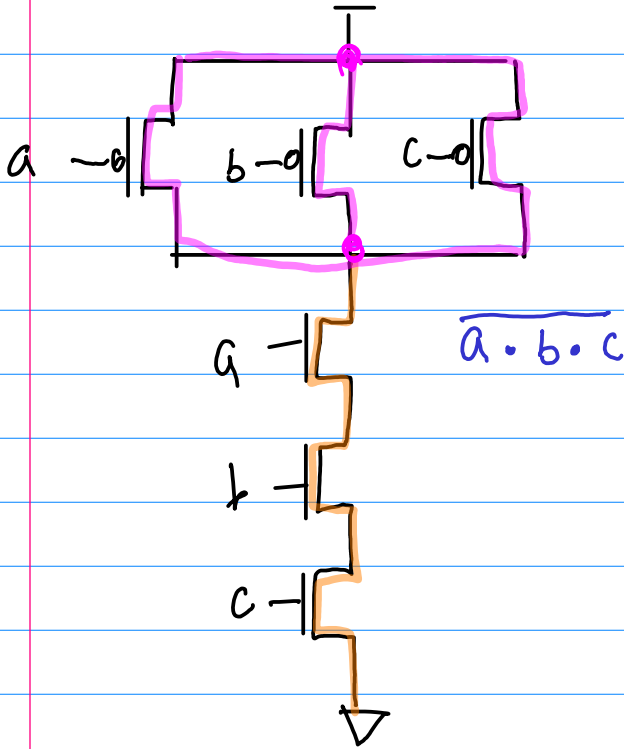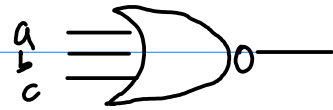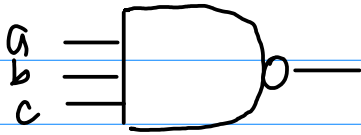

look like a  
physical layout

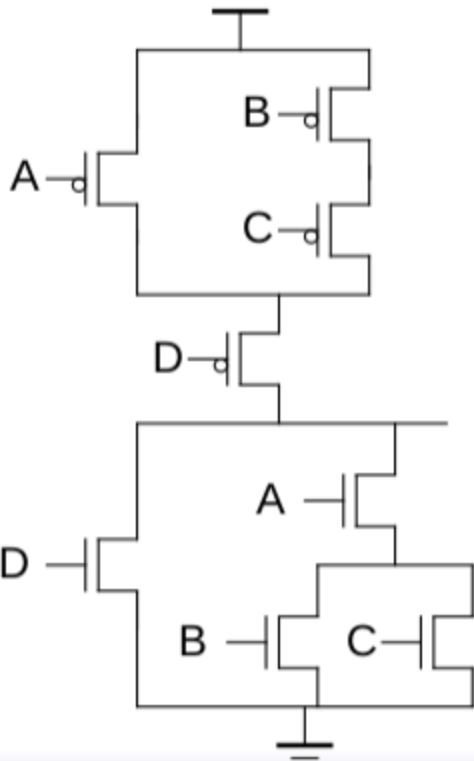


if  $(\bar{A} + (\bar{B} \cdot \bar{C})) \cdot \bar{D}$ ,  $\text{out} \Rightarrow 1$

$$(\bar{A} + (\bar{B} \cdot \bar{C})) \cdot \bar{D}$$


$$\text{OUT} = \overline{D + A \cdot (B + C)}$$

if  $D + A \cdot (B + C)$ ,  $\text{out} \Rightarrow 0$


$$D + A \cdot (B + C)$$

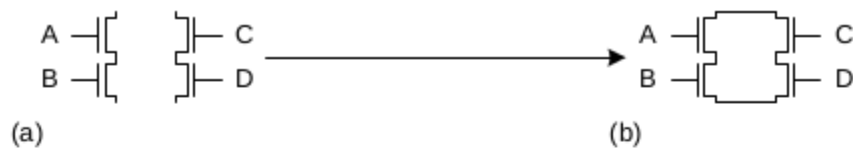

$$(A \cdot B) + (C \cdot D)$$

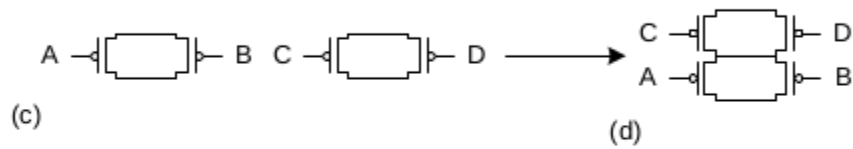

$$(C + D) \cdot (A + B)$$

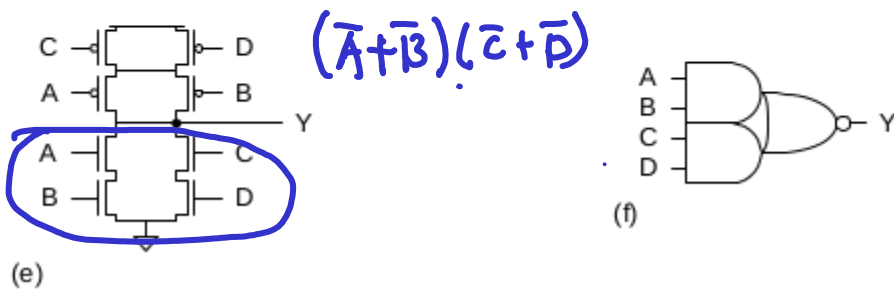

$$\underline{A \cdot B + C \cdot D}$$







$$\underline{(A \cdot B) + (C \cdot D)}$$

$$= \overline{A \cdot B} \cdot \overline{C \cdot D}$$



$$= (\bar{A} + \bar{B}) \cdot (\bar{C} + \bar{D})$$

# Finding (PUN) from (PDN)

$$OUT = \overline{D + A \cdot (B + C)}$$

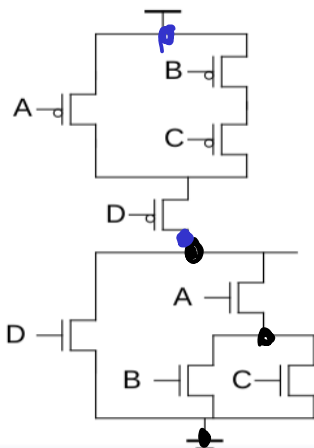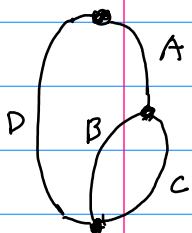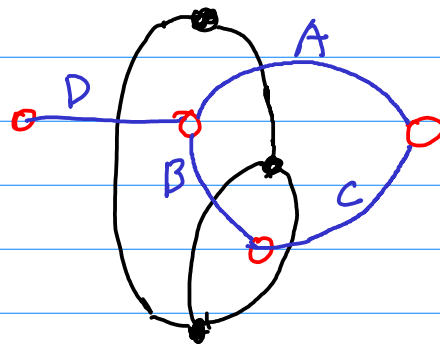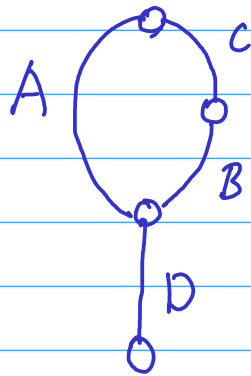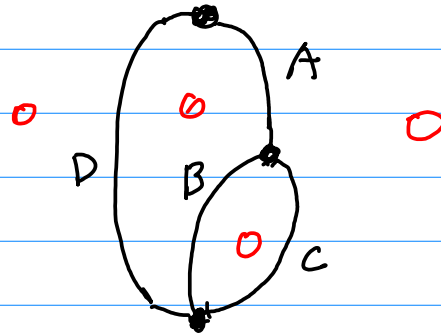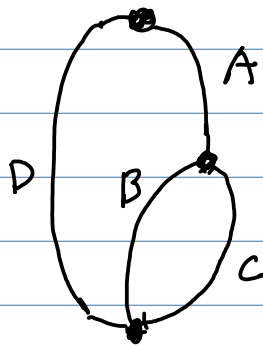









$$OUT = \overline{D + A \cdot (B + C)}$$

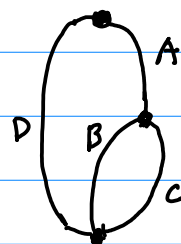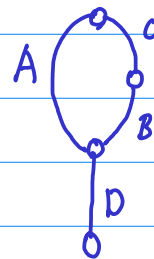

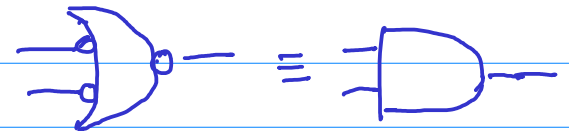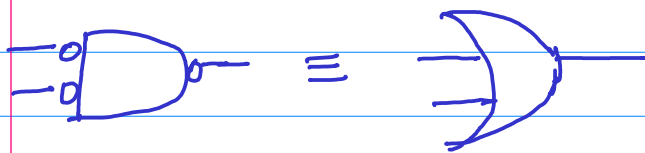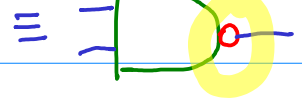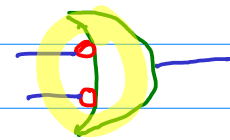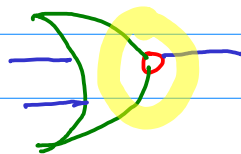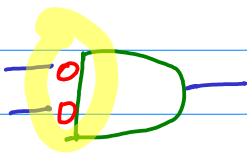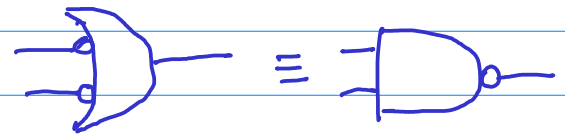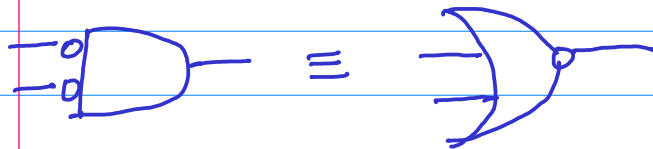
# Bubble Pushing and DeMorgan's Law


$$\overline{A} \cdot \overline{B} = \overline{(A + B)}$$

$$(\overline{A} + \overline{B}) = \overline{A \cdot B}$$










# Basic nMOS, pMOS Configurations

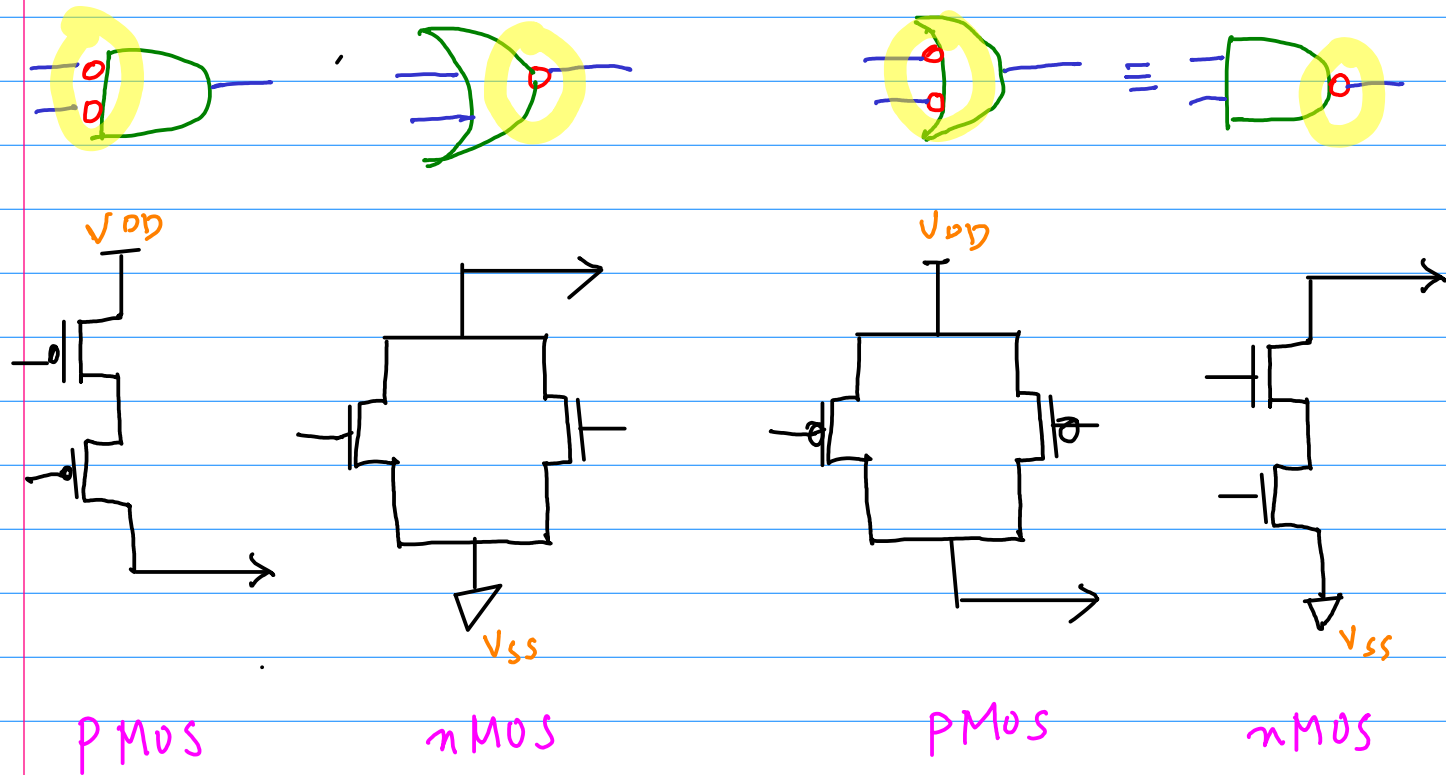






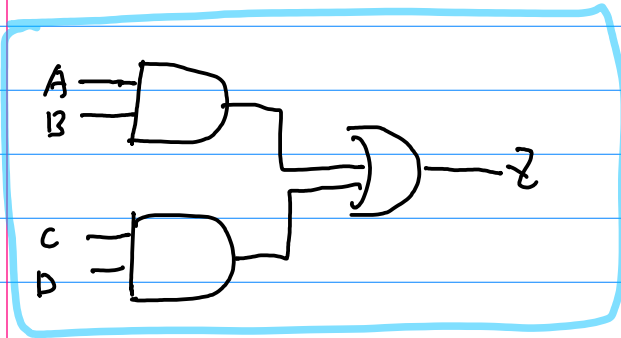



Sum of Product (SOP)

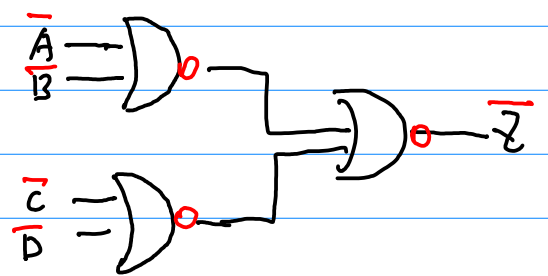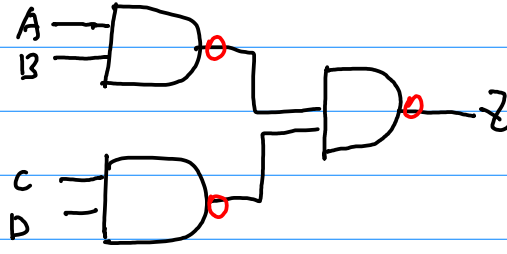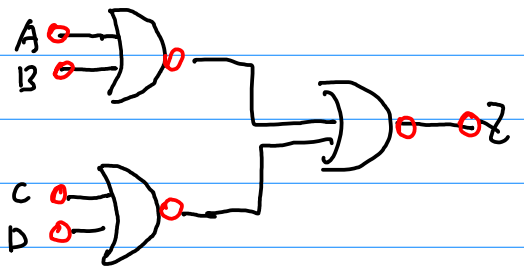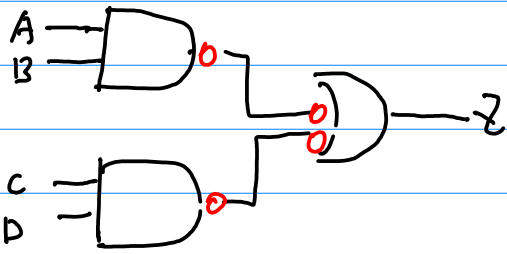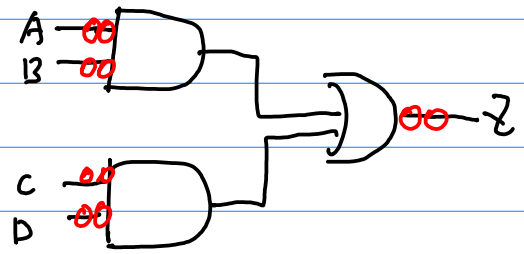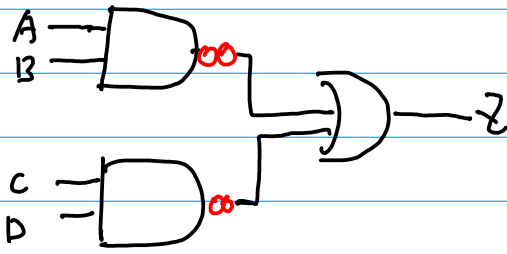

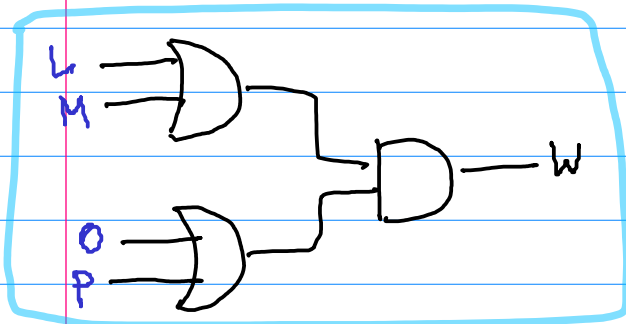


Product of Sum (POS)

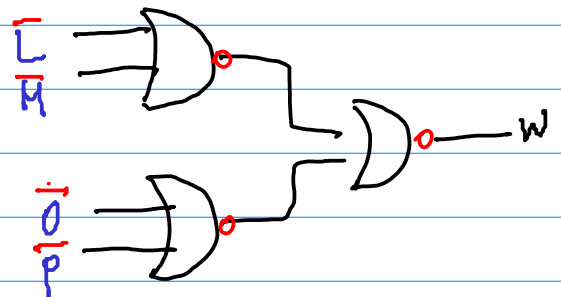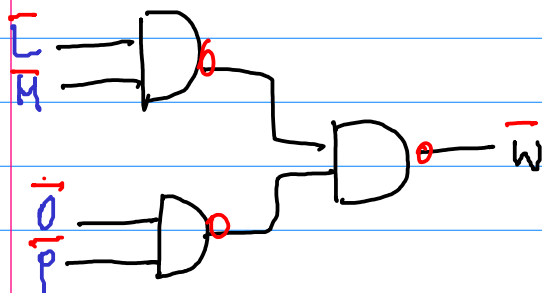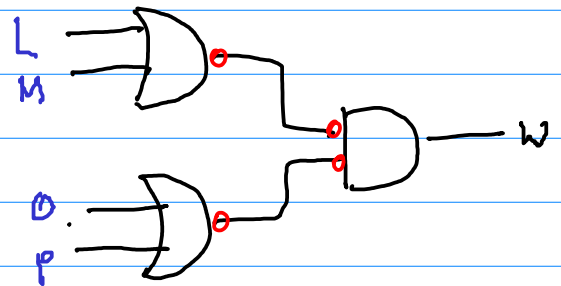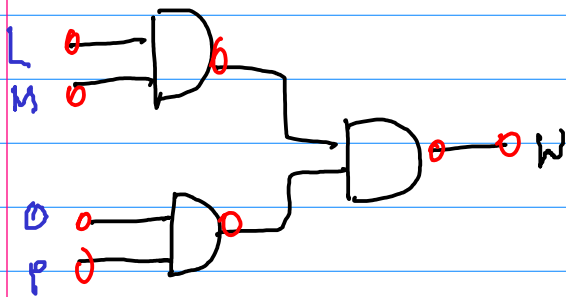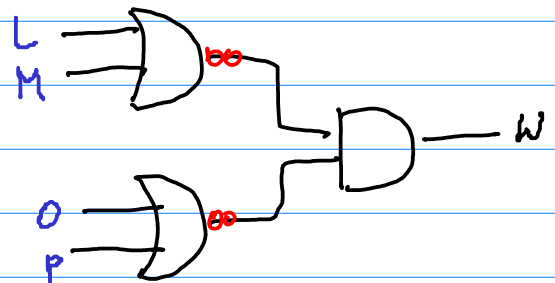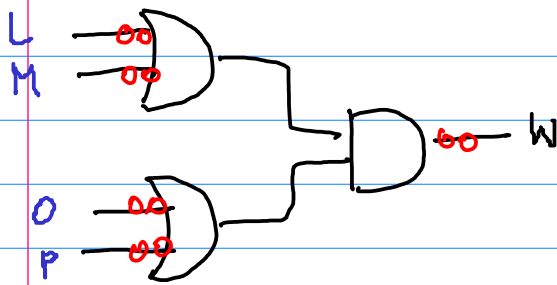


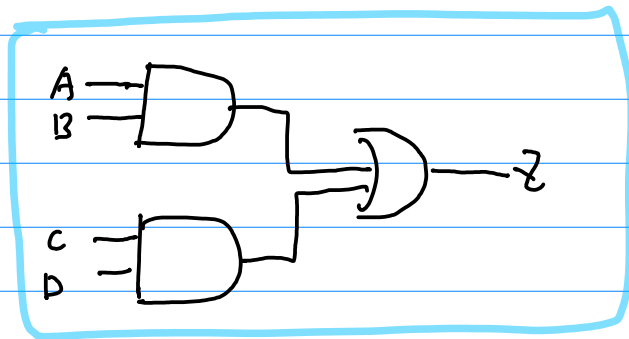


Sum of Product (SOP)

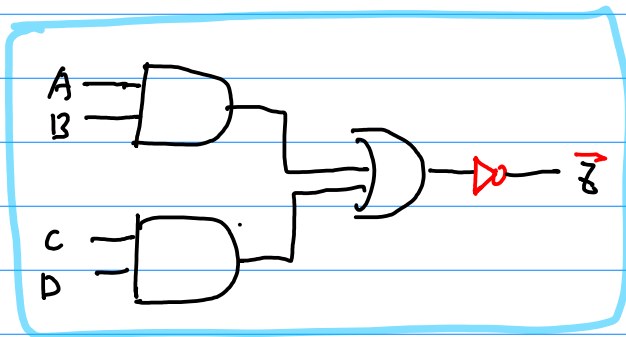

AND - OR - INV (AOI)

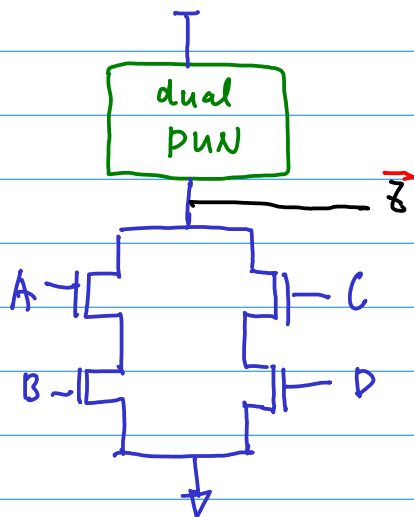


$$\overline{(A \cdot B + C \cdot D)}$$

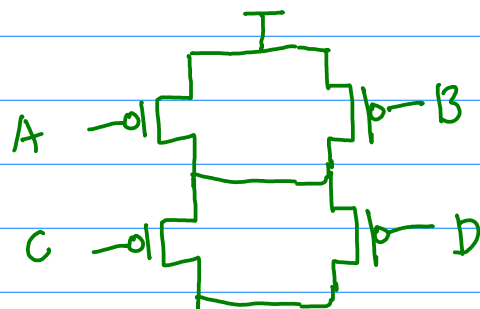


$$\overline{A \cdot B} \cdot \overline{C \cdot D}$$

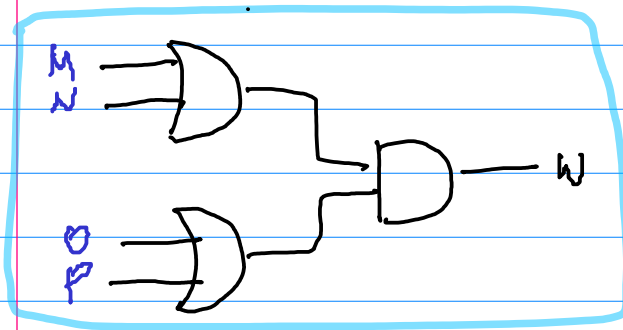
$$= (\overline{A} + \overline{B}) \cdot (\overline{C} + \overline{D})$$



Product of Sum (POS)

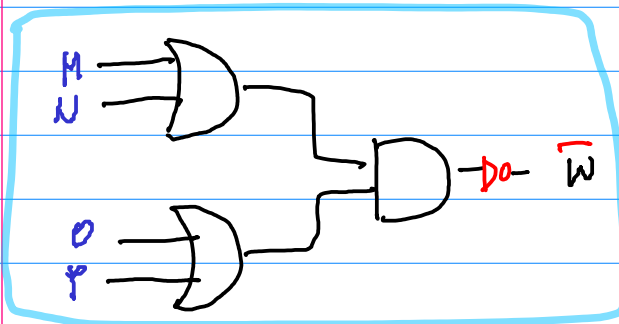


OR - AND - INV (OAI)

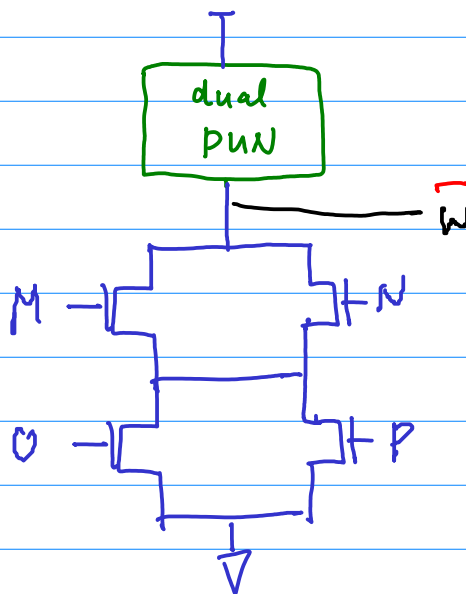


$$\overline{(M+N)(O+P)}$$
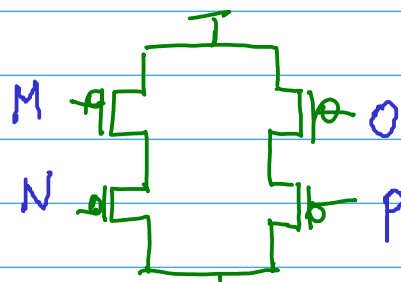
$$\begin{aligned} & \overline{(M+N)} + \overline{(O+P)} \\ &= (\overline{M} \cdot \overline{N}) + (\overline{O} \cdot \overline{P}) \end{aligned}$$




AOI , OAI

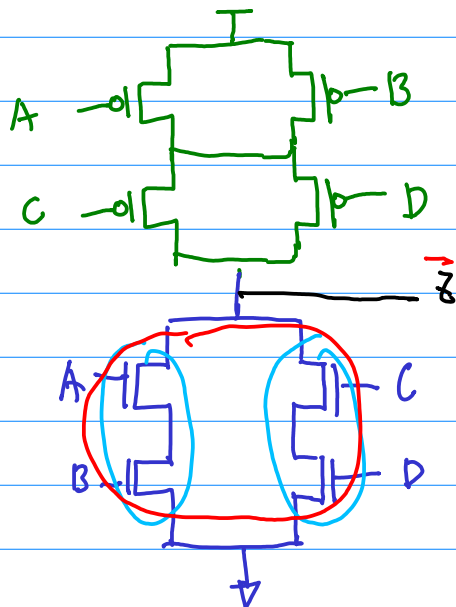

$$\overline{(A \cdot B + C \cdot D)}$$


AND - OR - INV

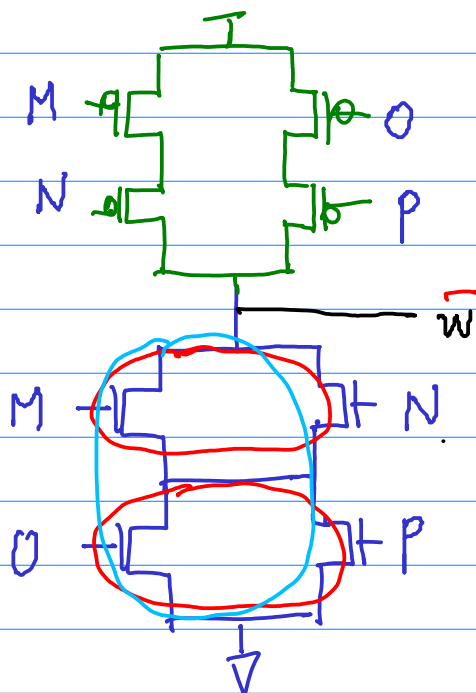

$$\overline{(M + N) \cdot (O + P)}$$

OR - AND - INV


# XNOR, XOR using AOI

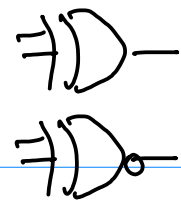

$$a \oplus b = \bar{a} \cdot b + a \bar{b}$$

$$\overline{a \oplus b} = ab + \bar{a}\bar{b}$$

XNOR  
(AOI)

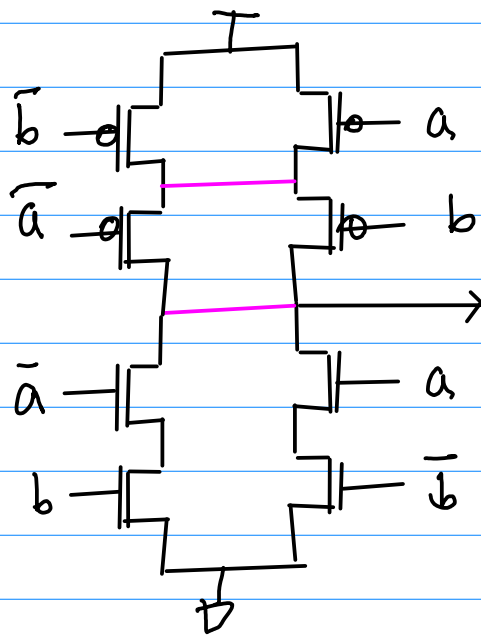

$$(a + \bar{b}) \cdot (\bar{a} + b)$$


$$= 0 + \bar{a}\bar{b} + ab + 0$$

$$= ab + \bar{a}\bar{b} = \overline{a \oplus b}$$

$$\overline{a \oplus b}$$

$$\bar{a}b + a\bar{b} = a \oplus b$$

XOR  
(AOI)

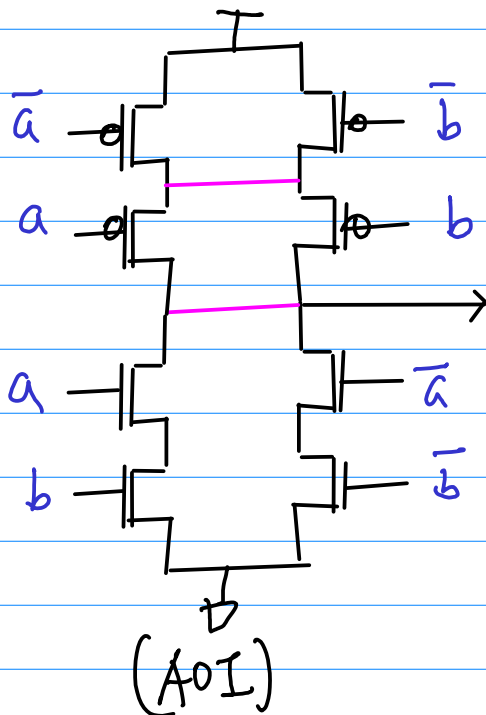

$$(\bar{a} + \bar{b}) \cdot (a + b) = \bar{a}b + \bar{a}\bar{b}$$

$$= a \oplus b$$

$$\overline{a \oplus b}$$


$$ab + \bar{a}\bar{b} = \overline{a \oplus b}$$

# XNOR, XOR using OAI

$$a \oplus b = \bar{a} \cdot b + a \bar{b}$$

$$\overline{a \oplus b} = ab + \bar{a}\bar{b}$$

XNOR  
(OAI)

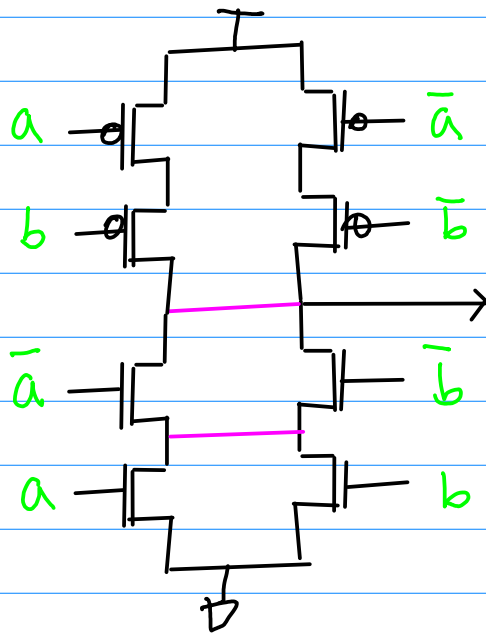


$$ab + \bar{a}\bar{b} = \overline{a \oplus b}$$

$$\overline{a \oplus b}$$

$$(\bar{a} + \bar{b}) \cdot (a + b)$$

$$= a\bar{b} + \bar{a}b = a \oplus b$$

XOR  
(OAI)

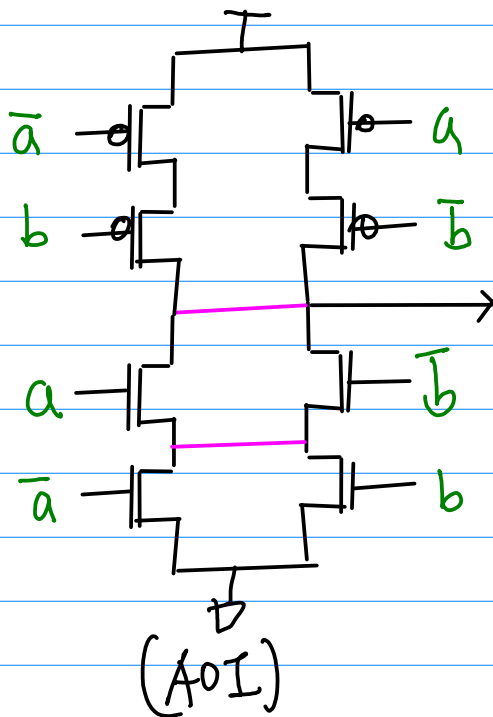

$$\bar{a}b + a\bar{b} = a \oplus b$$


$$\overline{a \oplus b}$$

$$(a + \bar{b}) \cdot (\bar{a} + b)$$

$$= ab + \bar{a}\bar{b} = \overline{a \oplus b}$$

\* Which one is better?

XNOR  
(AOI)

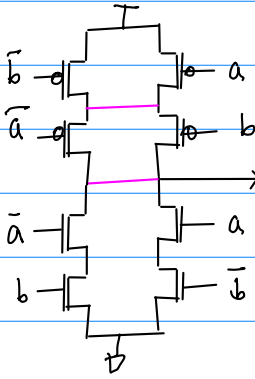

$$(a + \bar{b}) \cdot (\bar{a} + b)$$


$$= 0 + \bar{a}\bar{b} + a\bar{b} + 0$$

$$= a\bar{b} + \bar{a}\bar{b} = \overline{a \oplus b}$$

$$\overline{a \oplus b}$$

$$\bar{a}b + a\bar{b} = a \oplus b$$

XNOR  
(OAI)

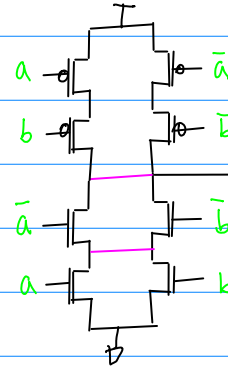


$$ab + \bar{a}\bar{b} = \overline{a \oplus b}$$

$$(\bar{a} + \bar{b}) \cdot (a + b)$$

$$= a\bar{b} + \bar{a}b = a \oplus b$$

XOR  
(AOI)

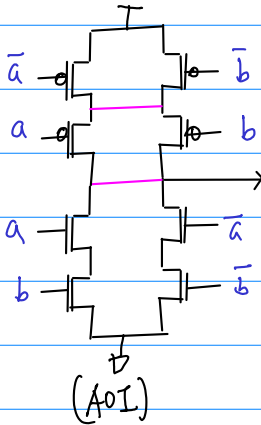


$$(\bar{a} + \bar{b}) \cdot (a + b) = a\bar{b} + \bar{a}b$$

$$= a \oplus b$$

$$\overline{a \oplus b}$$

$$ab + \bar{a}\bar{b} = \overline{a \oplus b}$$

XOR  
(OAI)

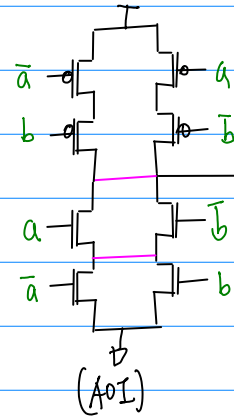


$$\bar{a}b + a\bar{b} = a \oplus b$$

$$(a + \bar{b}) \cdot (\bar{a} + b)$$

$$= a\bar{b} + \bar{a}b = \overline{a \oplus b}$$

# XNOR, XOR using PG

XNOR  
(PG)

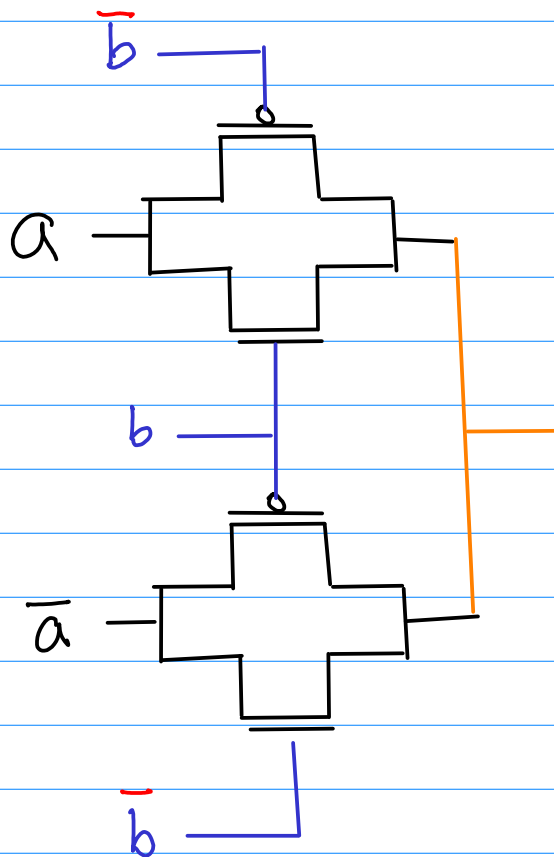


pass a if b

$$ab + \bar{a}\bar{b} = \overline{a \oplus b}$$

pass  $\bar{a}$  if  $\bar{b}$

XOR  
(PG)

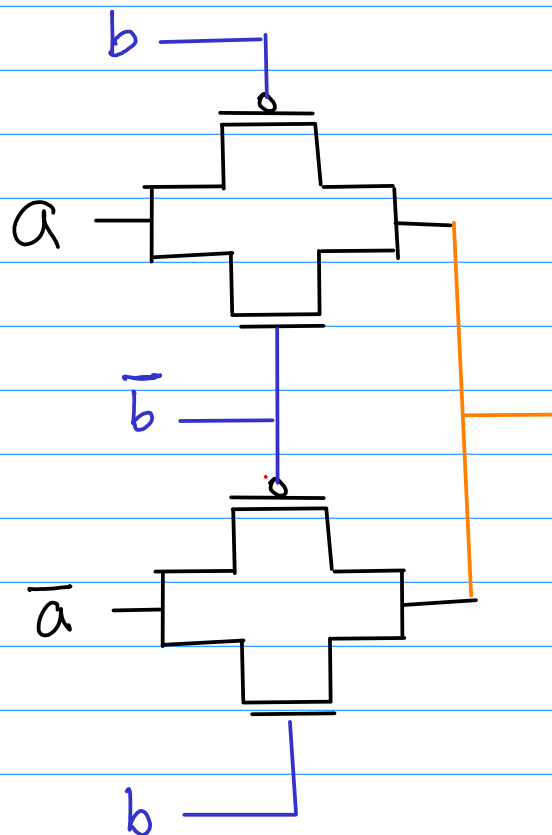


pass a if  $\bar{b}$

$$a\bar{b} + \bar{a}b = a \oplus b$$

pass  $\bar{a}$  if b

# minterm, Maxterm

## Boolean Function with minterms (1)

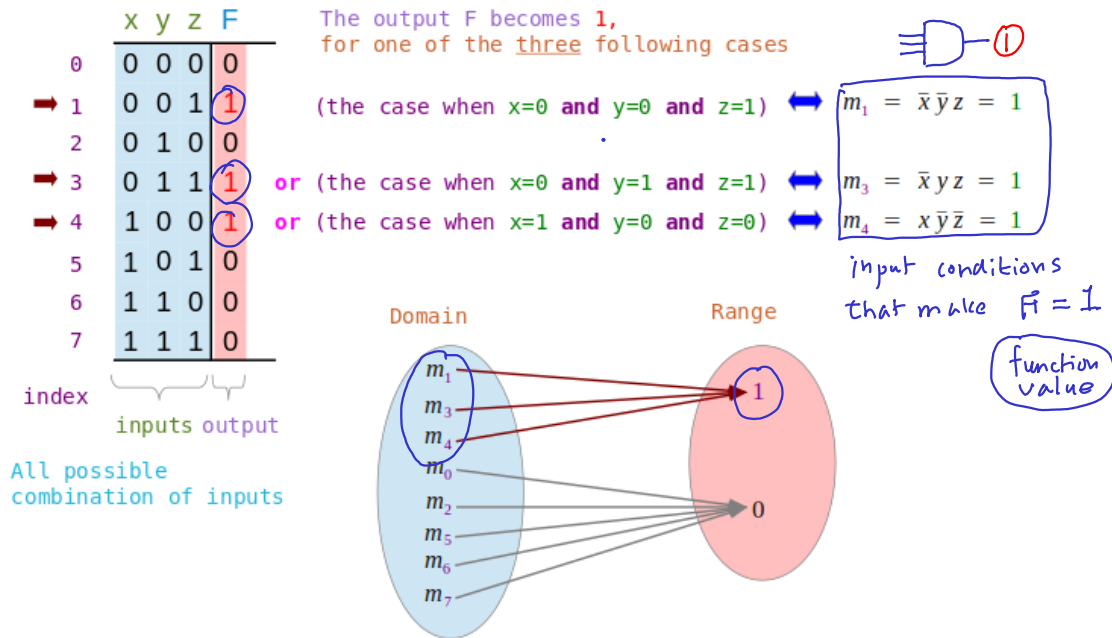


Truth Table (2A)

9

Young Won Lim  
9/18/13

## Boolean Function with Maxterms (1)

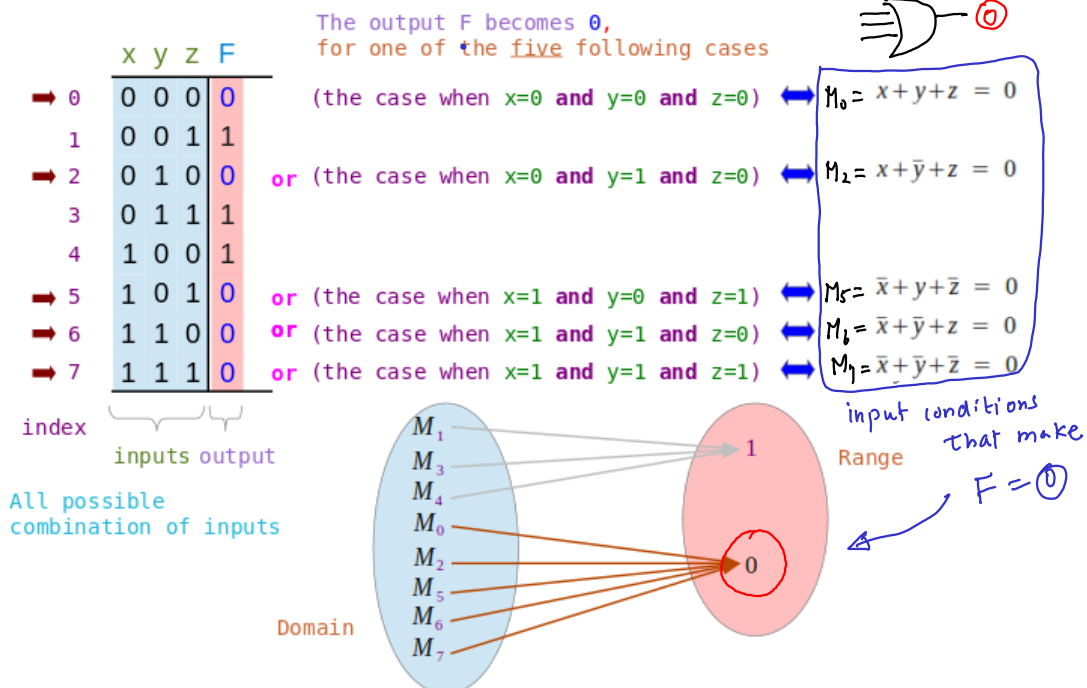

Truth Table (2A)

12

Young Won Lim  
9/18/13

# AOI, OAI using minterm, Maxterm

## Complimentary Relations

|   | x | y | z | F |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 2 | 0 | 1 | 0 | 0 |
| 3 | 0 | 1 | 1 | 1 |
| 4 | 1 | 0 | 0 | 1 |
| 5 | 1 | 0 | 1 | 0 |
| 6 | 1 | 1 | 0 | 0 |
| 7 | 1 | 1 | 1 | 0 |

index      inputs      output

All possible combination of inputs

$$m_i = \overline{M}_i$$

$$M_i = \overline{m}_i$$

$$F(x, y, z) = m_1 + m_3 + m_4$$

The output F becomes 1,  
either  $m_1=1$  or  $m_3=1$  or  $m_4=1$

For the output of an **or** gate to be 1,  
at least one must be 1

$$\overline{F}(x, y, z) = \overline{m}_0 + \overline{m}_2 + \overline{m}_5 + \overline{m}_6 + \overline{m}_7 \rightarrow \text{nMOS}$$

$$\Leftrightarrow F(x, y, z) = m_0 + m_2 + m_5 + m_6 + m_7$$

$$= \overline{m}_0 \cdot \overline{m}_2 \cdot \overline{m}_5 \cdot \overline{m}_6 \cdot \overline{m}_7 \rightarrow \text{pMOS}$$

$$F(x, y, z) = M_0 \cdot M_2 \cdot M_5 \cdot M_6 \cdot M_7$$

The output F becomes 0,  
either  $M_0=0$  or  $M_2=0$  or  $M_5=0$  or  $M_6=0$  or  $M_7=0$

For the output of an **and** gate to be 0,  
at least one input must be 0

AOI

Truth Table (2A)

15

Young Won Lim  
9/18/13

## Boolean Function Summary

|   | x | y | z | F |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 2 | 0 | 1 | 0 | 0 |
| 3 | 0 | 1 | 1 | 1 |
| 4 | 1 | 0 | 0 | 1 |
| 5 | 1 | 0 | 1 | 0 |
| 6 | 1 | 1 | 0 | 0 |
| 7 | 1 | 1 | 1 | 0 |

The output F becomes 1,

for the cases

1) when  $m_1=1$  or  $m_3=1$  or  $m_4=1$

$$F(x, y, z) = m_1 + m_3 + m_4 \Rightarrow F=1$$

2) when  $M_1=0$  or  $M_3=0$  or  $M_4=0$

$$\overline{F}(x, y, z) = M_1 \cdot M_3 \cdot M_4 \Rightarrow F=1 (\overline{F}=0)$$

pMOS

nMOS OAI

|   | x | y | z | F |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 2 | 0 | 1 | 0 | 0 |
| 3 | 0 | 1 | 1 | 1 |
| 4 | 1 | 0 | 0 | 1 |
| 5 | 1 | 0 | 1 | 0 |
| 6 | 1 | 1 | 0 | 0 |
| 7 | 1 | 1 | 1 | 0 |

The output F becomes 0,

for the cases

1) when  $m_0=1$  or  $m_2=1$  or  $m_5=1$  or  $m_6=1$  or  $m_7=1$

$$\overline{F}(x, y, z) = m_0 + m_2 + m_5 + m_6 + m_7 \Rightarrow F=0 (\overline{F}=1)$$

2) when  $M_0=0$  or  $M_2=0$  or  $M_5=0$  or  $M_6=0$  or  $M_7=0$

$$F(x, y, z) = M_0 \cdot M_2 \cdot M_5 \cdot M_6 \cdot M_7 \Rightarrow F=0$$

nMOS AOI

pMOS


Truth Table (2A)

16

Young Won Lim  
9/18/13

$$m_1 + m_3 + m_4 = \bar{F}$$
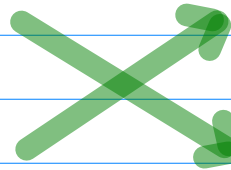
$$m_0 + m_2 + m_5 + m_6 + m_7 = \bar{F}$$



$$M_0 \cdot M_2 \cdot M_5 \cdot M_6 \cdot M_7 = F$$

$$M_1 \cdot M_3 \cdot M_4 = \bar{F}$$

( $\bar{F}$ )

$$m_1 + m_3 + m_4 = \boxed{1} = F$$

$$(m_1=1) \vee (m_3=1) \vee (m_4=1) \Leftrightarrow F=1$$

$$M_0 \cdot M_2 \cdot M_5 \cdot M_6 \cdot M_7 = \boxed{0} = F$$

$$(M_0=0) \wedge (M_2=0) \wedge (M_5=0) \wedge (M_6=0) \wedge (M_7=0) \Leftrightarrow F=0$$

( $\bar{F}$ )

$$m_0 + m_2 + m_5 + m_6 + m_7 = \boxed{1} = \bar{F}$$

$$(m_0=1) \vee (m_2=1) \vee (m_5=1) \vee (m_6=1) \vee (m_7=1) \Leftrightarrow F=0$$

$$M_1 \cdot M_3 \cdot M_4 = \boxed{0} = \bar{F}$$

$$(M_1=0) \wedge (M_3=0) \wedge (M_4=0) \Leftrightarrow F=1$$

$$\equiv D^{-1}$$

$$\equiv D^0$$




$$m_1 + m_3 + m_4 = \bar{F}$$

$$M_0 \cdot M_2 \cdot M_5 \cdot M_6 \cdot M_7 = F$$

$$m_0 + m_2 + m_5 + m_6 + m_7 = \bar{F}$$

$$M_1 \cdot M_3 \cdot M_4 = \bar{F}$$

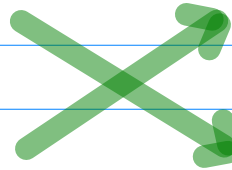



(F)

$$m_1 + m_3 + m_4 = \underline{1} = F$$

$$M_0 \cdot M_2 \cdot M_5 \cdot M_6 \cdot M_7 = \underline{0} = F$$



$$(m_1=1) \vee (m_3=1) \vee (m_4=1) \Leftrightarrow F=1$$
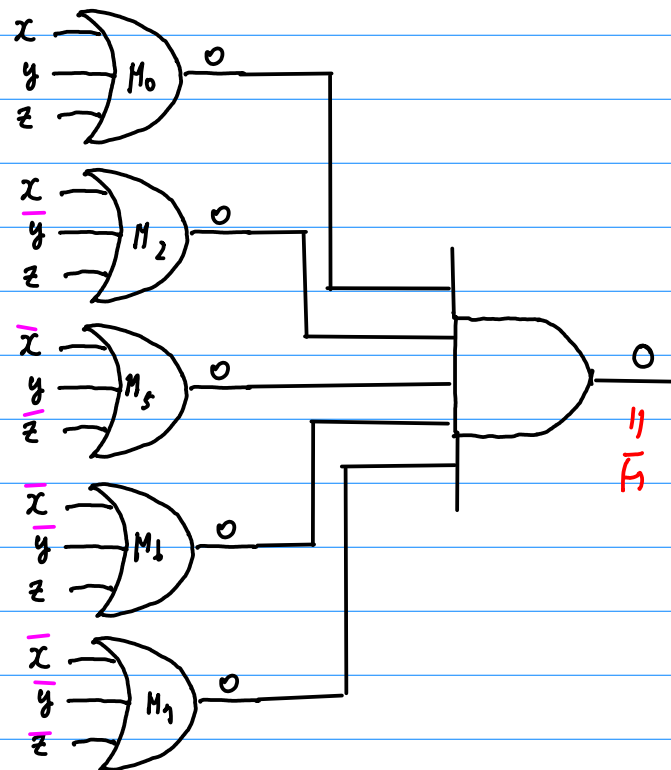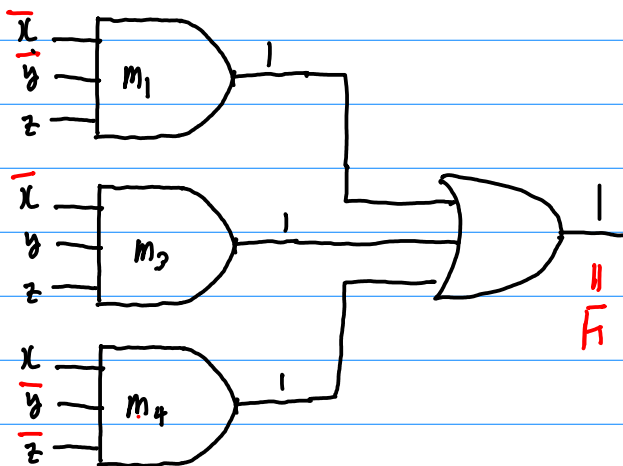
$$(M_0=0) \wedge (M_2=0) \wedge (M_5=0) \wedge (M_6=0) \wedge (M_7=0) \Leftrightarrow F=0$$



(F)

|   | x | y | z | $x+y+z$ | $x+\overline{y}+z$ | $\overline{x}+y+\overline{z}$ | $\overline{x}+\overline{y}+z$ | $\overline{x}+y+\overline{\overline{z}}$ |
|---|---|---|---|---------|--------------------|-------------------------------|-------------------------------|------------------------------------------|
| 0 | 0 | 0 | 0 | 0       | 1                  | 1                             | 1                             | 1                                        |
| 1 | 0 | 0 | 1 | 1       | 1                  | 1                             | 1                             | 1                                        |
| 2 | 0 | 1 | 0 | 1       | 0                  | 1                             | 1                             | 1                                        |
| 3 | 0 | 1 | 1 | 1       | 1                  | 1                             | 1                             | 1                                        |
| 4 | 1 | 0 | 0 | 1       | 1                  | 1                             | 1                             | 1                                        |
| 5 | 1 | 0 | 1 | 1       | 1                  | 0                             | 1                             | 1                                        |
| 6 | 1 | 1 | 0 | 1       | 1                  | 1                             | 0                             | 1                                        |
| 7 | 1 | 1 | 1 | 1       | 1                  | 1                             | 1                             | 0                                        |

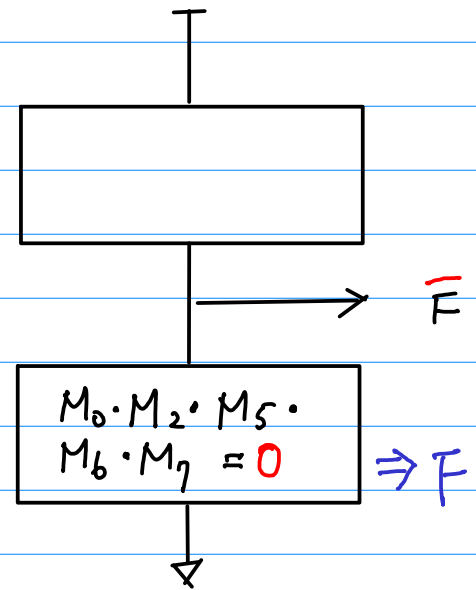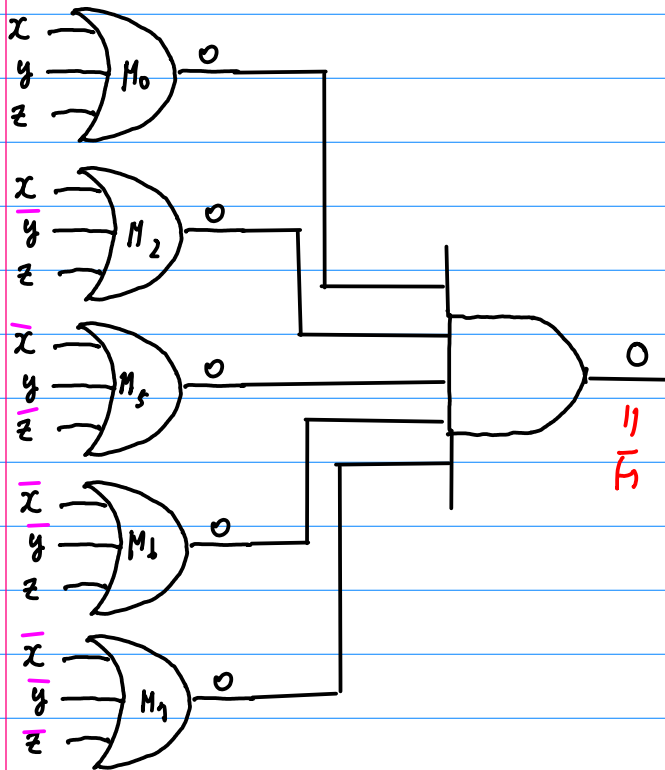

$$m_1 + m_3 + m_4 = F$$

$$M_0 \cdot M_2 \cdot M_5 \cdot M_6 \cdot M_7 = F$$

$$\rightarrow m_0 + m_2 + m_5 + m_6 + m_7 = \overline{F}$$

$$M_1 \cdot M_3 \cdot M_4 = \overline{F}$$


$\overline{F}$

$$m_0 + m_2 + m_5 + m_6 + m_7 = 1 = \overline{F}$$


$$M_1 \cdot M_3 \cdot M_4 = 0 = \overline{F}$$

$$(m_0=1) \vee (m_2=1) \vee (m_5=1) \vee (m_6=1) \vee (m_7=1) \Leftrightarrow F=0$$
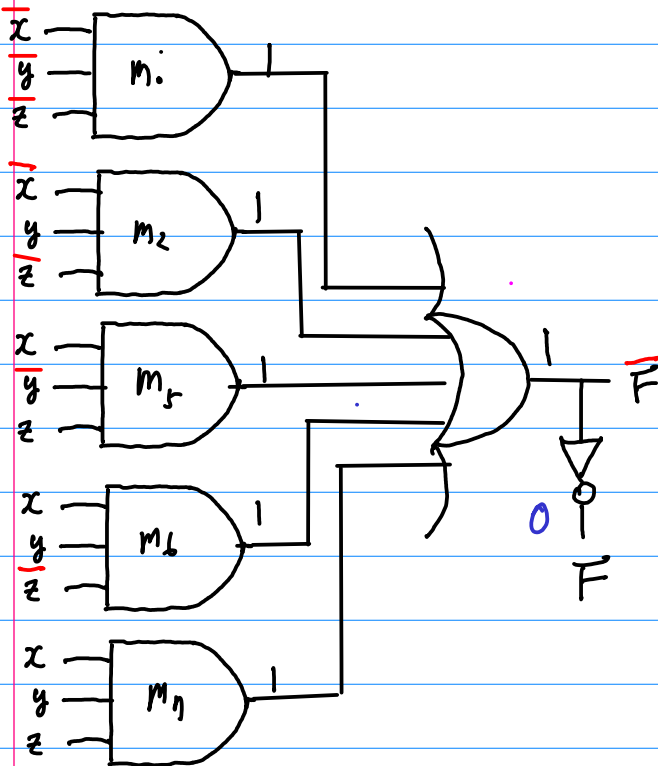
$$(M_1=0) \wedge (M_3=0) \wedge (M_4=0) \Leftrightarrow F=1$$




AOI

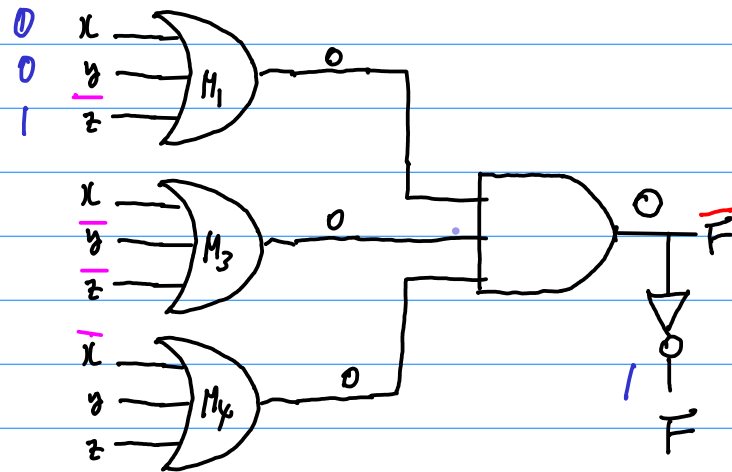

OAI


$\overline{F}$

|   | x | y | z | $x+y+\bar{z}$ | $x+\bar{y}+\bar{z}$ | $\bar{x}+y+z$ |
|---|---|---|---|---------------|---------------------|---------------|
| 0 | 0 | 0 | 0 | 1             | 1                   | 1             |
| ① | 0 | 0 | 1 | 0             | 1                   | 1             |
| 2 | 0 | 1 | 0 | 1             | 1                   | 1             |
| ③ | 0 | 1 | 1 | 1             | 0                   | 1             |
| ④ | 1 | 0 | 0 | 1             | 1                   | 0             |
| 5 | 1 | 0 | 1 | 1             | 1                   | 1             |
| 6 | 1 | 1 | 0 | 1             | 1                   | 1             |
| 7 | 1 | 1 | 1 | 1             | 1                   | 1             |

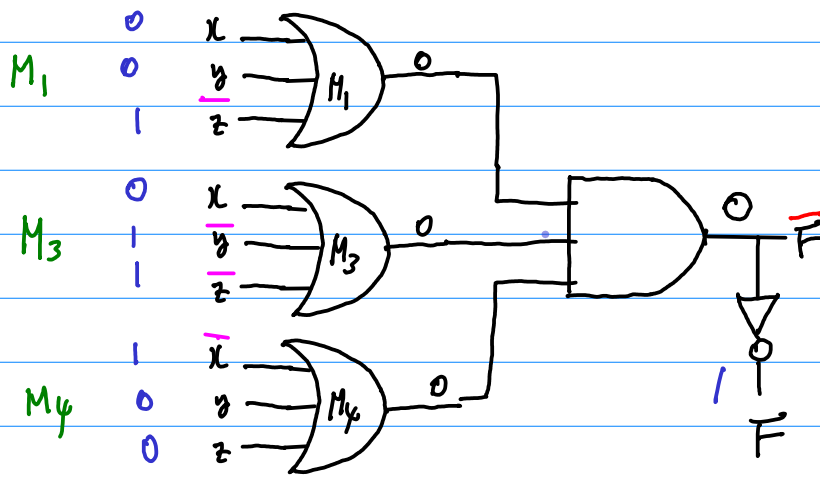





$$m_1 + m_3 + m_4 = F$$
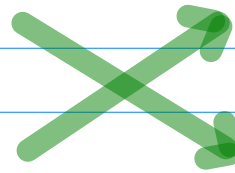
$$m_0 + m_2 + m_5 + m_6 + m_7 = \overline{F}$$





$$M_0 \cdot M_2 \cdot M_5 \cdot M_6 \cdot M_7 = F$$
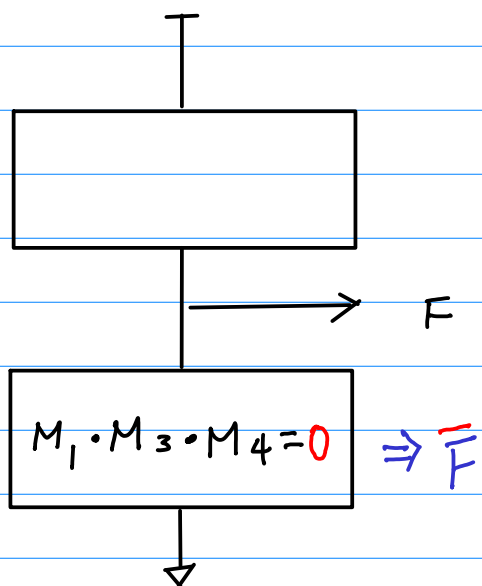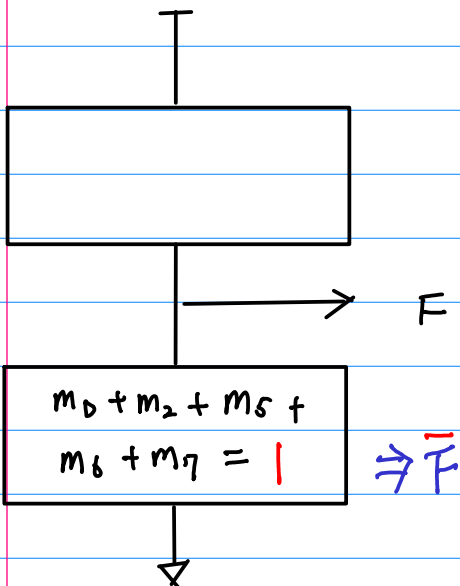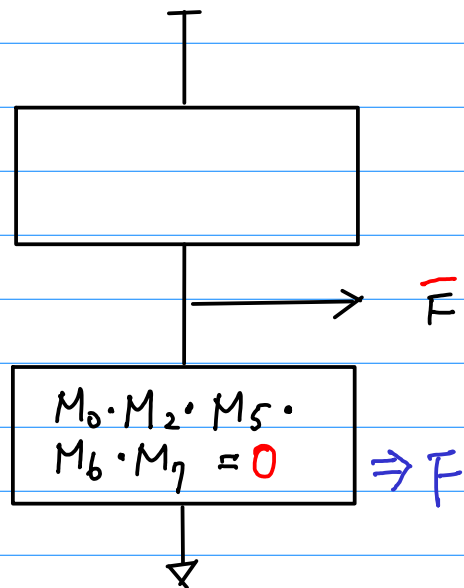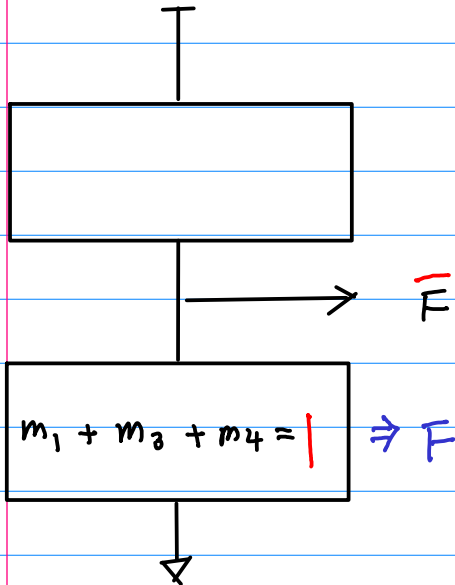
$$M_1 \cdot M_3 \cdot M_4 = \overline{F}$$



$$F(x, y, z) = m_1 + m_3 + m_4$$
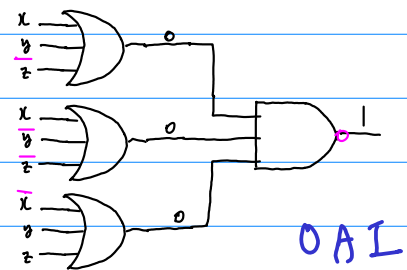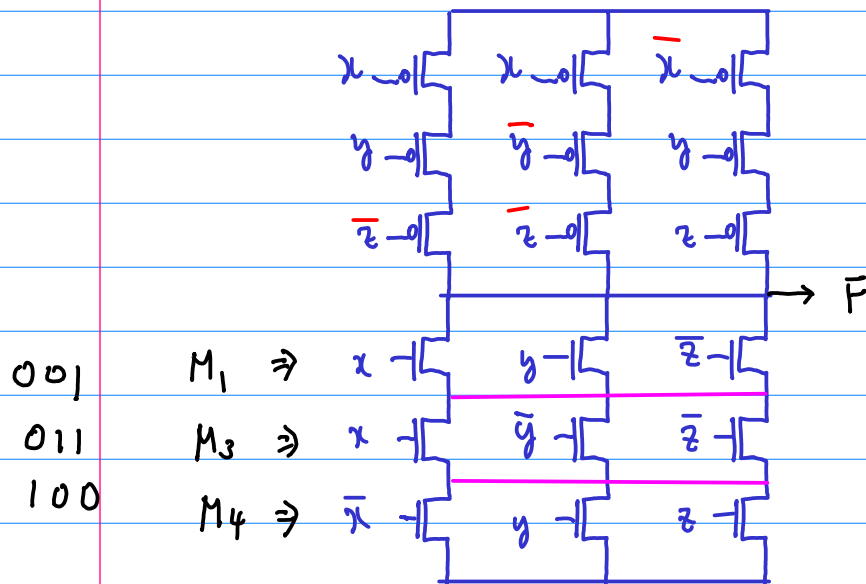
$$= \bar{x}\bar{y}z + \bar{x}y\bar{z} + x\bar{y}\bar{z}$$





$\bar{F}(x, y, z) = M_1 \cdot M_3 \cdot M_4$

$$(x + y + \bar{z})(x + \bar{y} + \bar{z})(\bar{x} + y + \bar{z})$$

smaller

$$F(x, y, z) = M_0 \cdot M_2 \cdot M_5 \cdot M_6 \cdot M_7$$

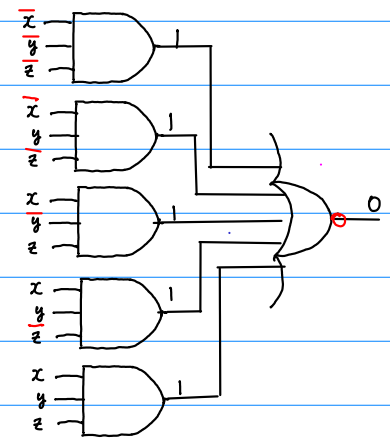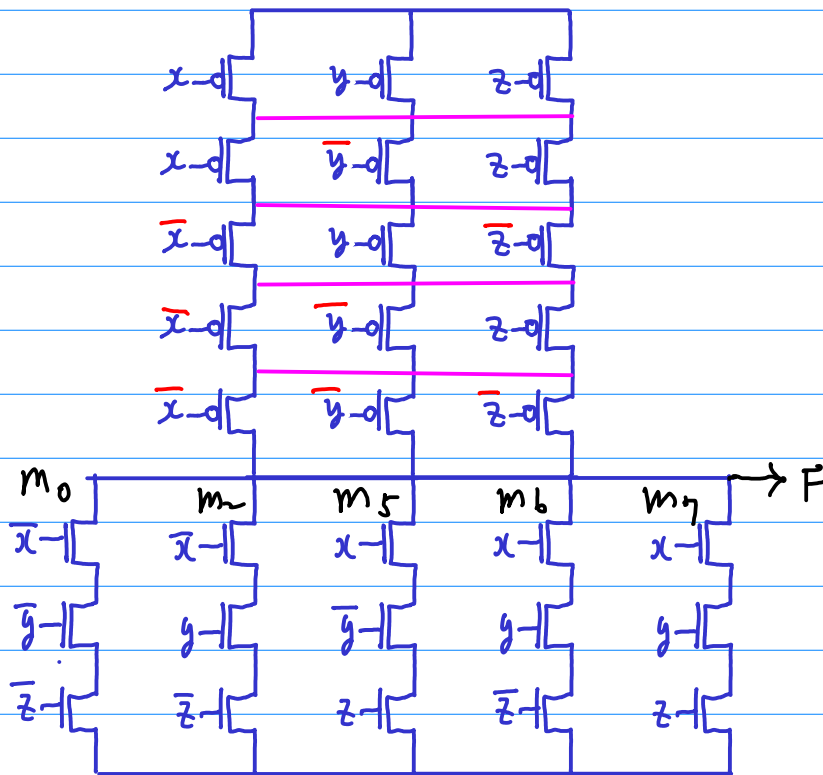
$$= (x+y+z)(x+\bar{y}+z)(\bar{x}+y+\bar{z})(\bar{x}+\bar{y}+z)(\bar{x}+\bar{y}+\bar{z})$$




$$\begin{aligned} \bar{F}(x, y, z) &= m_0 + m_2 + m_5 + m_6 + m_7 \\ &= \bar{x}\bar{y}\bar{z} + \bar{x}y\bar{z} + x\bar{y}\bar{z} + x\bar{y}z + x\bar{y}z \end{aligned}$$

AOT

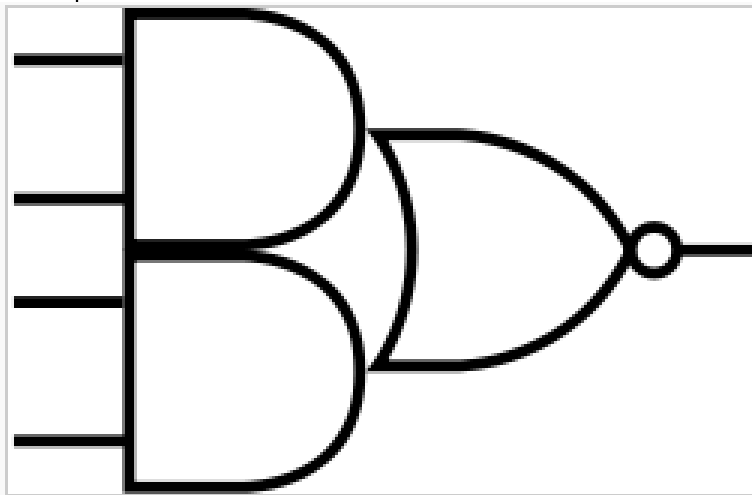
\* depend on the number of '1's in the truth table.



2-2 AOI Symbol


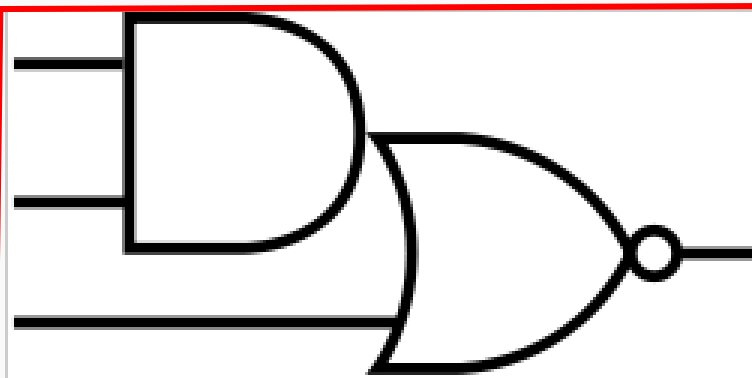


2-1 AOI Symbol

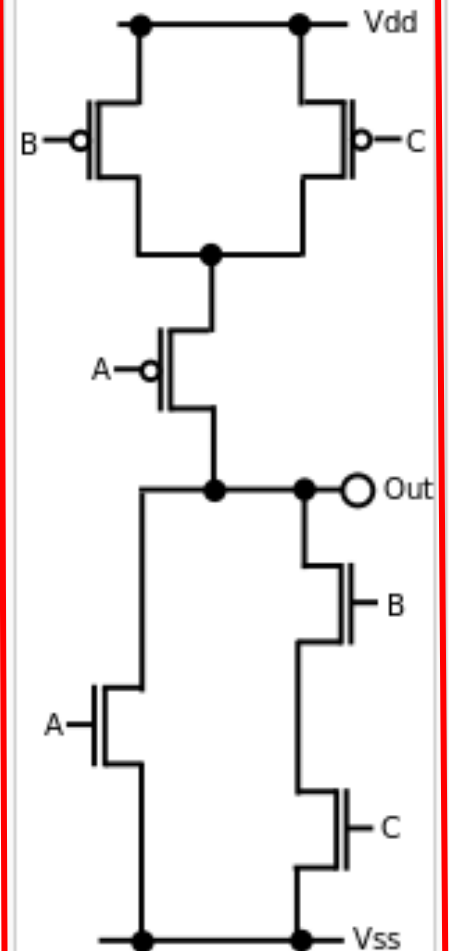


CMOS  
implementation of a  
2-1 AOI gate

$$4 + 2 + 4 = 8$$

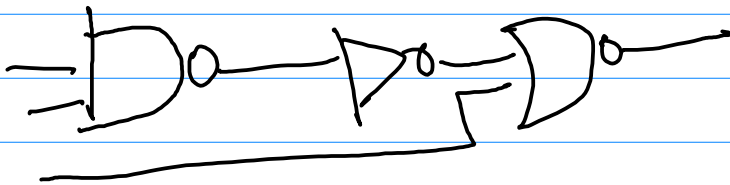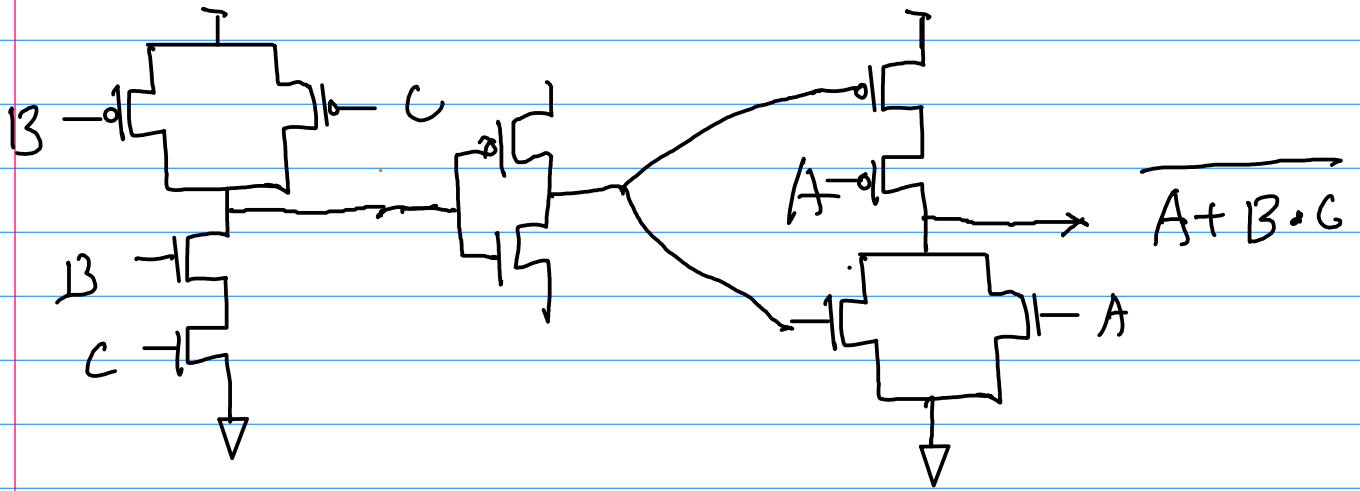

6

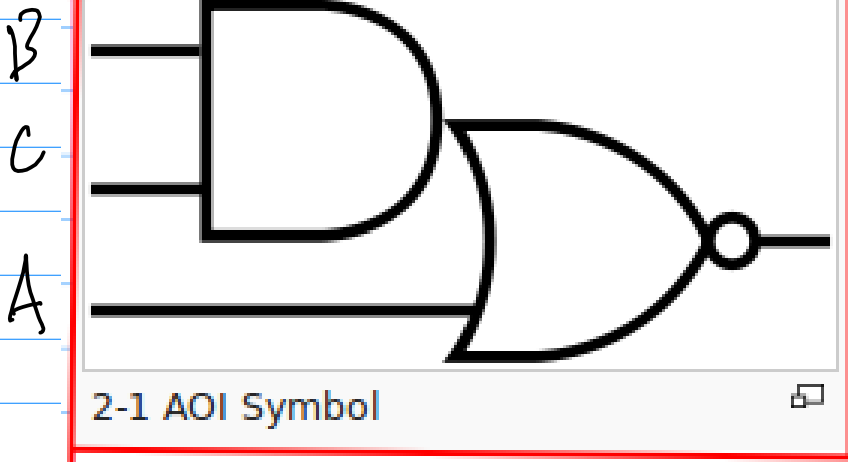

also included  
in a standard  
cell library

