

CMOS Combi-3 (H.3)

20151111

Copyright (c) 2015 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

References

Some Figures from the following sites

[1] <http://pages.hmc.edu/harris/cmosvlsi/4e/index.html>

Weste & Harris Book Site

[2] en.wikipedia.org

[3] Digital Integrated Circuits : A Design Perspective,

Jan M. Rabaey,

(<http://bwracs.eecs.berkeley.edu/Courses/lcBook/>)

[4] Digital Electronics and Design with VHDL

Pedroni

Cell Design

□ Standard Cells


- General purpose logic
- Can be synthesized
- Same height, varying width

□ Datapath Cells

- For regular, structured designs (arithmetic)
- Includes some wiring in the cell
- Fixed height and width




Standard Cell Layout Methodology – 1980s

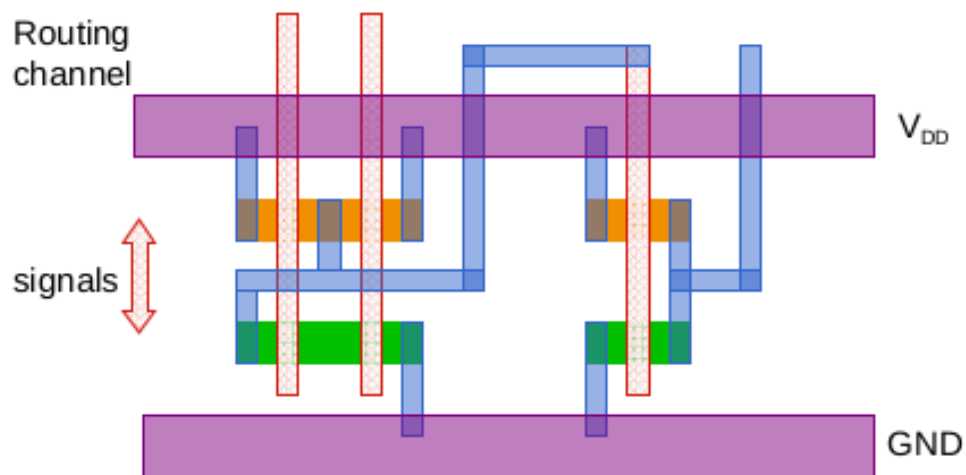

© Digital Integrated Circuits^{2nd}

Combinational Circuits


Standard Cell Layout Methodology – 1990s

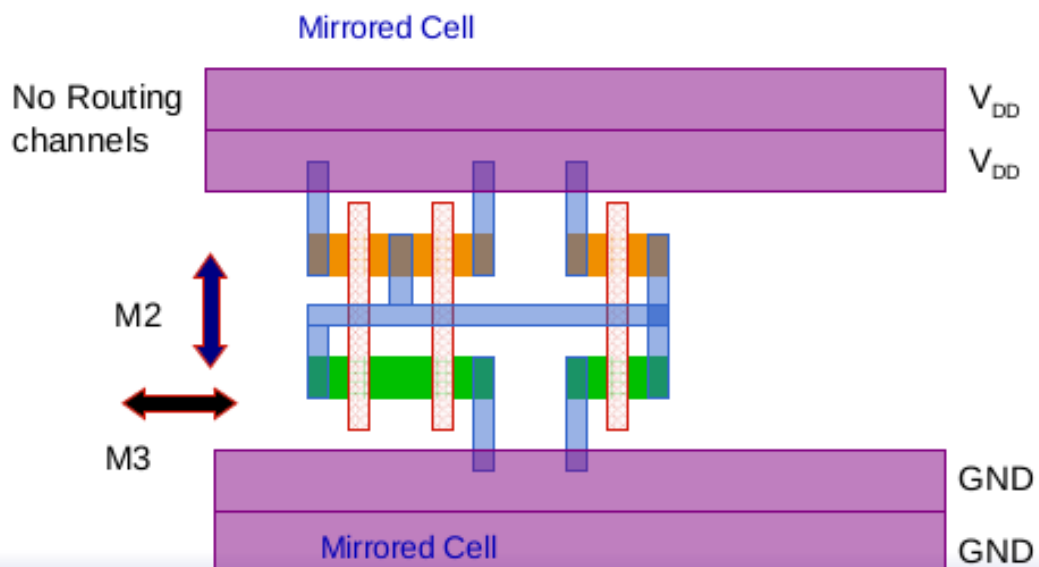

© Digital Integrated Circuits^{2nd}

Combinational Circuits


Standard Cells

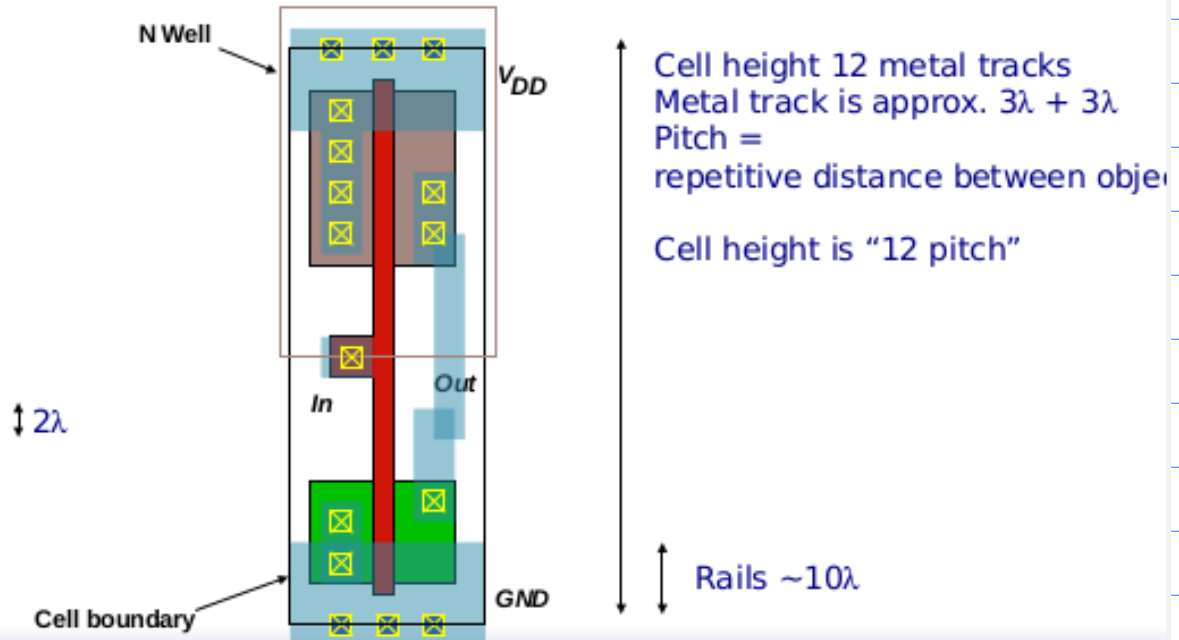

© Digital Integrated Circuits^{2nd}

Combinational Circuits


Standard Cells

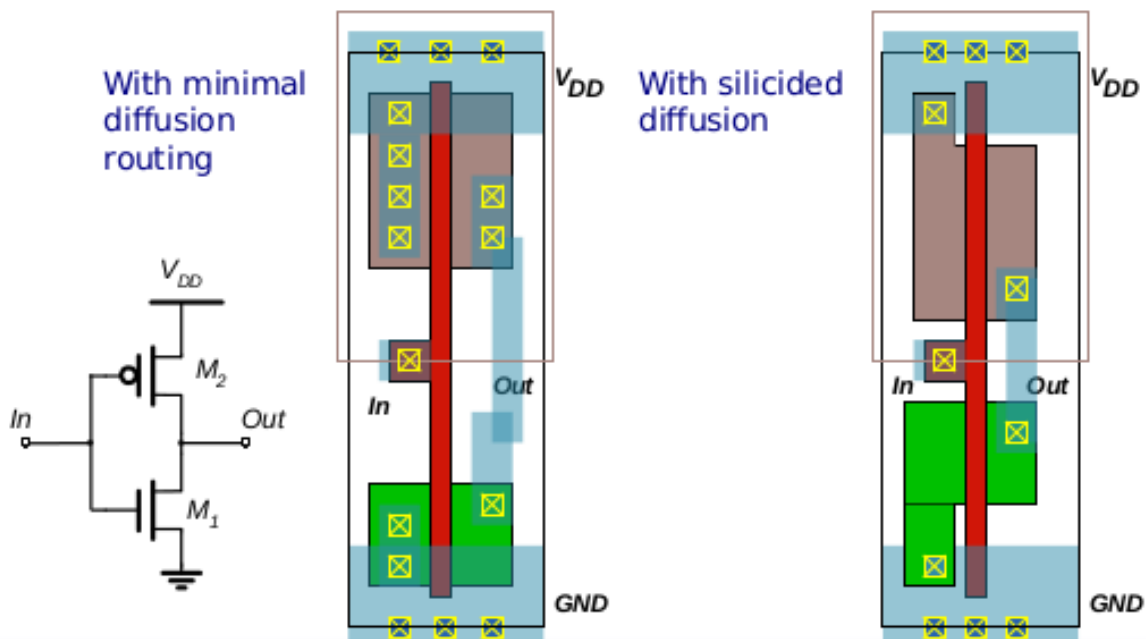


© Digital Integrated Circuits^{2nd}

Combinational Circuits

Standard Cells


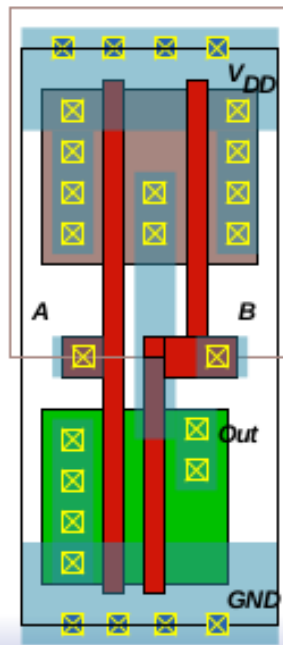


2-input NAND gate

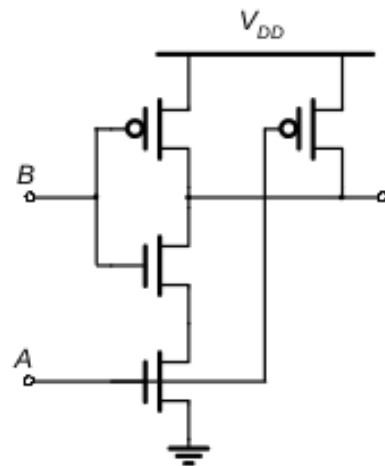


Standard Cells

With minimal diffusion routing

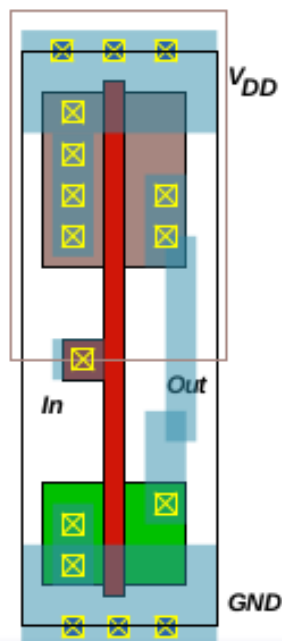
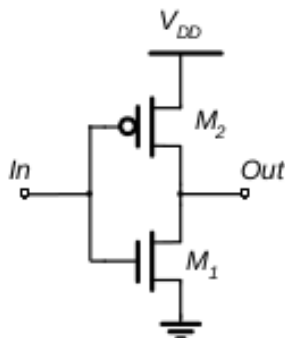


With silicided diffusion

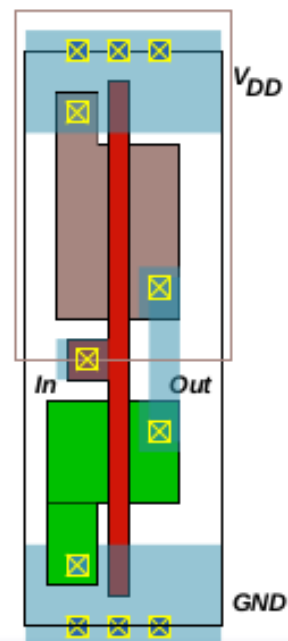


Stick Diagrams

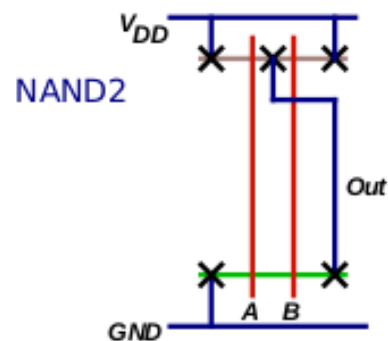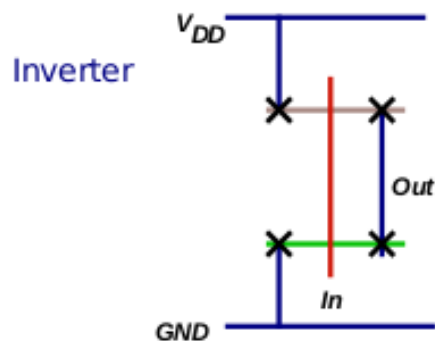Contains no dimensions
Represents relative positions of transistors





Two Versions of $C \cdot (A + B)$

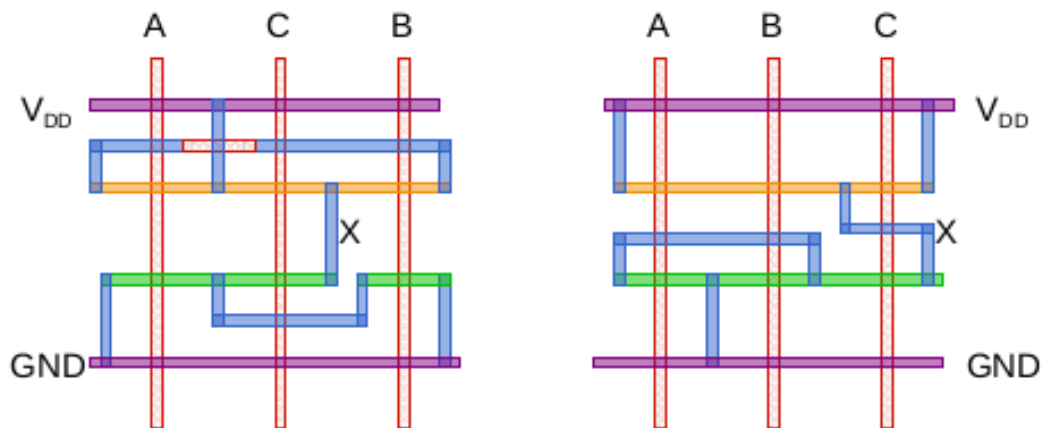

© Digital Integrated Circuits^{2nd}

Combinational Circuits

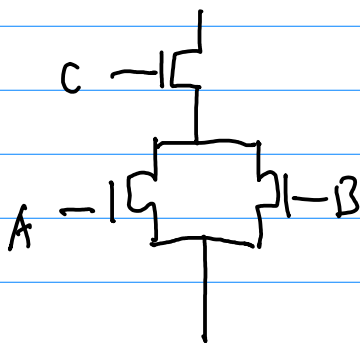

 

Behavioral Decoder

```
`timescale 1ns/100ps
```

```
module decoder(A, D);  
  input [2:0] A;  
  output [7:0] D;  
  reg [7:0] D;  
  
  always @(A)  
  begin  
    case (A)  
      0: D = 8'b00000001;  
      1: D = 8'b00000010;  
      2: D = 8'b00000100;  
      3: D = 8'b00001000;  
      4: D = 8'b00010000;  
      5: D = 8'b00100000;  
      6: D = 8'b01000000;  
      7: D = 8'b10000000;  
      default: D = 8'b'X;  
    endcase  
  end  
endmodule
```

behavioral

Synthesis

gate level design

decoder.v

```
`timescale 1ns/100ps
```

```
module decoder();  
  wire D0, D1, D2, D3, D4, D5, D6, D7;  
  reg x, y, z;  
  
  not (xb, x);  
  not (yb, y);  
  not (zb, z);  
  
  and (D0, xb, yb, zb); // D0 = minterm m0  
  and (D1, xb, yb, z ); // D1 = minterm m1  
  and (D2, xb, y , zb); // D2 = minterm m2  
  and (D3, xb, y , z ); // D3 = minterm m3  
  and (D4, x , yb, zb); // D4 = minterm m4  
  and (D5, x , yb, z ); // D5 = minterm m5  
  and (D6, x , y , zb); // D6 = minterm m6  
  and (D7, x , y , z ); // D7 = minterm m7
```

```
// Testbench Code goes here
```

```
initial begin
```

```
  $dumpfile("decoder.vcd");
```

```
  $dumpvars(0, decoder);
```

```
  $monitor ("[x y z] = %b%b%b [D0, D1, D2, D3]  
            = %b%b%b%b%b%b%b%b%b%b",  
            x, y, z, D0, D1, D2, D3, D4, D5, D6, D7);
```

```
  x = 0;
```

```
  y = 0;
```

```
  z = 0;
```

```
  #8 $finish;
```

```
end
```


```
always #4 x = ~x;
```


```
always #2 y = ~y;
```

```
always #1 z = ~z;
```

```
endmodule
```

Decoder Schematic

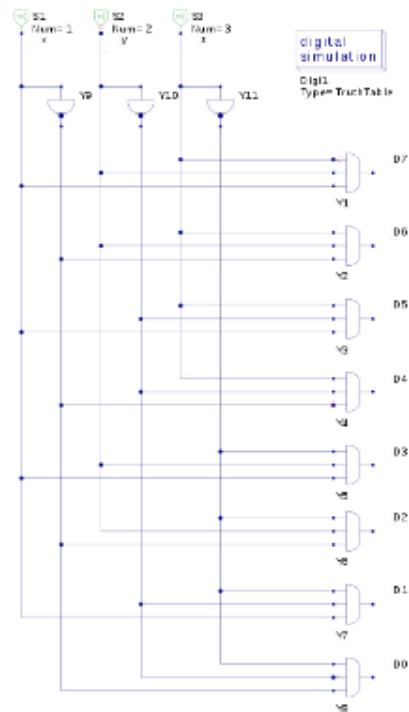

 


Synthesis

```
module decoder(A, D);  
  input [2:0] A;  
  output [7:0] D;  
  reg [7:0] D;  
  
  always @(A)  
  begin  
    case (A)  
      0: D = 8'b00000001;  
      1: D = 8'b00000010;  
      2: D = 8'b00000100;  
      3: D = 8'b00001000;  
      4: D = 8'b00010000;  
      5: D = 8'b00100000;  
      6: D = 8'b01000000;  
      7: D = 8'b10000000;  
      default: D = 8'b'X;  
    endcase  
  end  
end
```








```
module decoder();  
  wire D0, D1, D2, D3, D4, D5, D6, D7;  
  reg x, y, z;  
  
  not (xb, x);  
  not (yb, y);  
  not (zb, z);  
  
  and (D0, xb, yb, zb); // D0 = minterm m0  
  and (D1, xb, yb, z); // D1 = minterm m1  
  and (D2, xb, y, zb); // D2 = minterm m2  
  and (D3, xb, y, z); // D3 = minterm m3  
  and (D4, x, yb, zb); // D4 = minterm m4  
  and (D5, x, yb, z); // D5 = minterm m5  
  and (D6, x, y, zb); // D6 = minterm m6  
  and (D7, x, y, z); // D7 = minterm m7  
end
```

INV,
AND

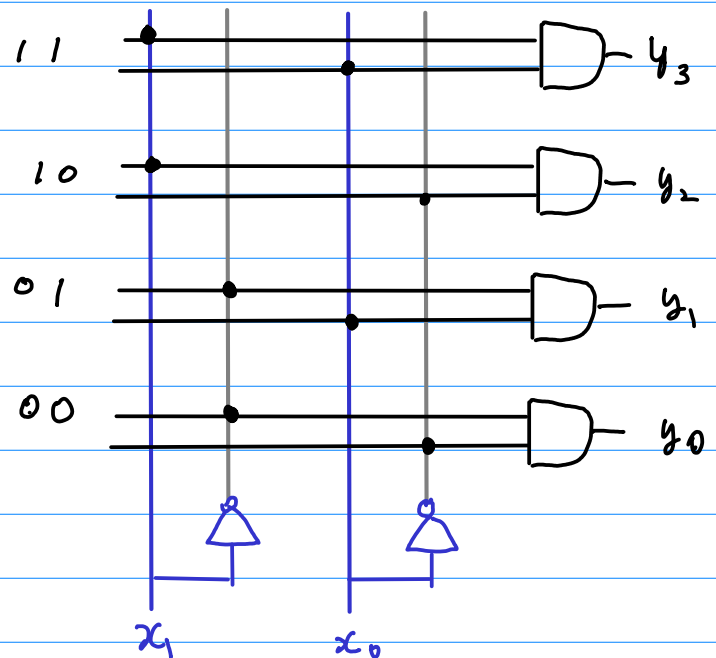


Standard Cell Library


pre defined
layout
collection

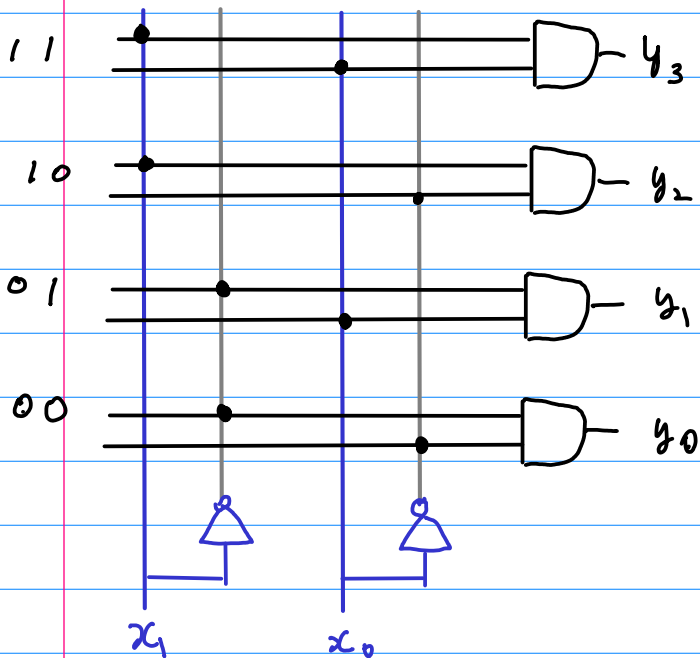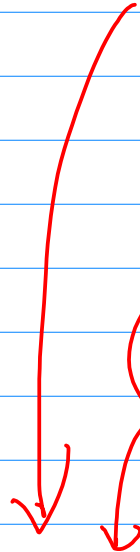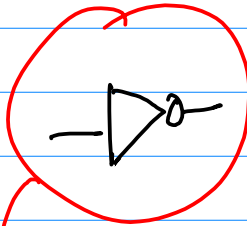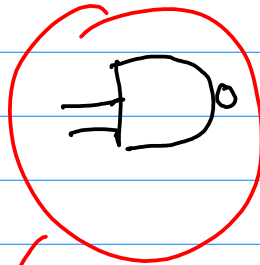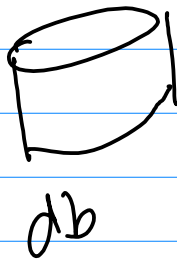

Standard Cells

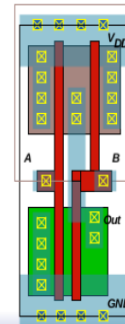

2-input NAND gate


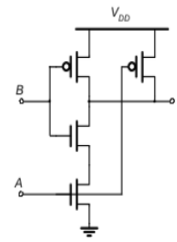


© Digital Integrated Circuits^{2nd}


Combinational Circuits

Standard Cells

With minimal
diffusion
routing

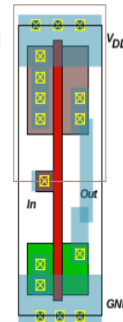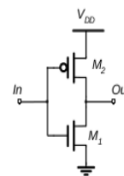

With silicided
diffusion

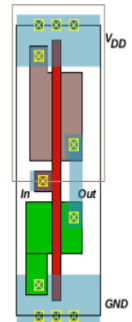

The figure 10 summarizes the followed process:

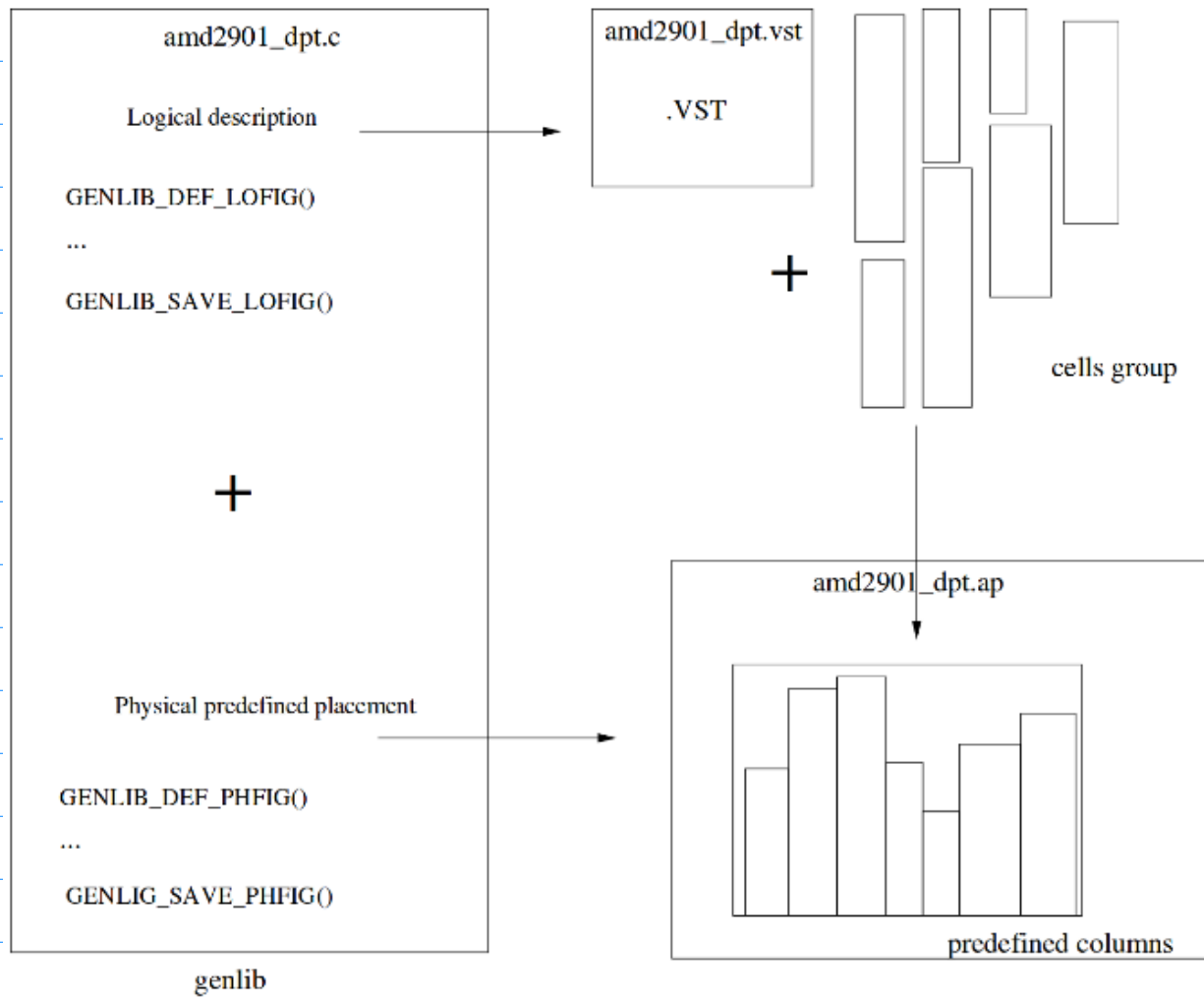


Figure 10: predefined placement

Placement

<https://github.com/clothbot/Alliance-VLSI-CAD-System>

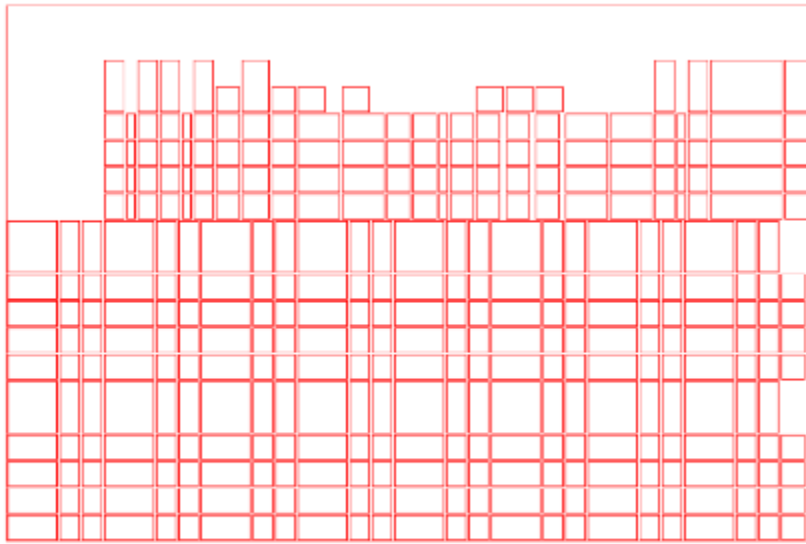


Figure 11: predefined Columns before placement of the part controls


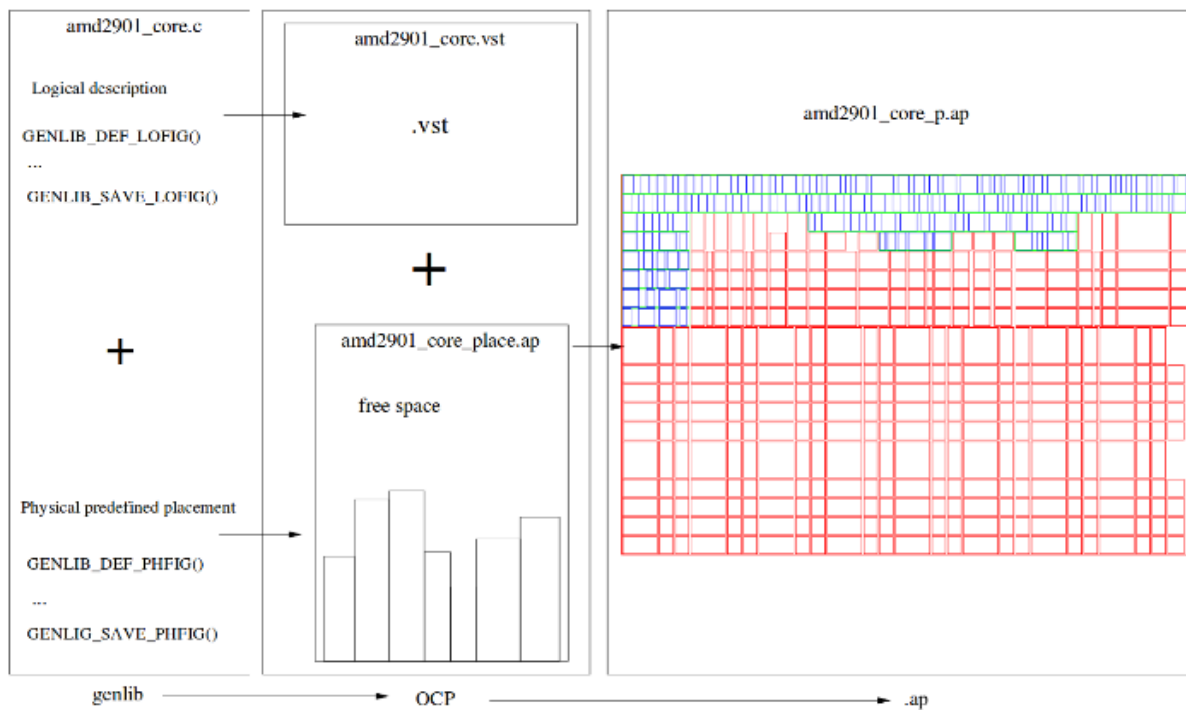
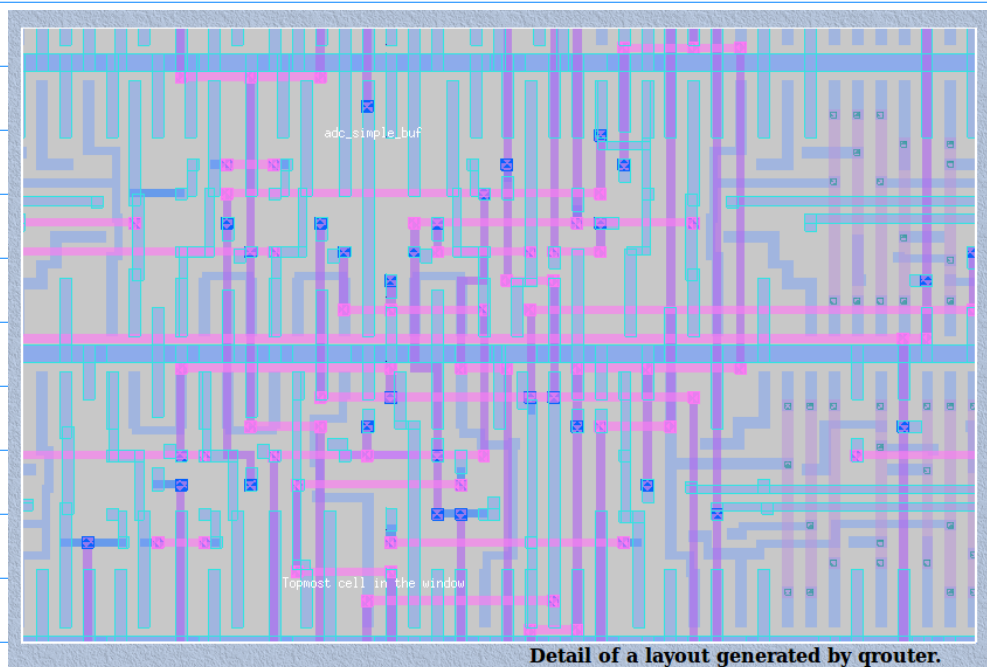



Figure 12: Placement

Route connection
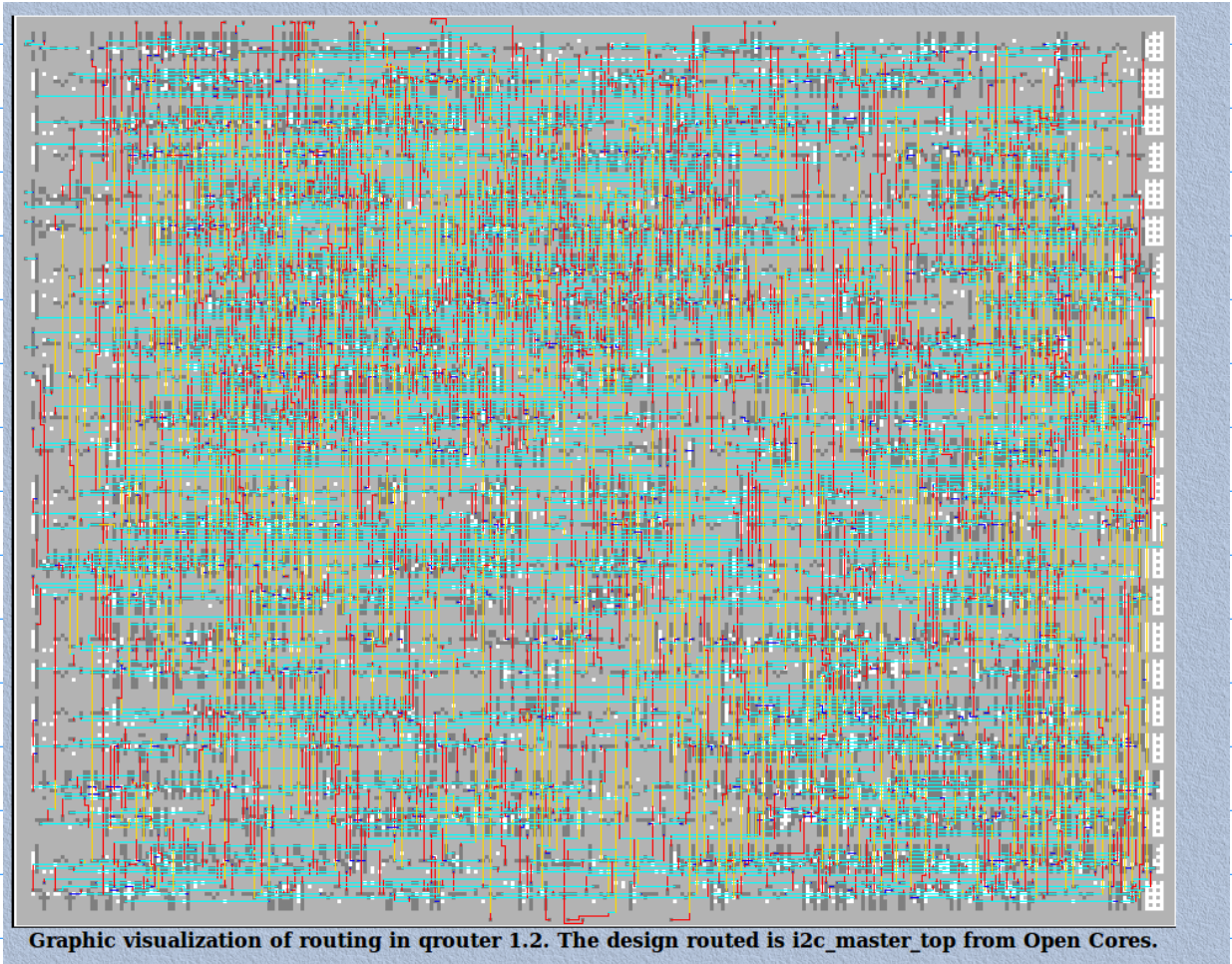
<http://opencircuitdesign.com/qrouter/index.html>



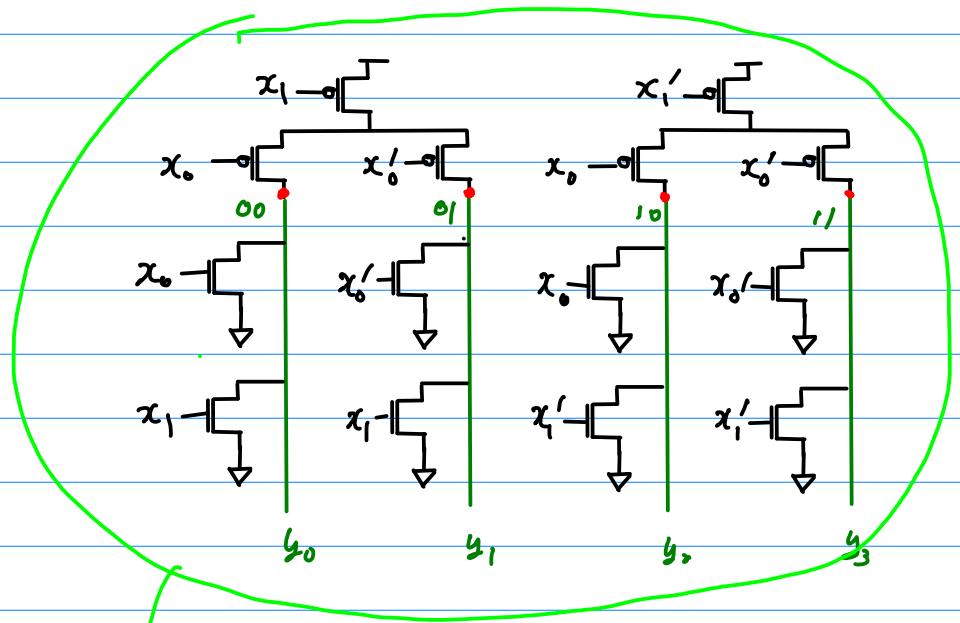Custom Design $\rightarrow$ my own layout for
my own CMOS design



draw a "Layout Design"

