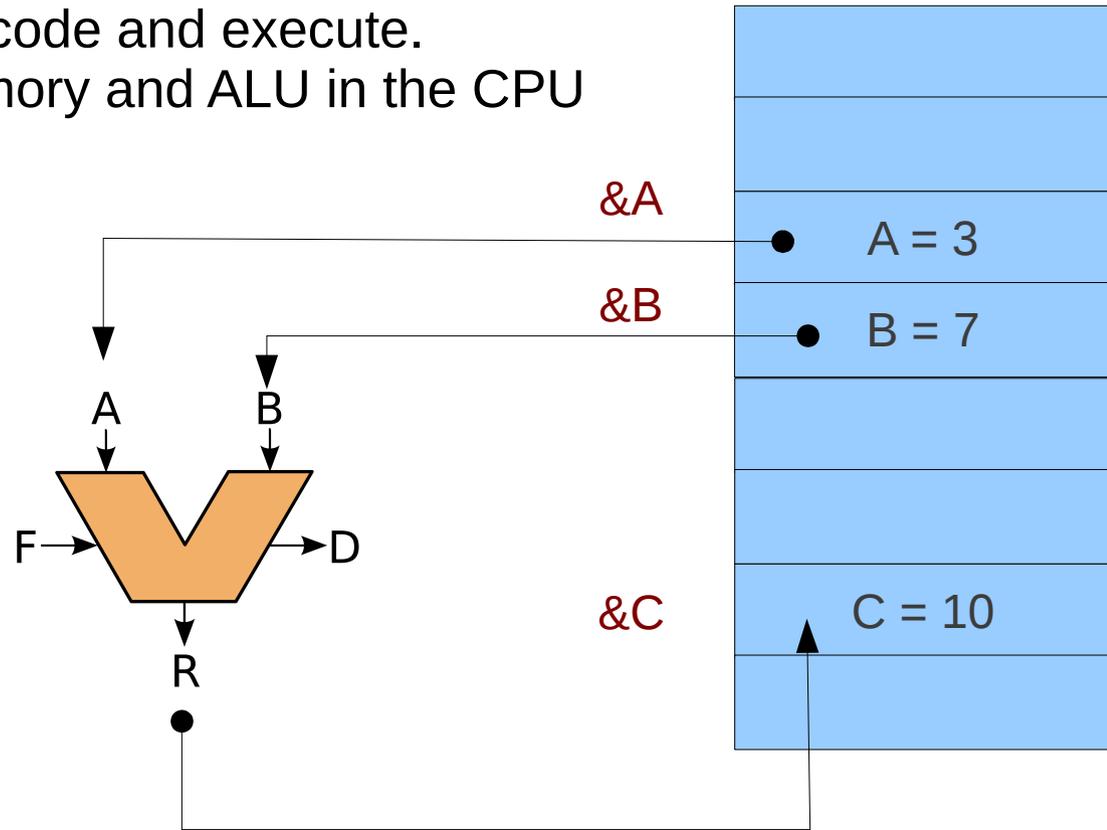


#1 Complete the following C code and execute.  
Explain what happens in Memory and ALU in the CPU

```
int A, B, C;  
int * p;
```

```
A = 3;  
B = 7;  
C = A + B;  
A = 2;  
B = 5;  
C = A + B;  
A = 3;  
B = 3;  
C = A + B;
```



```
printf("address of A = %x, data of A = %d \n", &A, A);  
printf("address of B = %x, data of B = %d \n", &B, B);  
printf("address of C = %x, data of C = %d \n", &C, C);
```


```
p = &A; printf("address of A = %x, data of A = %d \n", p, *p);  
p = &B; printf("address of A = %x, data of A = %d \n", p, *p);  
p = &B; printf("address of A = %x, data of A = %d \n", p, *p);
```

#2 Design the Hardware which will do the same thing in #1.

$A \rightarrow A_3 A_2 A_1 A_0$   
 $B \rightarrow B_3 B_2 B_1 B_0$   
 $C \rightarrow C_3 C_2 C_1 C_0$

$A = 3;$   
 $B = 7;$   
 $C = A + B;$   
 $A = 2;$   
 $B = 5;$   
 $C = A + B;$   
 $A = 3;$   
 $B = 3;$   
 $C = A + B;$

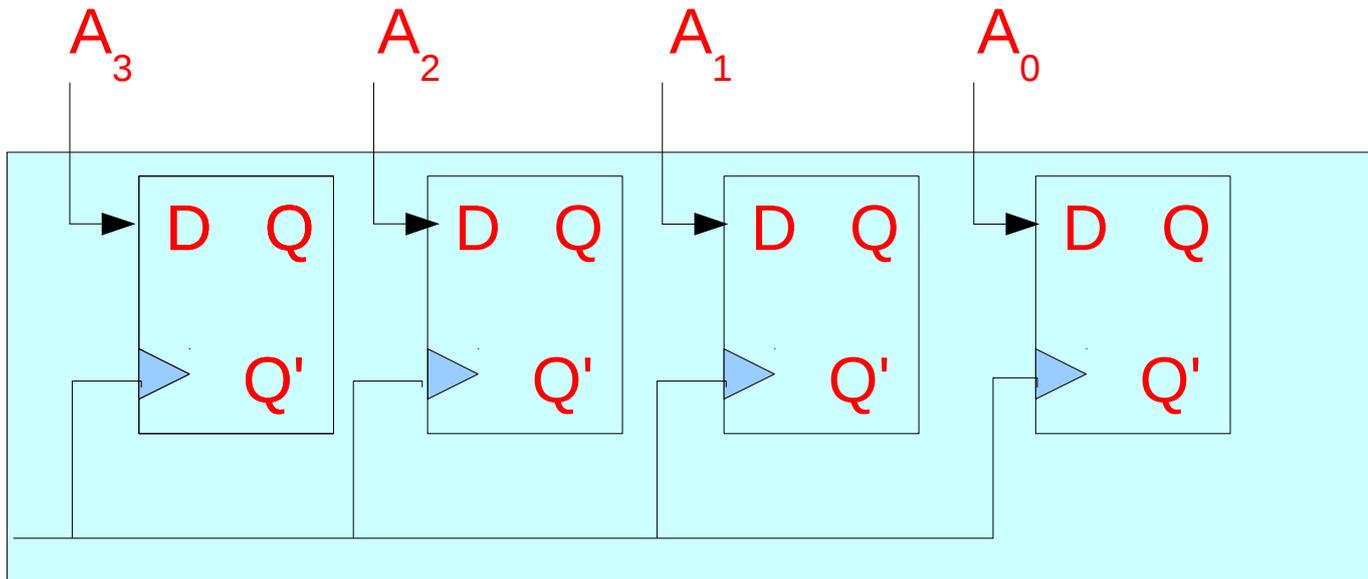- (a) What is a register and why do we need it?
- (b) Explain a register with a parallel load.





(c) Explain the hardware design to perform the following sequence of additions

$A = 3;$   
 $B = 7;$   
 $C = A + B;$   
 $A = 2;$   
 $B = 5;$   
 $C = A + B;$   
 $A = 3;$   
 $B = 3;$   
 $C = A + B;$

$A_3 A_2 A_1 A_0$

$B_3 B_2 B_1 B_0$

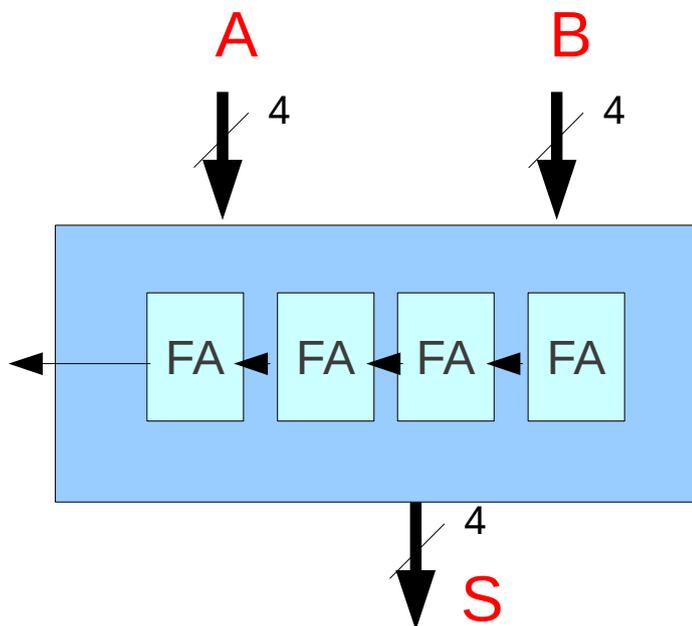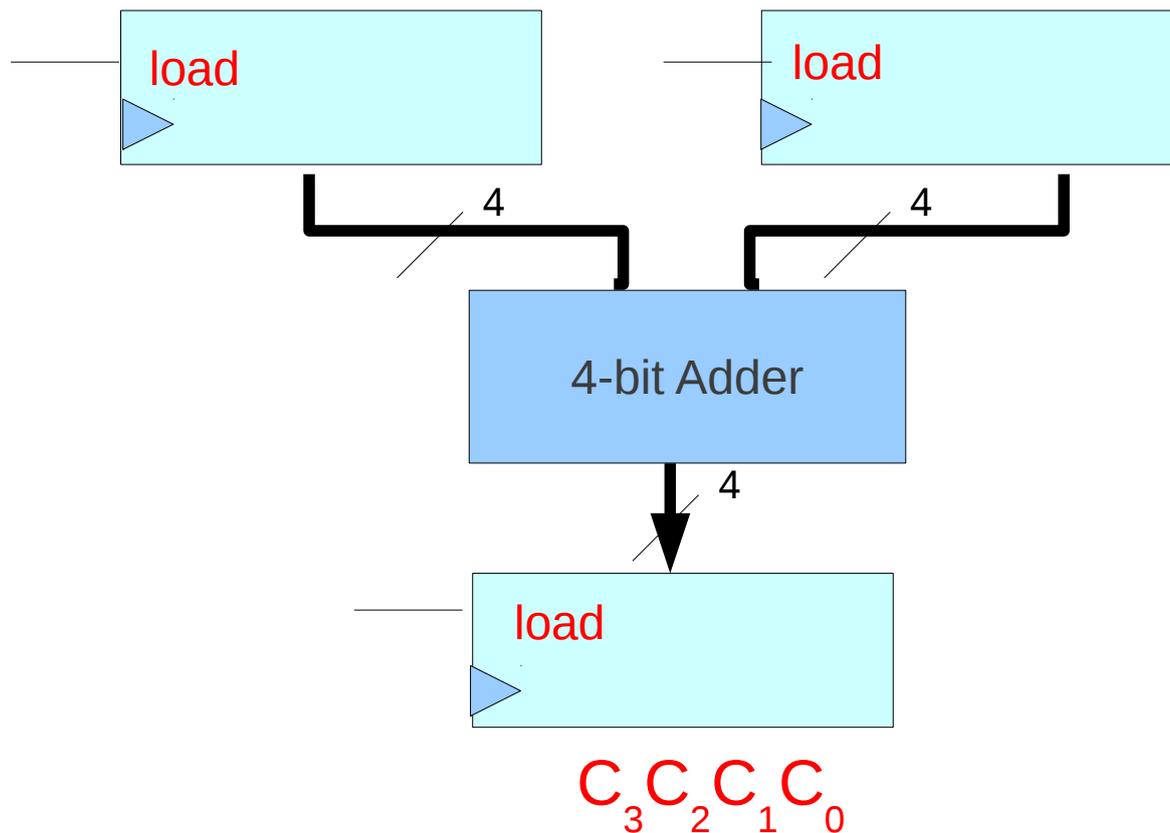

(d) Draw an example of waveforms using this hardware design

#2 Read the pdf file about the classical implementation of edge triggered FF. Summarize the operations of the FF.