

# Diode Theroy (H.1)

20170331


Copyright (c) 2017 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

**Reverse Bias**

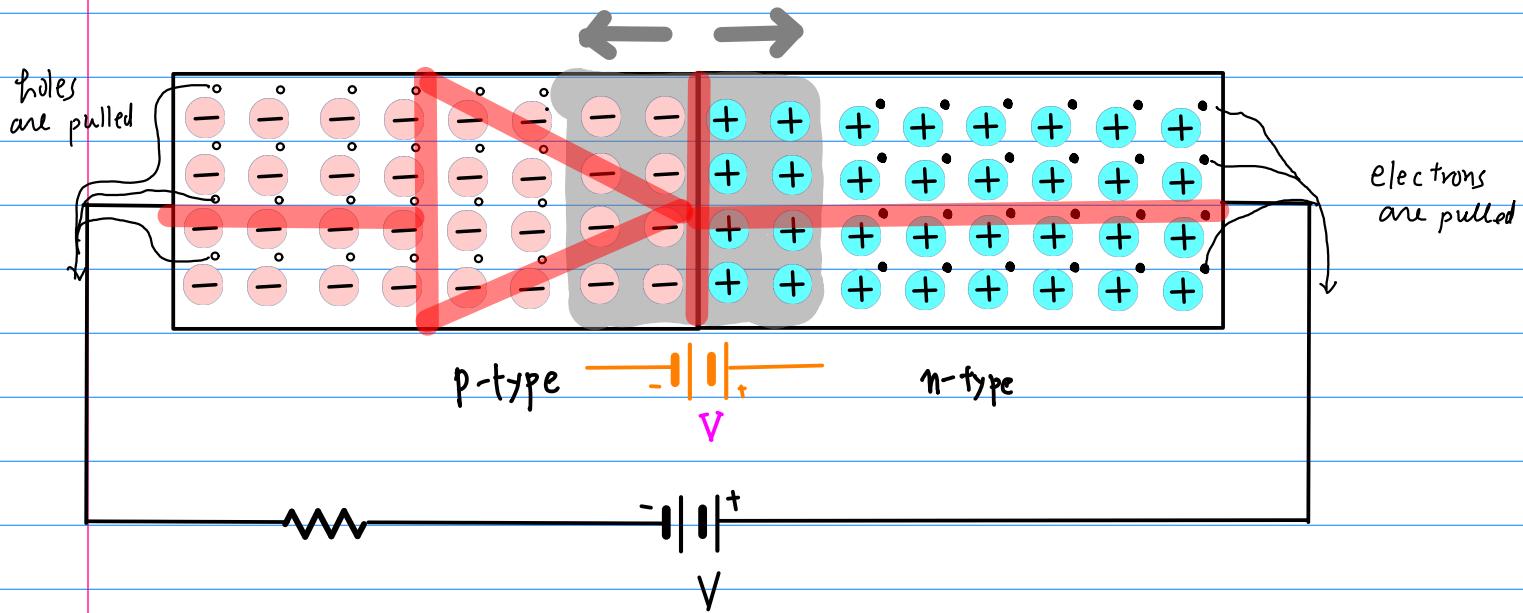
**Bias**

- increase depletion region
- no current flowing





**Forward Bias**

**Continuous Current flow**


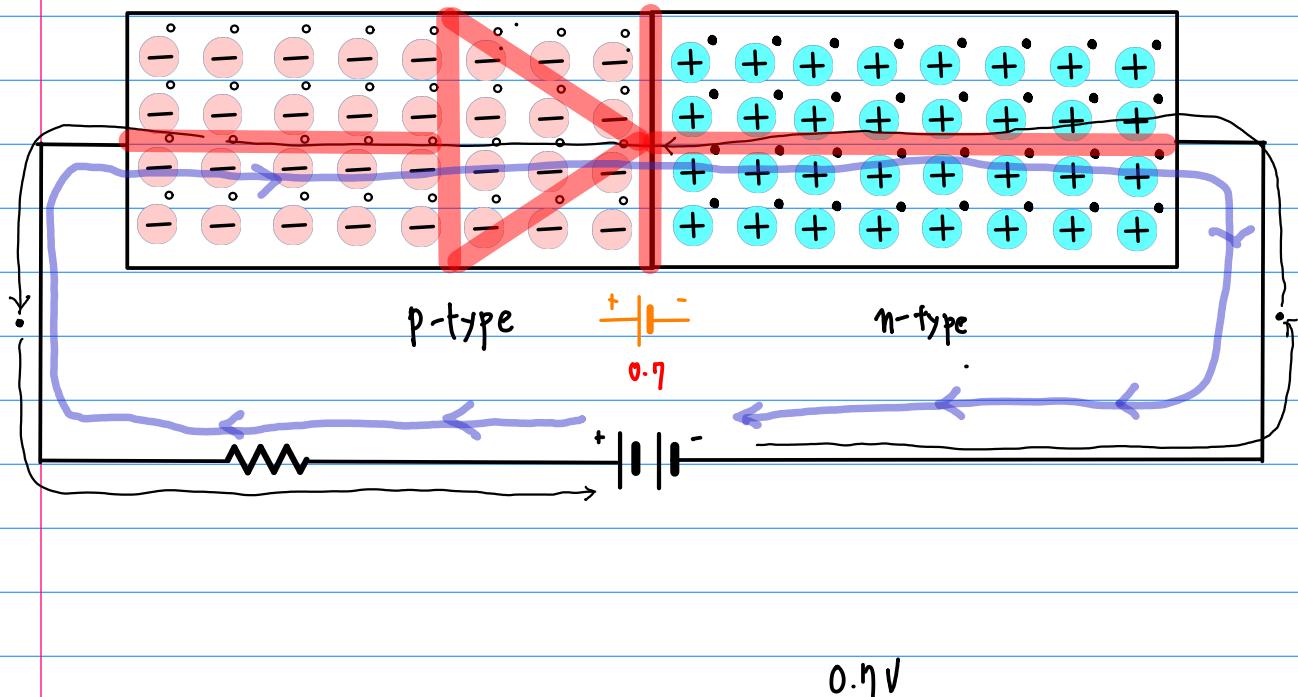


forward bias

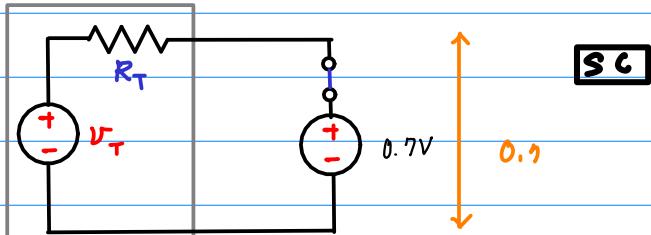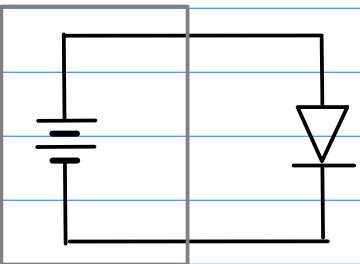

SC



reverse bias

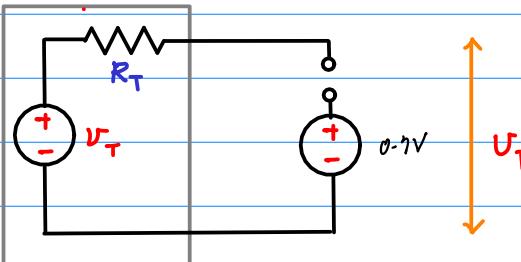
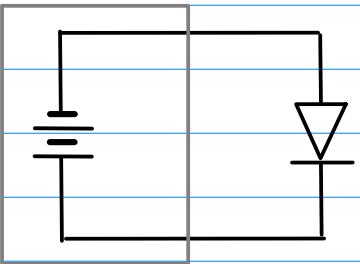




OC




ideal

model

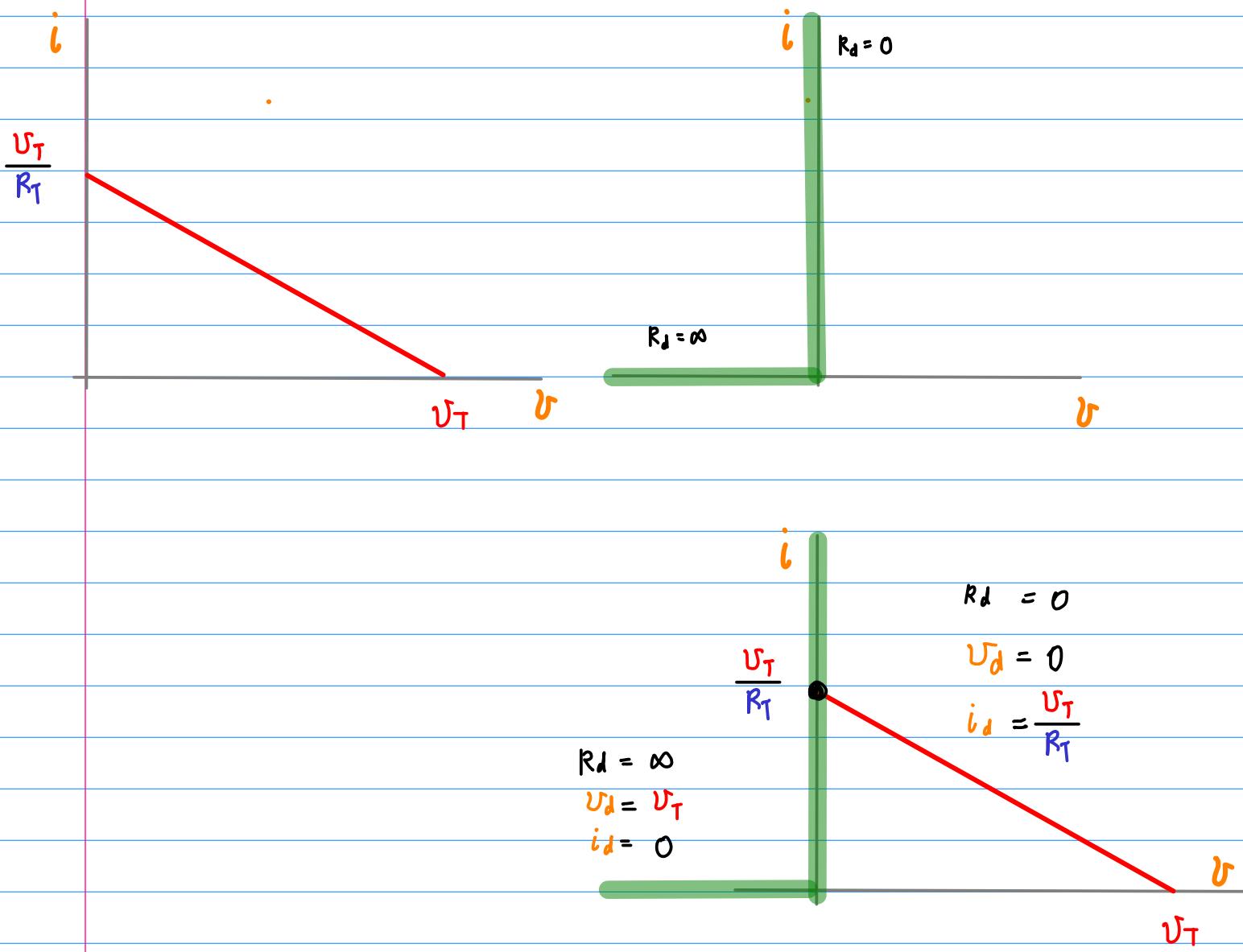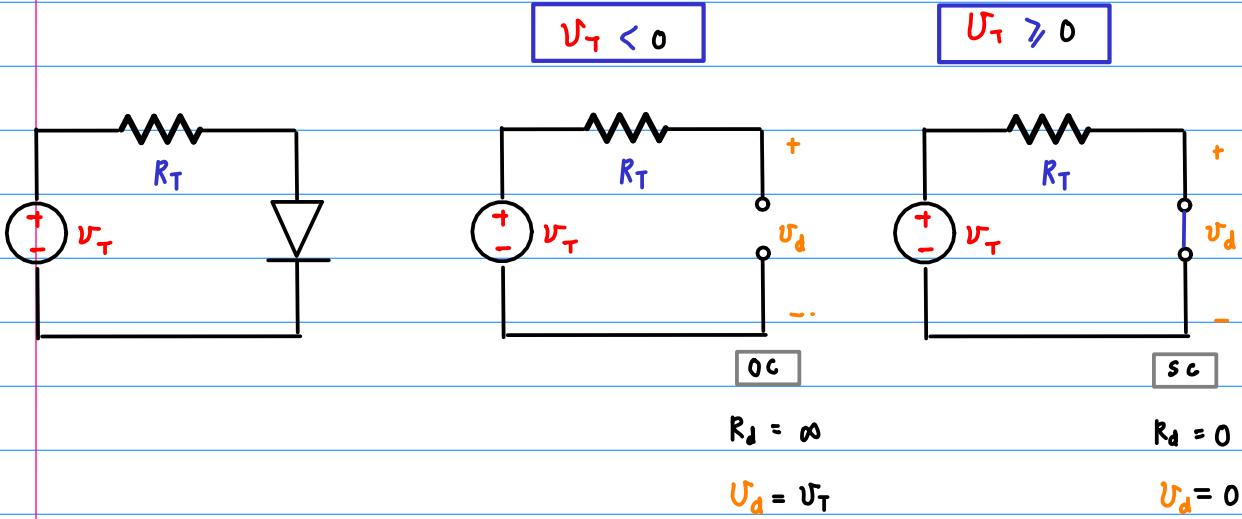

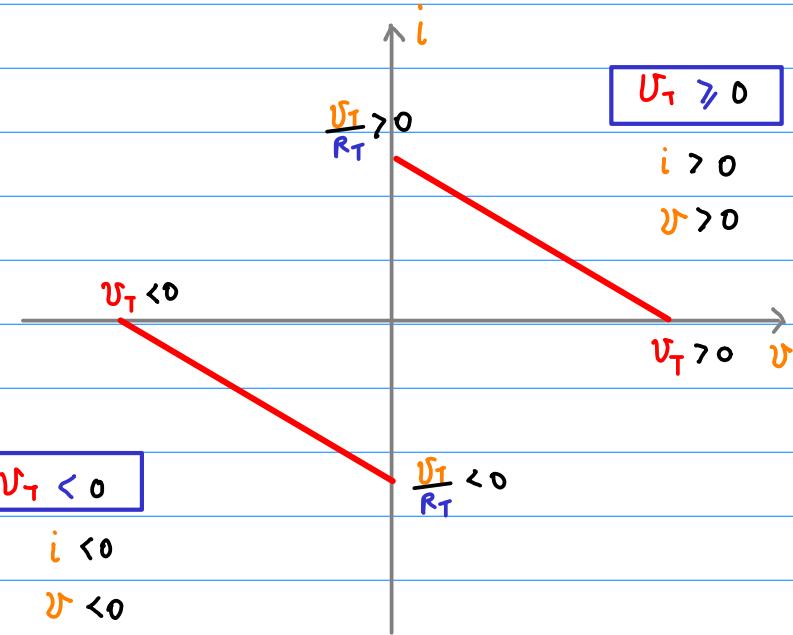
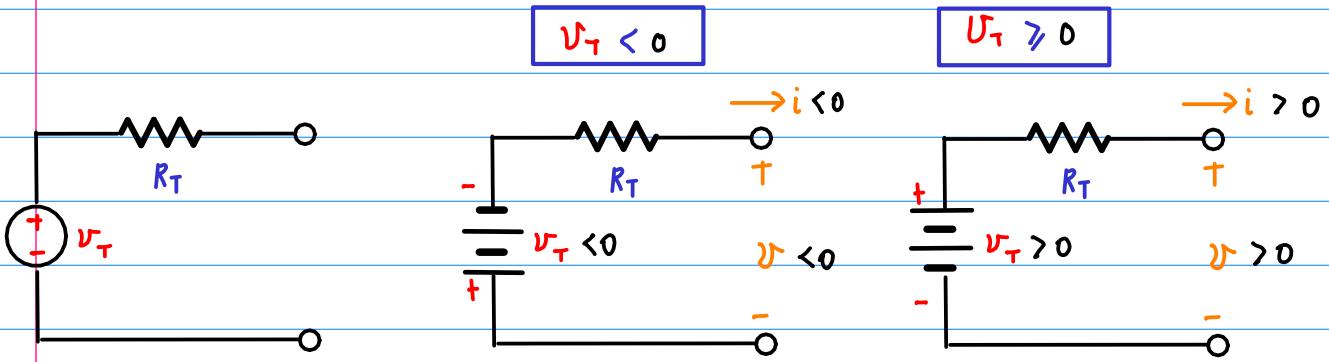


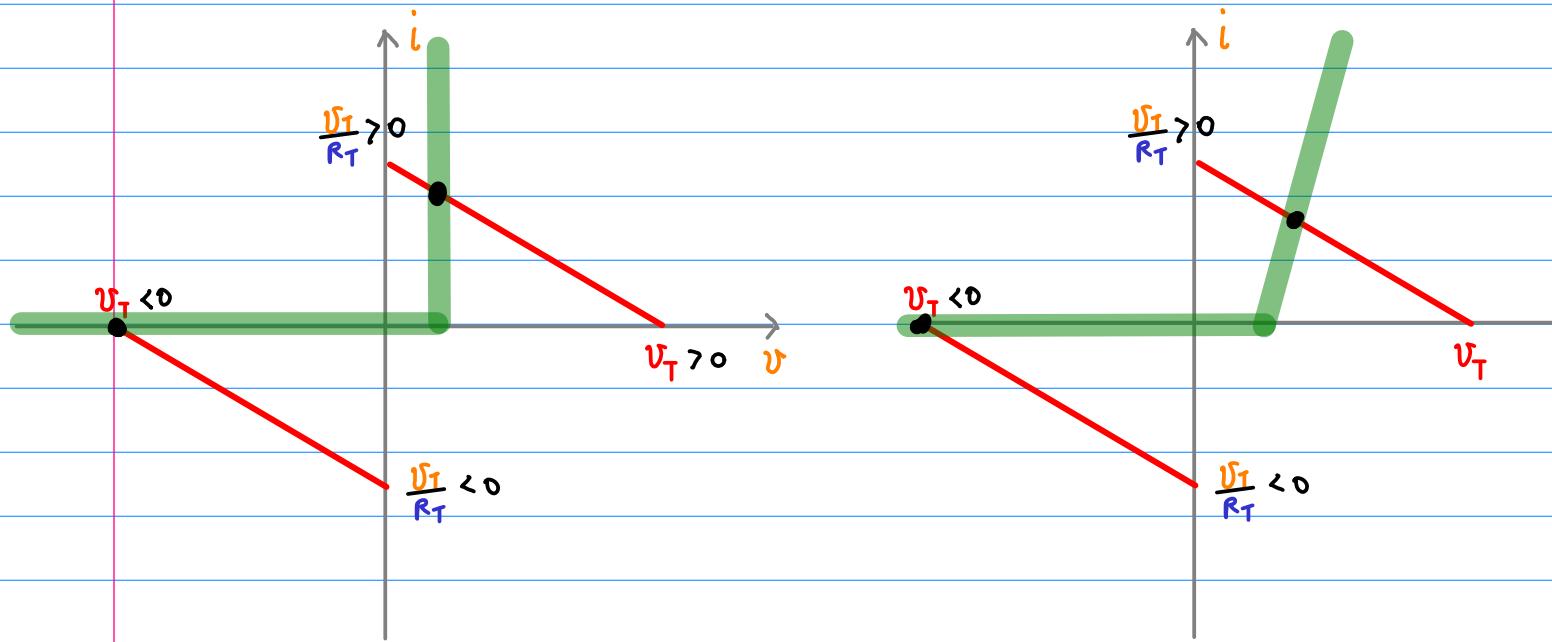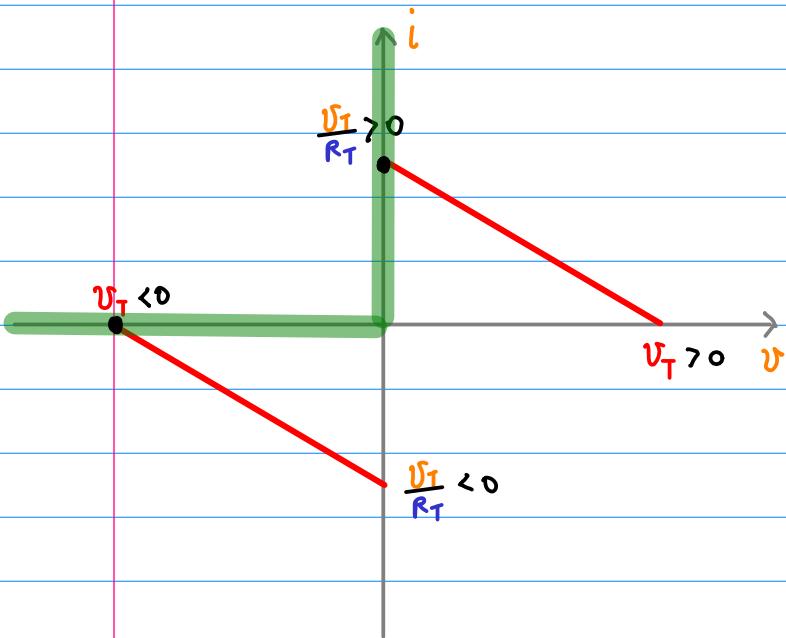

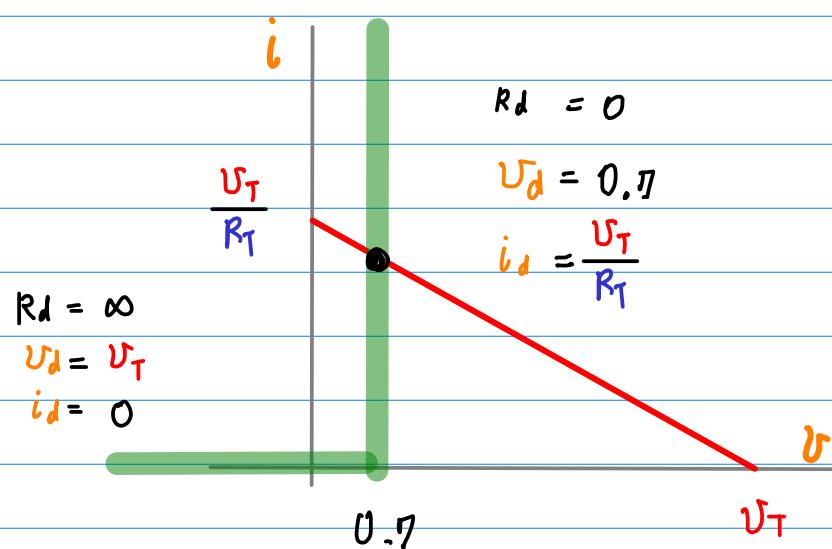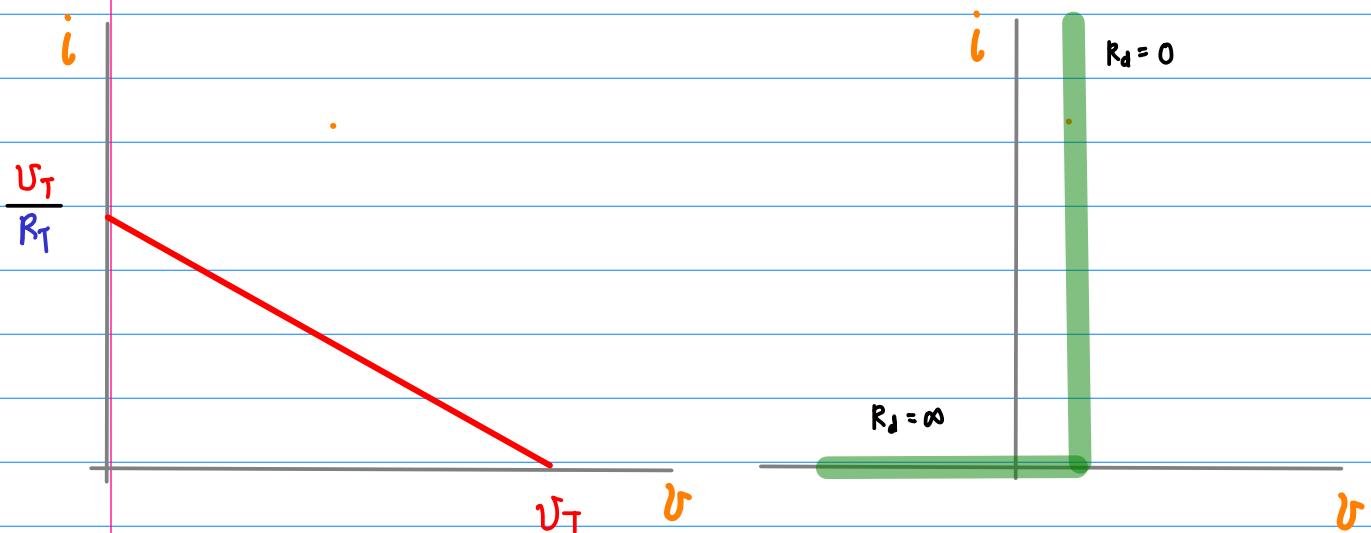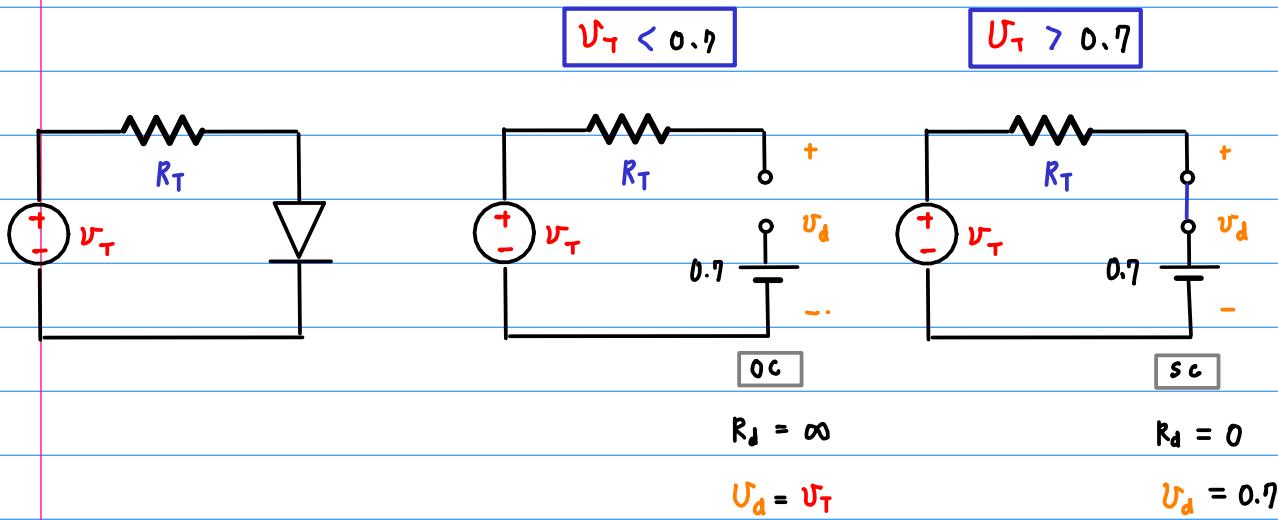

$$U_T < 0.7$$

$$U_T > 0.7$$

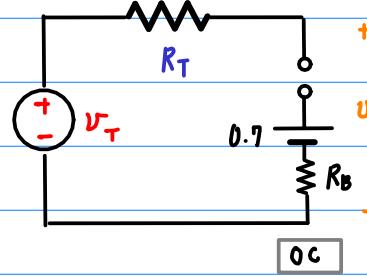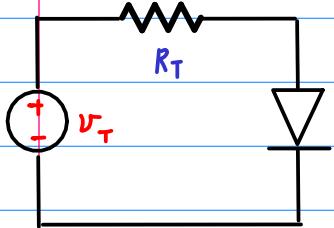

$$R_d = \infty$$

$$U_d = U_T$$

$$R_d = 0$$

$$U_d = 0.7 + i_d R_B$$

*i*

$$\frac{U_T}{R_T}$$

$$U_T \quad U$$

*i*

$$R_d = R_B$$

$$R_d = \infty$$

*i*

*i*

$$R_d = 0$$

$$U_d = 0.7 + i_d R_B$$

$$R_d = \infty$$

$$U_d = U_T$$

$$i_d = 0$$



$$0.7$$


$$U_T$$


# Increasing $V_T$

$V_d$  in the vicinity of 0.7


whenever the diode is on

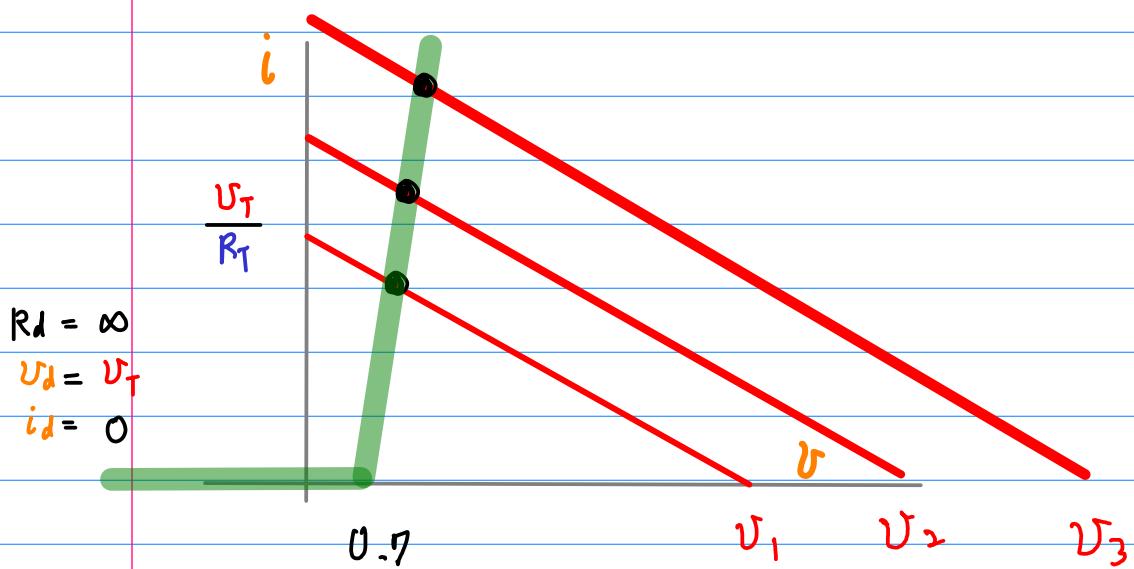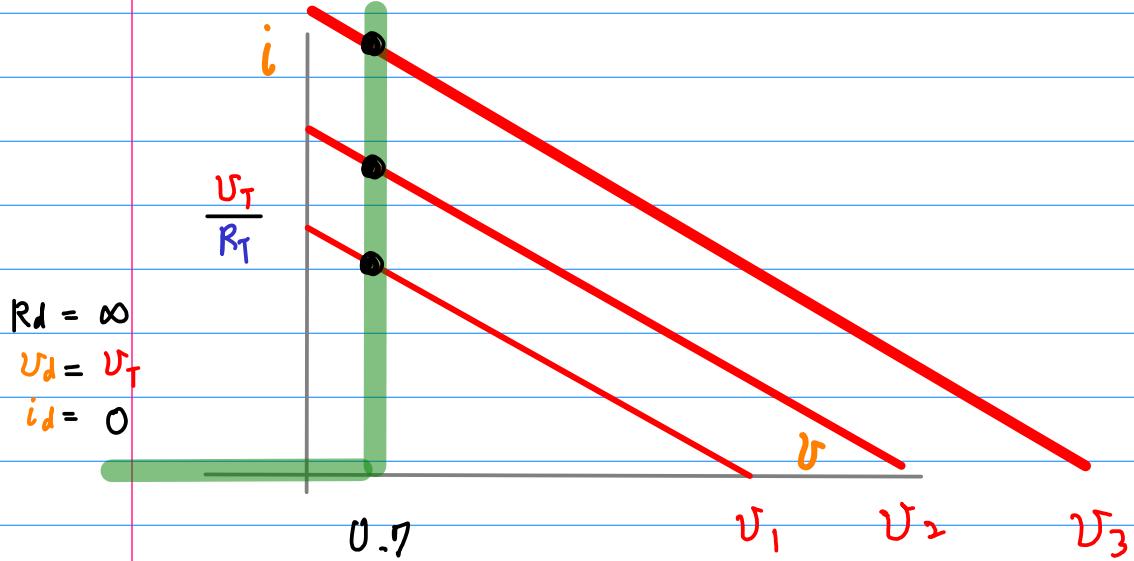

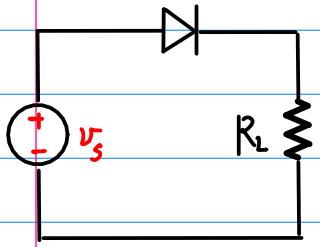

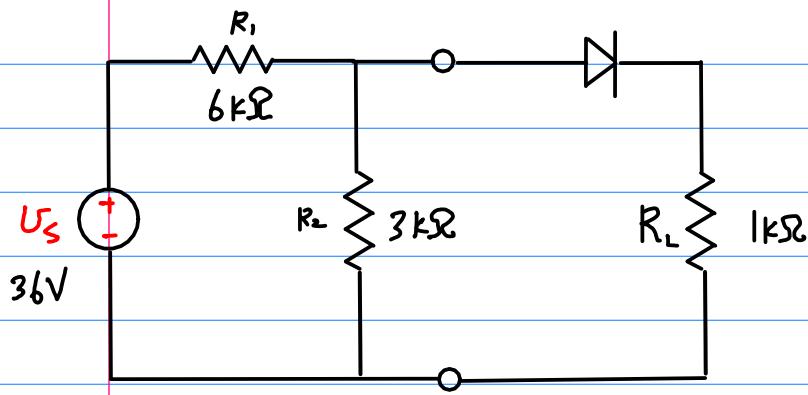



Assume ideal diode is on

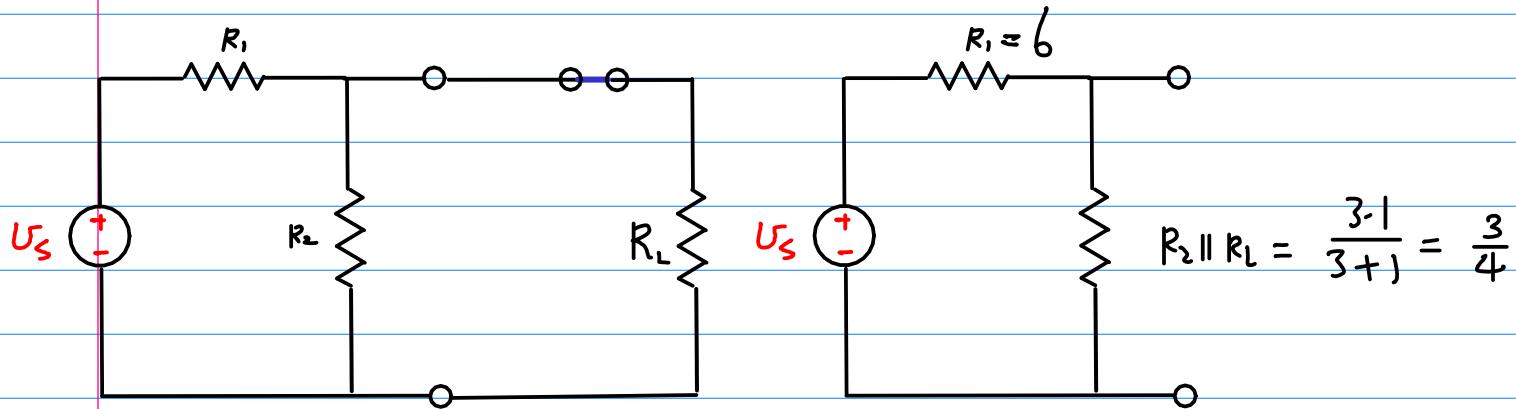

Voltage divider


$$6 : \frac{3}{4} = 24 : 3 \\ = 8 : 1$$

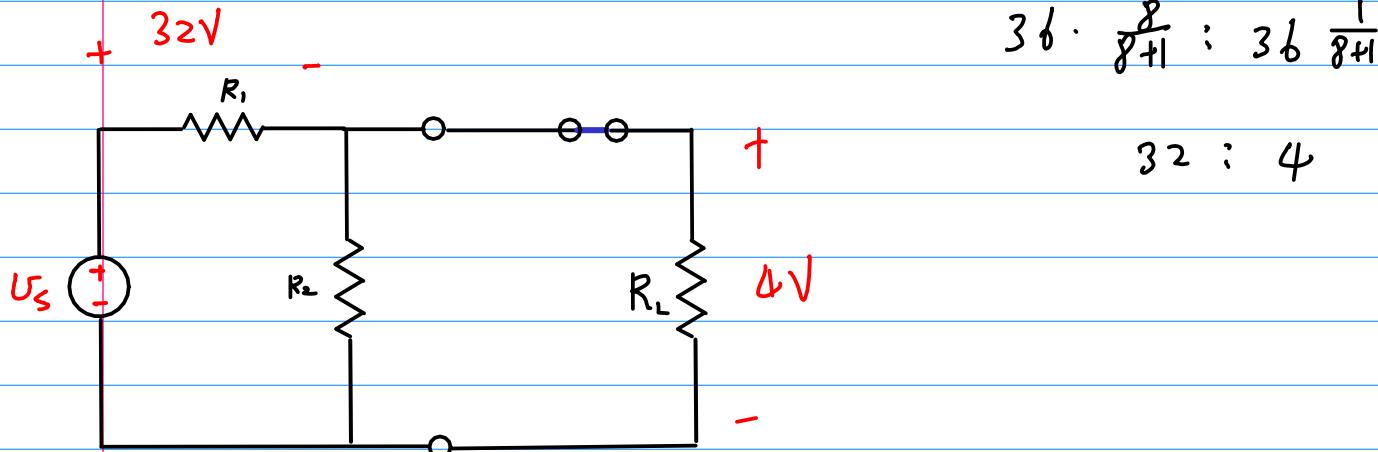

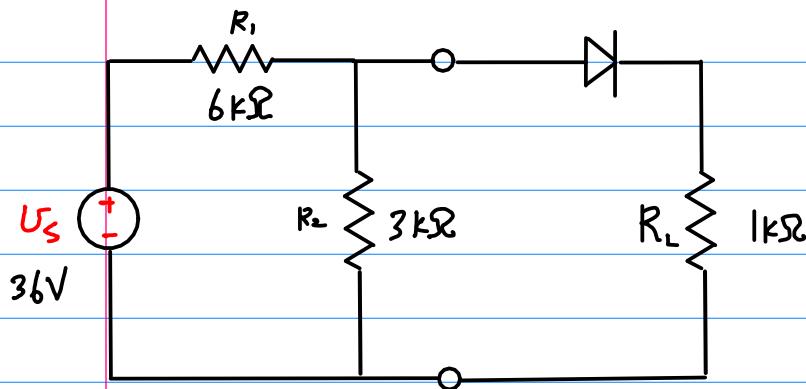


Reduce Series Circuit


Use Thevenin Eq

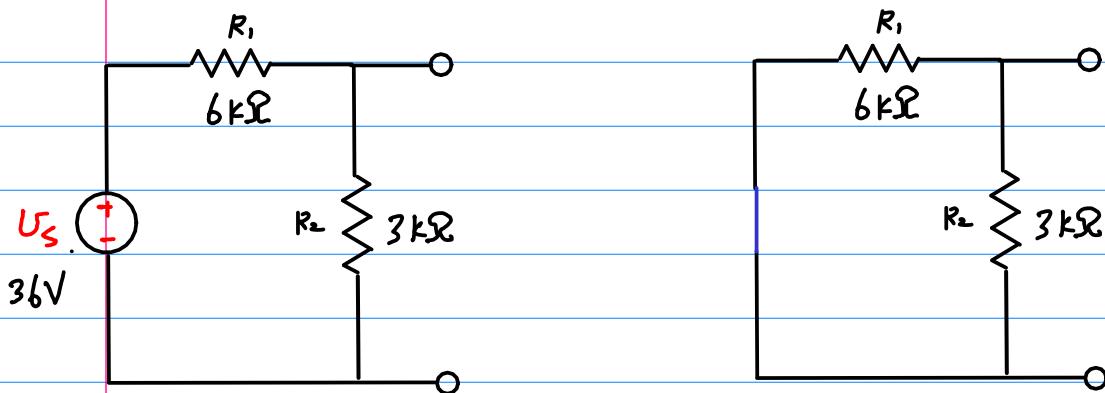

$$R_T = \frac{3+6}{3+6} = 2$$

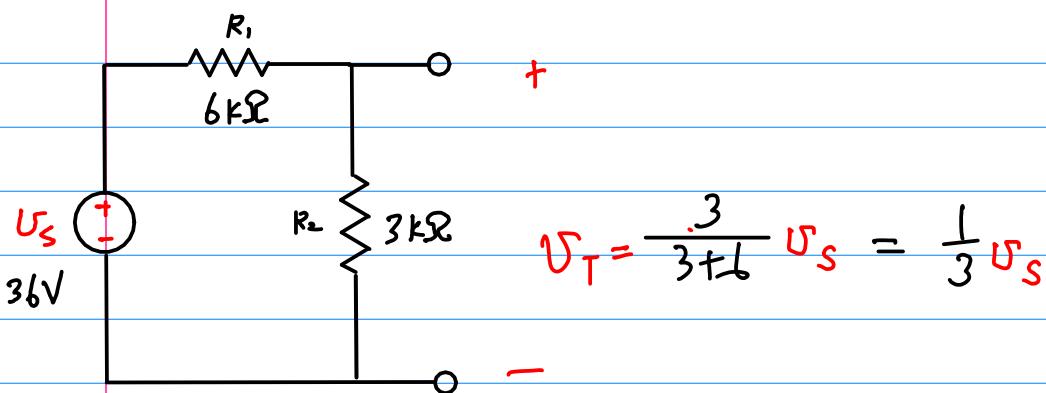
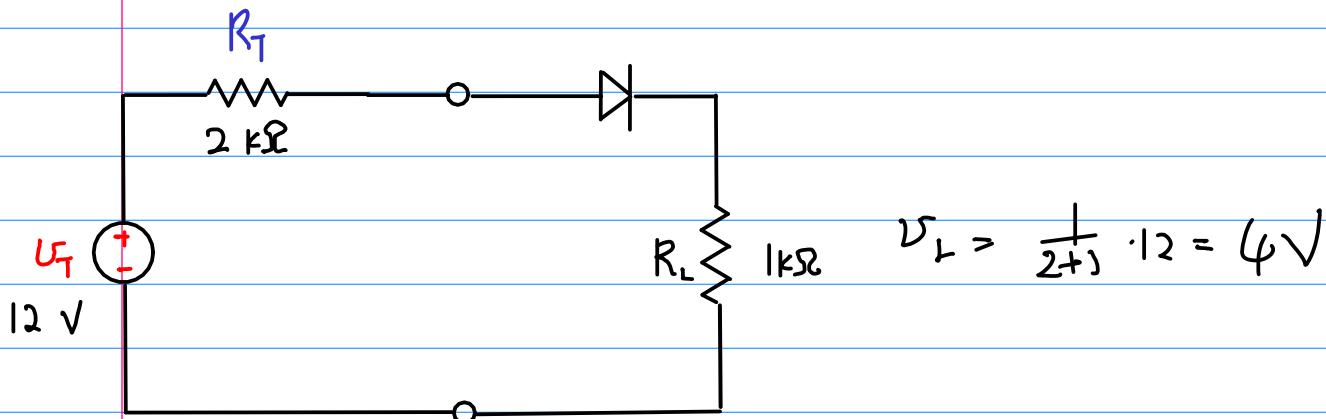
$$V_T = \frac{3}{3+6} V_S = \frac{1}{3} V_S$$



$$V_L = \frac{1}{2+1} \cdot 12 = 4\text{V}$$