

Logic Families Dynamic-2 (H.2)

20151215

Copyright (c) 2015 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

References

Some Figures from the following sites

- [1] <http://pages.hmc.edu/harris/cmosvlsi/4e/index.html>
Weste & Harris Book Site
- [2] en.wikipedia.org
- [3] Digital Integrated Circuits : A Design Perspective,
Jan M. Rabaey,
(<http://bwrcs.eecs.berkeley.edu/Classes/IcBook/>)
- [4] Digital Electronics and Design with VHDL
Pedroni

Other MOS Architectures

Static MOS

Pseudo-nMOS Logic

Transmission-gate Logic

BiCMOS Logic

Dynamic MOS


Dynamic Logic

Domino Logic


C2MOS Logic

Logical Efforts and Dynamic Logic

Unfooted Inverter

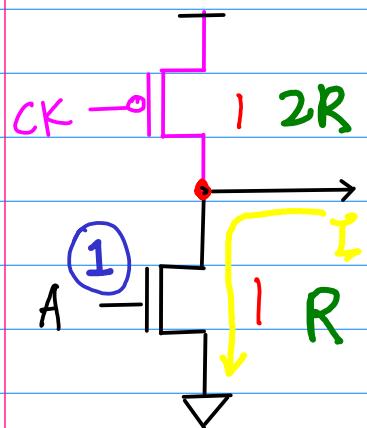


Unit Inverter

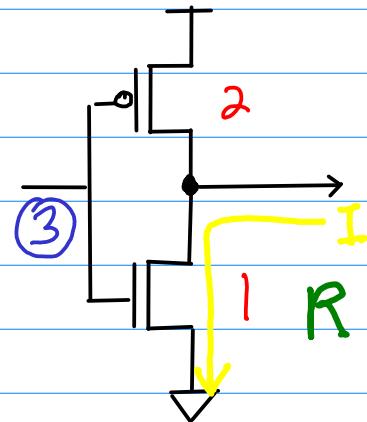


$$g_d = \frac{1}{3} < 1$$

improved down logical effort
faster fall time

Footed Inverter

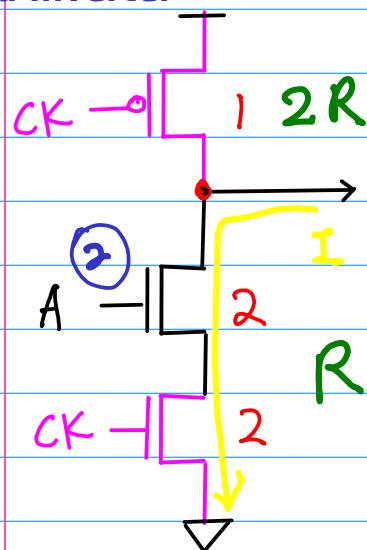


Unit Inverter

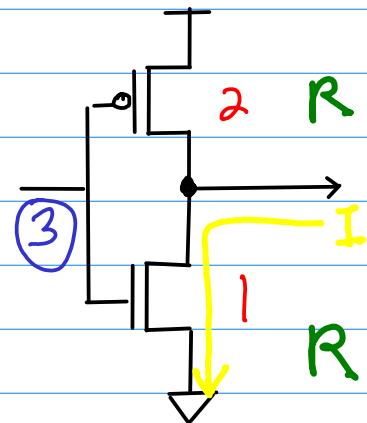

$$g_d = \frac{2}{3} < 1$$

improved down logical effort
faster fall time

Precharge and Foot Transistors

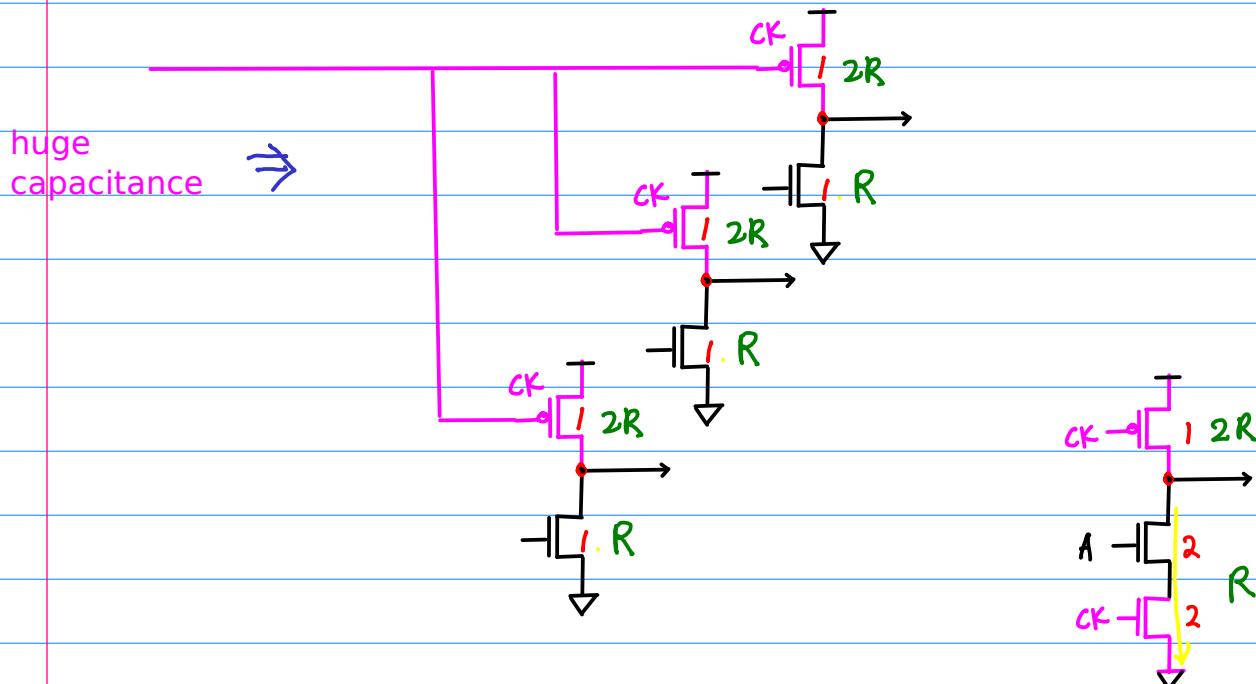

{ Unfooted
Footed

Footed

$(\frac{W}{L})_P$	Precharge Transistor	$(\frac{W}{L})_n$	Foot Transistor
* $R_p \uparrow$, rise delay \uparrow		* $R_n \downarrow$, fall delay \downarrow	
* $C \downarrow$		* $C \uparrow$	

$C \downarrow$ more important because precharge does not require fast rise delay


$R \downarrow$ more important for the fast fall delay during evaluate phase

$CK=0$
precharge


$CK=1$
evaluate

Dynamic Logic and Pseudo-nMOS Logic


Pseudo-nMOS

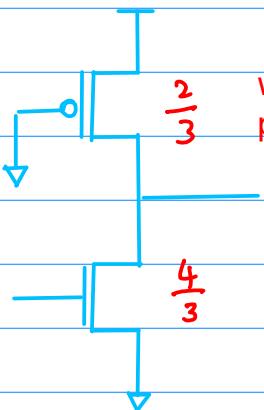

Unfooted

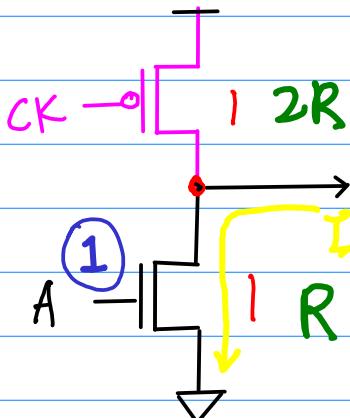

Footed

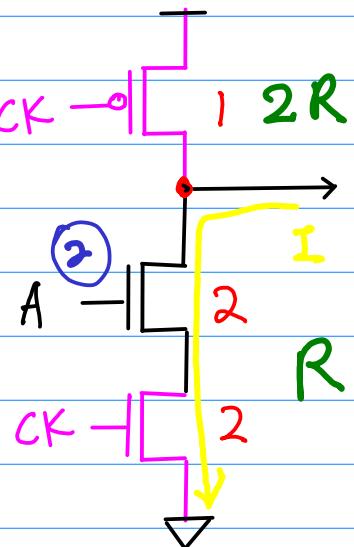

$$\left(\frac{W}{L}\right)_P = \frac{1}{2} \left(\frac{W}{L}\right)_n$$

$$\frac{1}{4}$$

$$R_p = 4 R_n$$

$$\left(\frac{W}{L}\right)_P = 1 \left(\frac{W}{L}\right)_n$$

$$\cdot \frac{1}{2}$$

$$R_p = 2 R_n$$

$$\cdot \frac{1}{4}$$

$$R_p = 4 R_n$$

$$\frac{1}{3} \sim \frac{1}{6}$$

