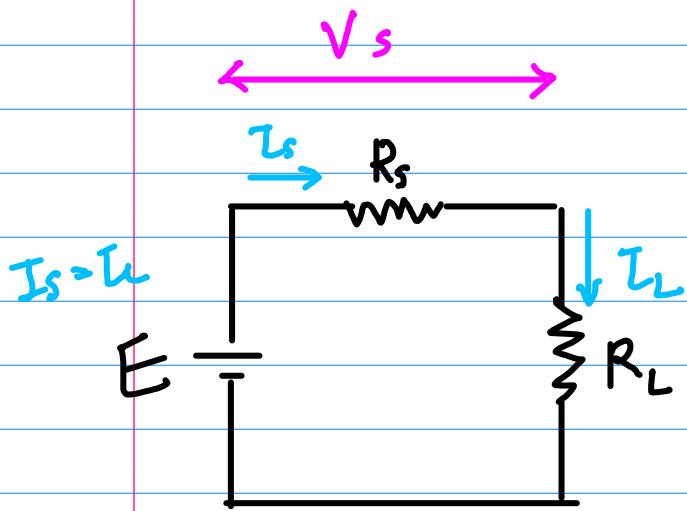



Network Analysis (H1)

Copyright (c) 2015 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".




Voltage Divider

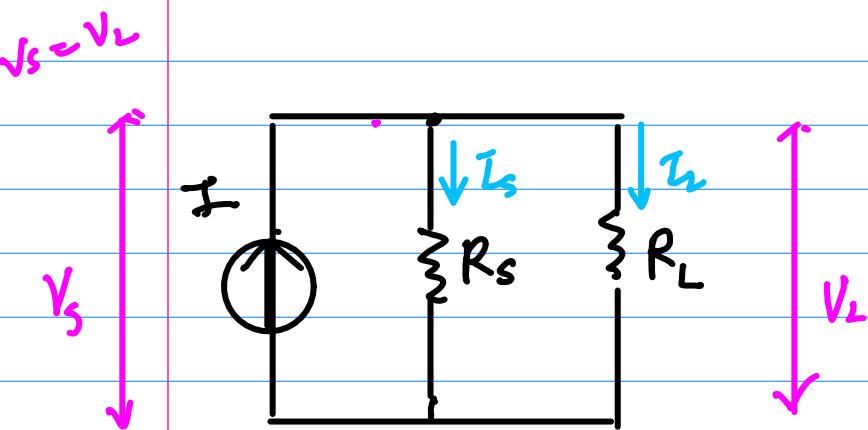

Current Divider


$$\text{Vs}$$

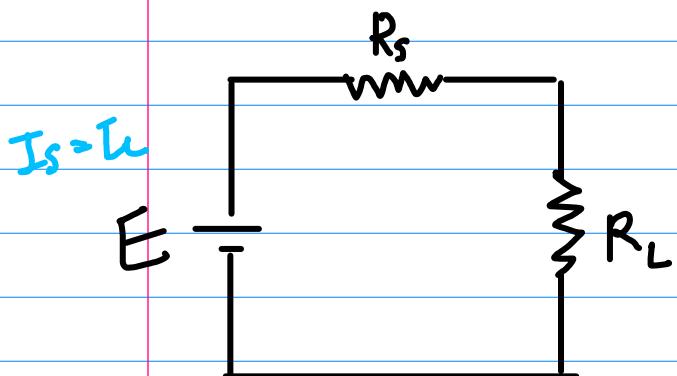

Voltage Divider



$$V_s : V_L = R_s : R_L$$

$$V_s = V_L$$

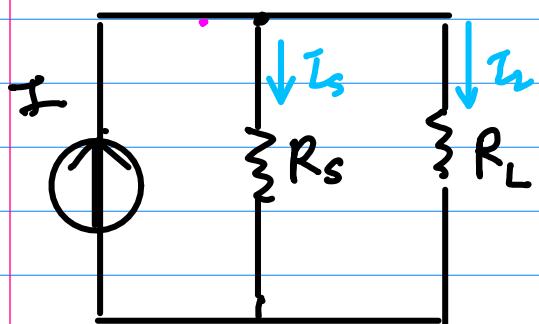


Current Divider

$$I_s : I_L = R_L : R_s$$

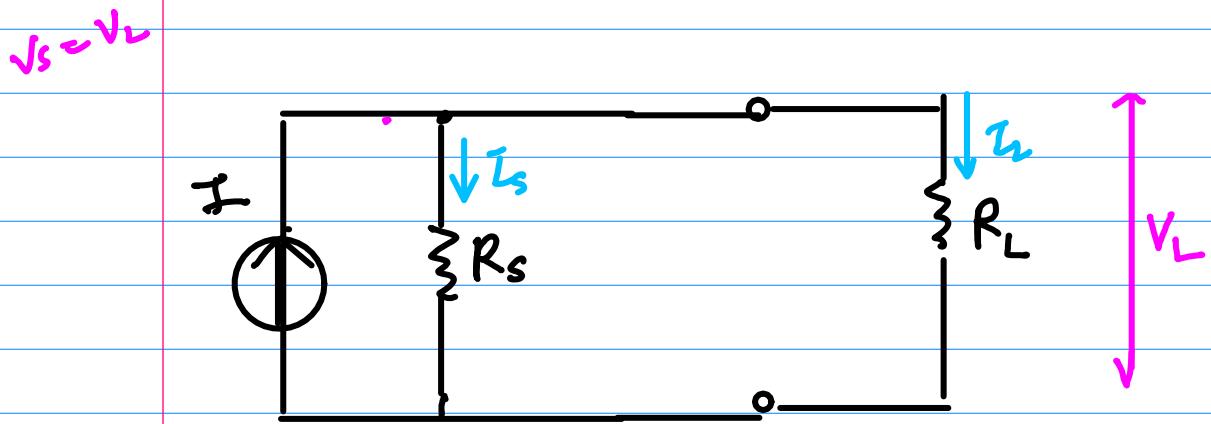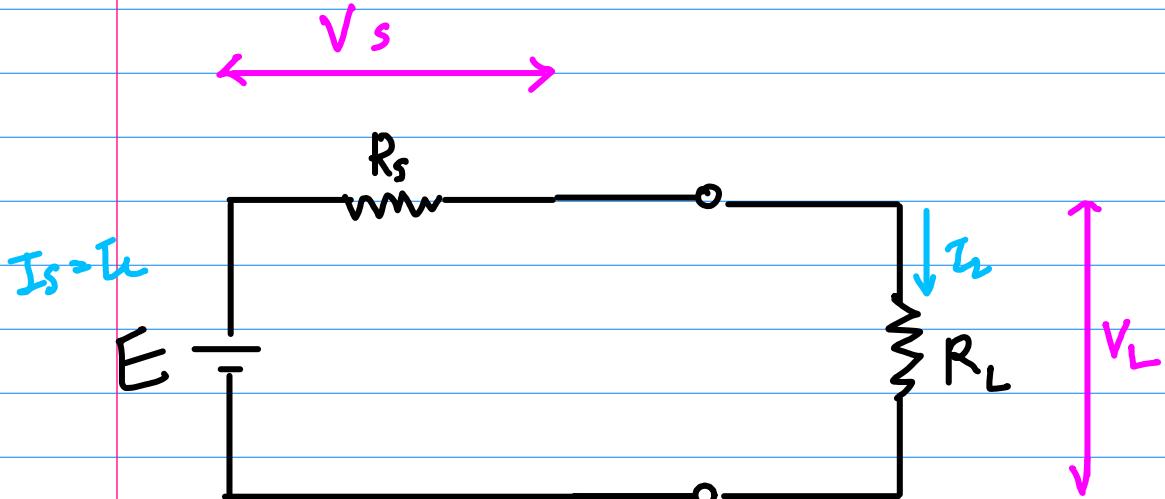


$$V_s$$

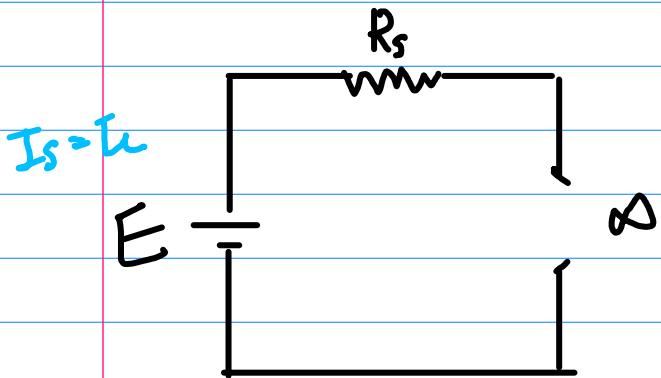

Voltage Divider

$$V_s : V_L = R_s : \infty$$

$$V_s = V_L$$

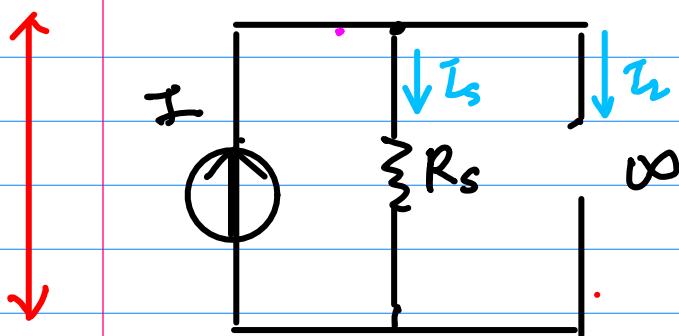

Current Divider

$$I_S : I_L = \infty : R_s$$

$$V = Z \cdot R_s$$

$$V_s$$


$$I_s = \frac{E}{R_s}$$

$$I = \frac{E}{R_s}$$

Voltage Divider

$$\frac{V_s}{E} : \frac{V_L}{E} = \frac{R_s}{R_s + 0}$$

$$V_s = V_L$$

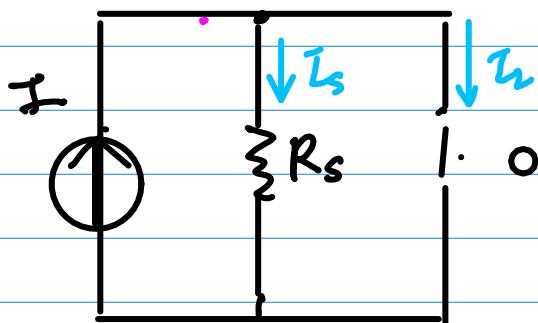

Current Divider

$$\frac{I_s}{E} : \frac{I_L}{E} = \frac{0}{R_s} : \frac{1}{R_s}$$

$$V_s$$

$$I_S = I_L$$

$$6 \text{ V}$$

2

4


$$V_L$$

Voltage Divider

$$V_s : V_L = 2 : 4$$

$$6 \text{ V} \approx 2 \text{ V}, 4 \text{ V}$$

$$I_S = I_L$$

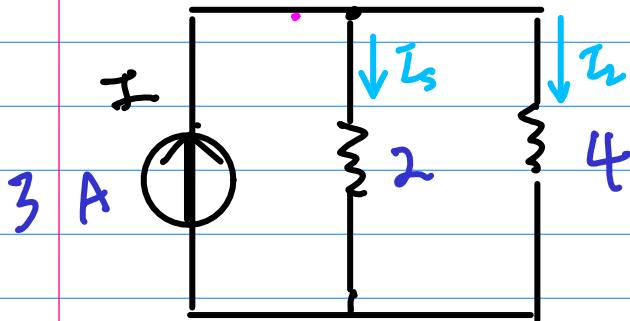


Current Divider

$$I_S : I_L = 4 : 2$$

$$1 \text{ A} \approx \frac{2}{3} \text{ A}, \frac{1}{3} \text{ A}$$

$$3 \text{ A} \approx 2 \text{ A}, 1 \text{ A}$$


$$\xleftarrow{\sqrt{s}}$$


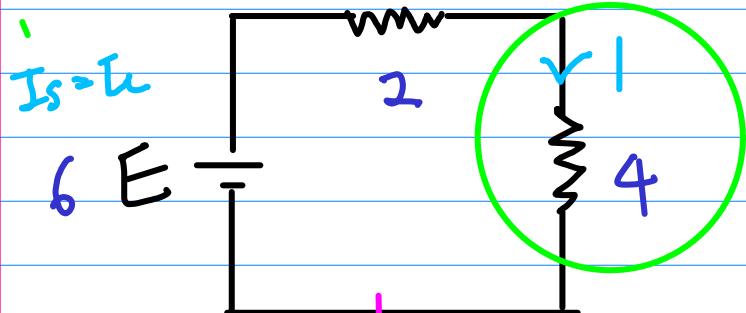



$$Z = I \cdot Z$$

$$Z = 3$$

$$\sqrt{s} = V_L$$

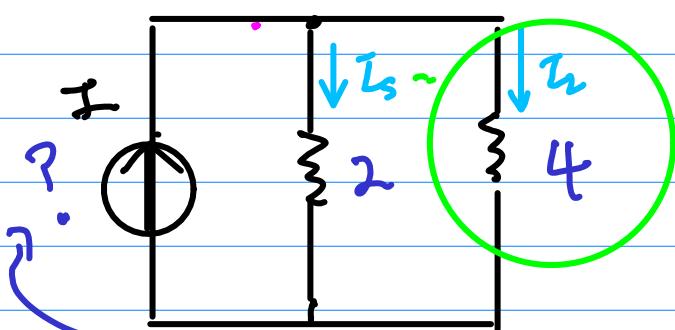


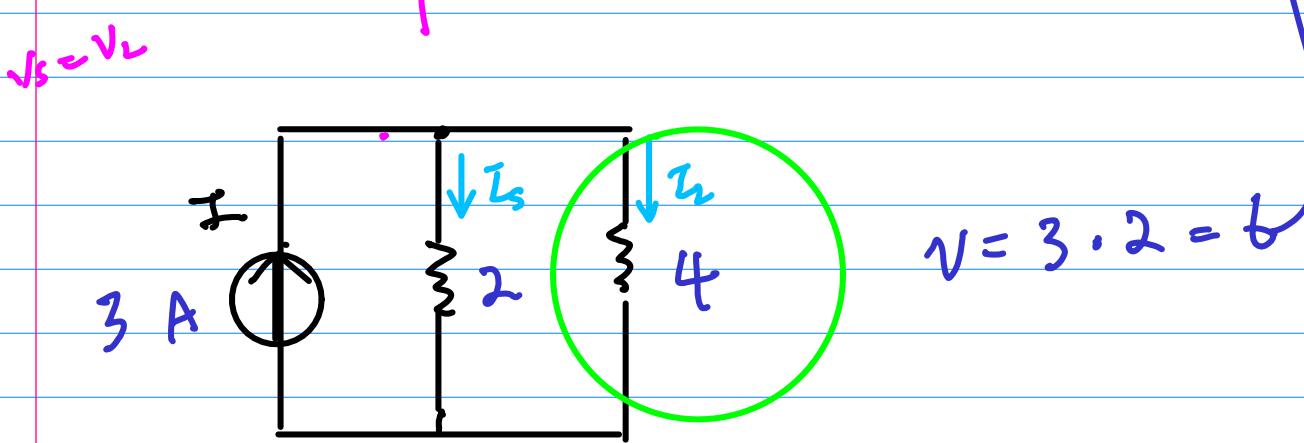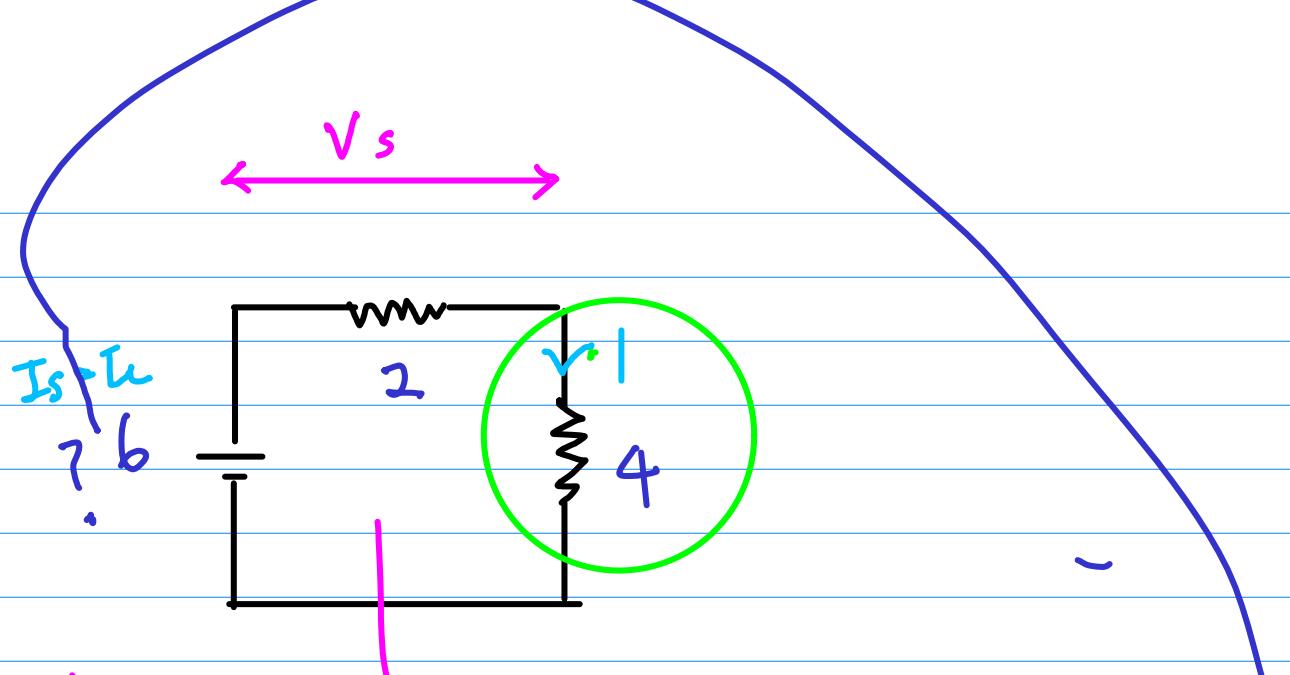

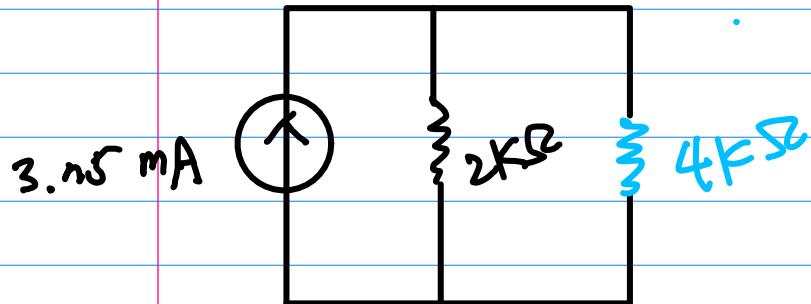

$$I_L \approx 3.15 \times \frac{1}{3}$$

$$V_L = \frac{4}{3} \times 3.15$$




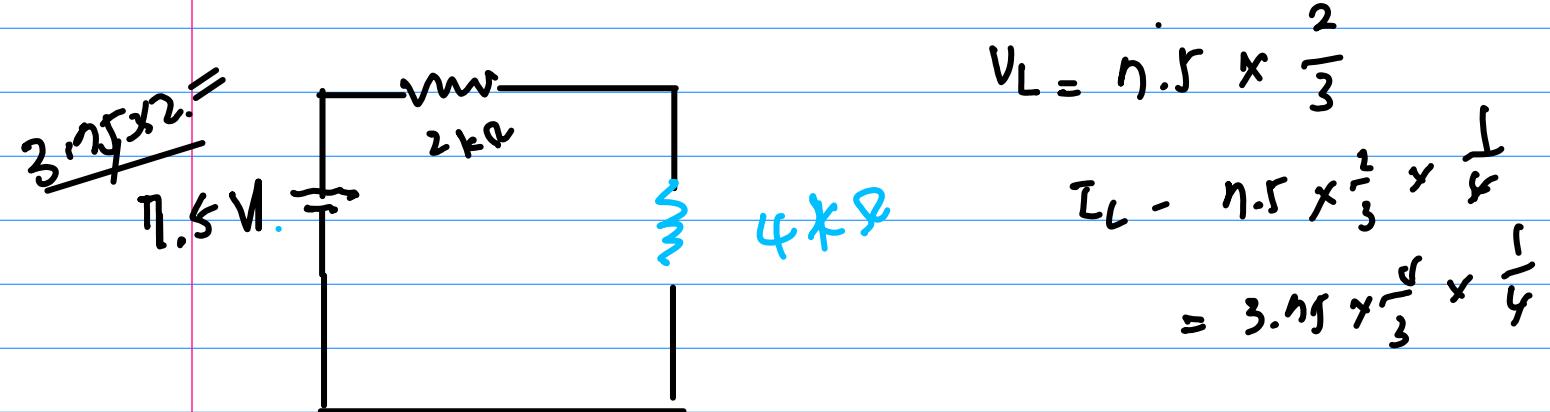


$$V_L = 7.5 \times \frac{2}{3}$$

$$\begin{aligned} I_L &= 7.5 \times \frac{2}{3} \times \frac{1}{4} \\ &= 3.15 \times \frac{4}{3} \times \frac{1}{4} \end{aligned}$$

5.625

$$15V - 5.625 \times 2$$

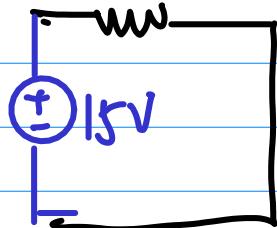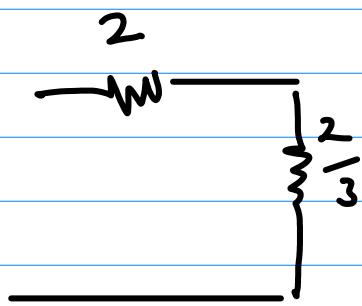
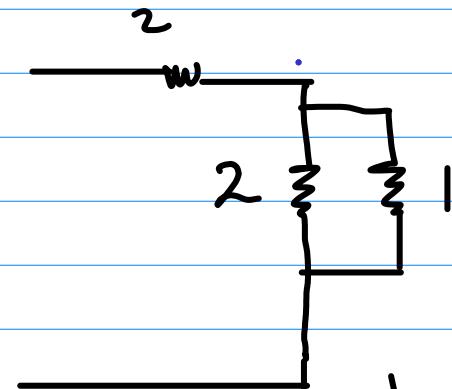
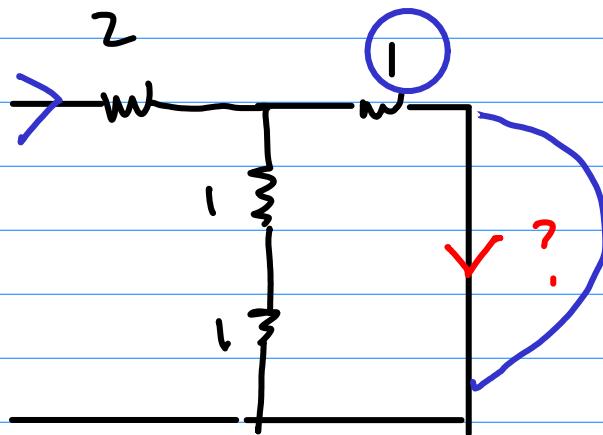




$$\frac{\frac{8}{3}F_r}{\frac{1}{2} + \frac{1}{1}} = \frac{\frac{3}{2}}{\frac{2}{3}}$$

$$15 \times \frac{3}{8} = 5 \quad 2 + \frac{2}{3} = \frac{8}{3}$$



$$I_e = \frac{V}{R} =$$

$$= \frac{15}{8} = 5$$

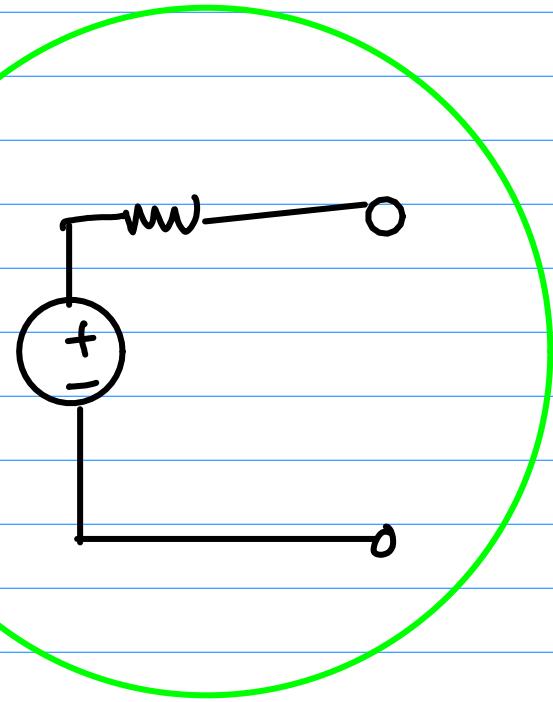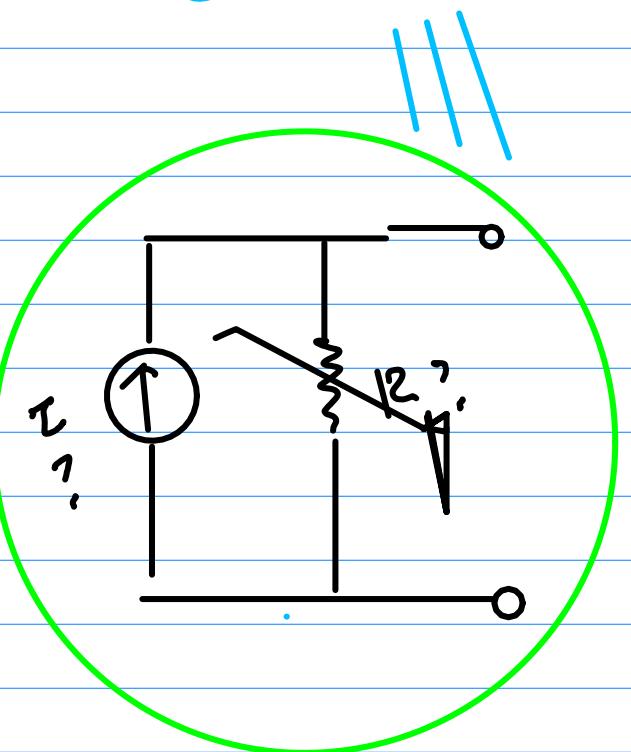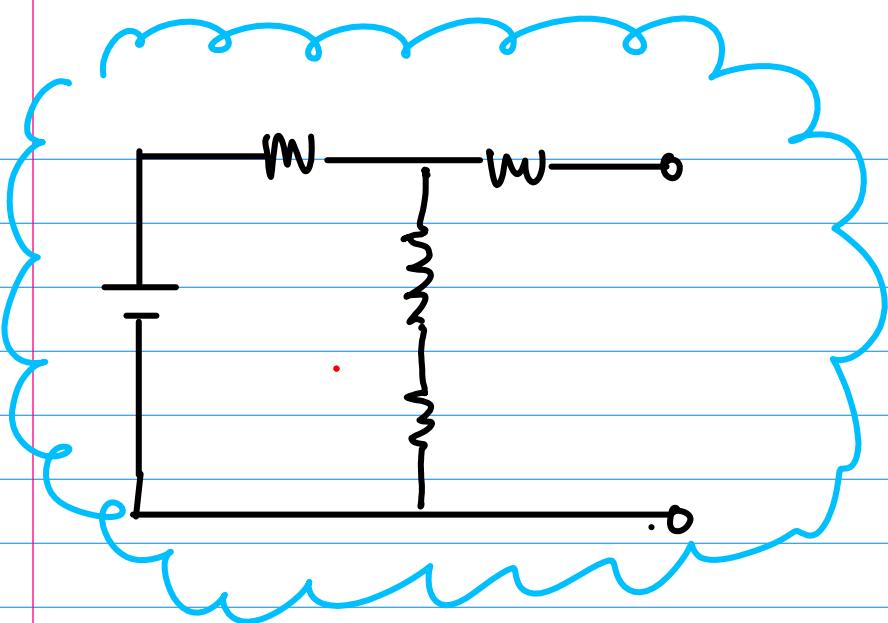

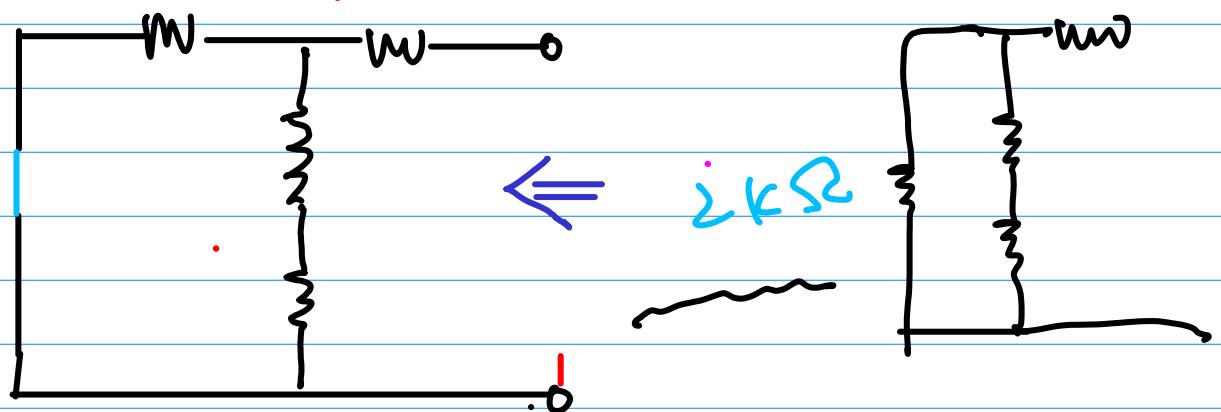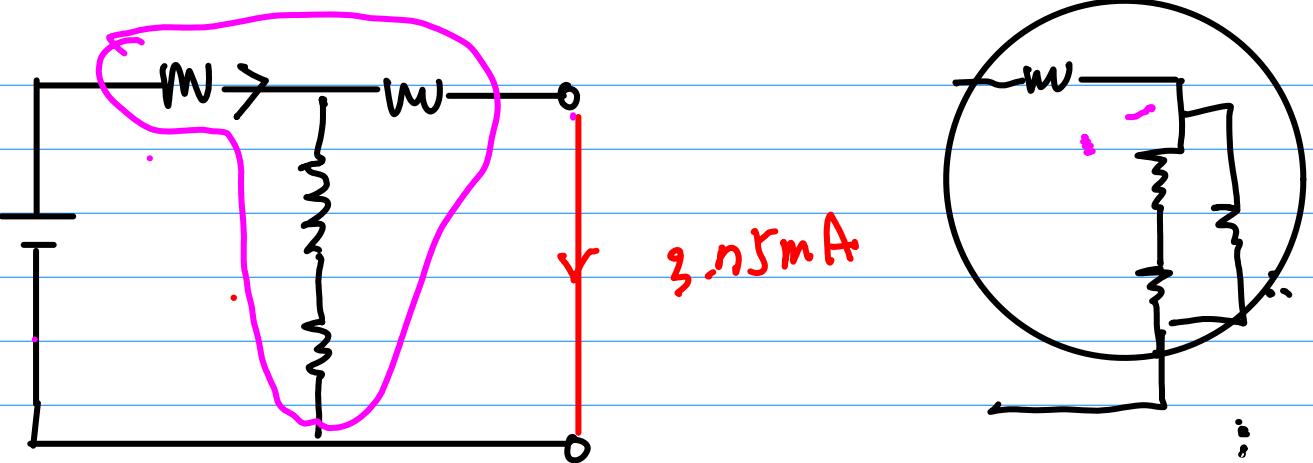

Mesh analysis

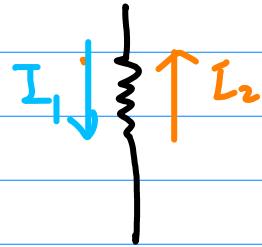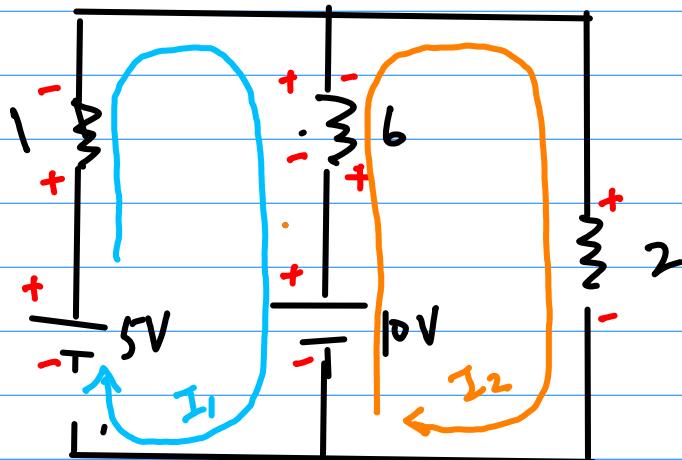


$$5 - 1(I_1) - 6(I_1 - I_2) - 10 = 0$$

$$10 - 6(I_2 - I_1) - 2(I_2) = 0$$

$$-7I_1 + 6I_2 = 5$$

$$6I_1 - 8I_2 = -10$$

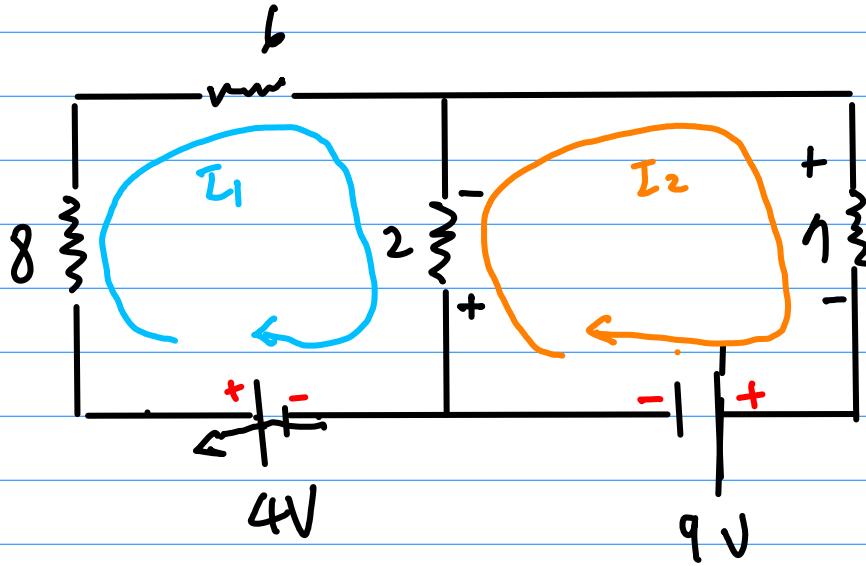


$$4 - 8(I_1) - 6(I_1) - 2(I_1 - I_2) = 0$$

$$-16I_1 + 2I_2 = -4$$

$$\textcircled{-9} - 2(I_2 - I_1) - 7(I_2) = 0$$

$$2I_1 - 9I_2 = 9$$

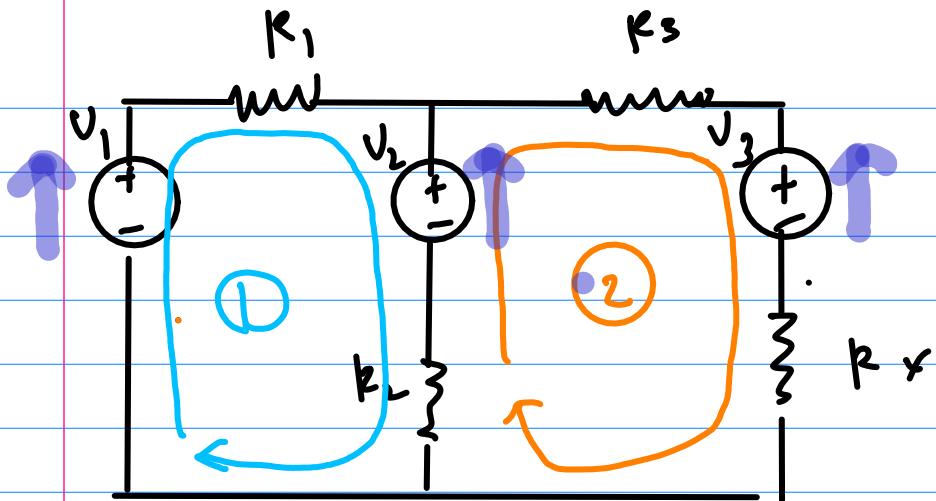


$$V_1 - R_1 (I_1) - V_2 - R_2 (I_1 - I_2) = 0$$

$$(V_2 - R_3 (I_2)) (-V_3) - R_x (I_2) - R_2 (I_2 - I_1) = 0$$

$$V_2 - V_3 - (R_2 + R_3 + R_x) I_2 + R_2 I_1 = 0$$
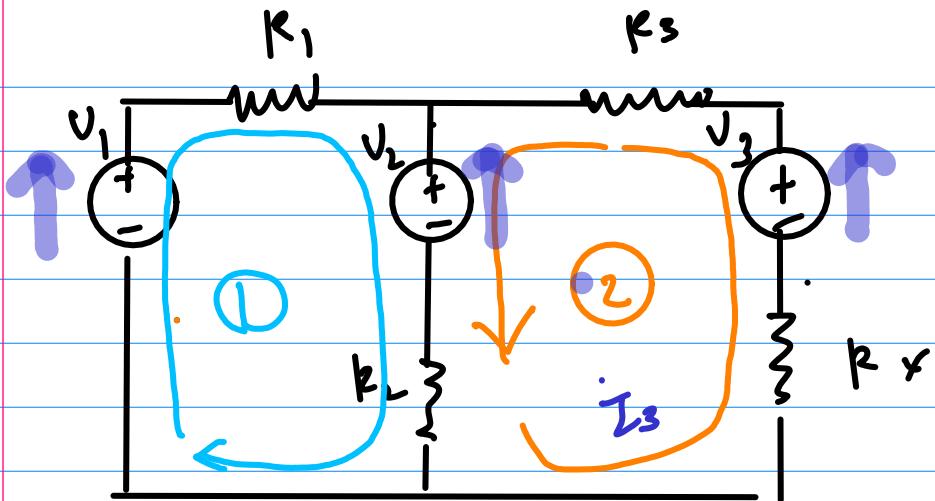
$$-V_2 + V_3 + (R_2 + R_3 + R_x) I_2 - R_2 I_1 = 0$$




$$-V_2 - R_2 (I_3 + I_1) - R_x (I_3) + V_3 - R_3 (I_3) = 0$$

$$-V_2 + V_3 - (R_2 + R_3 + R_x) I_3 - R_2 I_1 = 0$$

$$-V_2 + V_3 + (R_2 + R_3 + R_x) I_2 - R_2 I_1 = 0$$


0121 3.8 p85 22 3.19

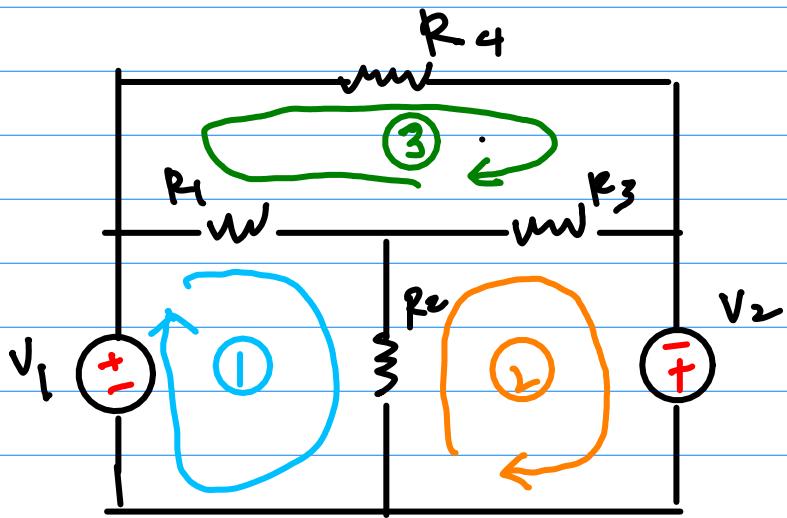

$$\textcircled{1} \quad V_1 - R_1 (I_1 - I_3) - R_2 (I_1 - I_2) = 0$$

$$\textcircled{2} \quad -R_2 (I_2 - I_1) - R_3 (I_2 - I_3) + V_2 = 0$$
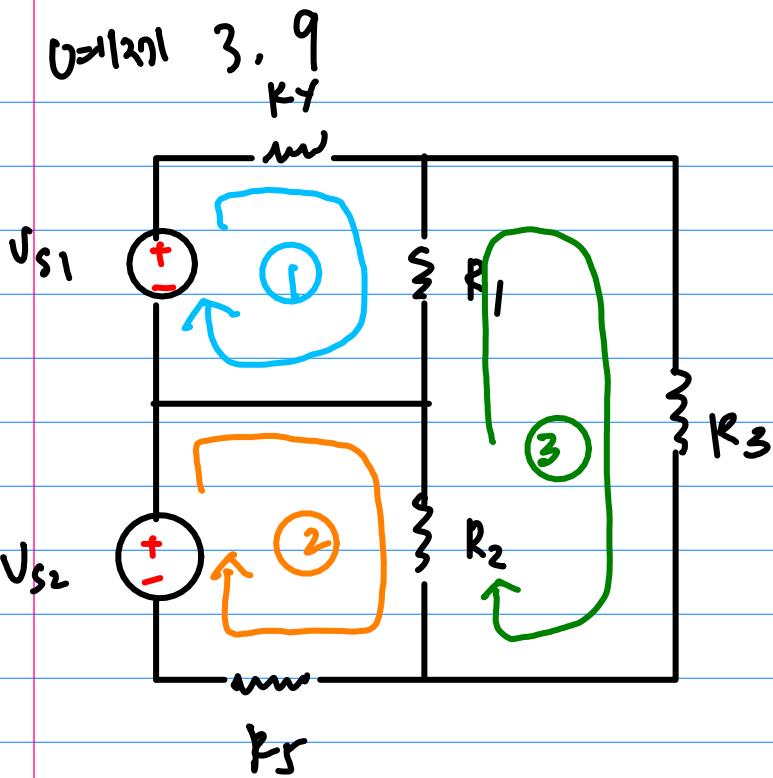
$$\textcircled{3} \quad -R_1 (I_3 - I_4) - R_4 (I_3 - I_1) - R_3 (I_3 - I_2) = 0$$



$$① +V_{S1} - R_4 (I_1) - R_1 (I_1 - I_3) = 0$$

$$② V_{S2} - R_2 (I_2 - I_3) - R_5 (I_2) = 0$$

$$③ -R_1 (I_3 - I_1) - R_3 (I_3) - R_2 (I_3 - I_2) = 0$$

p85 2014r.

$$\begin{aligned} -15 i_1 - 10 i_2 &= 1 \\ -10 i_1 + 20 i_2 &= 8 \end{aligned}$$

$$\begin{bmatrix} 15 & -10 \\ -10 & 20 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 1 \\ 8 \end{bmatrix}$$

$$\begin{vmatrix} 15 & -10 \\ -10 & 20 \end{vmatrix} = +300 - (-100) = 200$$

$$\begin{vmatrix} 1 & -10 \\ 8 & 20 \end{vmatrix} = 20 + 80 = 100 \quad \frac{100}{200}$$

$$\begin{vmatrix} 15 & 1 \\ -10 & 8 \end{vmatrix} = 120 + 60 = 180 \quad \frac{180}{200}$$

