

FSM Examples

Copyright (c) 2011 - 2015 Young W. Lim.


Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.

Latches and FF's

FSM Inputs and Outputs

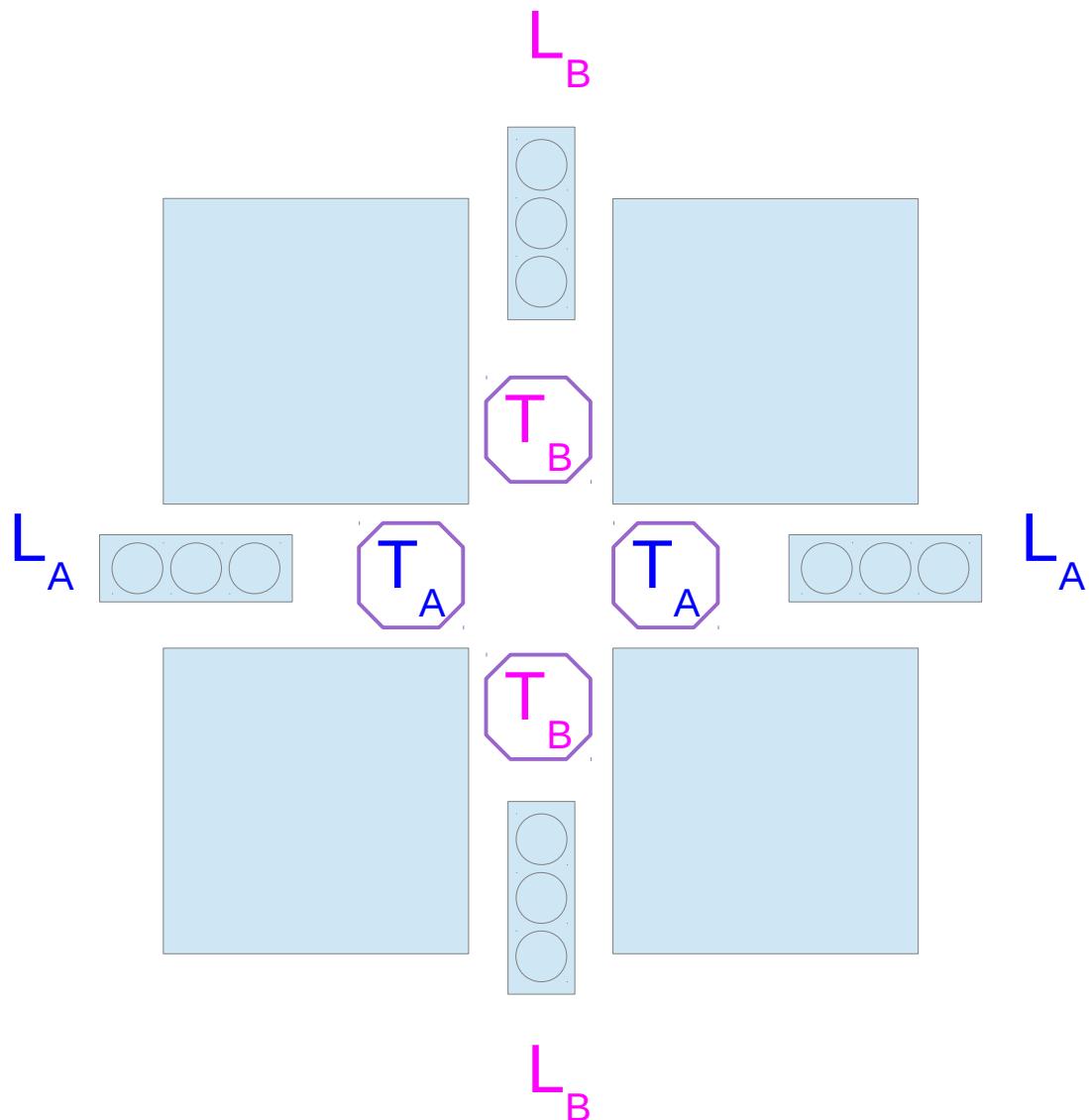


Traffic Lights - Outputs

L_A L_B

Sensor - Inputs

T_A T_B

States

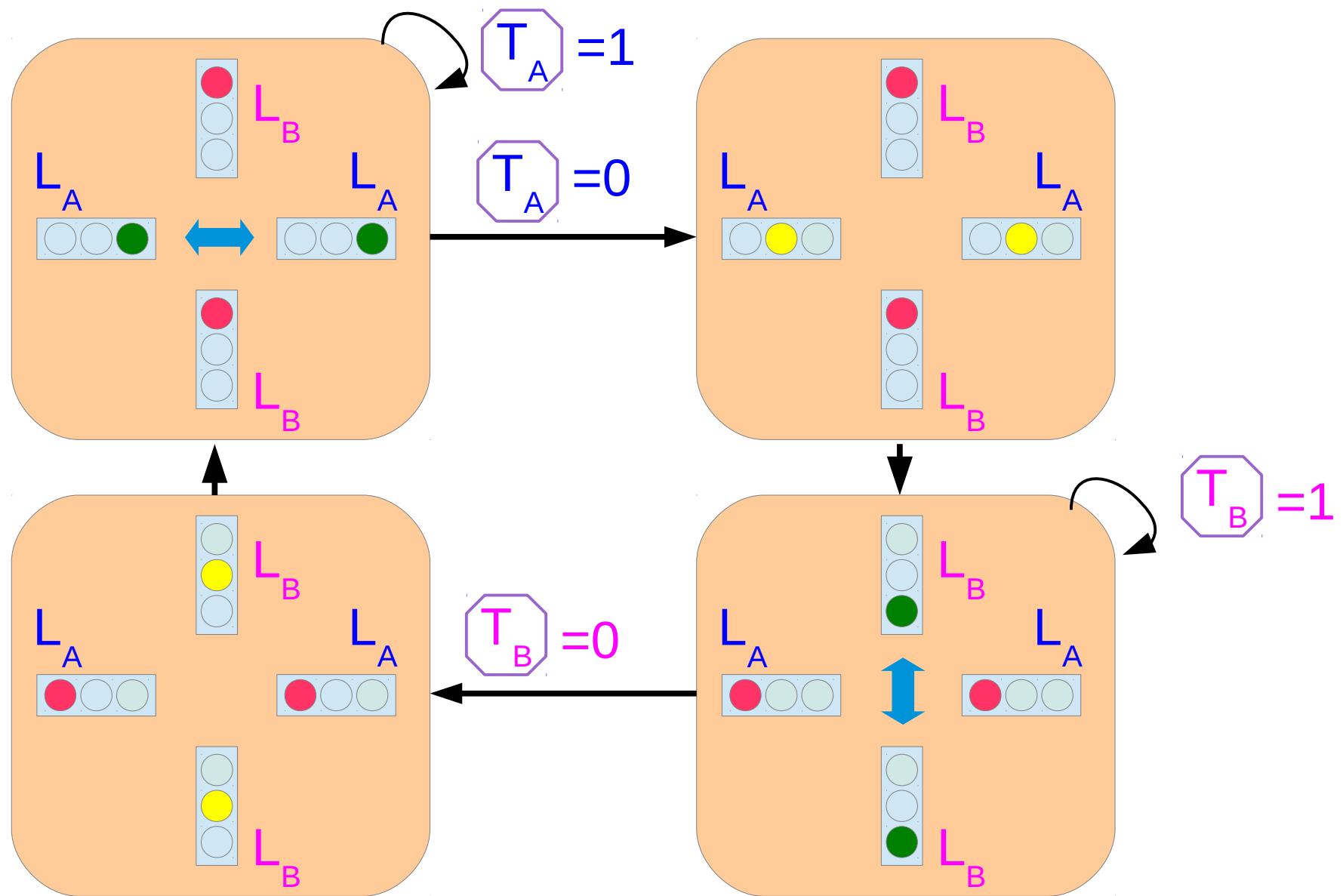

Moore FSM State Transition Table

S_1	S_0	T_A	T_B	S'_1	S'_0
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

S_1	S_0	T_A	T_B	S'_1
0	0	0	X	0
0	0	1	X	0
0	1	X	X	1
1	0	X	0	1
1	0	X	1	1
1	1	X	X	0

$\overline{S}_1 S_0$

$S_1 \overline{S}_0 T_B$

$S_1 \overline{S}_0 T_B$

S_1	S_0	T_A	T_B	S'_0
0	0	0	X	1
0	0	1	X	0
0	1	X	X	0
1	0	X	0	1
1	0	X	1	0
1	1	X	X	0

$S_1 \overline{S}_0 \overline{T}_A$


$S_1 \overline{S}_0 \overline{T}_B$

$$\begin{aligned} S'_1 &= \overline{S}_1 S_0 + S_1 \overline{S}_0 \\ &= S_1 \oplus S_0 \end{aligned}$$

$$S'_0 = \overline{S}_1 \overline{S}_0 \overline{T}_A + S_1 \overline{S}_0 \overline{T}_B$$

States

S_1	S_2	L_{A1}	L_{A0}	L_{B1}	L_{B0}
0 0	0 0	1 0			
0 1	0 1	1 0			
1 0	1 0	0 0			
1 1	1 0	0 1			

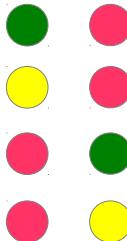

S_1	S_2	L_{A1}
0 0	0	
0 1	0	
	1 0	1
	1 1	1

$$L_{A1} = S_1$$

S_1	S_2	L_{A0}
0 0	0	
	0 1	1
1 0	0	
1 1	0	

$$L_{A0} = \overline{S}_1 S_0$$

- 00
- 01
- 10




S_1	S_2	L_{B1}
	0 0	1
	0 1	1
1 0		0
1 1		0

$$L_{B1} = \overline{S}_1$$


S_1	S_2	L_{B0}
0 0		0
0 1		0
1 0		0
1 1		1

$$L_{B0} = S_1 S_0$$

Moore FSM (1)

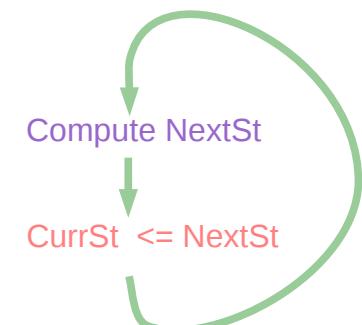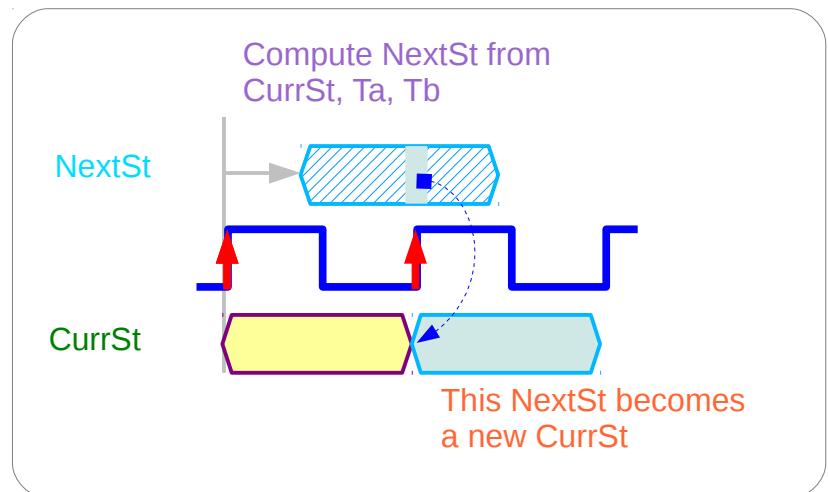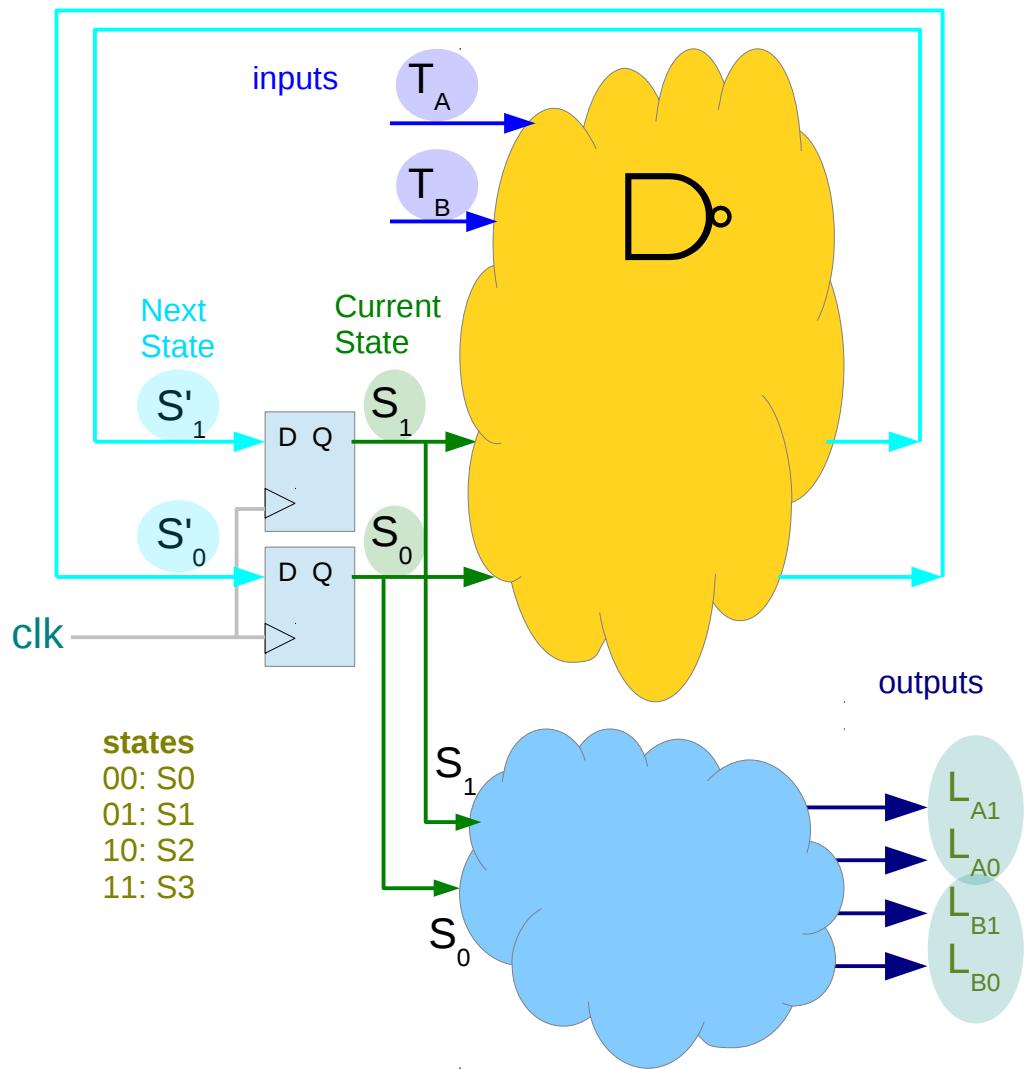

Moore FSM

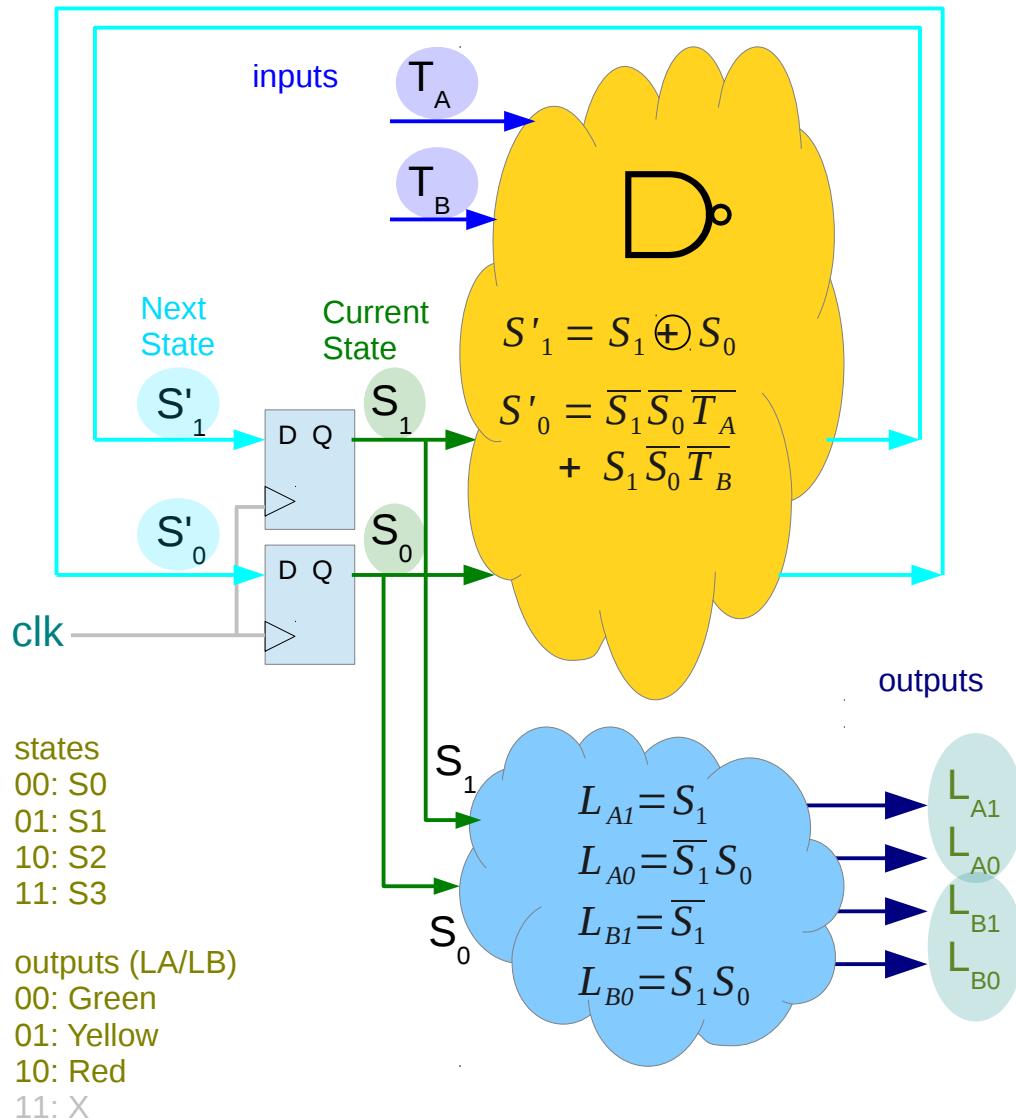

Inputs
Current State

T_A T_B
 S_1 S_0

Next States

$$S'_1 = S_1 \oplus S_0$$

$$S'_0 = \overline{S_1} \overline{S_0} T_A + S_1 \overline{S_0} T_B$$

Current State S_1 S_0

Outputs

$L_{A1} = S_1$	$L_{B1} = \overline{S}_1$
$L_{A0} = \overline{S_1} S_0$	$L_{B0} = S_1 S_0$

Verilog Gate Level Design - testbench

```
`timescale 1ns/100ps

module traffic_controller_testbench;
parameter cycle = 40;
reg clock;
always
begin
#(cycle/2) clock=~clock;
end

traffic_controller DUT (.clock(clock),
.reset(reset),
.TA(TA),
.TB(TB),
.LA(LA),
.LB(LB) );

reg      reset;
reg      TA, TB;
wire [1:0] LA, LB;

initial
begin
clock = 1;
reset = 1;
TA = 1;
TB = 0;

#1;
#(cycle)    reset = 0;
#(cycle)    TB = 1;
#(cycle)    TA = 0;
#(cycle*3)  TA = 1;
#(cycle*3)  TB = 0;
#(cycle*3)  TA = 0;
end

initial
begin
$dumpfile("traffic.vcd");
$dumpvars(0, DUT);
#(cycle * 10);
$finish;
end

endmodule
```

Verilog Gate Level Design – traffic_gate.v

```
module traffic_controller(clock, reset, TA, TB, LA, LB);
    input clock, reset;
    input TA, TB;
    output [1:0] LA, LB;

    reg [1:0] S;
    wire [1:0] NextS;

    always @(posedge clock)
        begin: SEQ
            if (reset)
                #8 S = 2'b00;
            else
                #8 S = NextS;
        end


        not #8 (S1b, S[1]);
        not #8 (S0b, S[0]);
        not #8 (TAb, TA);
        not #8 (TBb, TB);

        xor #8 (NextS[1], S[1], S[0]);
        or #8 (NextS[0], NS1, NS2);
        and #8 (NS1, S1b, S0b, TAb);
        and #8 (NS2, S[1], S0b, TBb);


        buf #8 (LA[1], S[1]);
        and #8 (LA[0], S1b, S[0]);
        not #8 (LB[1], S[1]);
        and #8 (LB[0], S[1], S[0]);

    endmodule
```


VCD Output with zero delay

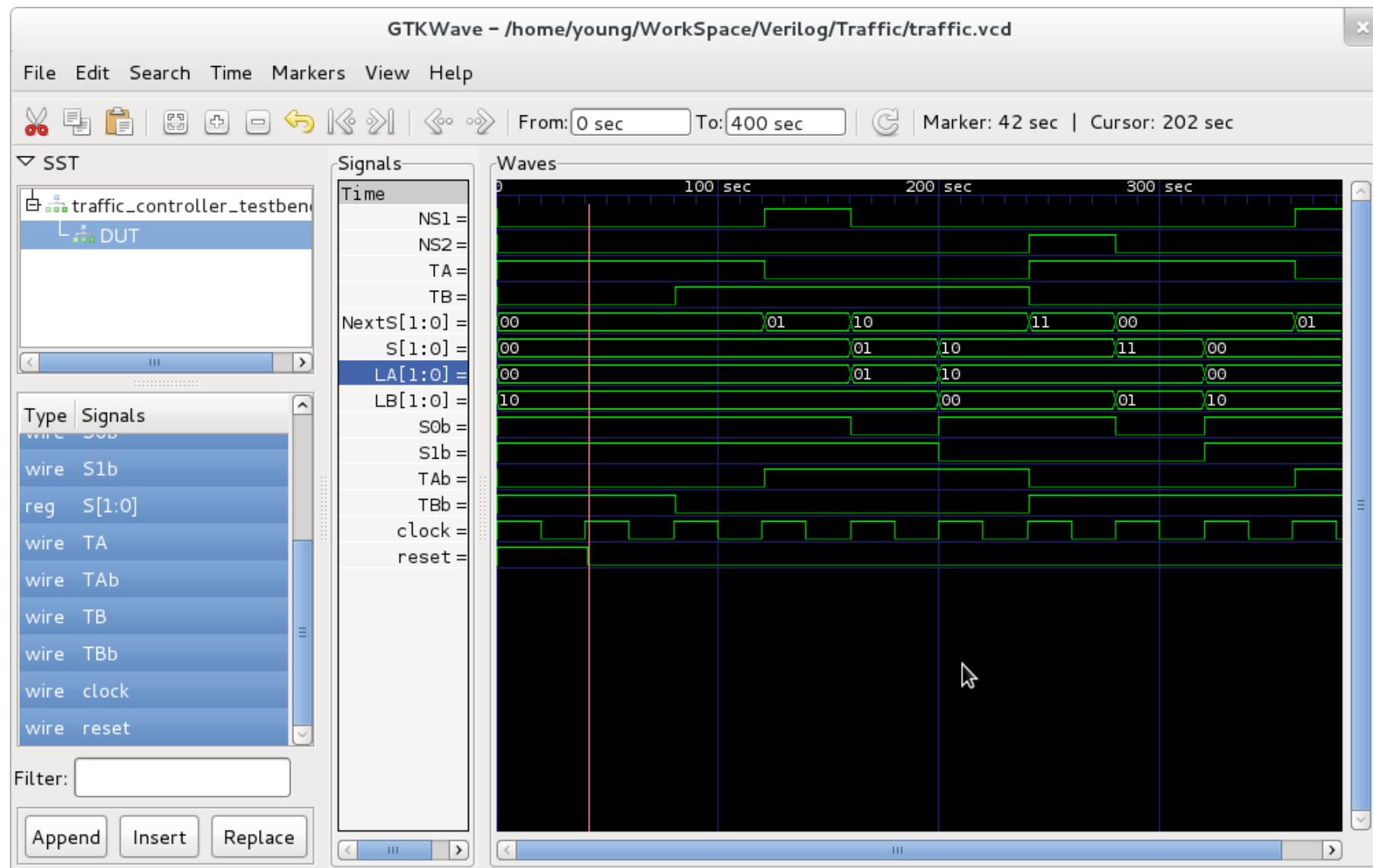


VCD Output with gate delays

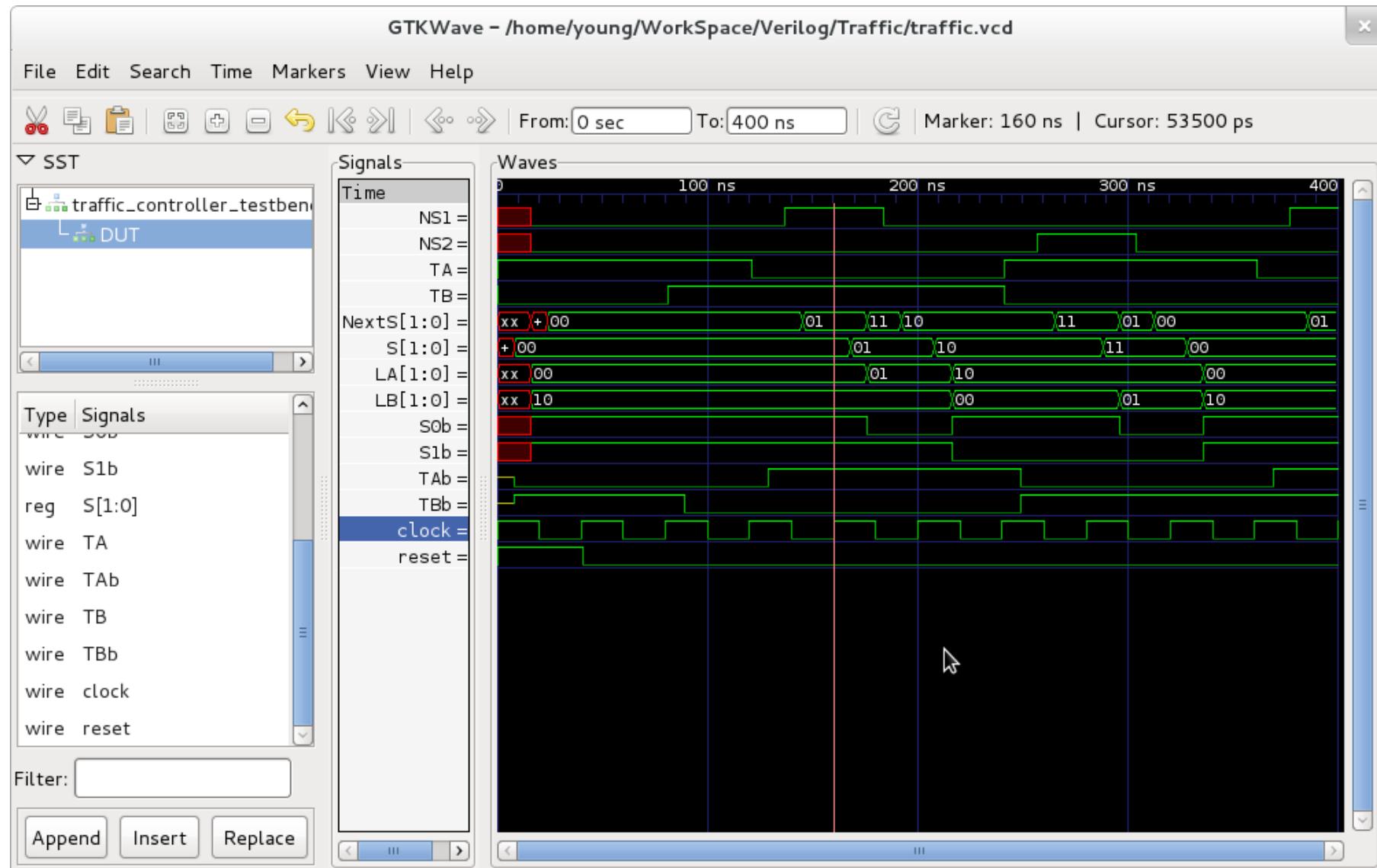


VCD Output with gate delays

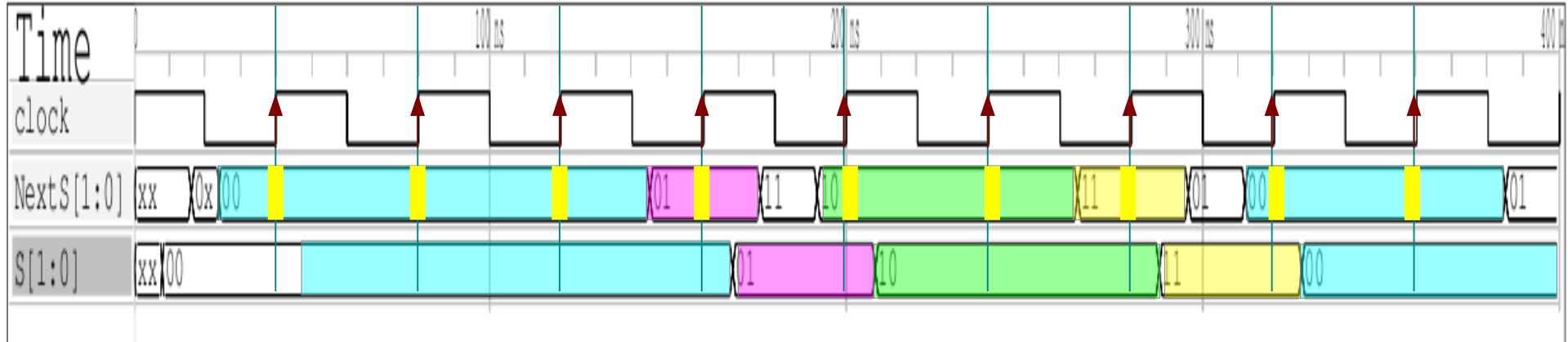

Output Delay

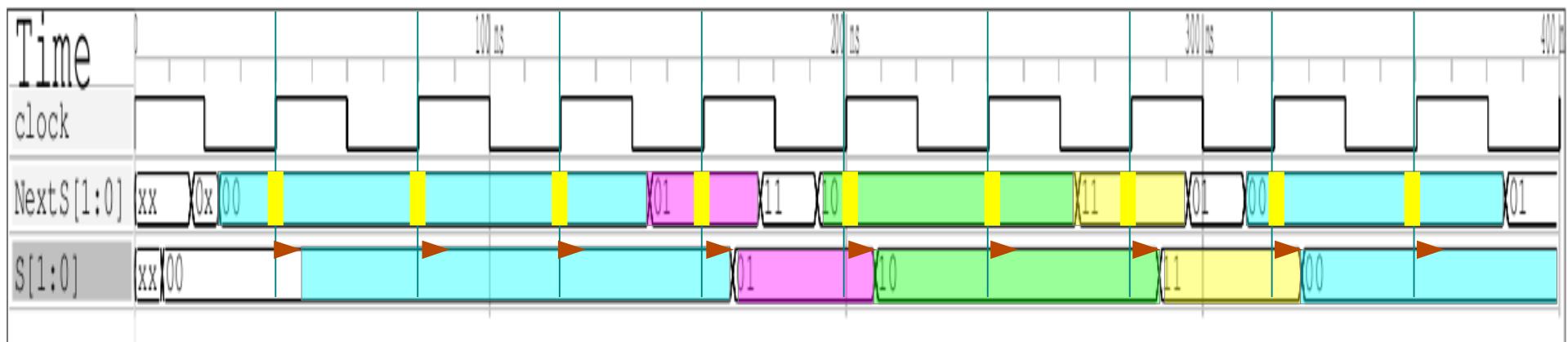

Divide By N Counter FSM

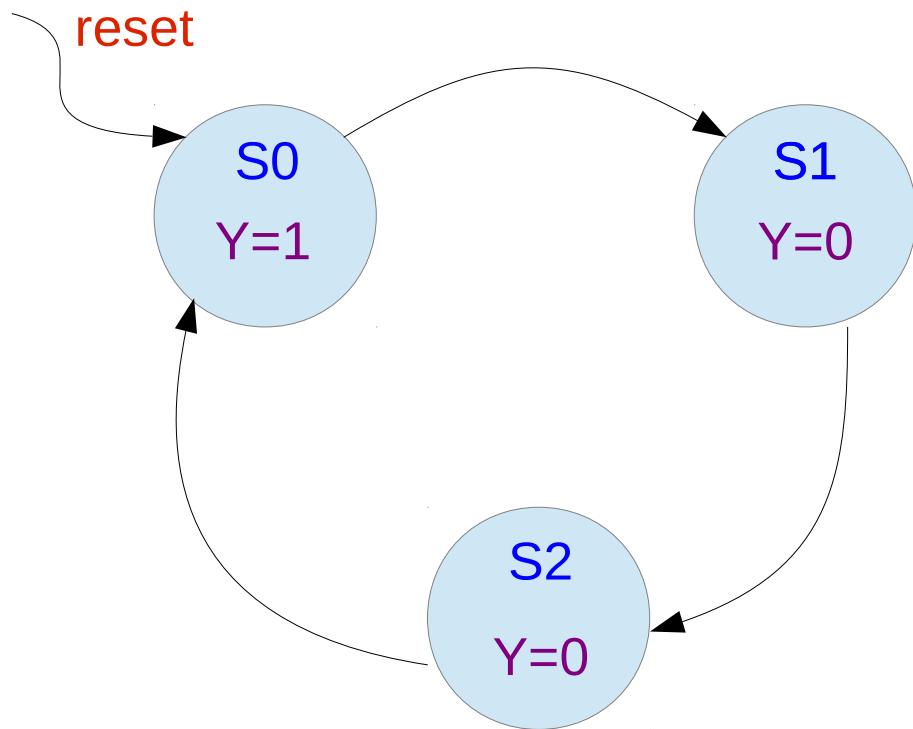

Input: none

Output: Y=1 every 3 cycles

State Transition Table

Curr St	Next St
S0	S1
S1	S2
S2	S0

Output Table

Curr St	Output
S0	1
S1	0
S2	0

Encoding States

State Transition Table

Curr St	Next St
S0	S1
S1	S2
S2	S0

Output Table

Curr St	Output
S0	1
S1	0
S2	0

State Transition Table

Curr St	Next St
S0	S1
S1	S2
S2	S0

Output Table

Curr St	Output
S0	1
S1	0
S2	0

S_1	S_0	S'_1	S'_0
0	0	0	1
0	1	1	0
1	0	0	0

S_1	S_0	Y
0	0	1
0	1	0
1	0	0

$$S'_1 = \overline{S}_1 S_0$$

$$S'_0 = \overline{S}_1 \overline{S}_0$$




$$Y = \overline{S}_1 \overline{S}_0$$

$$\begin{aligned} S'_2 &= \overline{S}_2 S_1 \overline{S}_0 & \Rightarrow S_1 \\ S'_1 &= \overline{S}_2 \overline{S}_1 S_0 & \Rightarrow S_0 \\ S'_0 &= S_2 \overline{S}_1 \overline{S}_0 & \Rightarrow S_2 \end{aligned}$$


$$Y = \overline{S}_2 \overline{S}_1 S_0 \Rightarrow S_0$$

Resolution Time

FF Timing (Ideal)

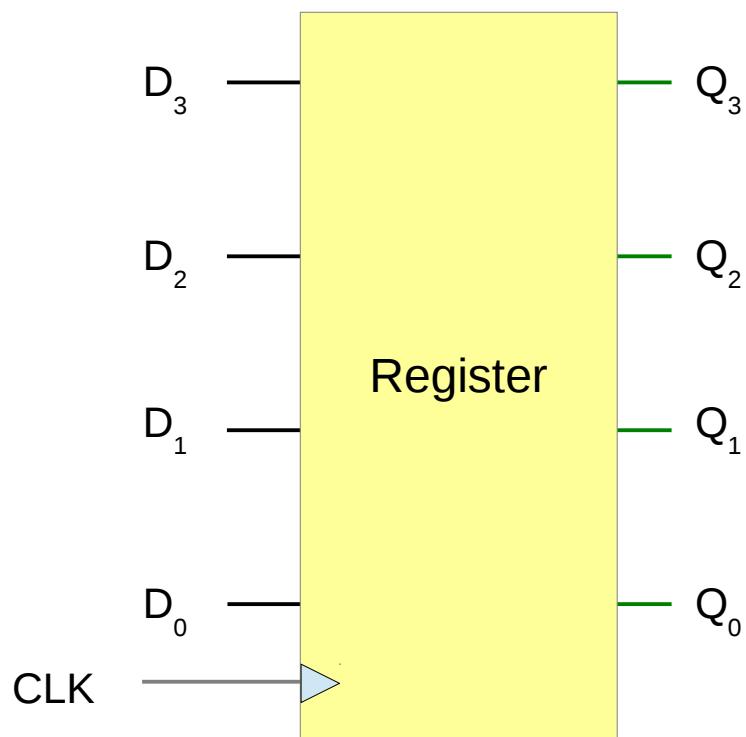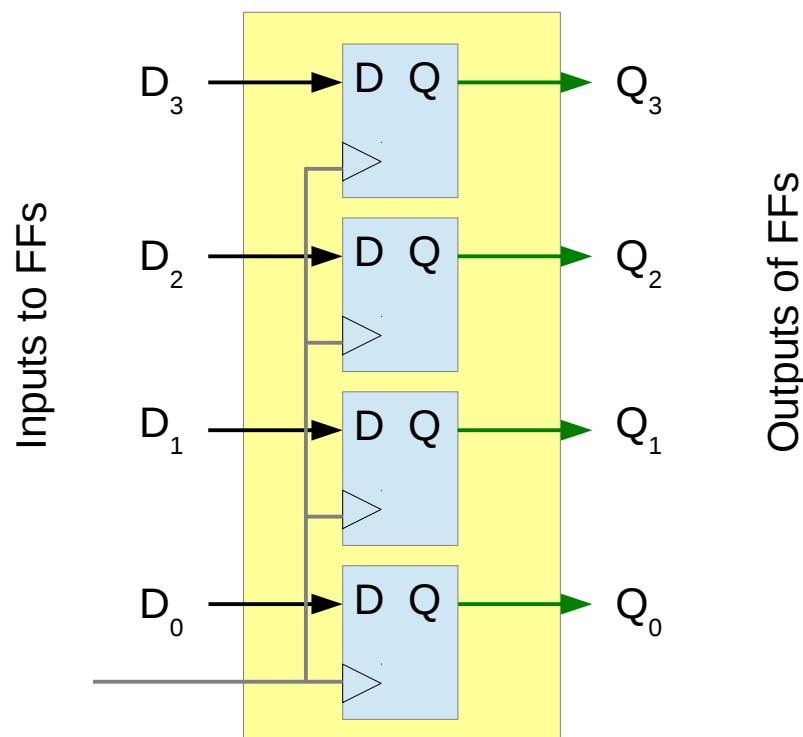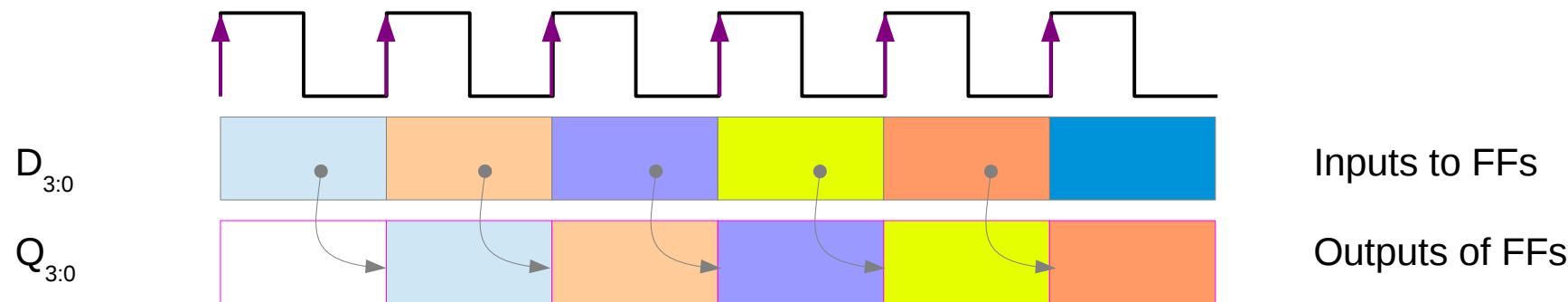


Sequence of States

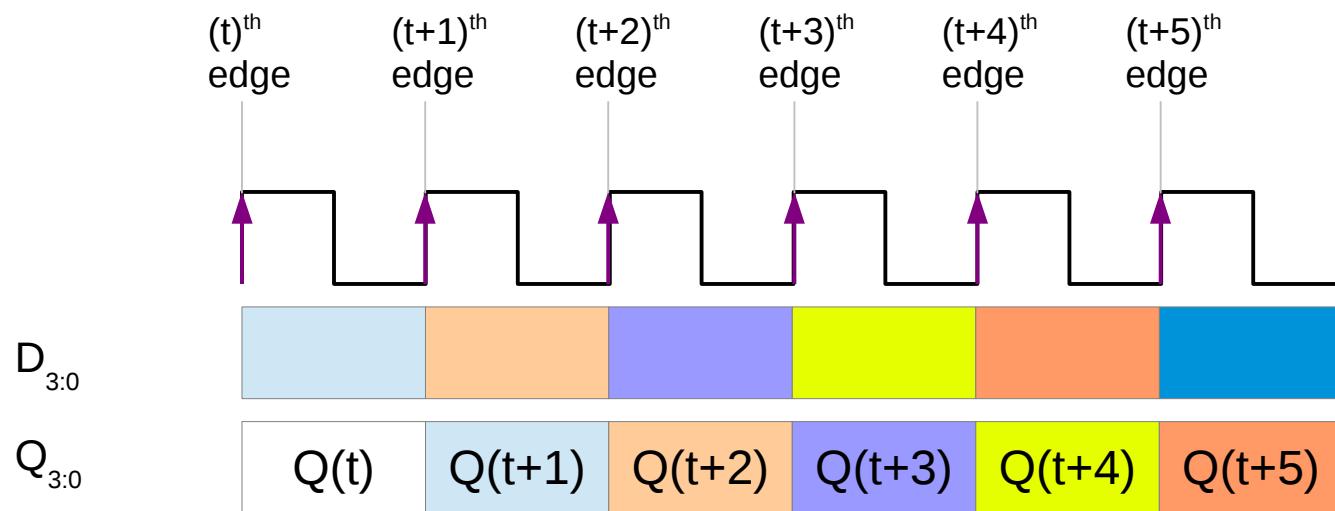

Inputs to FFs



Outputs of FFs

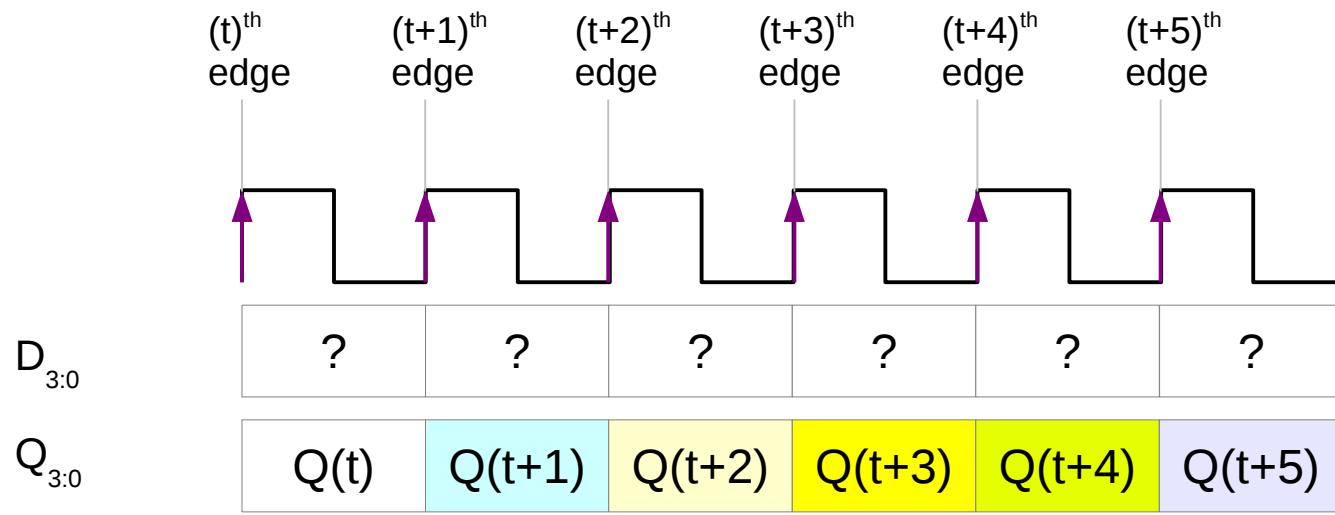



Find inputs to FFs

which will make outputs
in this sequence

When NextSt becomes CurrSt

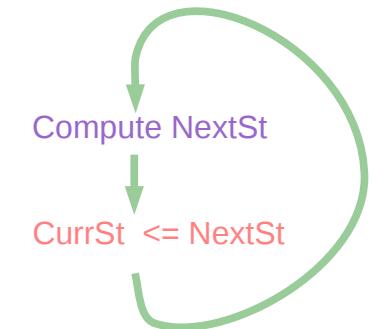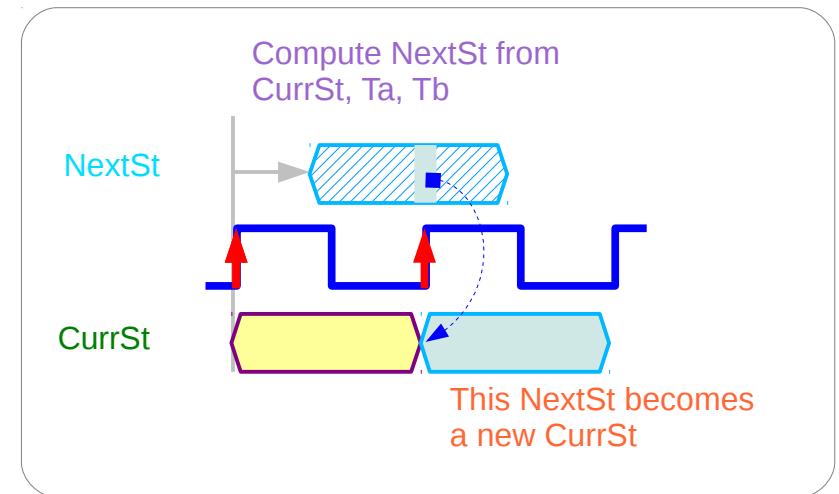

Finding FF Inputs

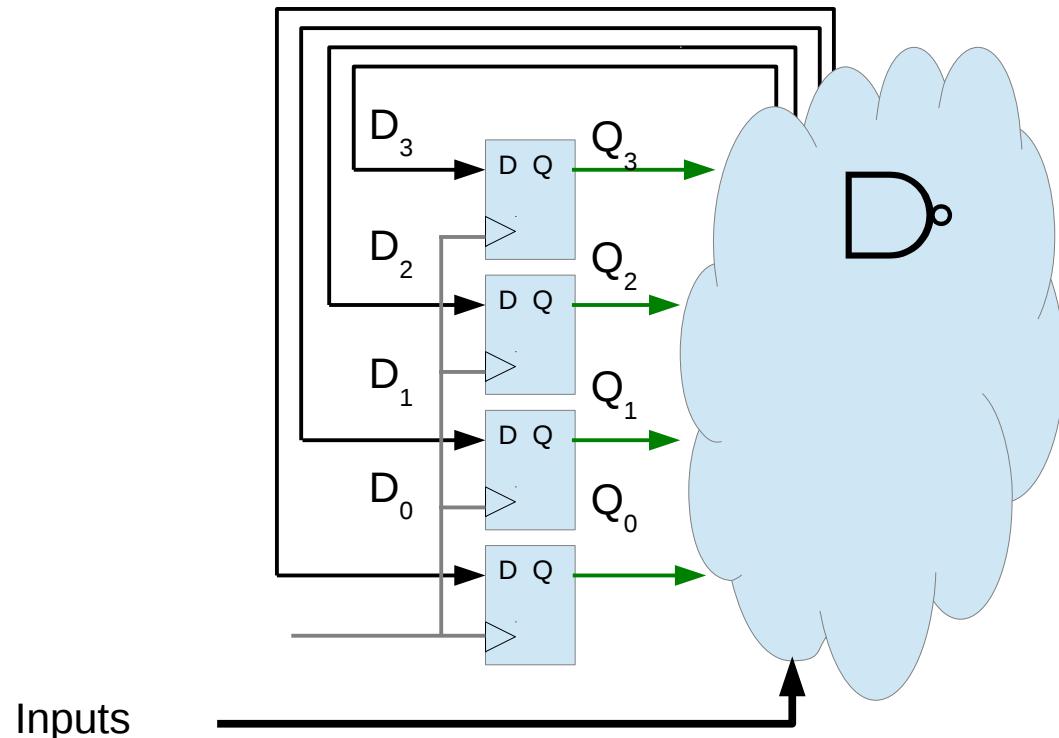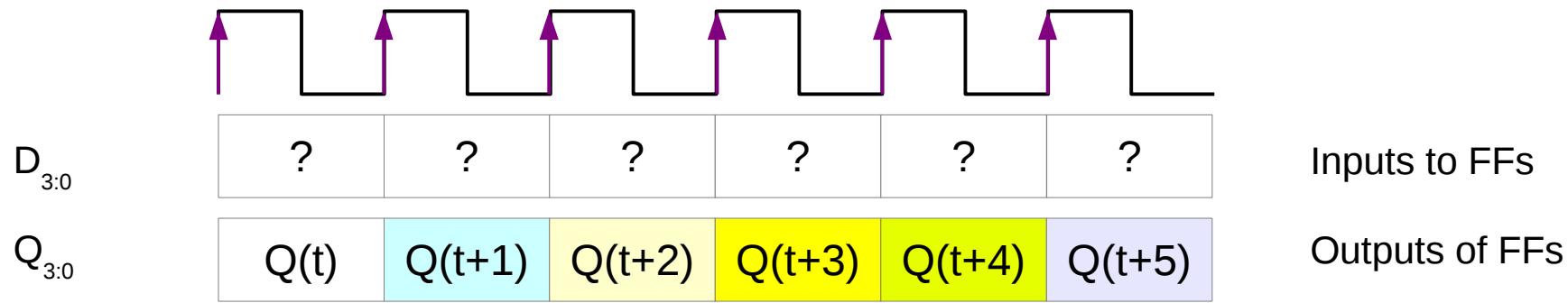


During the t^{th} clock edge period,

Compute the next state $Q(t+1)$ using the current state $Q(t)$ and other external inputs


Place it to FF inputs

After the next clock edge, $(t+1)^{\text{th}}$, the computed next state $Q(t+1)$ becomes the current state


Method of Finding FF Inputs

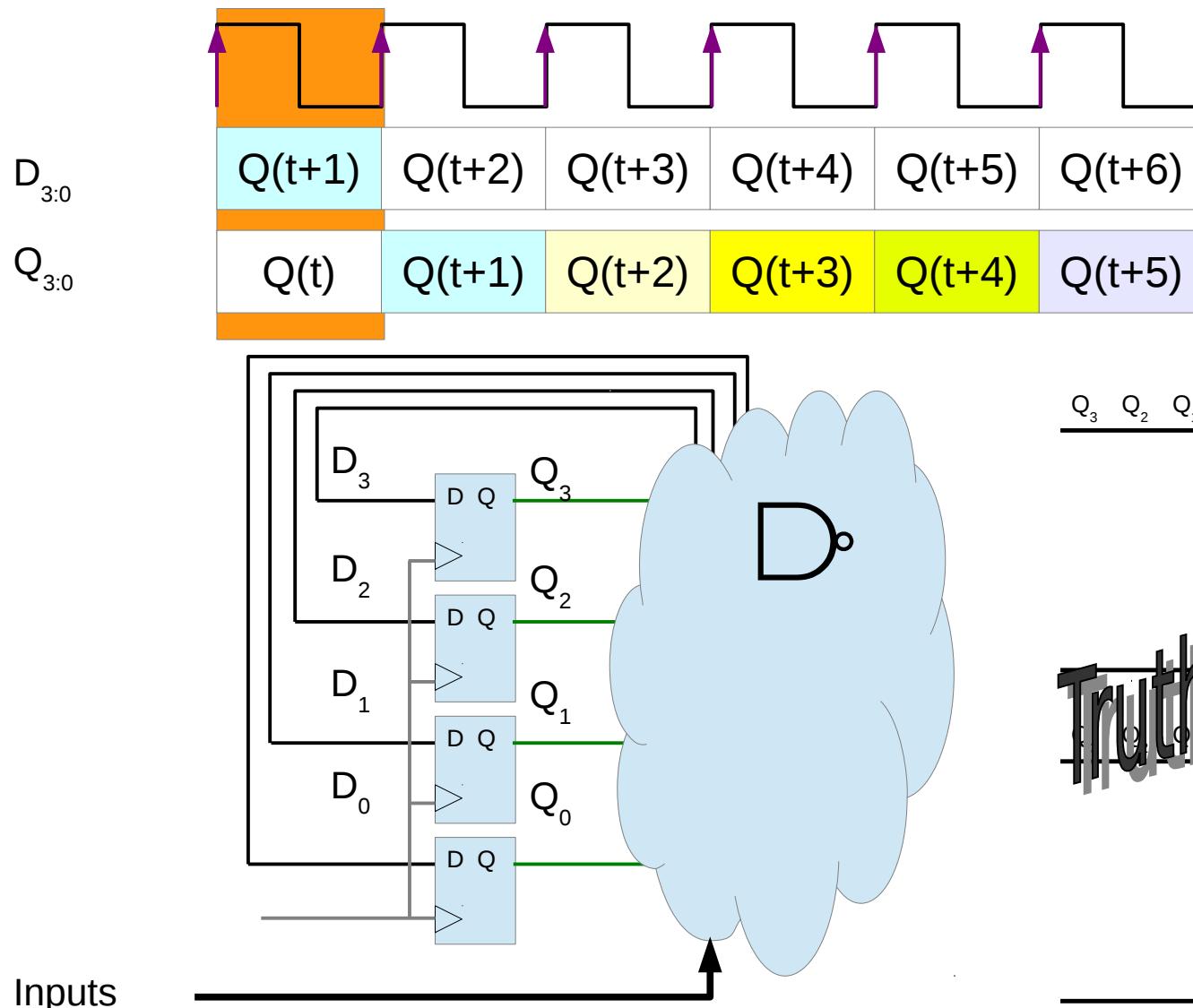


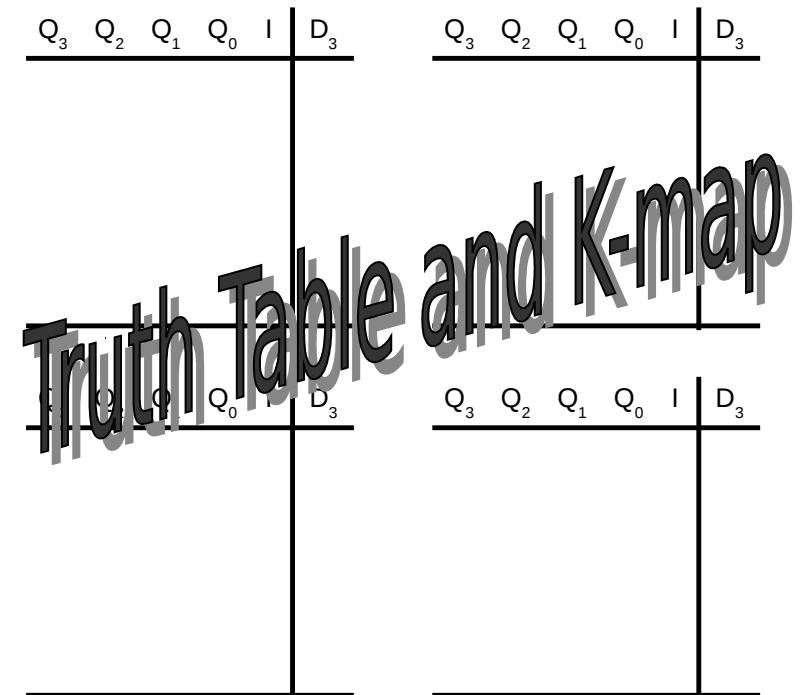
Find the **boolean functions**
D₃, D₂, D₁, D₀
in terms of Q₃, Q₂, Q₁, Q₀,
and external inputs
for all possible cases.



State Transition

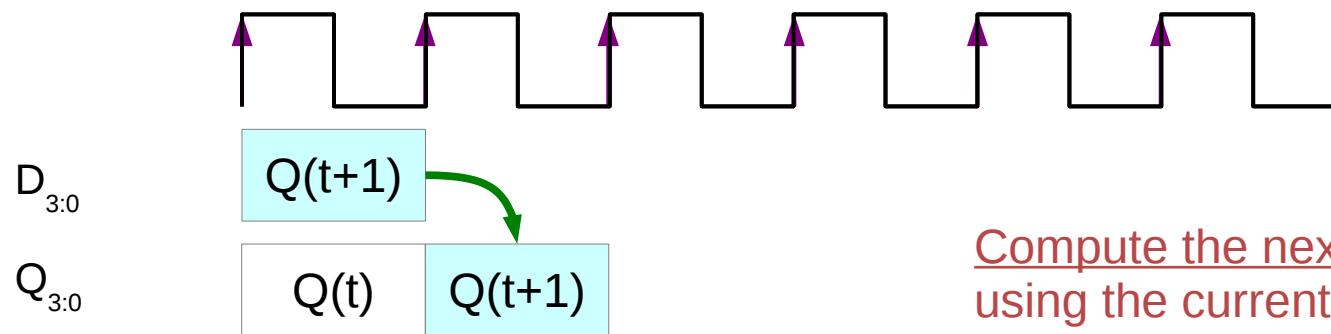


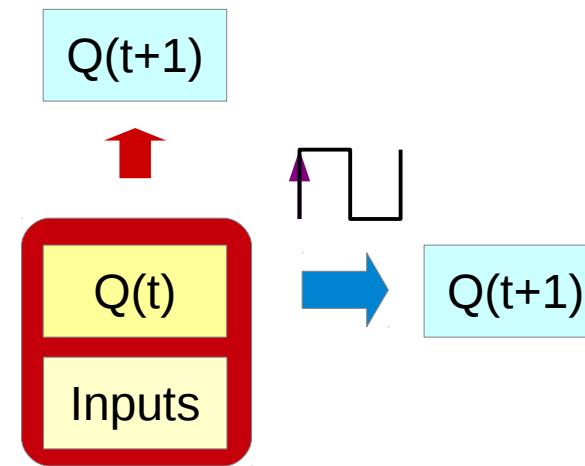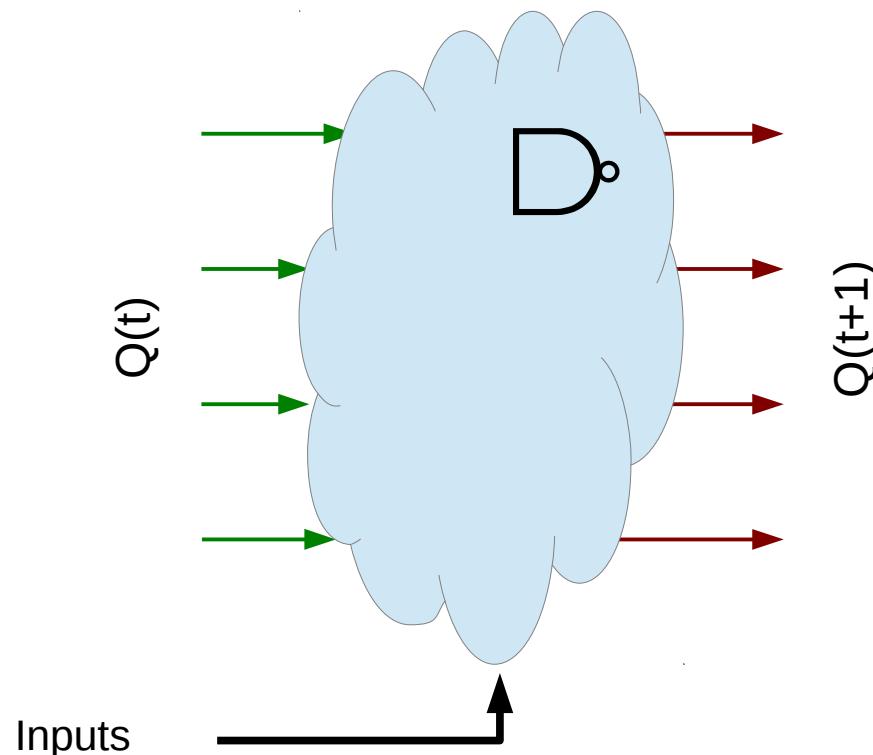Compute the next state
using the current state
and external inputs
in the current clock cycle




After the next clock edge,
the computed next state (FF Inputs)
becomes the current state (FF Outputs)

Moore FSM

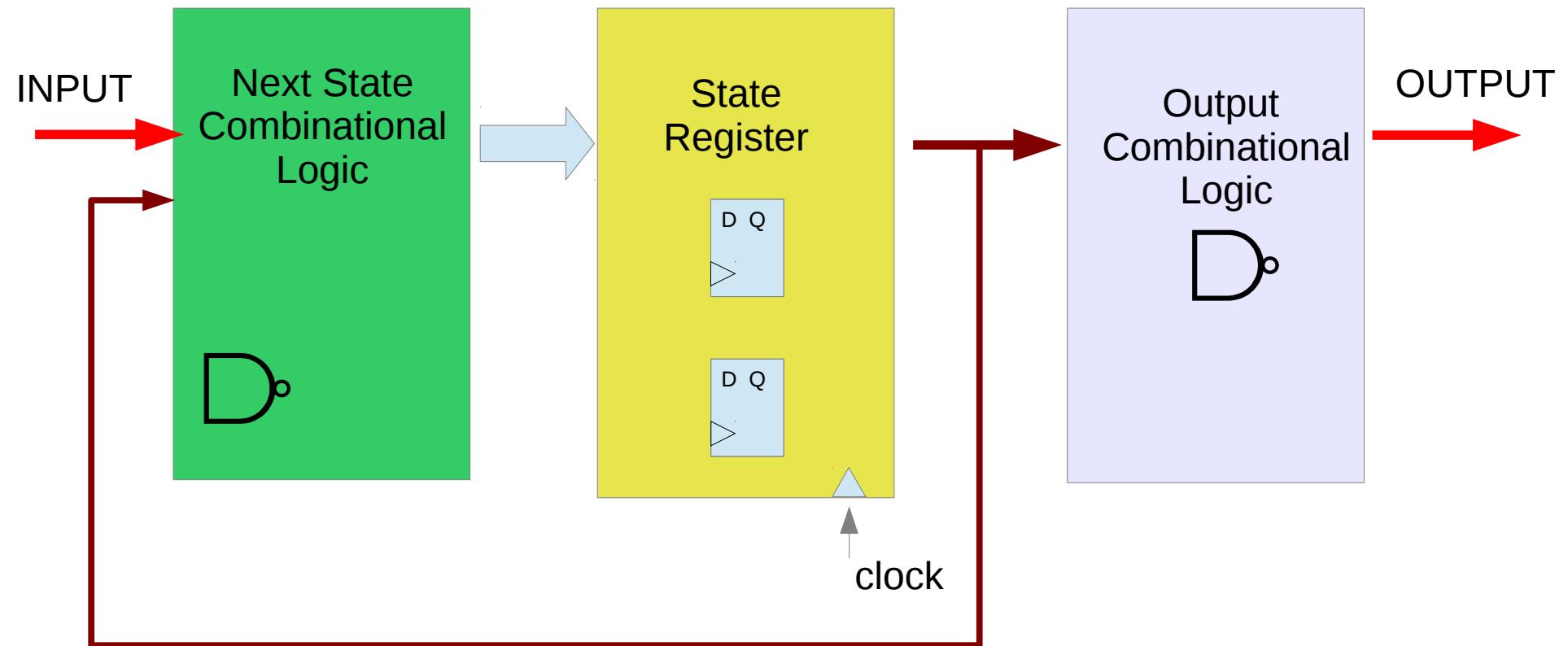

Mealy Machine

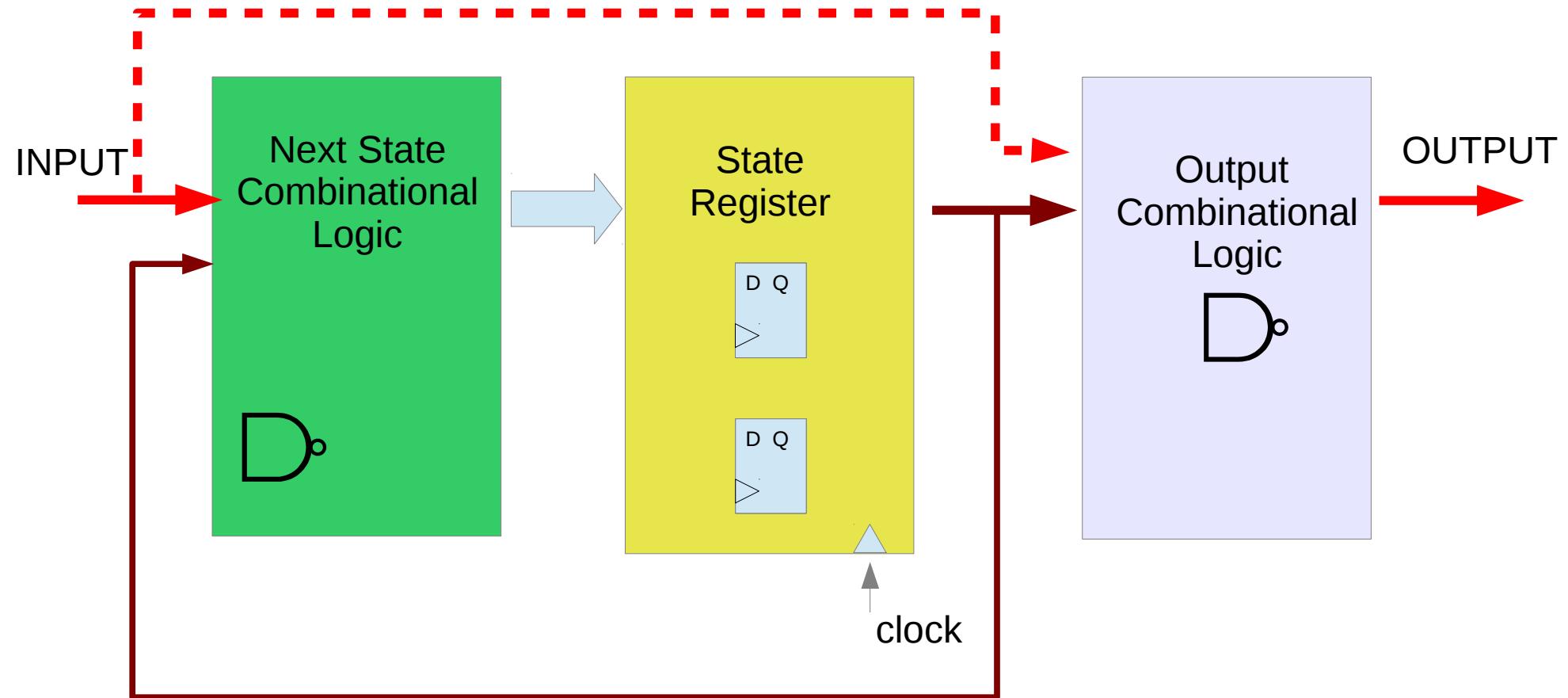

References

- [1] <http://en.wikipedia.org/>
- [2] M. M. Mano, C. R. Kime, "Logic and Computer Design Fundamentals", 4th ed.
- [3] J. Stephenson, Understanding Metastability in FPGAs. Altera Corporation white paper. July 2009.