


SOC HW #1

20160326

Copyright (c) 2015 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

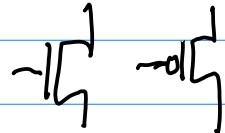1.5 CMOS combinational circuit Transistor



$$(a) Y = A = \bar{A}$$


$$(b) Y = A\bar{B} + \bar{A}B = A \oplus B$$

A, \bar{A}, B, \bar{B}

$$(c) Y = \bar{A}\bar{B} + AB = \overline{A \oplus B}$$

$$(d) Y = AB + BC + AC$$

1.7 CMOS 4-input NOR

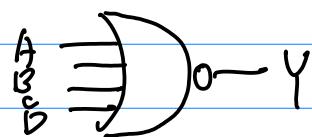

1.19 $A_0, \bar{A}_0, A_1, \bar{A}_1$


decoder

$$Y_0 = \bar{A}_1 \bar{A}_0 \quad 00$$

$$Y_1 = \bar{A}_1 A_0 \quad 01$$

$$Y_2 = A_1 \bar{A}_0 \quad 10$$

$$Y_3 = A_1 A_0 \quad 11$$

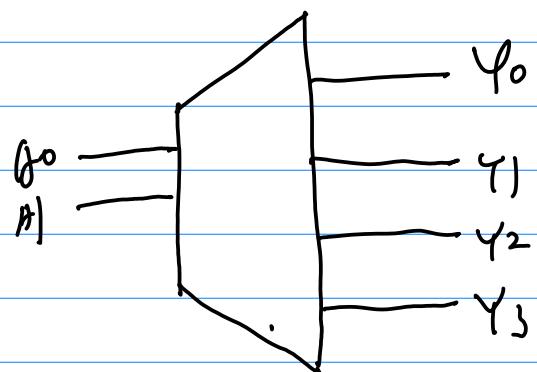


1. 21

$$F = \overline{(A+B) \cdot (C+D)}$$

(a) Transistor level schematic

(b)

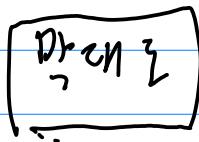

color pen

1.5

CMOS


combinational

circuit

Transistor


$$\sim \boxed{1} \quad \sim \boxed{0}$$

$$(a) \quad Y = A = \bar{\bar{A}}$$

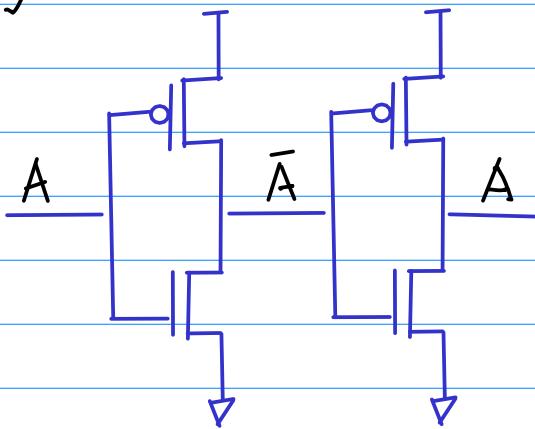

$$(b) Y = A\bar{B} + \bar{A}B = A \oplus B$$

XOR
(AOI)

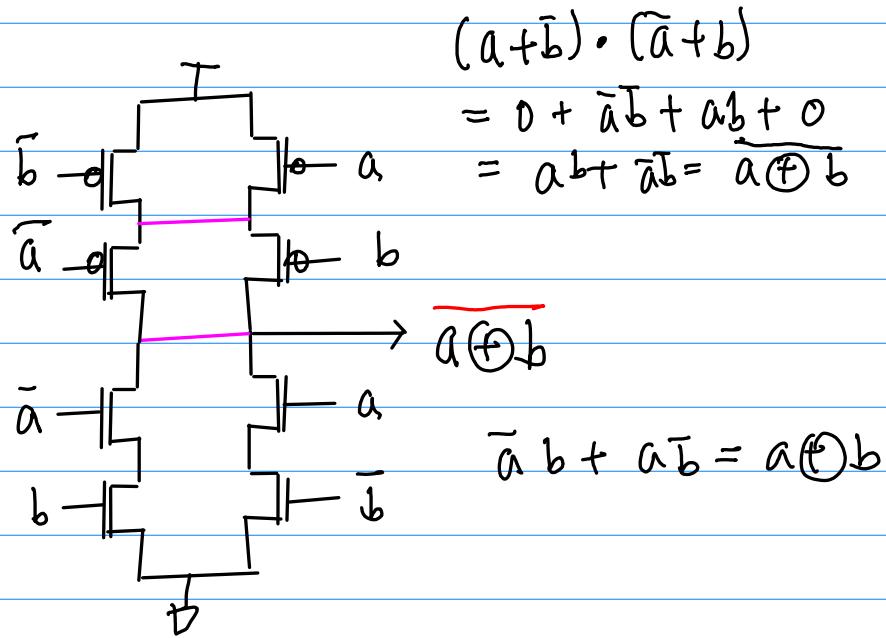


$$\begin{aligned} & (a+b) \cdot (\bar{a}+b) \\ &= 0 + \bar{a}b + ab + 0 \\ &= ab + \bar{a}b = \underline{\bar{a} \oplus b} \end{aligned}$$

$$\bar{a}b + a\bar{b} = \underline{a \oplus b}$$

$$(c) Y = \bar{A}\bar{B} + AB = \overline{A \oplus B}$$

XNOR
(AOI)

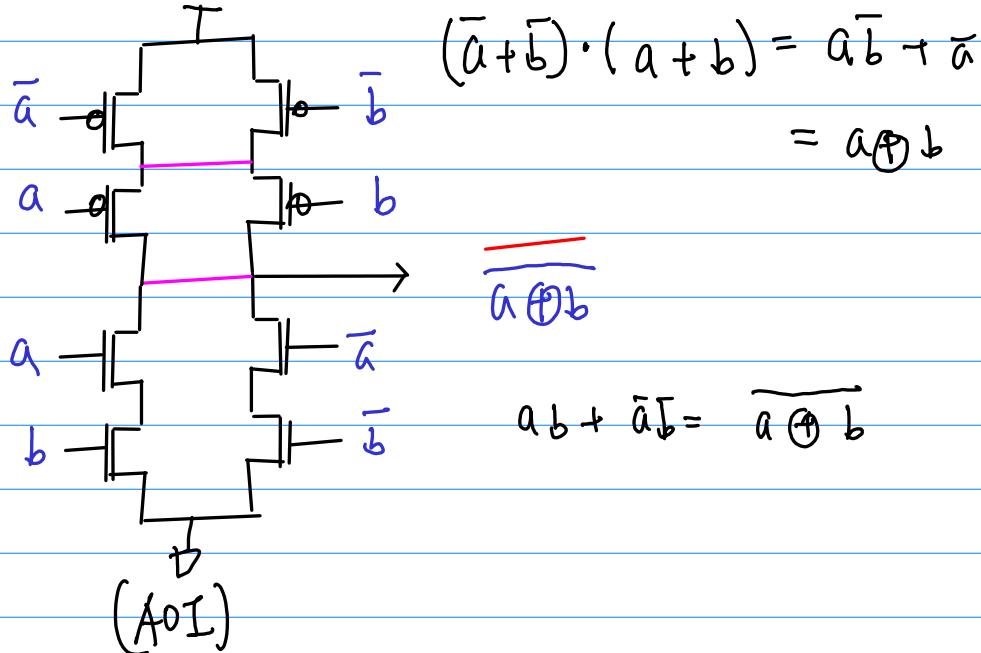

$$\begin{aligned} & (\bar{a}+\bar{b}) \cdot (a+b) = a\bar{b} + \bar{a}b \\ &= \underline{a \oplus b} \end{aligned}$$


$$ab + \bar{a}\bar{b} = \underline{\overline{a \oplus b}}$$

$\overline{a \oplus b}$
(AOI)

$$(d) Y = \overline{AB + BC + AC} \text{ pmos pnn}$$


$$\bar{Y} = \overline{\overline{AB + BC + AC}} = \overline{\overline{AB}} \cdot \overline{\overline{BC}} \cdot \overline{\overline{AC}}$$
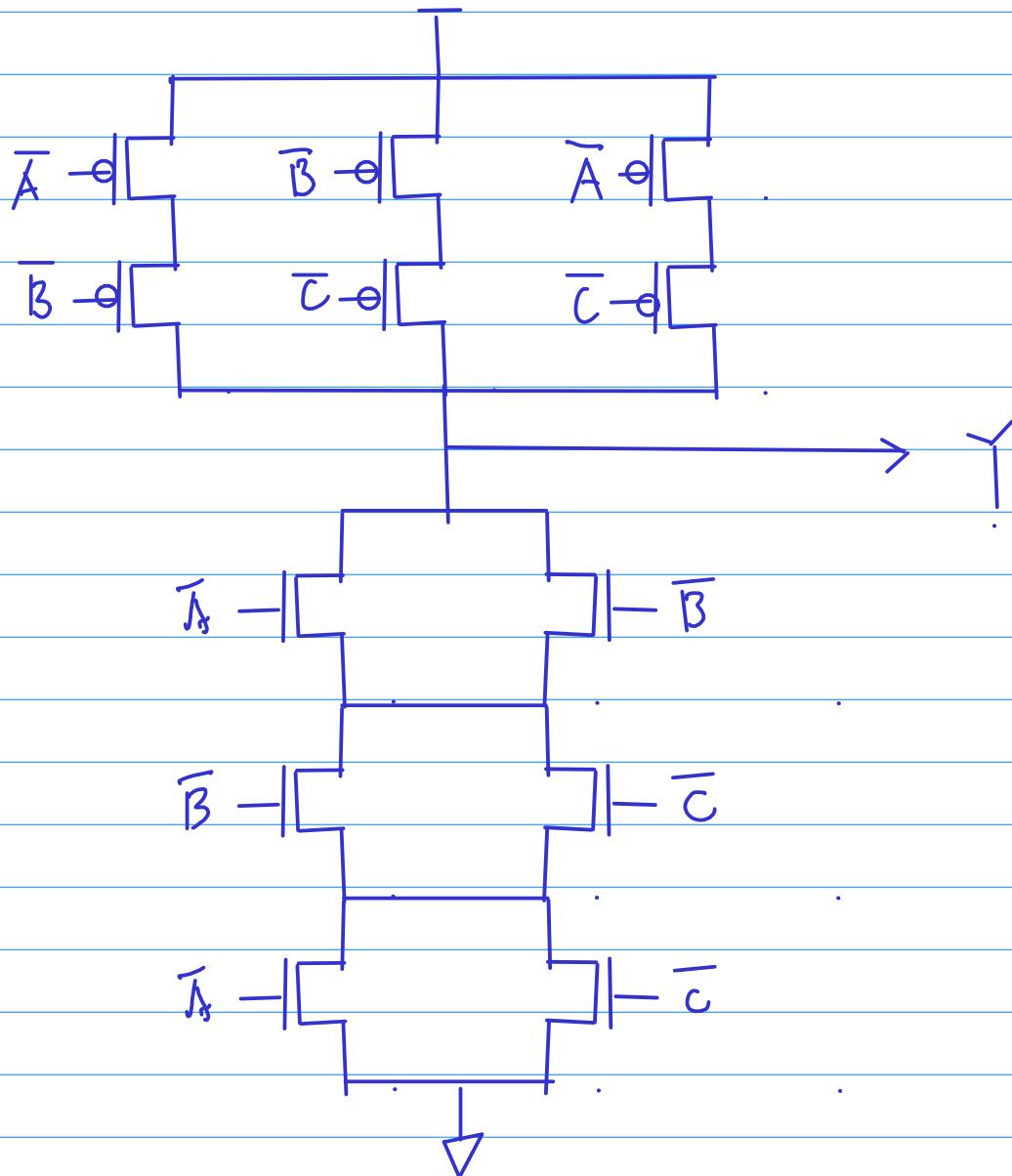
$$= (\bar{A} + \bar{B}) \cdot (\bar{B} + \bar{C}) \cdot (\bar{A} + \bar{C}) \text{ nmos ppn}$$



1.7


CMOS 4-input NOR

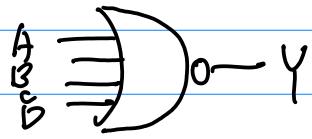


$$Y = \overline{\overline{A} + \overline{B} + \overline{C} + \overline{D}}$$


nMOS
P_{DN}

$$\overline{Y} = \overline{\overline{A} + \overline{B} + \overline{C} + \overline{D}} = A + B + C + D$$

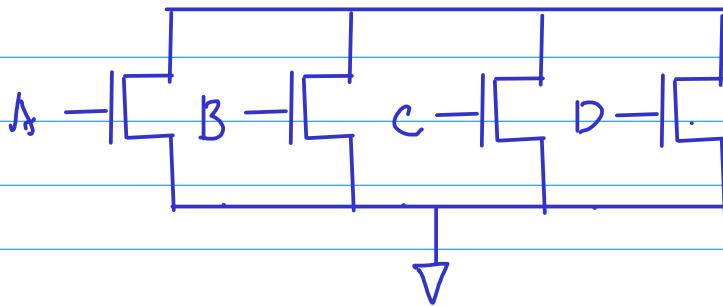PMOS
P_{UN}
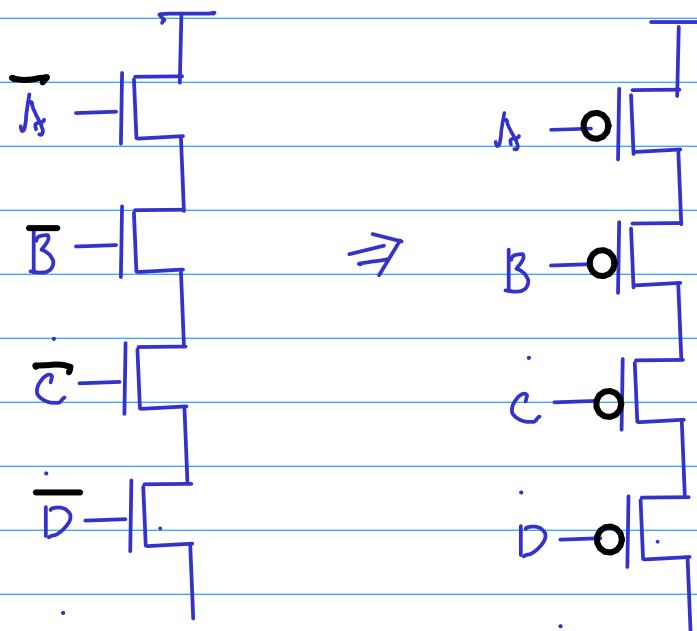
$$Y = \overline{\overline{A} + \overline{B} + \overline{C} + \overline{D}} = \overline{A} \cdot \overline{B} \cdot \overline{C} \cdot \overline{D}$$



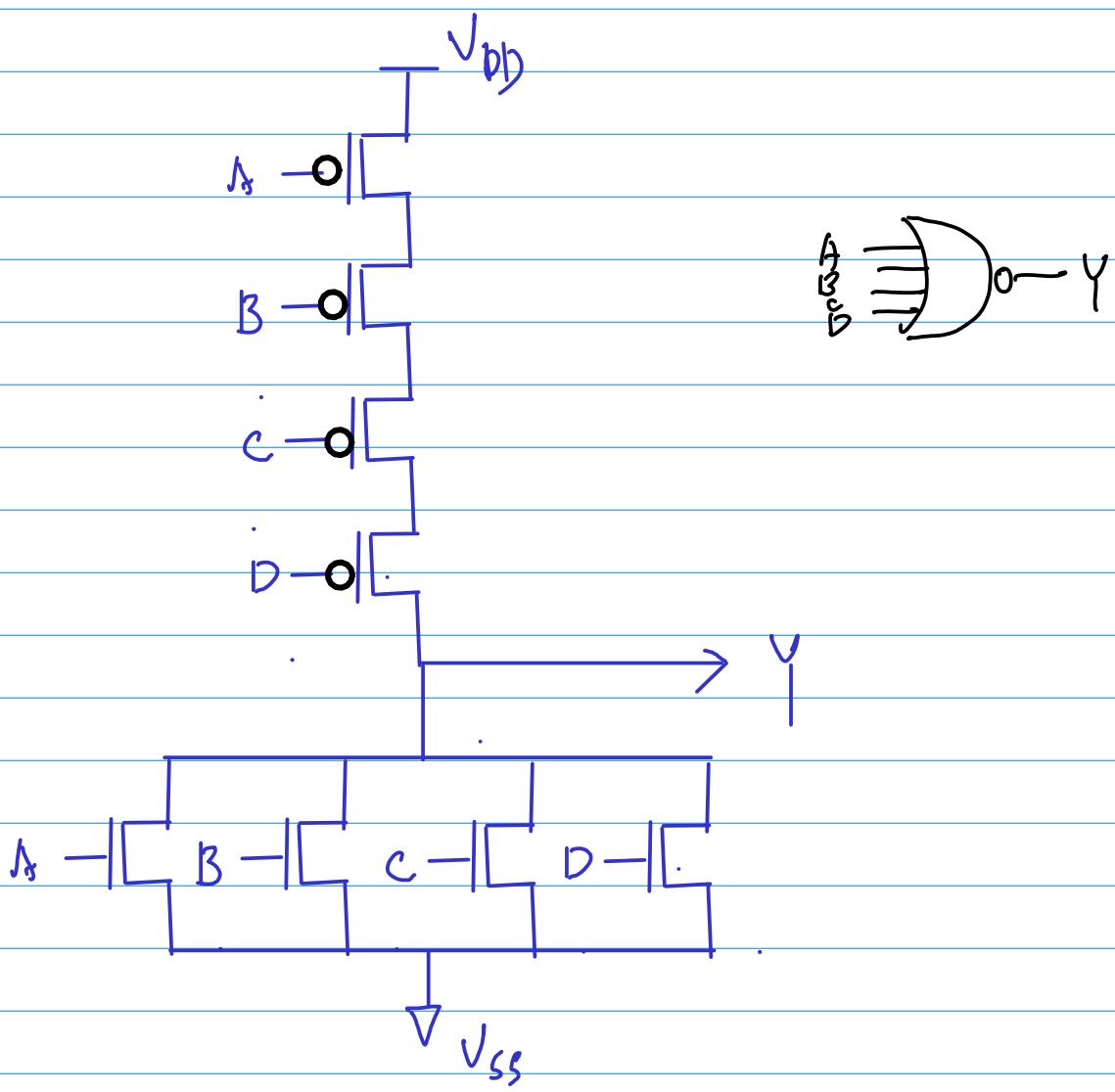

1.19

 $A_0, \bar{A}_0, A_1, \bar{A}_1$



decoder



$$Y_0 = \bar{A}_1 \bar{A}_0 \quad 00$$

$$Y_1 = \bar{A}_1 A_0 \quad 01$$

$$Y_2 = A_1 \bar{A}_0 \quad 10$$


$$Y_3 = A_1 A_0 \quad 11$$

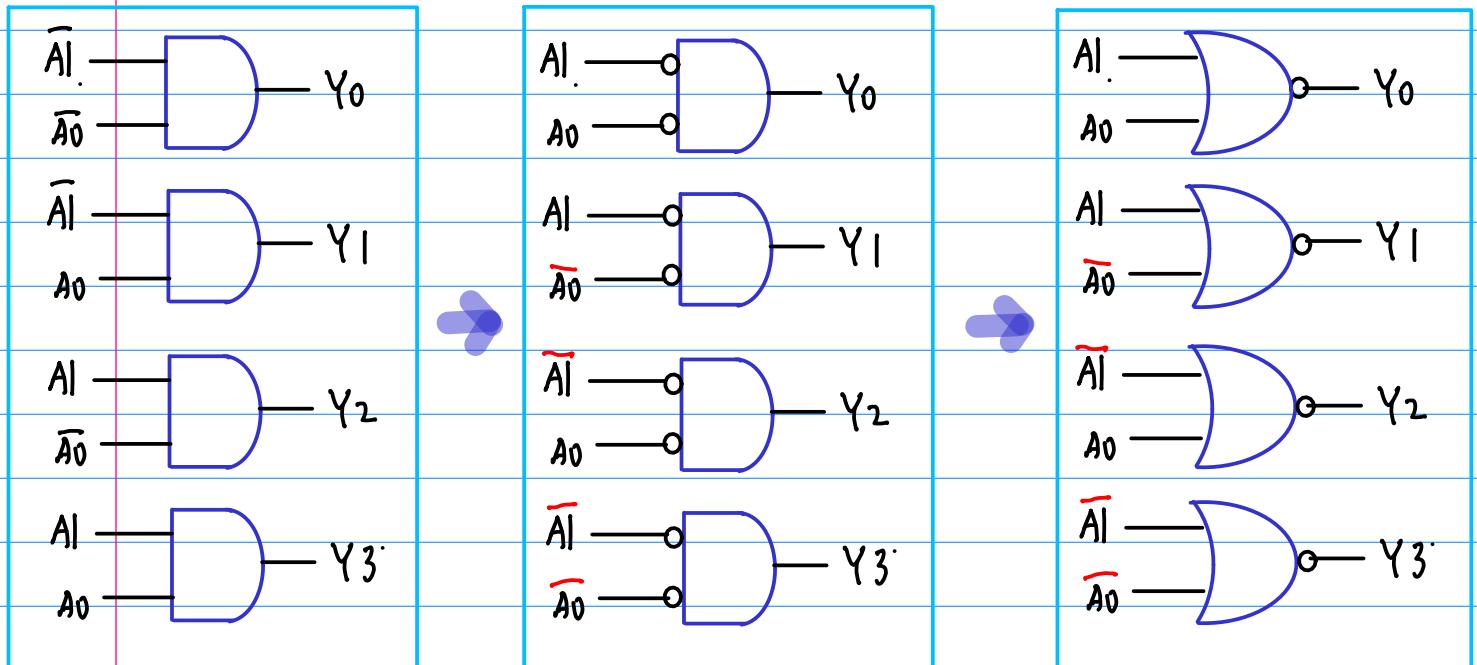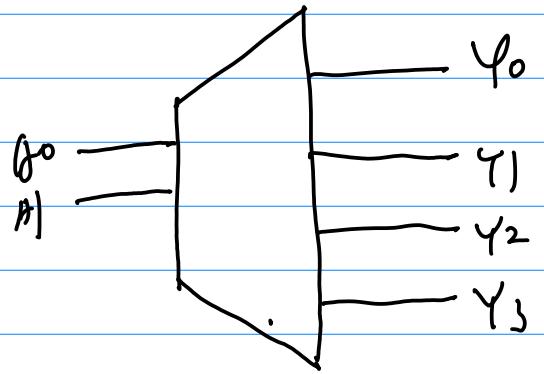

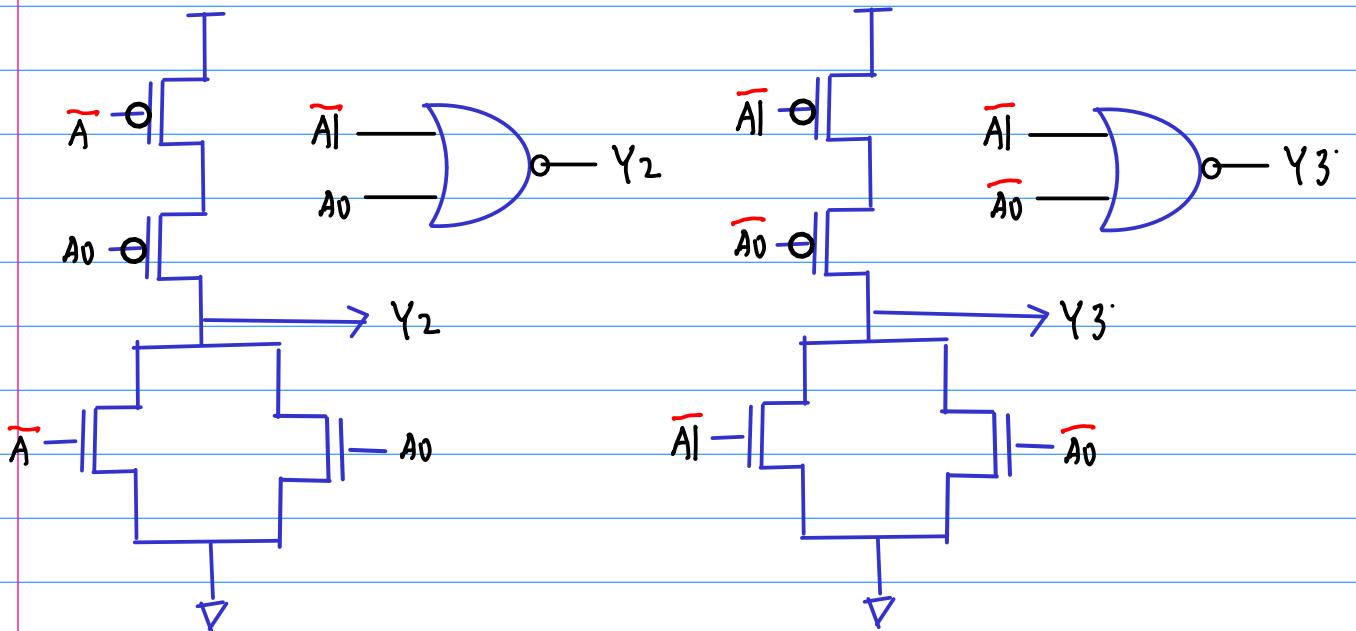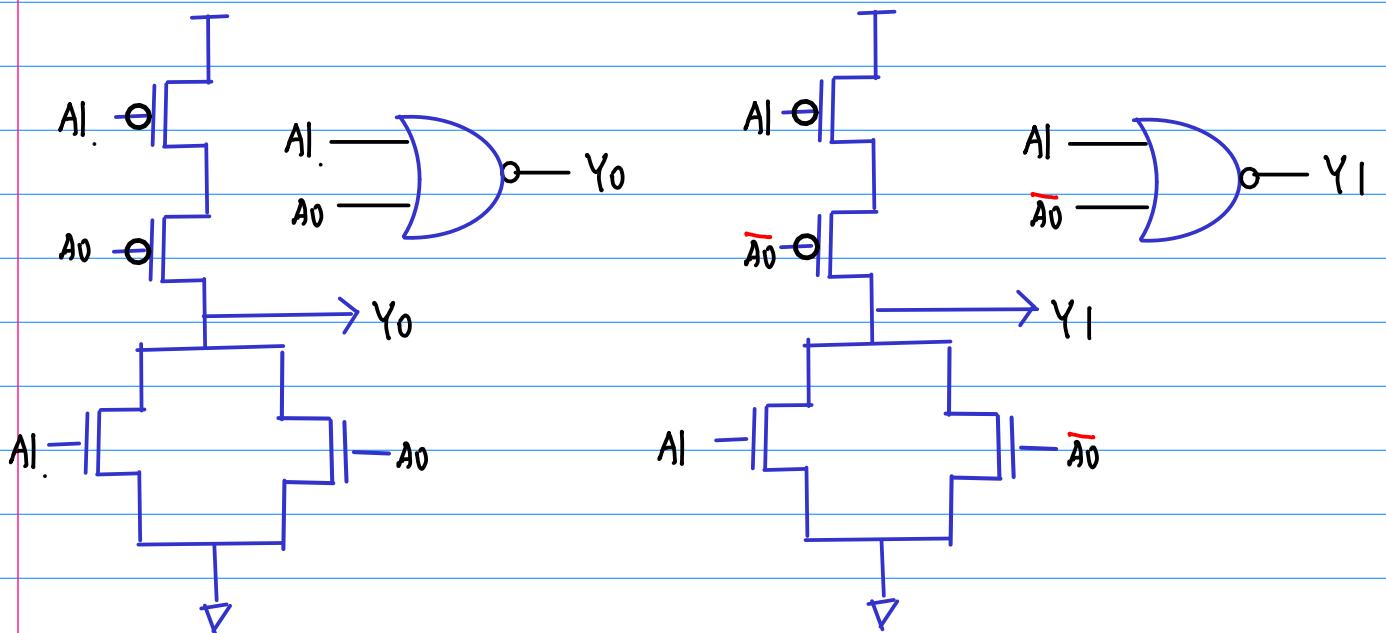


$$1.21 \quad F = \overline{(A+B) \cdot (C+D)}$$

(a) Transistor level schematic

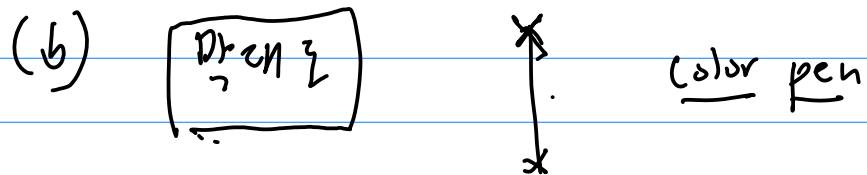


NMOS PPN $F = \overline{(A+B) \cdot (C+D)} = (A+B) \cdot (C+D)$

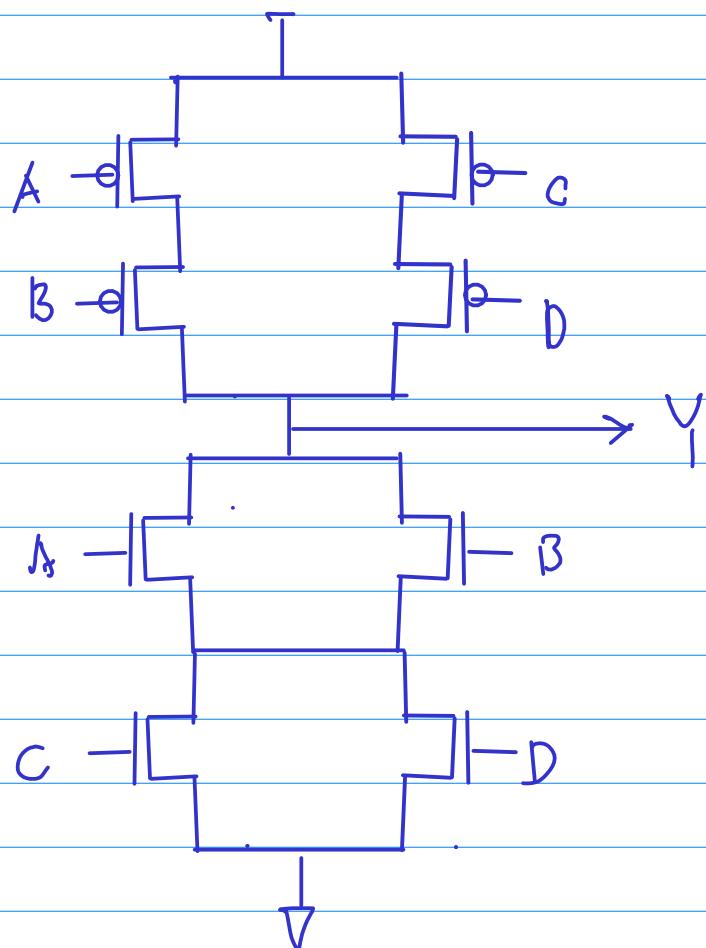
PMOS PNP $F = \overline{(A+B) \cdot (C+D)} = \overline{(A+B)} + (\overline{C+D}) = (\overline{A} \cdot \overline{B}) + (\overline{C} \cdot \overline{D})$



Stick Diagram

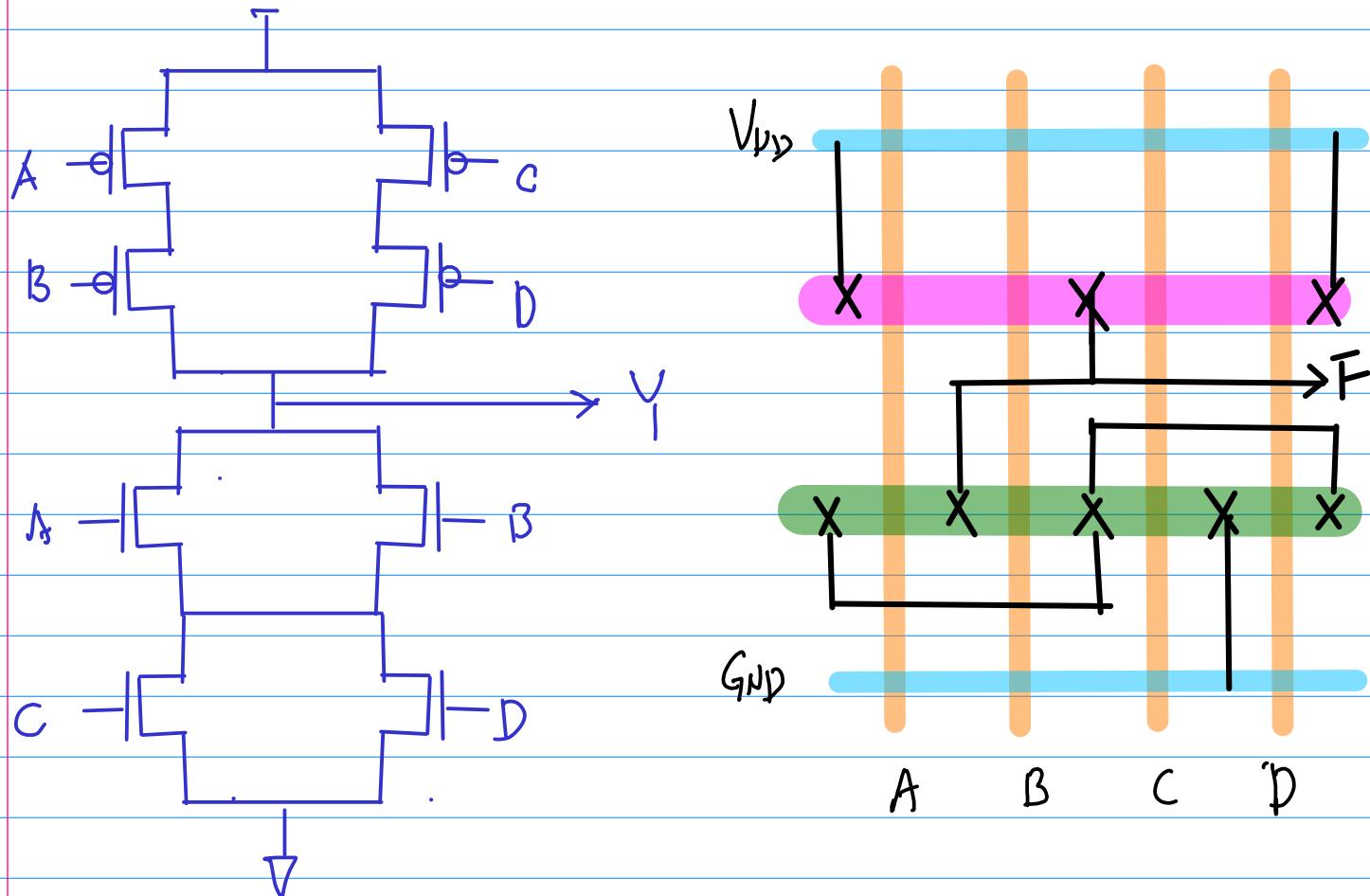

(f) Weste's Book

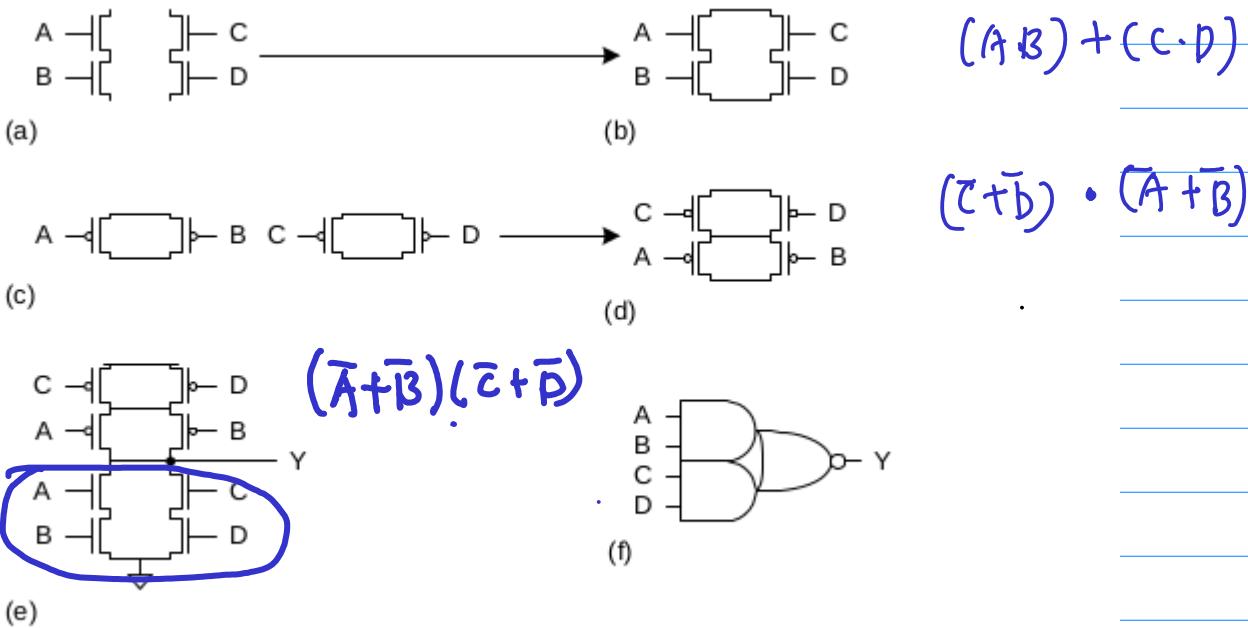



$$\underline{\overline{AB} + CD}$$

$$\underline{(A \cdot B) + (C \cdot D)}$$

$$= \overline{A \cdot B} \cdot \overline{C \cdot D}$$

$$= (\bar{A} + \bar{B}) \cdot (\bar{C} + \bar{D})$$

Basic nMOS, pMOS Configurations

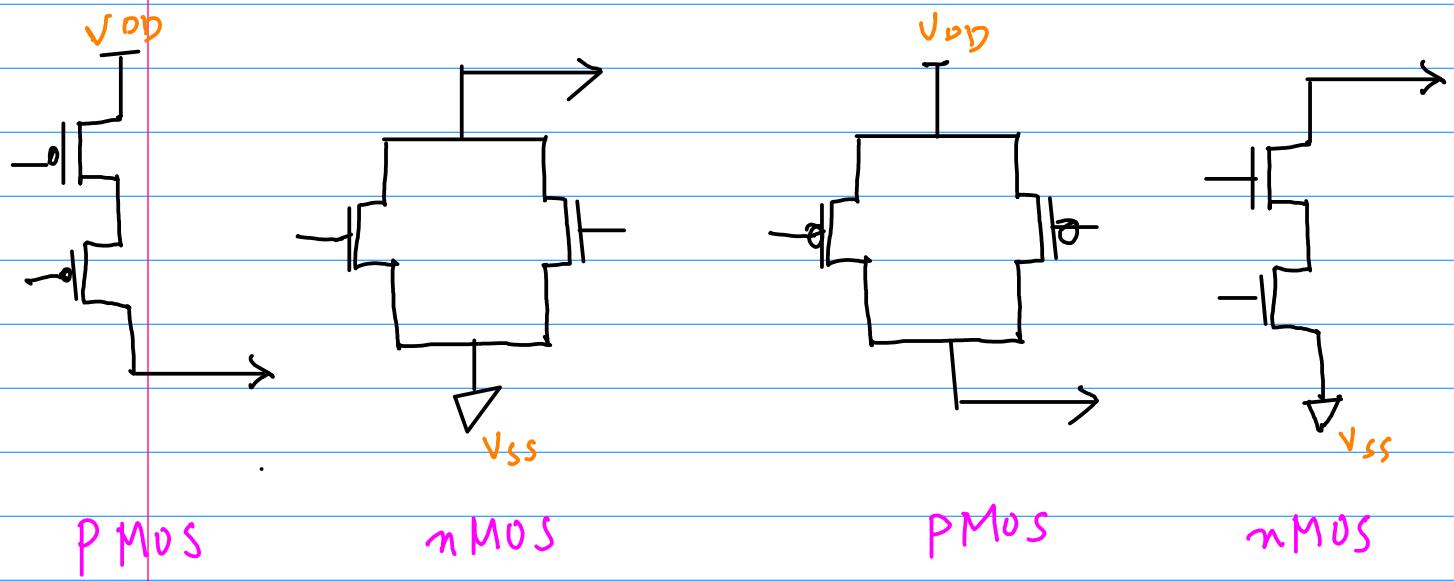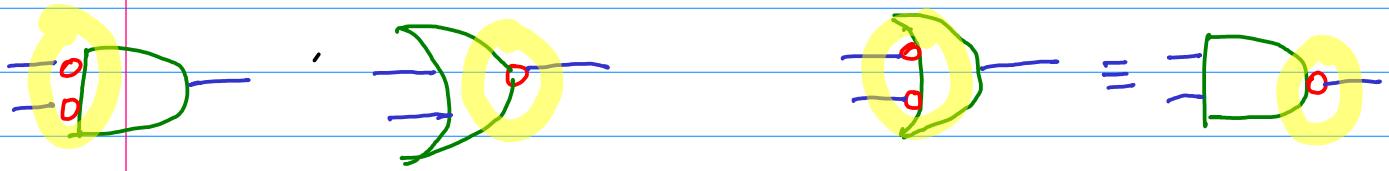


XNOR, XOR using OAI

$$a \oplus b = \bar{a} \cdot b + a \bar{b}$$

$$\overline{\bar{a} \oplus b} = ab + \bar{a}\bar{b}$$

XNOR

(OAI)

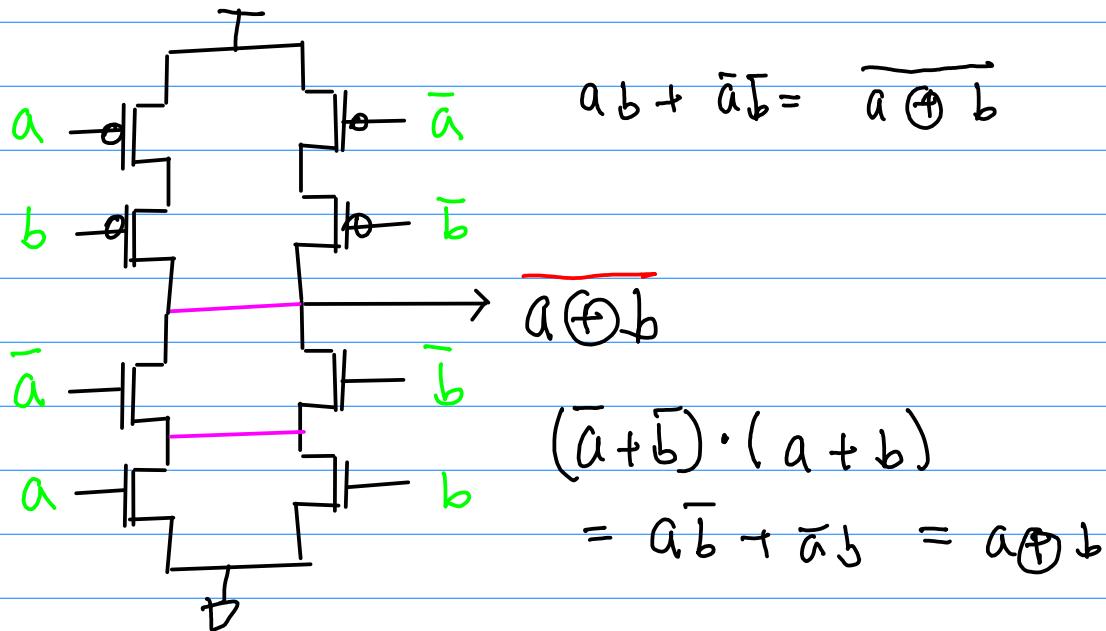

$$ab + \bar{a}\bar{b} = \overline{\bar{a} \oplus b}$$


$$a \oplus b$$

$$(\bar{a} + \bar{b}) \cdot (a + b)$$

$$= a\bar{b} + \bar{a}b = a \oplus b$$

XOR

(OAI)

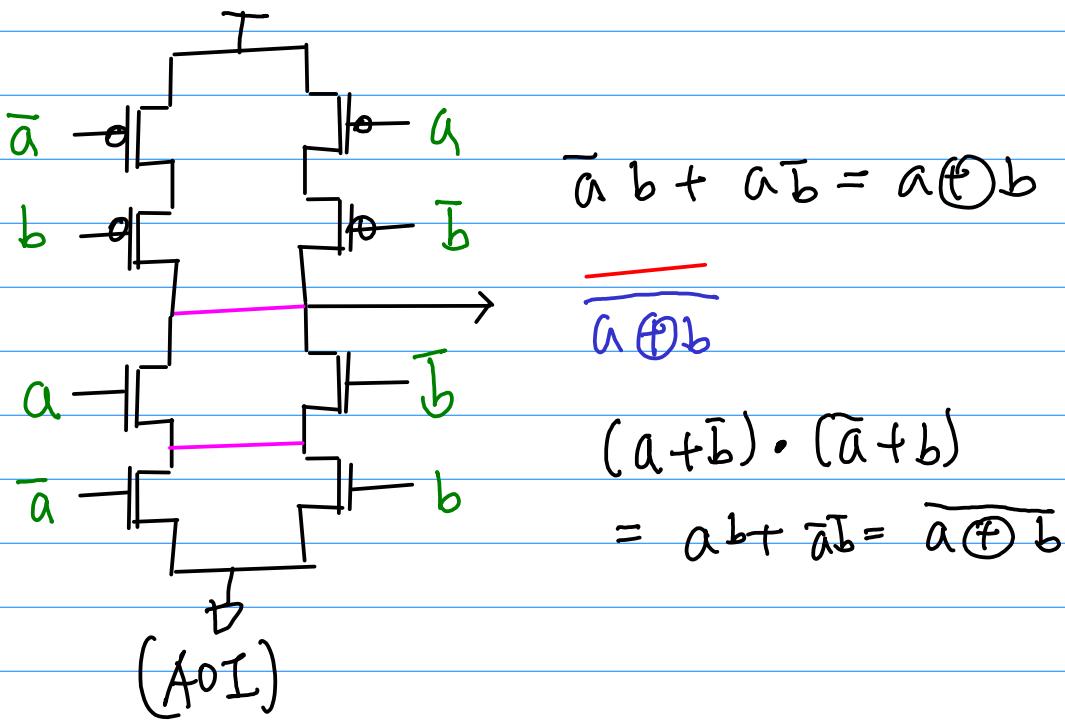

$$\bar{a}b + a\bar{b} = a \oplus b$$





$$\overline{\bar{a} \oplus b}$$

$$(a + \bar{b}) \cdot (\bar{a} + b)$$

$$= ab + \bar{a}\bar{b} = \overline{\bar{a} \oplus b}$$



(AOI)

* Which one is better?

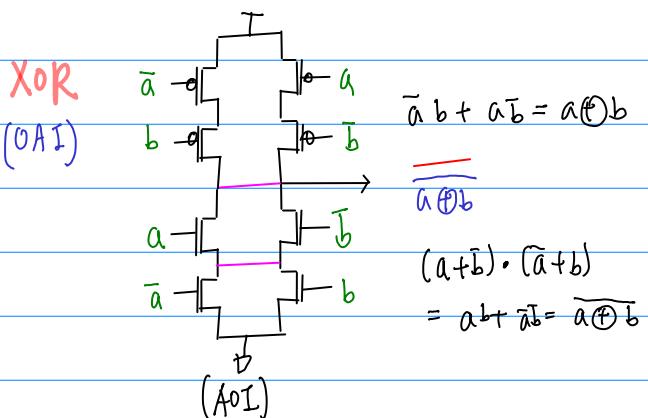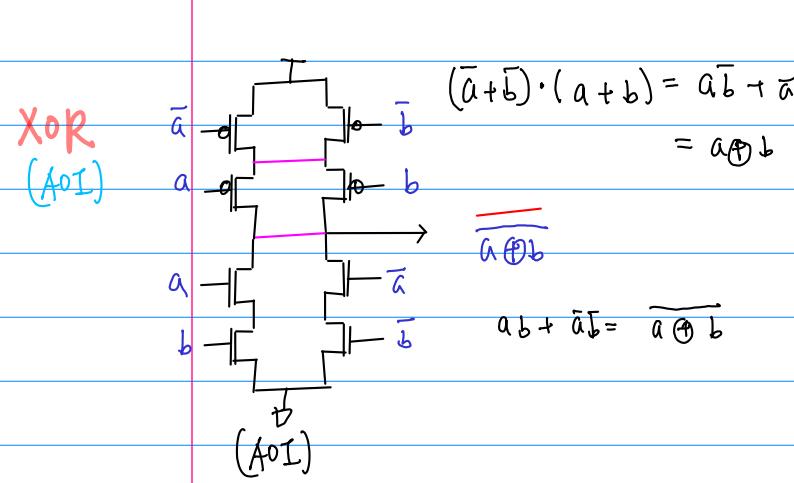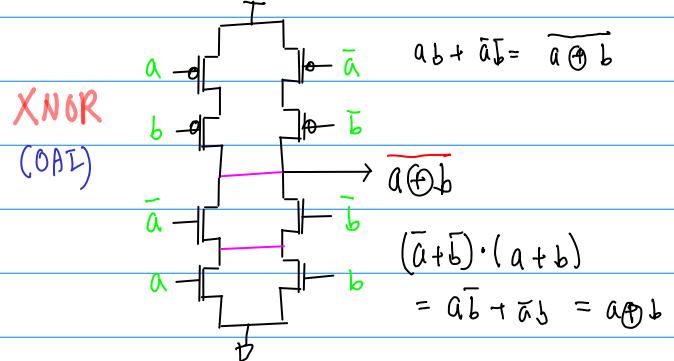
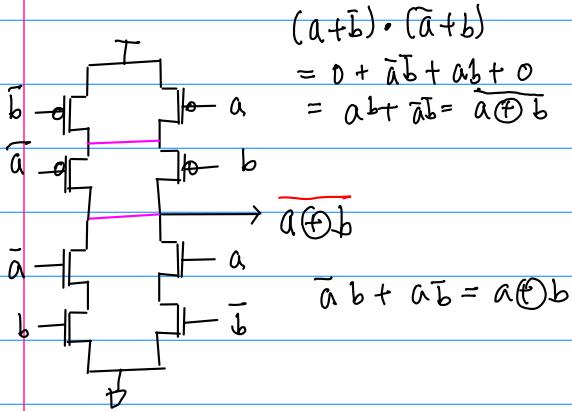


Decoder

x_1	x_0	y_3	y_2	y_1	y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

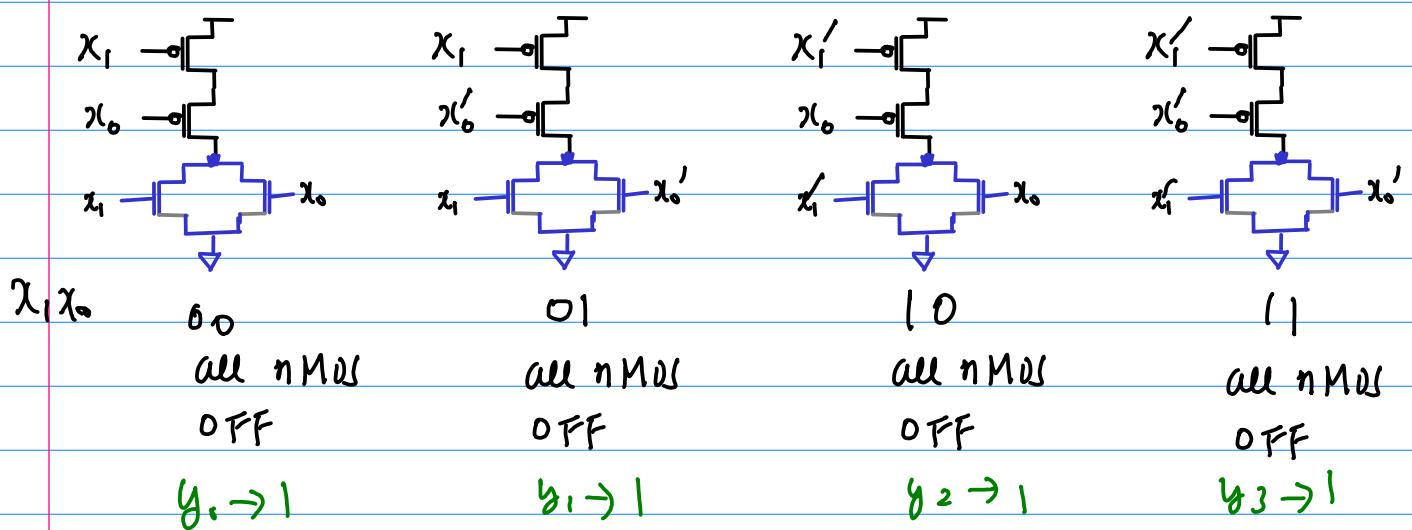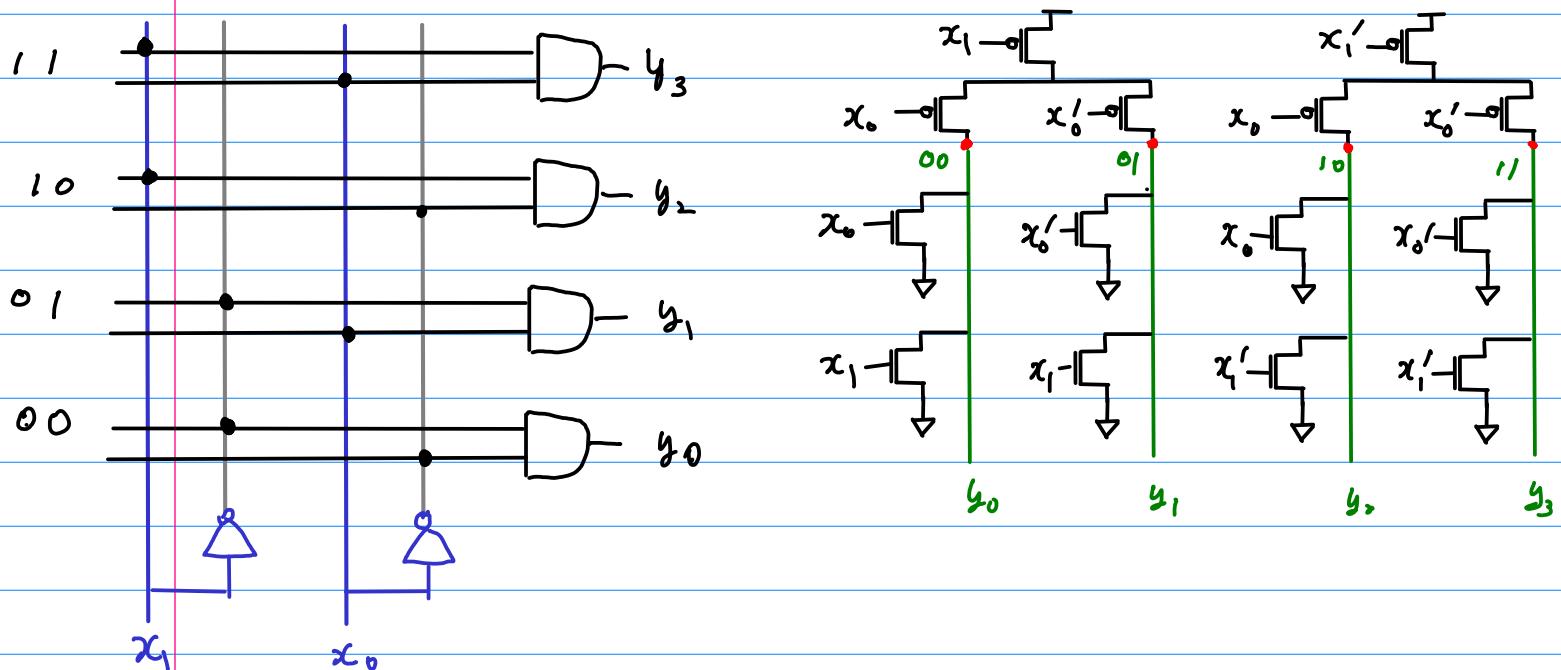

x_1	x_0	y_3	y_2	y_1	y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

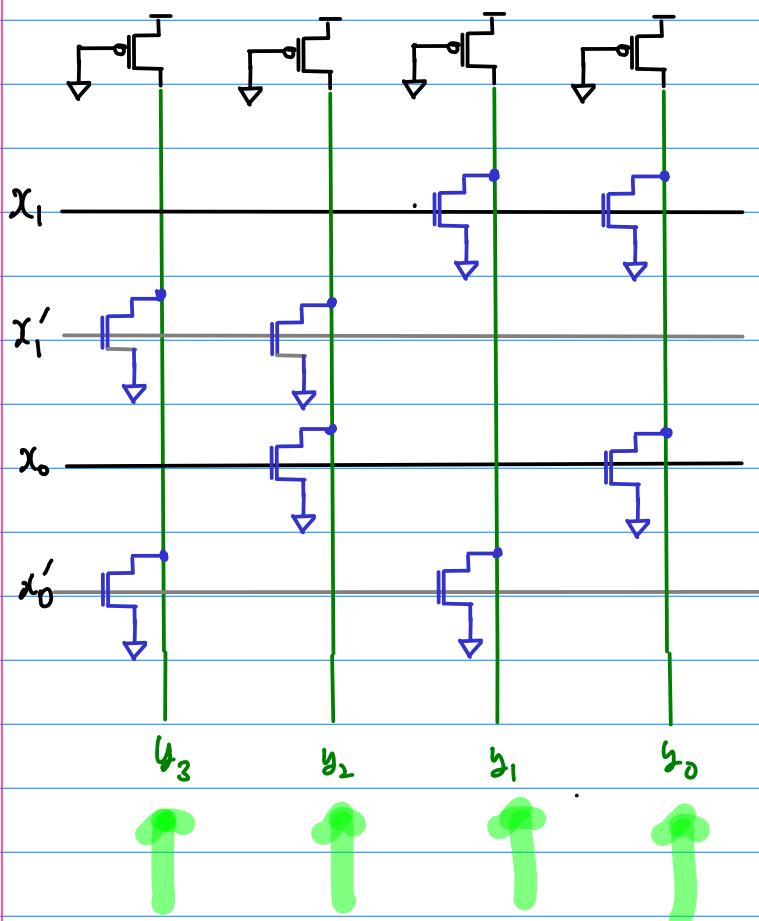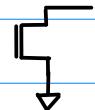

$x_1 x_0$	11	10	01	00
all nMOS	all nMOS	all nMOS	all nMOS	
OFF	OFF	OFF	OFF	

