

# Impedance

---

Copyright (c) 2015 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to [youngwlim@hotmail.com](mailto:youngwlim@hotmail.com).

This document was produced by using OpenOffice and Octave.

# Sinusoidal voltage and current

$$i_C = C \cdot \frac{dv_C}{dt}$$

$$v_L = L \cdot \frac{di_L}{dt}$$

$$\begin{aligned} v_C &= A \cos(\omega t) \\ i_C &= -\omega C A \sin(\omega t) \\ &= \omega C A \cos(\omega t + \pi/2) \end{aligned}$$

$$\begin{aligned} i_L &= A \sin(\omega t) \\ &= A \cos(\omega t - \pi/2) \\ v_L &= \omega L A \cos(\omega t) \end{aligned}$$

$$\frac{v_C}{i_C} = \frac{1}{\omega C} \frac{\cos(\omega t)}{\cos(\omega t + \pi/2)}$$

$$\frac{v_L}{i_L} = \omega L \frac{\cos(\omega t)}{\cos(\omega t - \pi/2)}$$

$$[i_C, v_C]$$

  
leads by 90

$$[v_L, i_L]$$


  
leads by 90

# Leading and Lagging Current

$$i_C = C \cdot \frac{dv_C}{dt}$$

$$\begin{aligned} v_C &= \cos(2\pi t) \\ i_C &= -\pi \sin(2\pi t) \\ &= \pi \cos(2\pi t + \pi/2) \end{aligned}$$


$$C=0.5$$

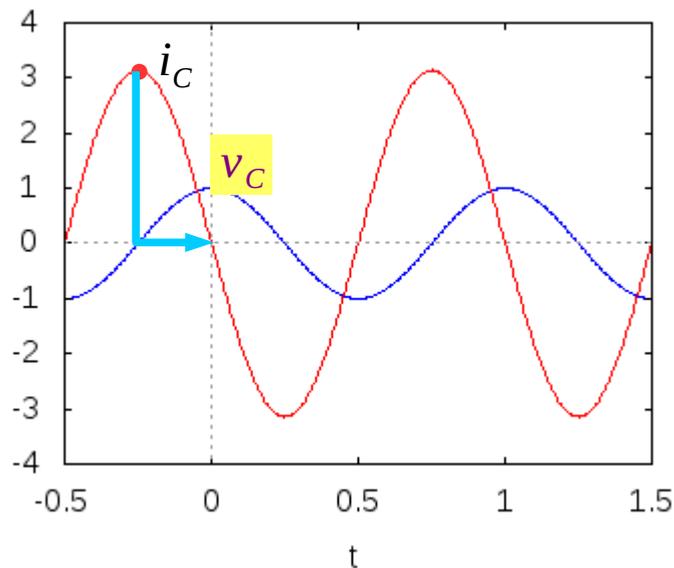

$$v_L = L \cdot \frac{di_L}{dt}$$



$$\begin{aligned} i_L &= \sin(2\pi t) \\ &= \cos(2\pi t - \pi/2) \\ v_L &= \pi \cos(2\pi t) \end{aligned}$$

$$L=0.5$$


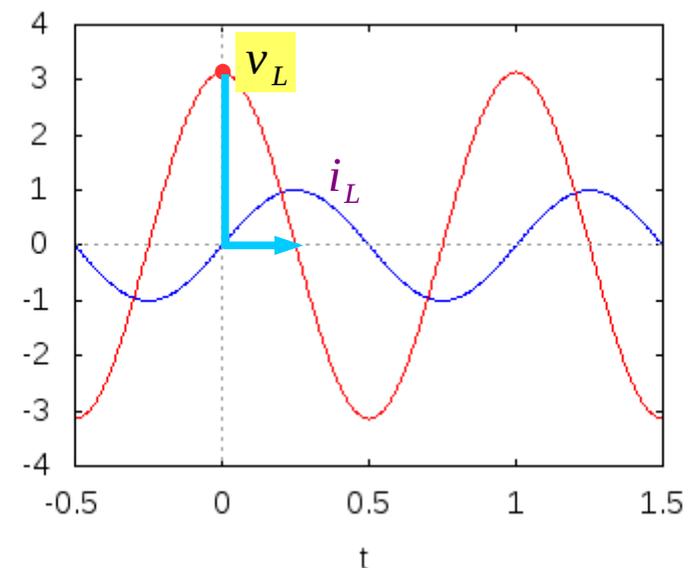


# Leading and Lagging Current


$$i_C = C \cdot \frac{dv_C}{dt}$$

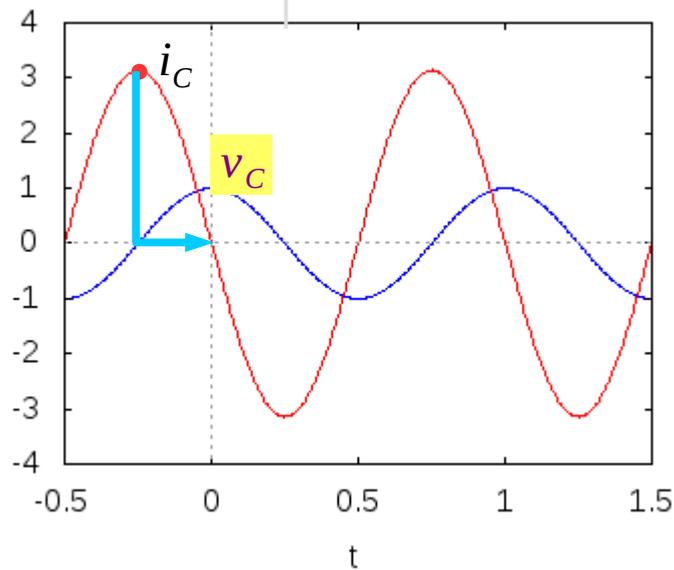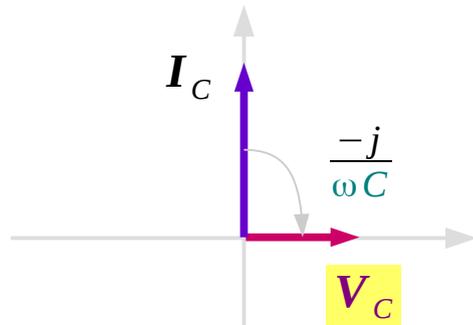

$$v_L = L \cdot \frac{di_L}{dt}$$

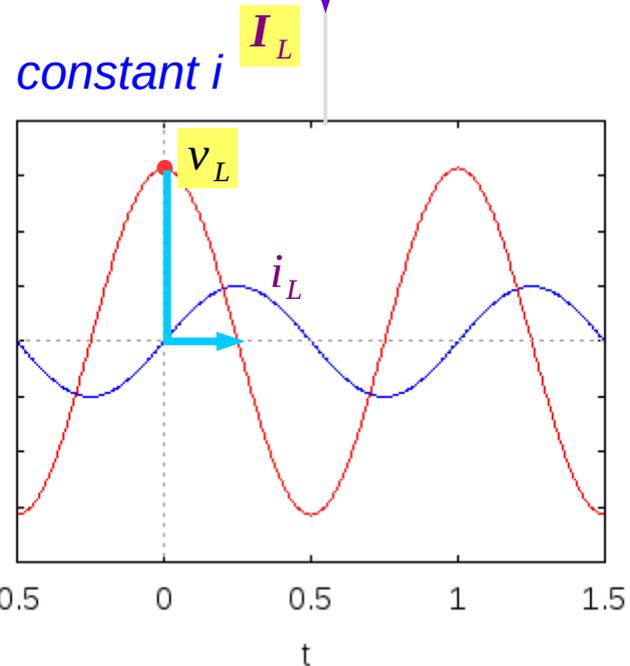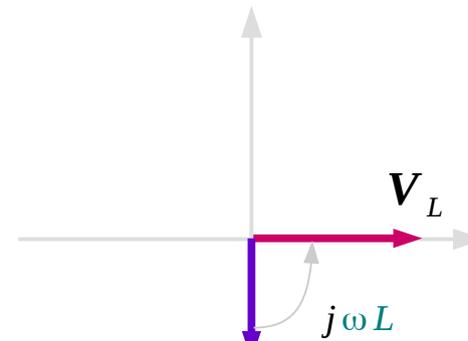


# Phasor and Ohm's Law

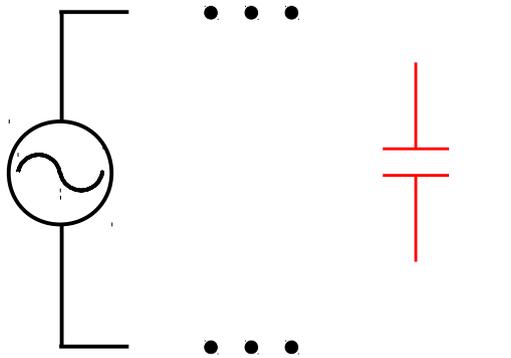

*sinusoidal  
i, v source*





*sinusoidal  
i, v*

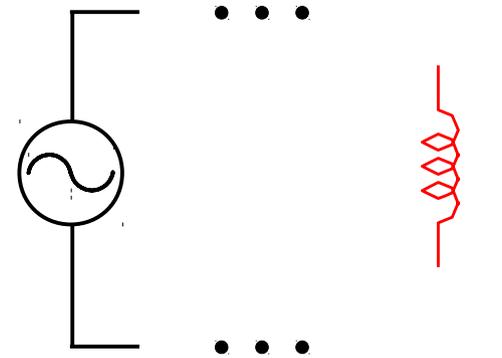

*sinusoidal  
i, v source*



*sinusoidal  
i, v*

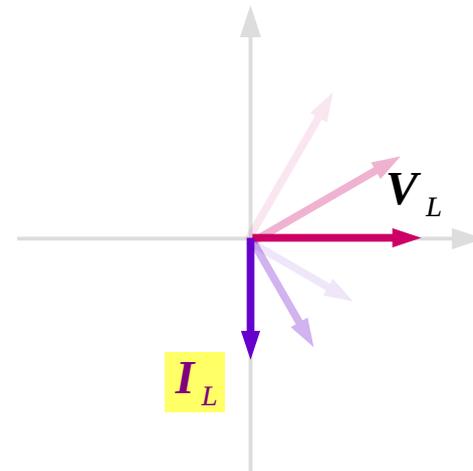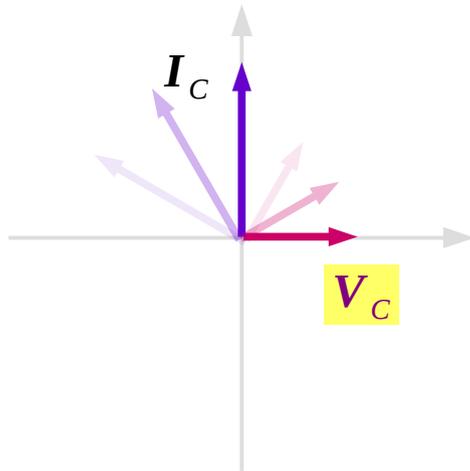

# Impedance : a complex scaling factor

$$\begin{aligned}V_C &= A \angle 0 \\ I_C &= \omega C A \angle \pi/2\end{aligned}$$

$$Z_C = \frac{V_C}{I_C} \quad \leftarrow \text{phasor}$$
$$\quad \quad \quad \leftarrow \text{phasor}$$

↓

*a complex scaling factor*

$$V_C = I_C \cdot Z_C = I_C \left( \frac{1}{\omega C} \angle -\pi/2 \right)$$

$$Z_C = \frac{-j}{\omega C} = \frac{1}{j \omega C}$$

$$\begin{aligned}I_L &= A \angle -\pi/2 \\ V_L &= \omega L A \angle 0\end{aligned}$$

$$Z_L = \frac{V_L}{I_L} \quad \leftarrow \text{phasor}$$
$$\quad \quad \quad \leftarrow \text{phasor}$$

↓

*a complex scaling factor*


$$V_L = I_L \cdot Z_L = I_L (\omega L \angle +\pi/2)$$

$$Z_L = j \omega L$$
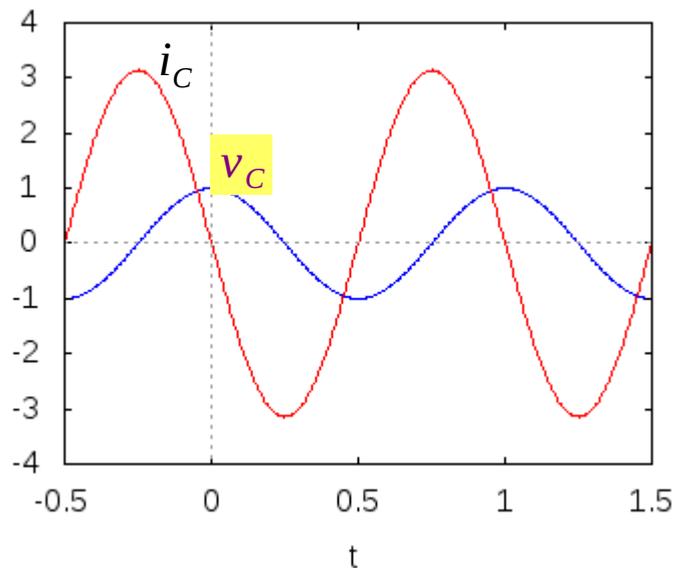
# Ohm's Law


$$\begin{aligned}V_C &= A \angle 0 \\ I_C &= \omega C A \angle \pi/2\end{aligned}$$

$$\begin{aligned}Z_C &= \frac{V_C}{I_C} = \frac{1}{\omega C} \angle -\pi/2 \\ &= \frac{-j}{\omega C} = \frac{1}{j\omega C}\end{aligned}$$




$$\begin{aligned}I_L &= A \angle -\pi/2 \\ V_L &= \omega L A \angle 0\end{aligned}$$
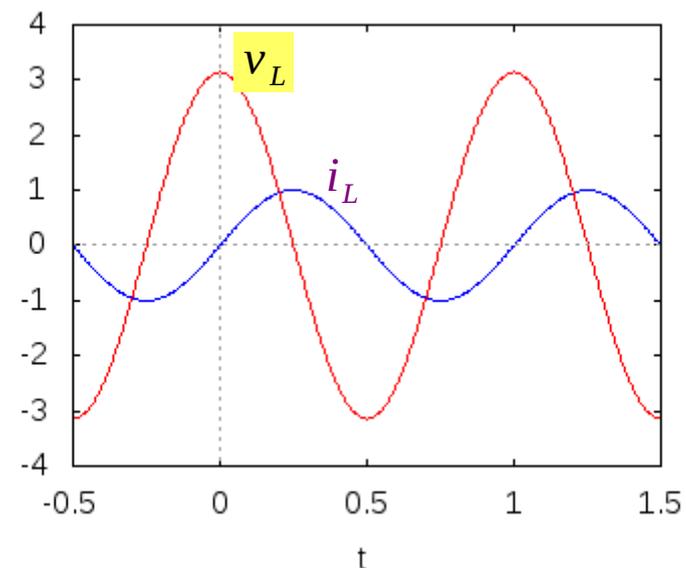
$$\begin{aligned}Z_L &= \frac{V_L}{I_L} = \omega L \angle +\pi/2 \\ &= j\omega L\end{aligned}$$




# Phasor Example (1)


$$A \angle 0$$

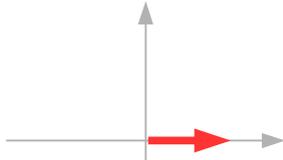



$$A \angle +\pi/2$$

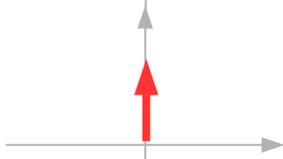


$$A \angle -\pi/2$$

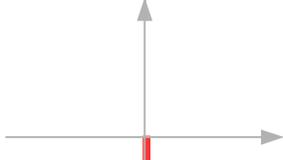


$$A \angle -\pi$$

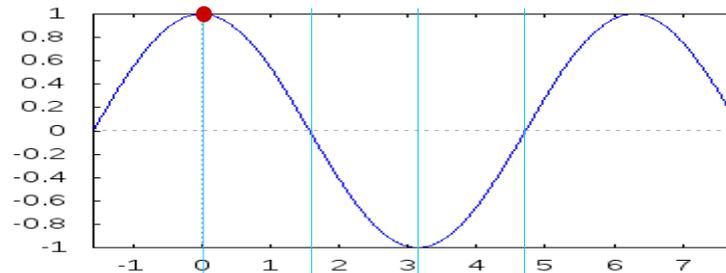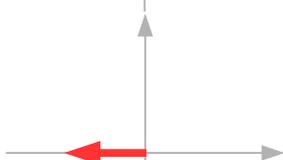


$$A \cos(\omega t + 0)$$

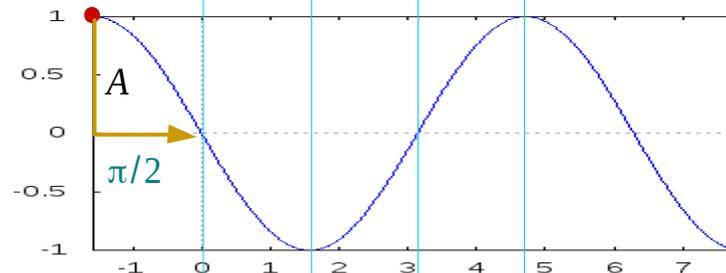

$$A \cos(\omega t + \pi/2)$$

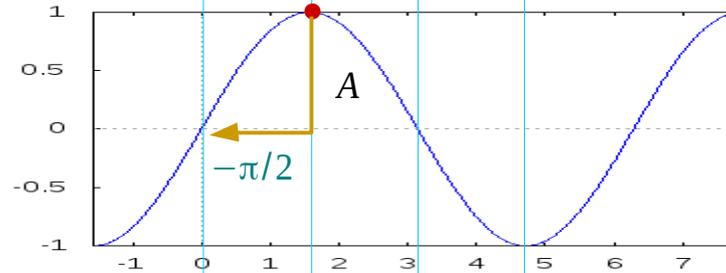



$$A \cos(\omega t - \pi/2)$$

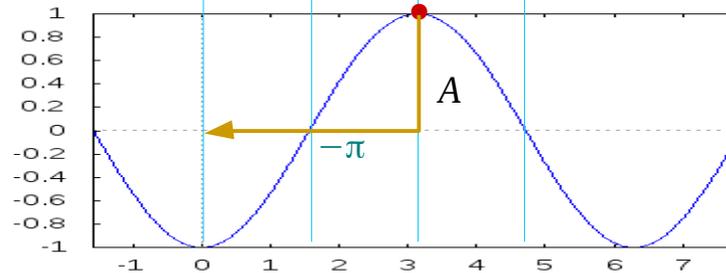

$$A \cos(\omega t - \pi)$$



# Phasor Example (2)

$$A \angle 0$$

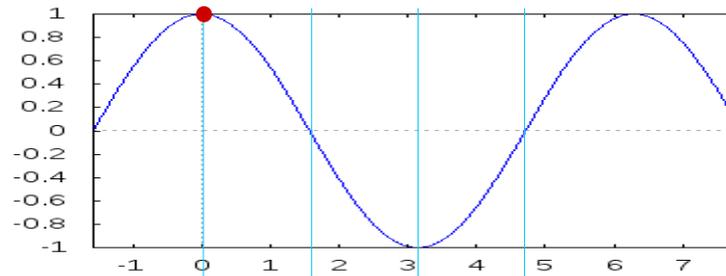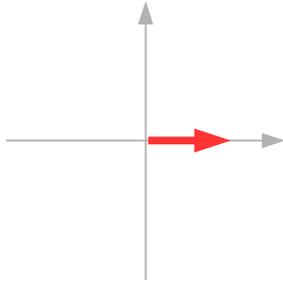

$$A \cos(\omega t + 0)$$

$$2A \angle -\pi/2$$

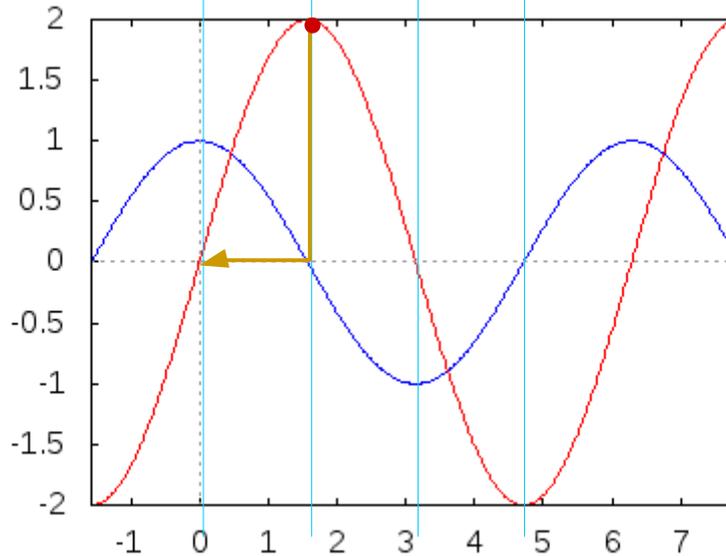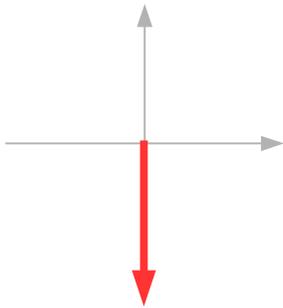

$$2A \cos(\omega t - \pi/2)$$

# Phasor

$$A \cos(\omega t + \theta)$$

$$= A \cos(\omega t) \cos(\theta) - A \sin(\omega t) \sin(\theta)$$

$$= A \cos(\theta) \cos(\omega t) - A \sin(\theta) \sin(\omega t)$$

$$= X \cos(\omega t) - Y \sin(\omega t)$$

$$A \cos(\theta) = X$$

$$A \sin(\theta) = Y$$


$$A = \sqrt{X^2 + Y^2}$$

$$\tan \theta = \frac{Y}{X}$$

$$\theta > 0 \text{ leading}$$

$$\theta < 0 \text{ lagging}$$

$$A \angle \theta$$

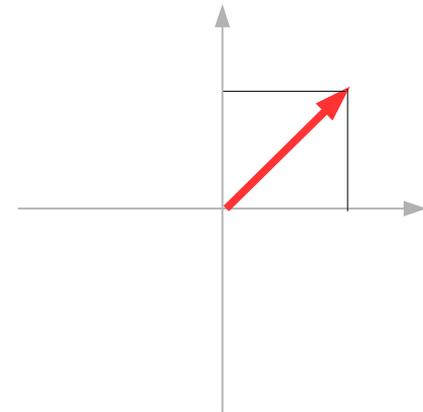

$$(X, Y) = (A \cos \theta, A \sin \theta)$$

$$X + jY = A \cos \theta + j A \sin \theta$$

# Linear Combination of $\cos(\omega t)$ & $\sin(\omega t)$

$$X \cos(\omega t) + Y \sin(\omega t)$$

$$\begin{aligned} & X \cos(\omega t) + Y \sin(\omega t) \\ &= \sqrt{X^2 + Y^2} \left[ \frac{X}{\sqrt{X^2 + Y^2}} \cos(\omega t) + \frac{Y}{\sqrt{X^2 + Y^2}} \sin(\omega t) \right] \\ &= \sqrt{A^2 + B^2} [\cos(\theta) \cos(\omega t) + \sin(\theta) \sin(\omega t)] \\ &= \sqrt{X^2 + Y^2} \cos(\theta - \omega t) \\ &= \sqrt{X^2 + Y^2} \cos(\omega t - \theta) \end{aligned}$$

$$\sqrt{X^2 + Y^2} \cos(\omega t - \theta)$$

$$\begin{aligned} & X \cos(\omega t) + Y \sin(\omega t) \\ &= \sqrt{X^2 + Y^2} \cos(\omega t - \theta) \end{aligned}$$

$$\cos(\theta) = \frac{X}{\sqrt{X^2 + Y^2}}$$

$$\sin(\theta) = \frac{Y}{\sqrt{X^2 + Y^2}}$$


$$X \cos(\omega t) - Y \sin(\omega t)$$

$$\begin{aligned} & \frac{X}{A} \cos(\omega t) - \frac{Y}{A} \sin(\omega t) \\ & \cos(\theta) \cos(\omega t) - \sin(\theta) \sin(\omega t) \end{aligned}$$


$$\sqrt{X^2 + Y^2} \cos(\omega t + \theta)$$

$$A \cos(\omega t + \theta)$$


# RC Circuit

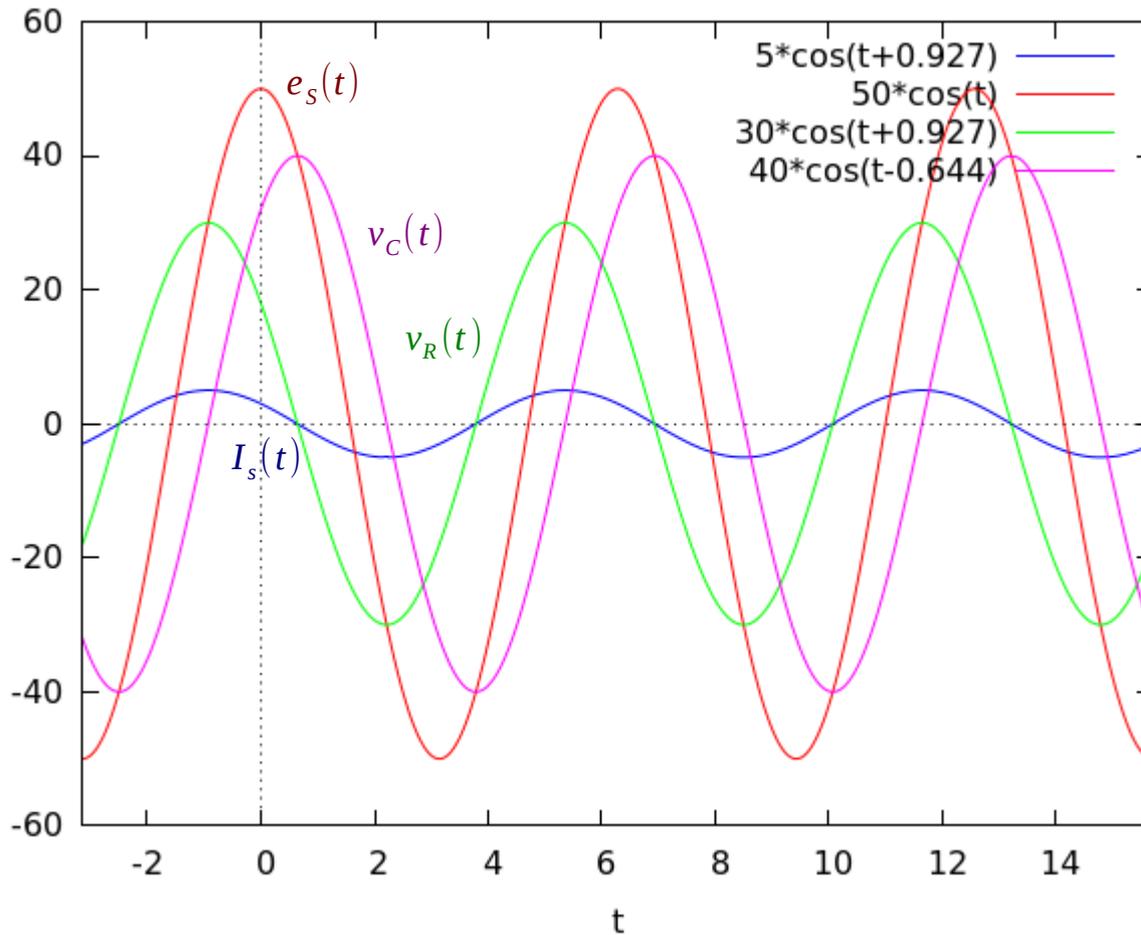

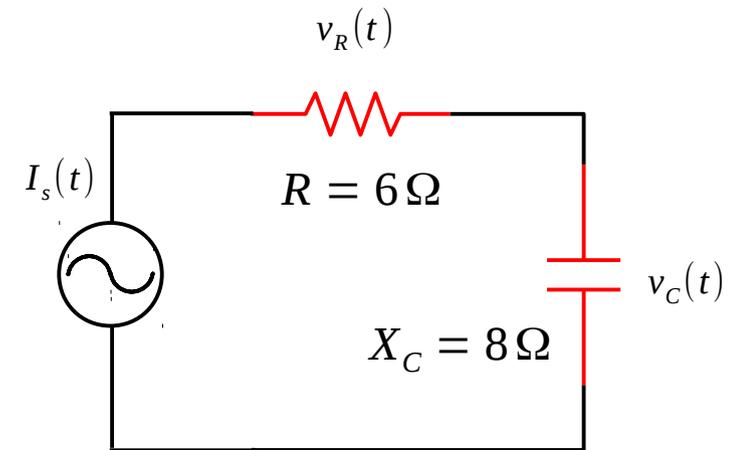(%035)  $I_s(t) := 5 \cos(\omega t + 0.927)$   
(%036)  $e_s(t) := 50 \cos(\omega t)$   
(%037)  $v_r(t) := 30 \cos(\omega t + 0.927)$   
(%038)  $v_c(t) := 40 \cos(\omega t - 0.644)$




# Current Source

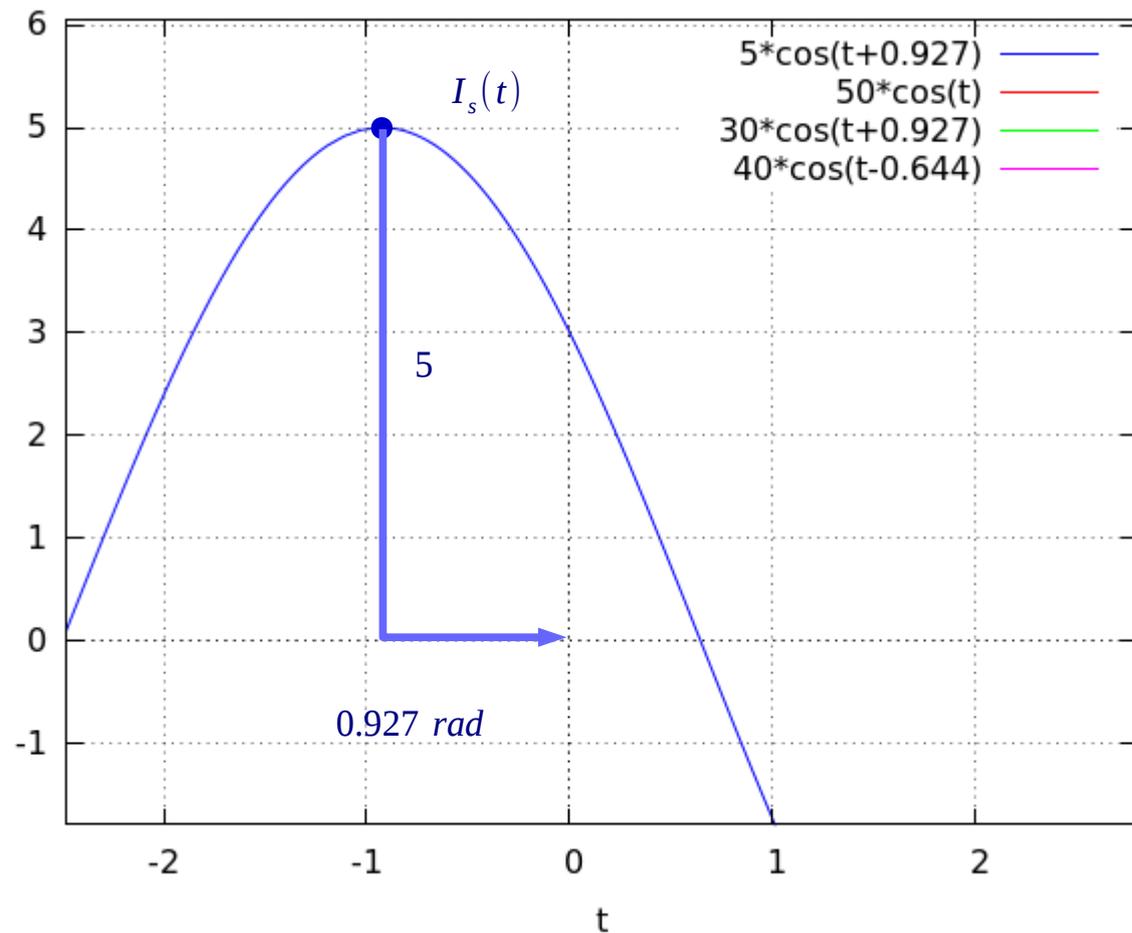

```
(%035) Is(t):=5 cos(ω t+0.927)  
(%036) es(t):=50 cos(ω t)  
(%037) vr(t):=30 cos(ω t+0.927)  
(%038) vc(t):=40 cos(ω t-0.644)
```

# Resistor

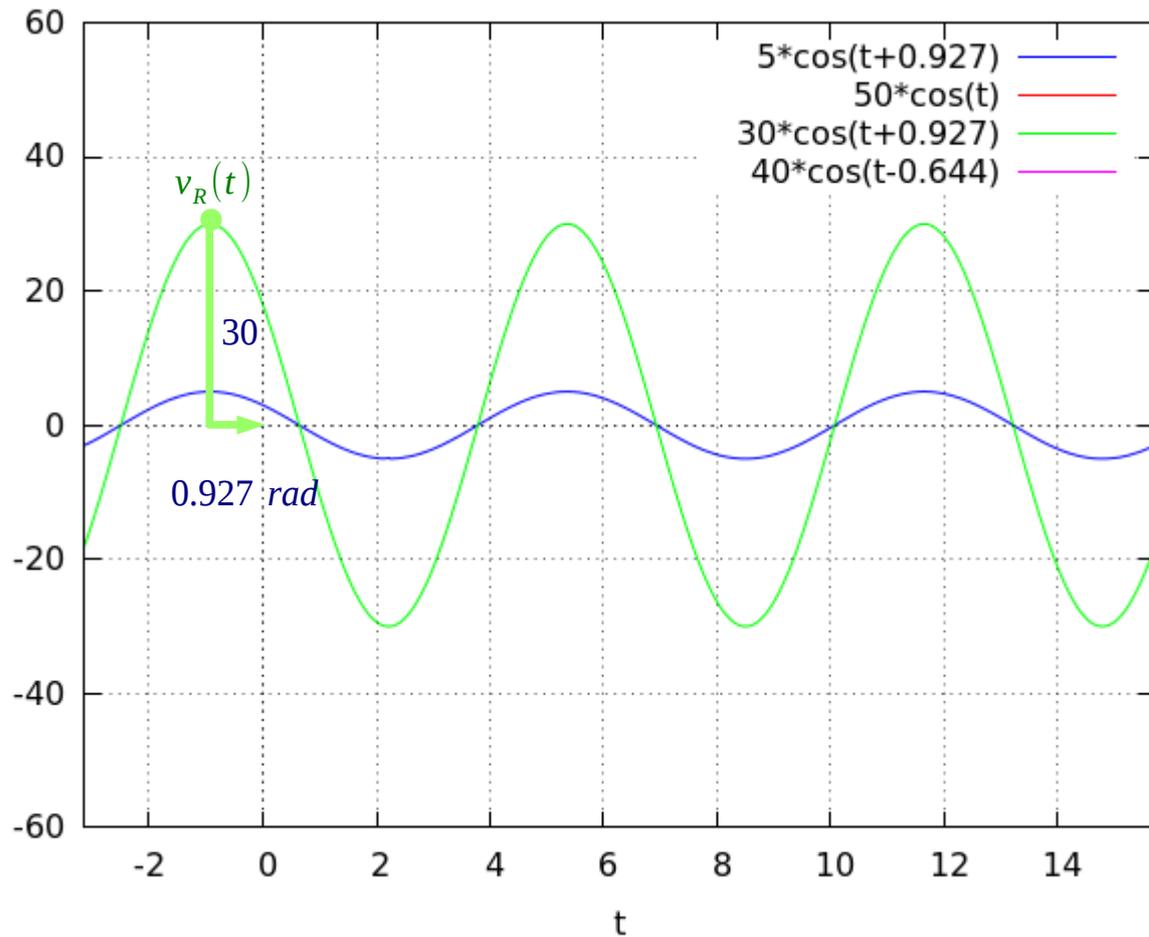

```

(%035) Is(t):=5 cos(ω t+0.927)
(%036) es(t):=50 cos(ω t)
(%037) vr(t):=30 cos(ω t+0.927)
(%038) vc(t):=40 cos(ω t-0.644)
    
```


$$v_R = i_R \cdot R$$

$[i_R, v_R]$   
  
 same phase

$$R = 6 \Omega \quad Is(t) \rightarrow 5$$

$$Is(t) \cdot 6 \Omega \rightarrow 30$$

# Capacitor

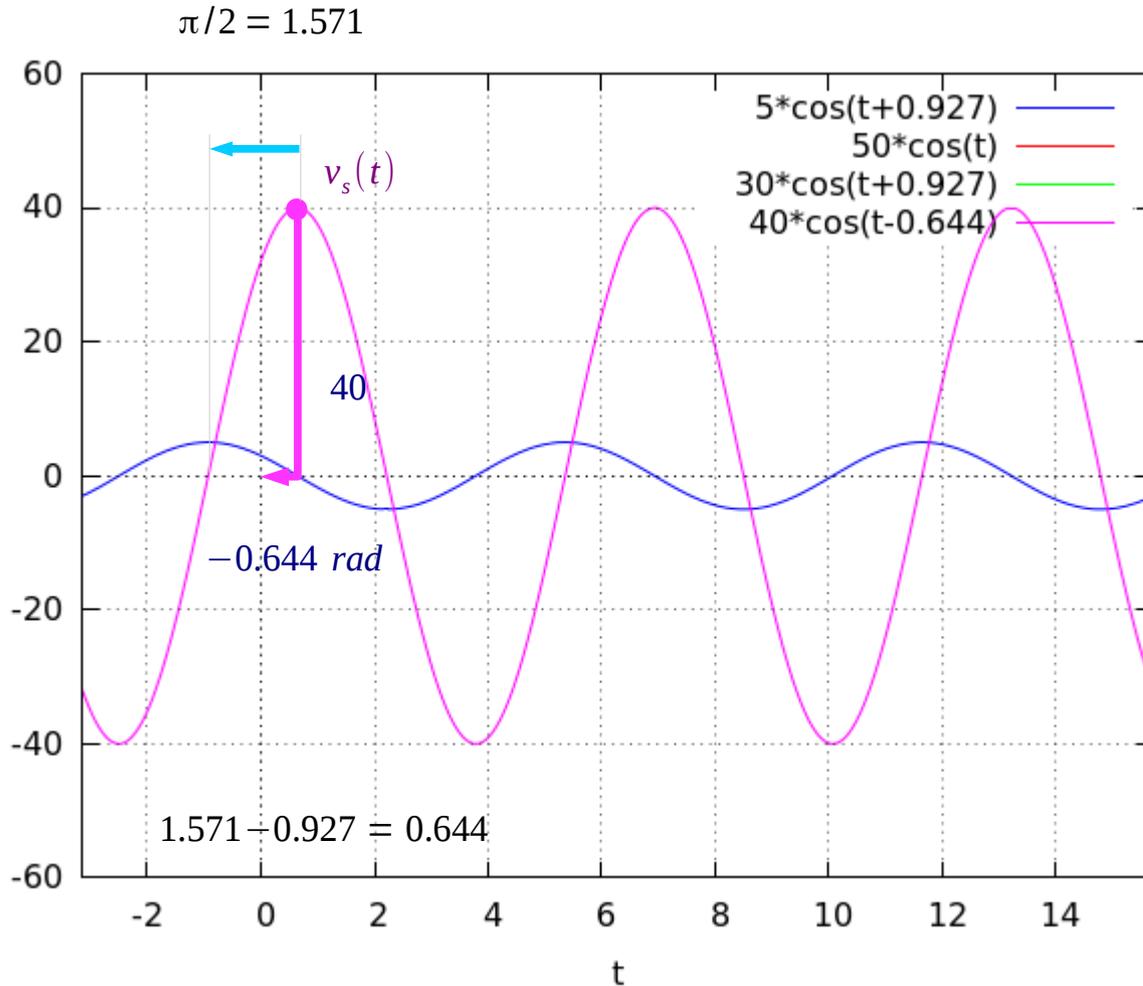

```
(%035) Is(t):=5 cos(ω t+0.927)
(%036) es(t):=50 cos(ω t)
(%037) vr(t):=30 cos(ω t+0.927)
(%038) vc(t):=40 cos(ω t-0.644)
```

$$i_C = C \cdot \frac{dv_C}{dt}$$

$[i_C, v_C]$


↑  
leads by 90

$$X_C = 8 \Omega$$

$$I_s(t) \rightarrow 5$$

$$I_s(t) \cdot 8 \Omega \rightarrow 40$$

$$v_R(t) + v_C(t)$$

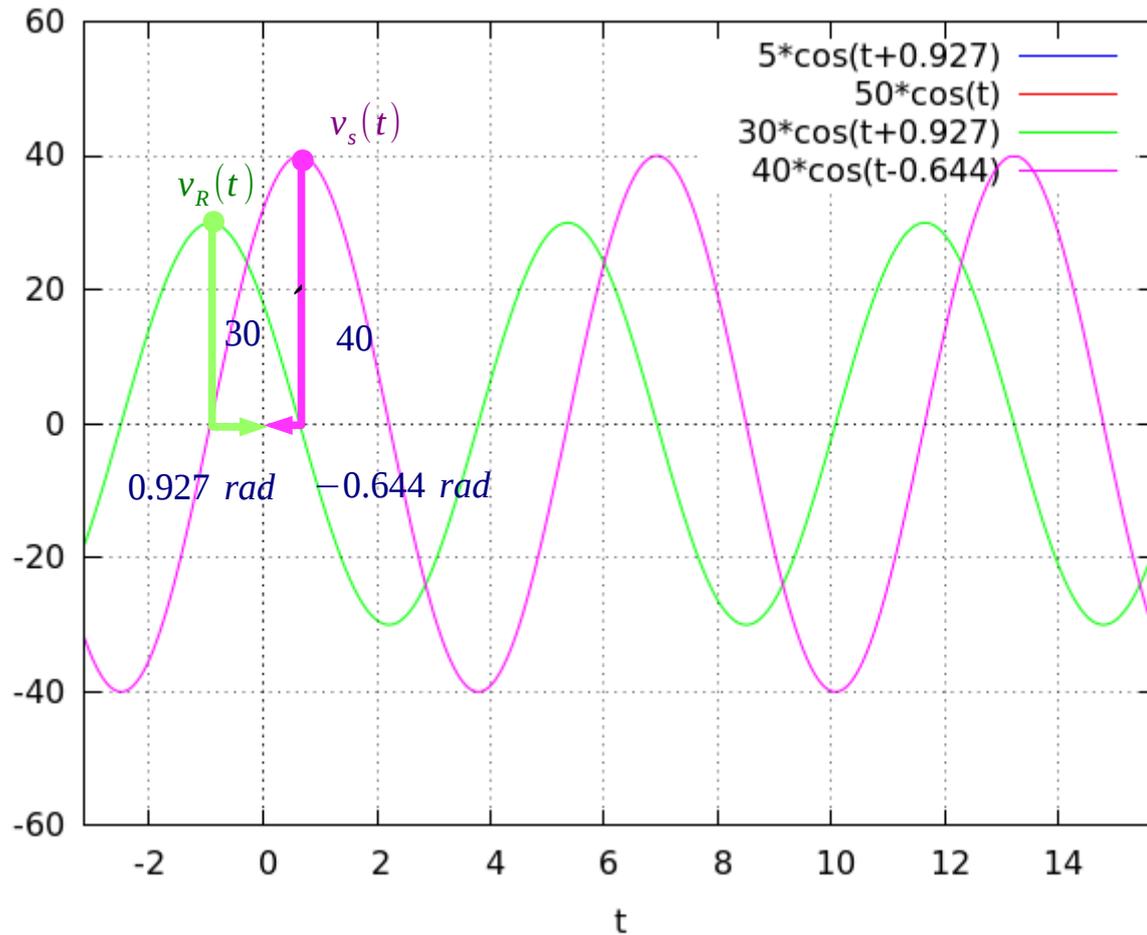

```

(%035) Is(t):=5 cos(ω t+0.927)
(%036) es(t):=50 cos(ω t)
(%037) vr(t):=30 cos(ω t+0.927)
(%038) vc(t):=40 cos(ω t-0.644)
  
```

# Phasor Addition

$$A_1 \cos(\omega t + \theta_1) = A_1 \cos(\omega t) \cos(\theta_1) - A_1 \sin(\omega t) \sin(\theta_1)$$

$$A_2 \cos(\omega t + \theta_2) = A_2 \cos(\omega t) \cos(\theta_2) - A_2 \sin(\omega t) \sin(\theta_2)$$

$$(\%035) \text{ Is}(t) := 5 \cos(\omega t + 0.927)$$

$$(\%036) \text{ es}(t) := 50 \cos(\omega t)$$

$$(\%037) \text{ vr}(t) := 30 \cos(\omega t + 0.927)$$

$$(\%038) \text{ vc}(t) := 40 \cos(\omega t - 0.644)$$

$$A_1 \cos(\omega t + \theta_1) + A_2 \cos(\omega t + \theta_2) = X \cos(\omega t) - Y \sin(\omega t) = A \cos(\omega + \theta)$$

$$X = A_1 \cos(\theta_1) + A_2 \cos(\theta_2)$$

$$Y = A_1 \sin(\theta_1) + A_2 \sin(\theta_2)$$

$$X = 50.0$$

$$Y = 0.0$$

$$A = \sqrt{50.0^2 + 0.0^2} = 50.0$$

$$\theta = \tan^{-1} \frac{0.0}{50.81} = 0$$


$$A_1 \cos(\theta_1) = 30 \cos(0.927) = 18.0$$

$$A_1 \sin(\theta_1) = 30 \sin(0.927) = 24.0$$

$$A_2 \cos(\theta_1) = 40 \cos(-0.644) = 32.0$$


$$A_2 \sin(\theta_1) = 40 \sin(-0.644) = -24.0$$

# Is(t) and Es(t)

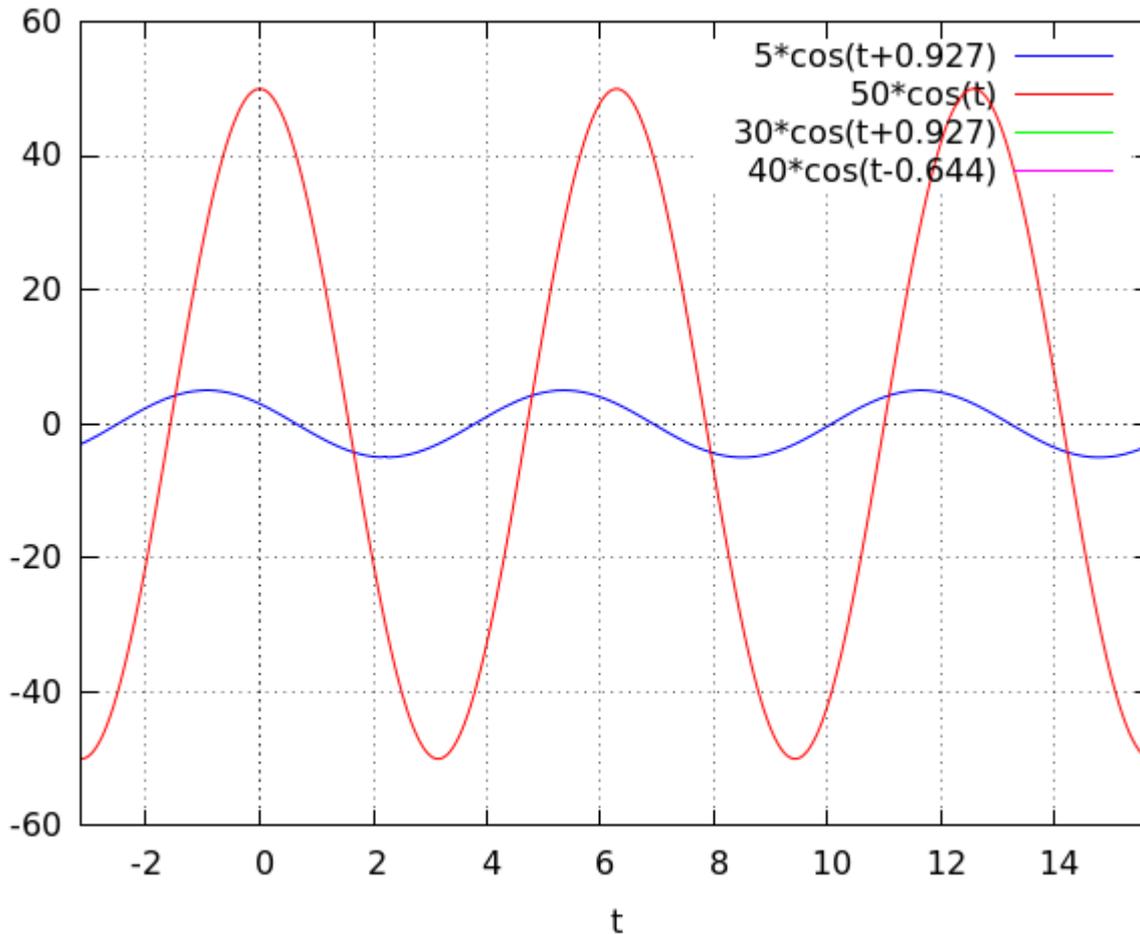

$$I_s Z_T = (5 \angle 0.927) \cdot (10 \angle -0.927) = 50 \angle 0$$






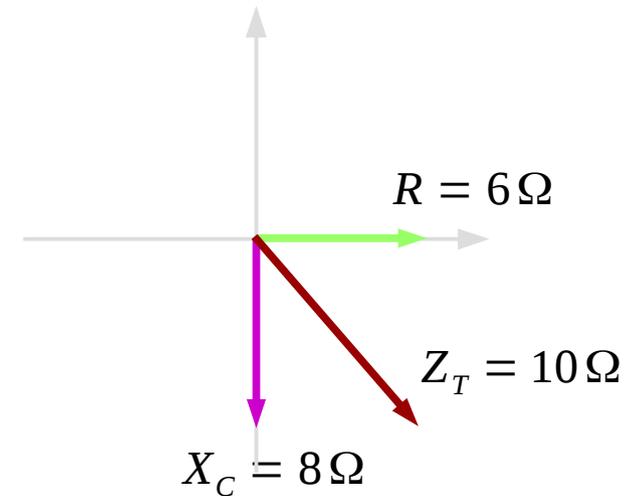
```
(%035) Is(t):=5 cos(ω t+0.927)
(%036) es(t):=50 cos(ω t)
(%037) vr(t):=30 cos(ω t+0.927)
(%038) vc(t):=40 cos(ω t-0.644)
```








$$Z_T = 10 \angle -0.927$$

$$E_s = I_s Z_T$$

# Phasor

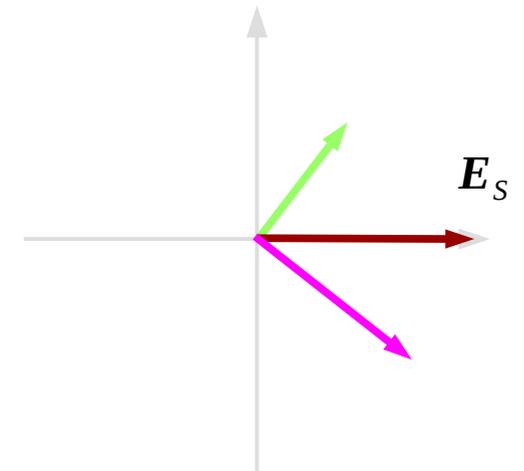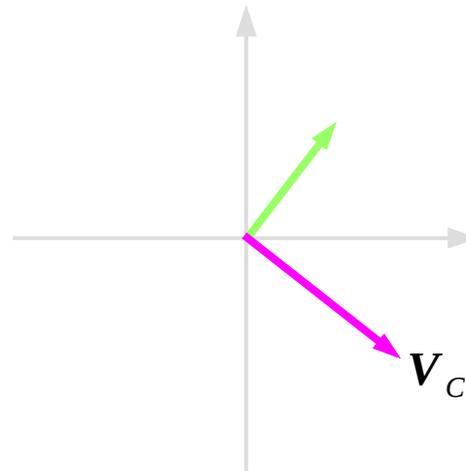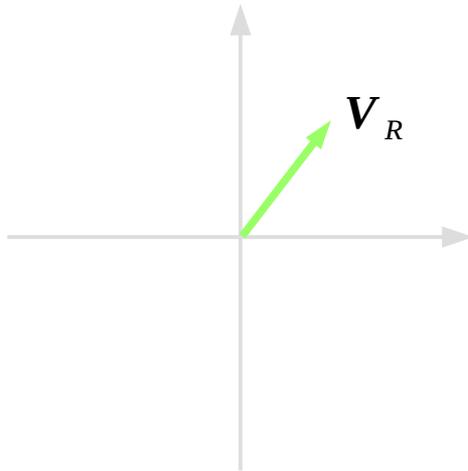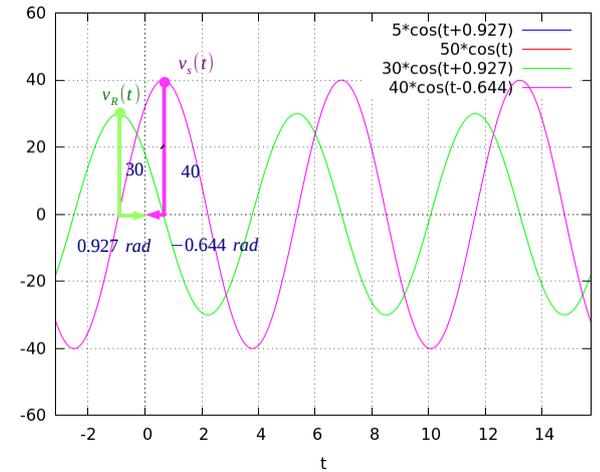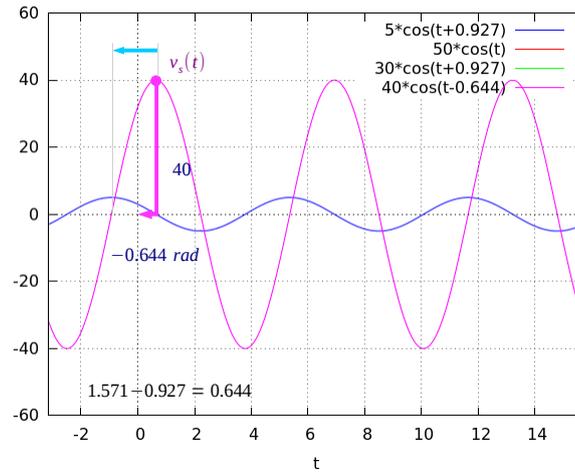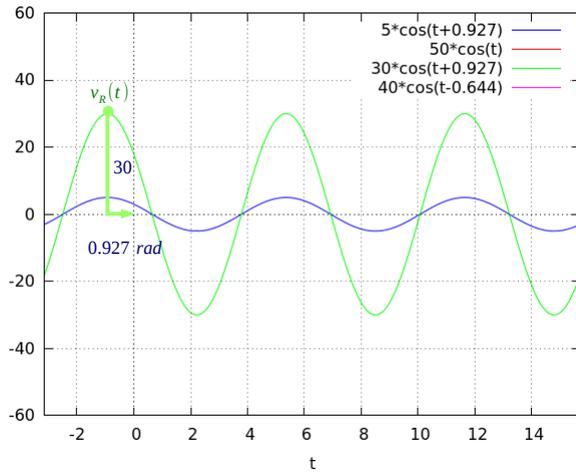

# Phasor

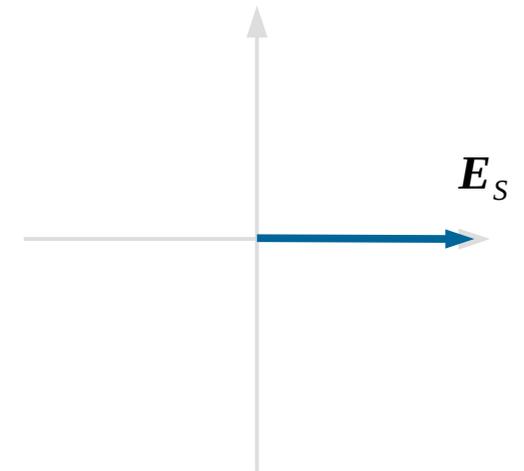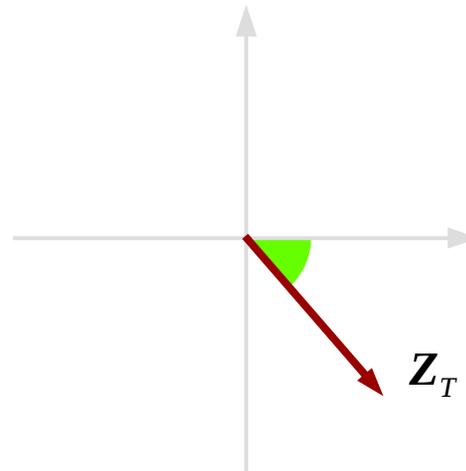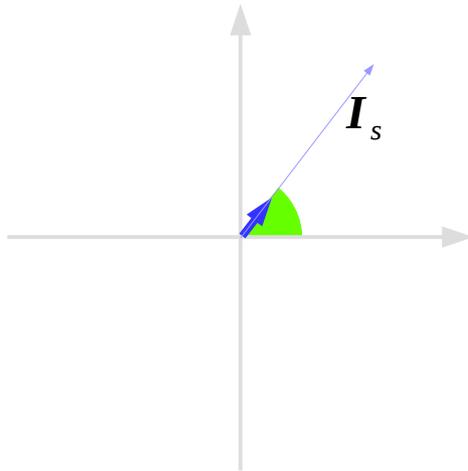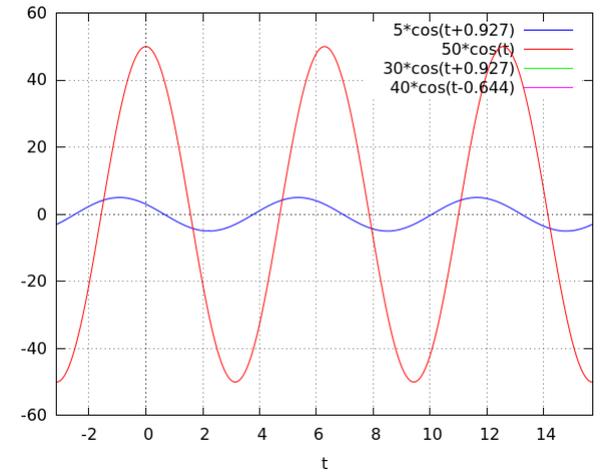
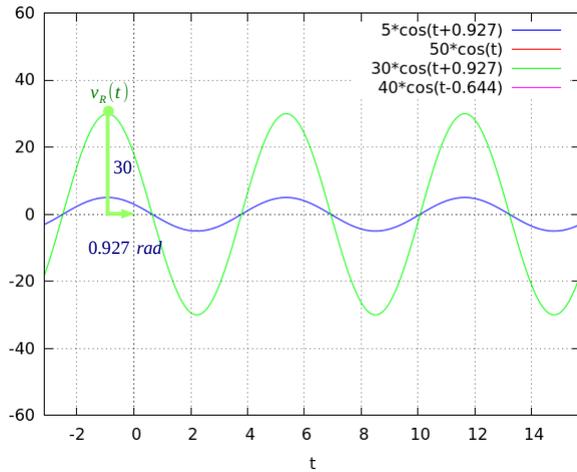


# Sinusoidal Functions

- **everlasting** sinusoid function

state at  $t = 0^-$  = state at  $t = 0^+$


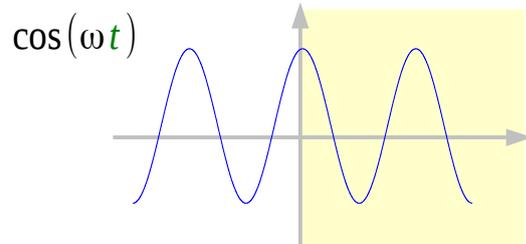
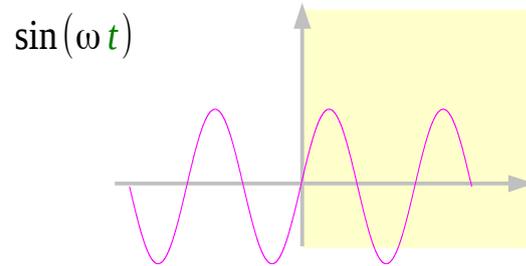
continuous state between  $t = 0^-$  &  $0^+$



- **causal** sinusoid function

zero state at  $t = 0^-$

non-zero state at  $t = 0^+$

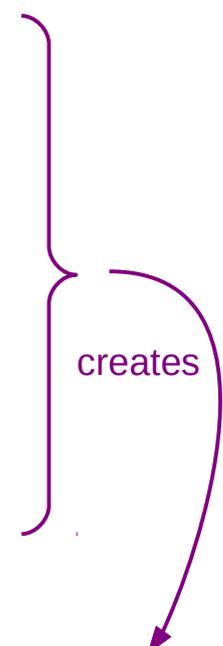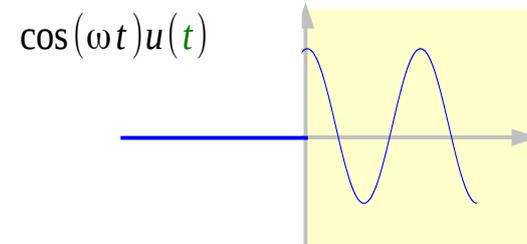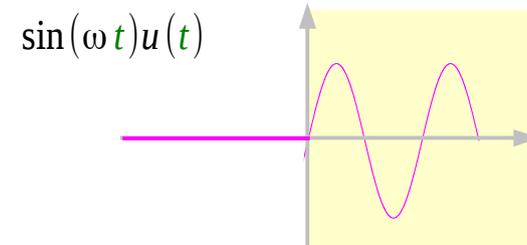


zero conditions at time  $t = 0^-$




non-zero conditions at time  $t = 0^+$



# Steady State Response

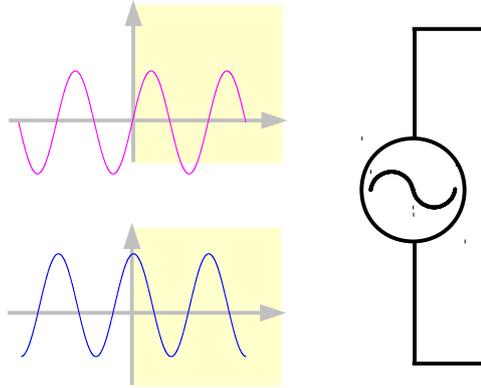

*Can apply impedance method*

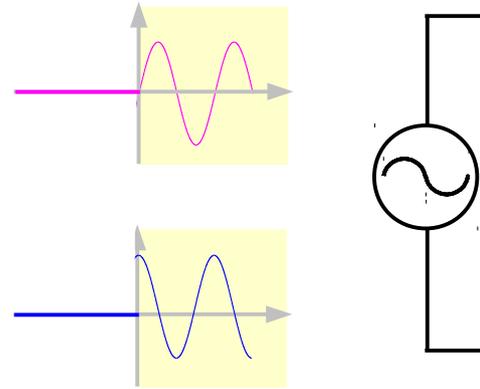

*Cannot apply impedance method*

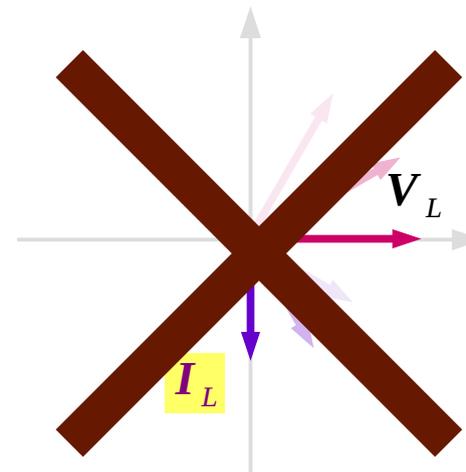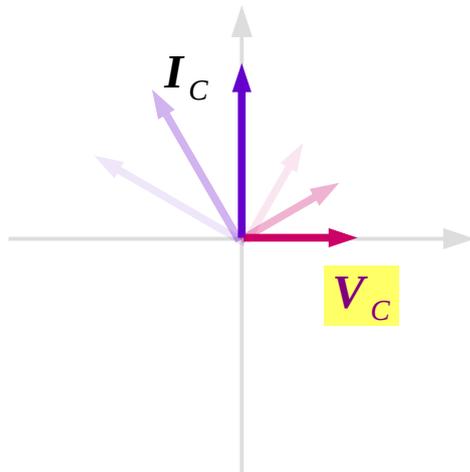

## References

[1] <http://en.wikipedia.org/>

[2] J.H. McClellan, et al., Signal Processing First, Pearson Prentice Hall, 2003