

Logic Circuit Design

NAND-1

20171009

Copyright (c) 2015 - 2016 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".



References

Some Figures from the following sites


[1] <http://pages.hmc.edu/harris/cmosvlsi/4e/index.html>
Weste & Harris Book Site

[2] Introduction to VLSI Circuits and Systems, Uyemura


[2] en.wikipedia.org

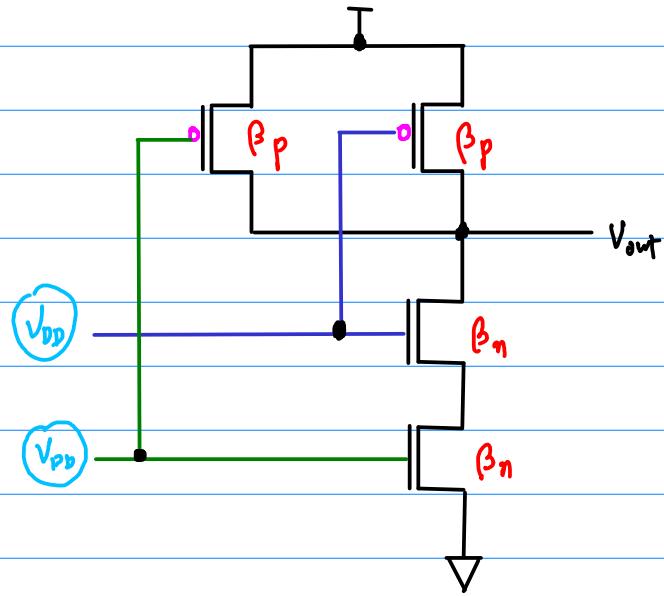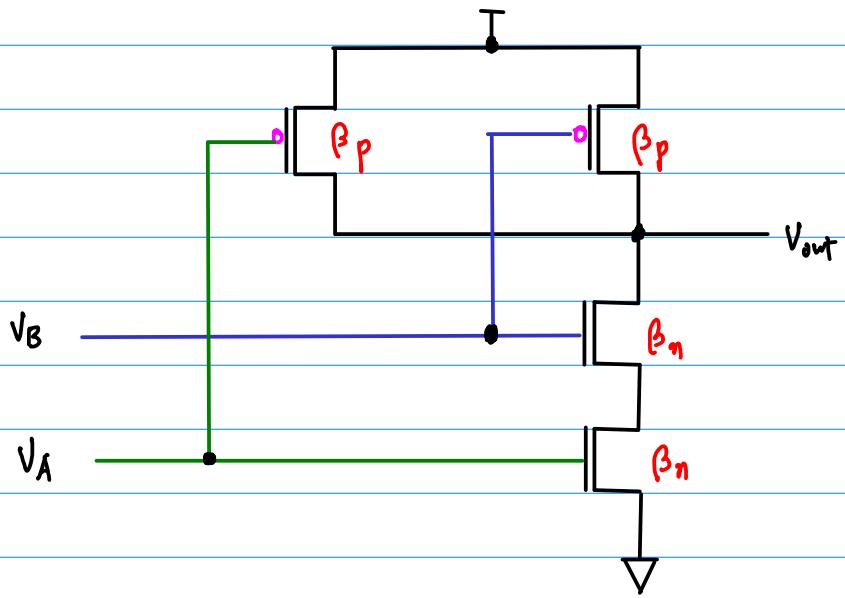


I

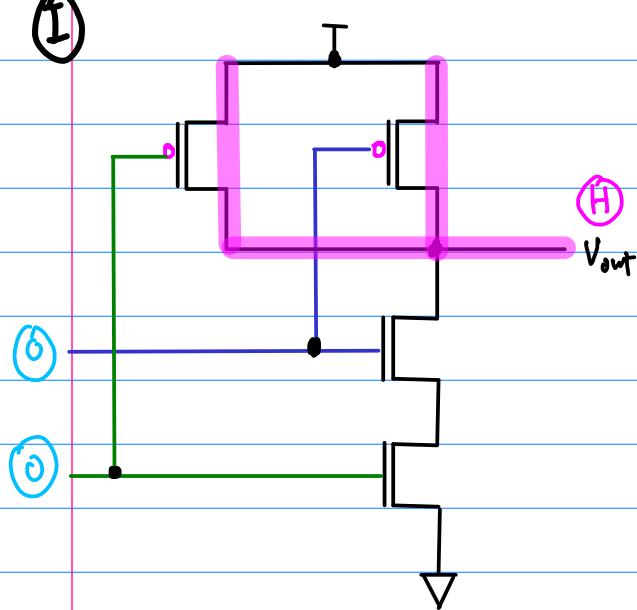


II



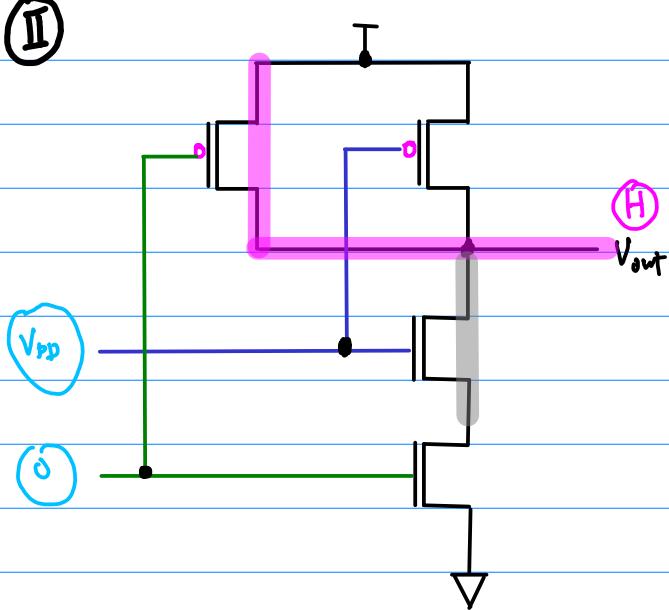



III

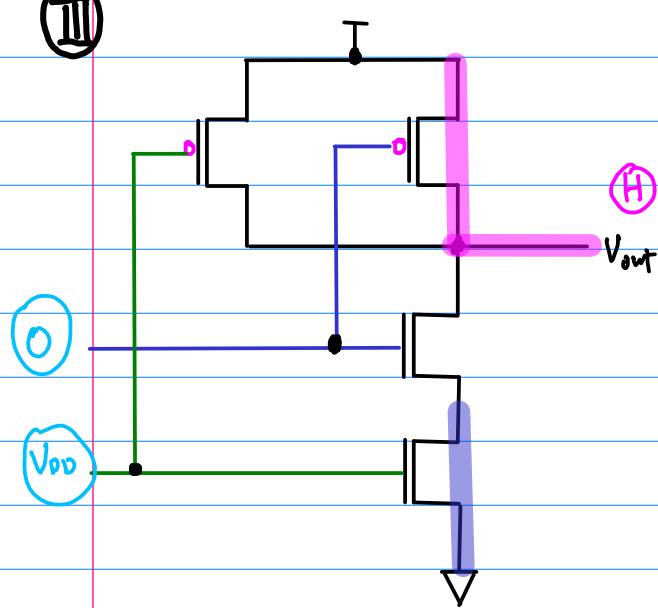


IV

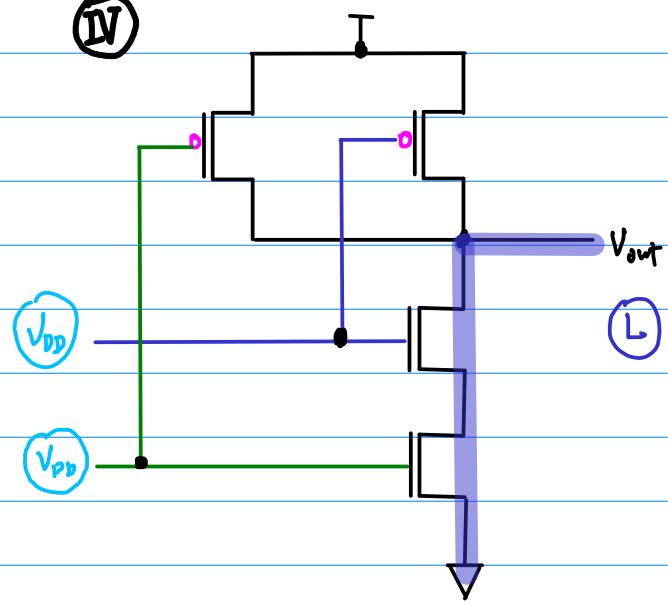

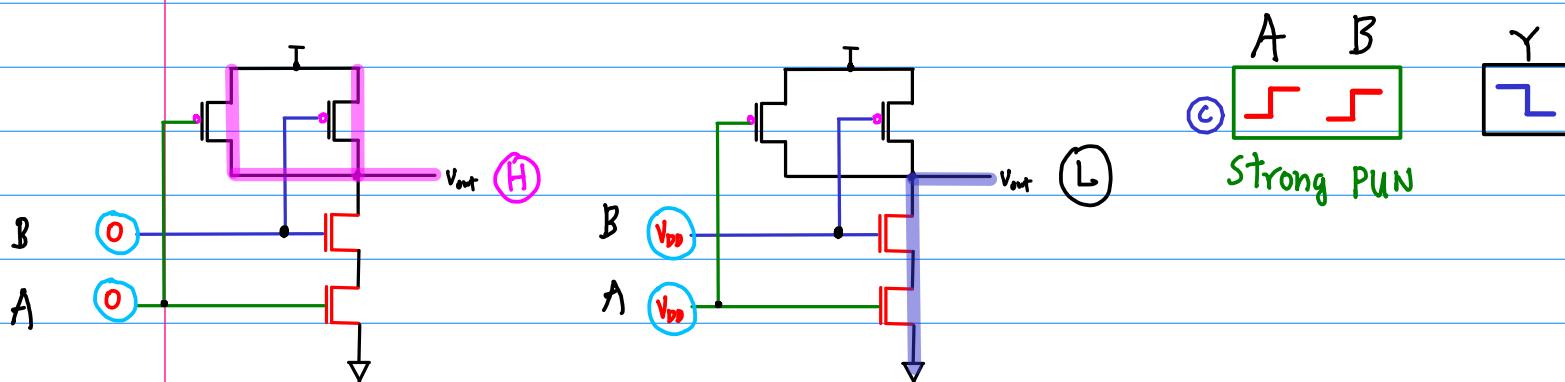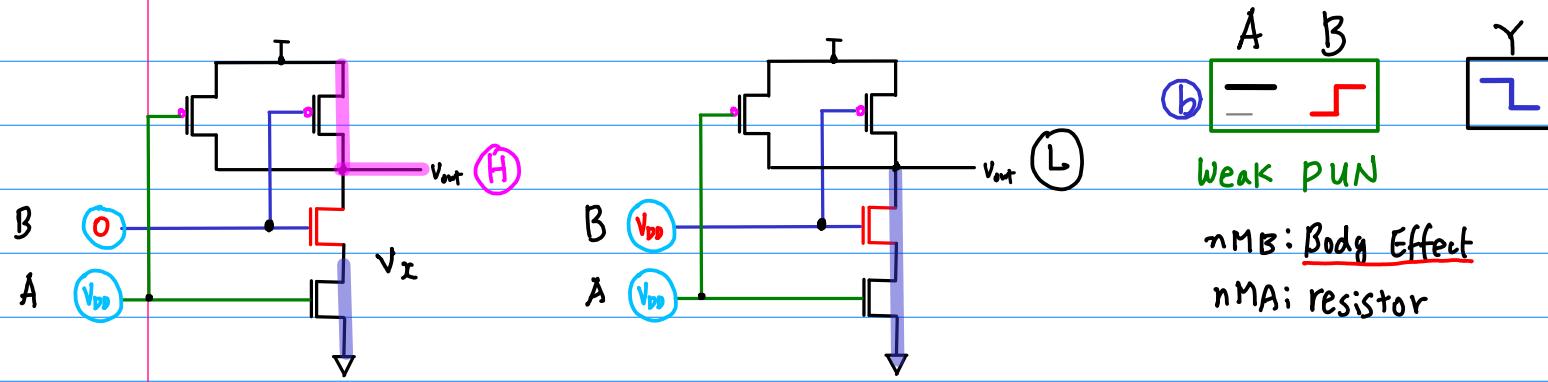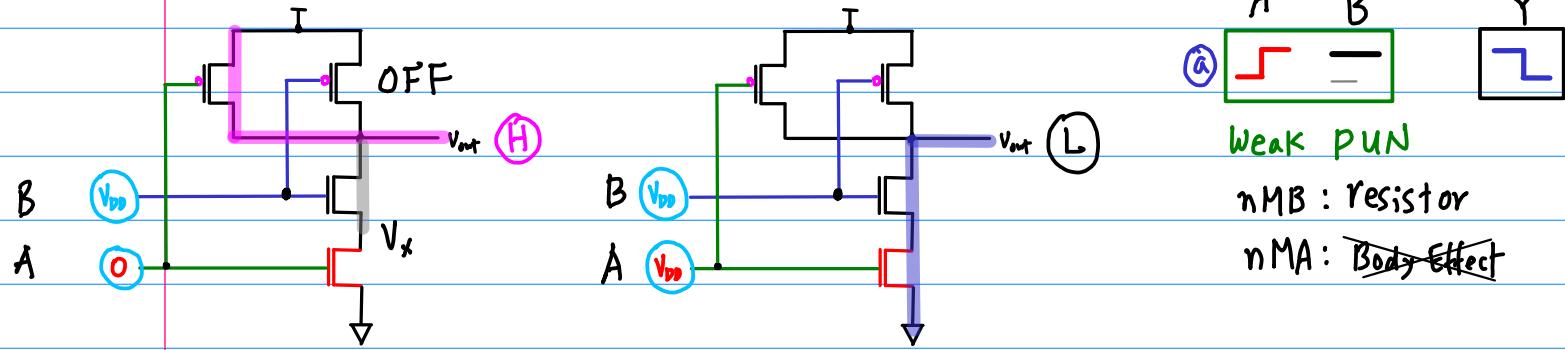

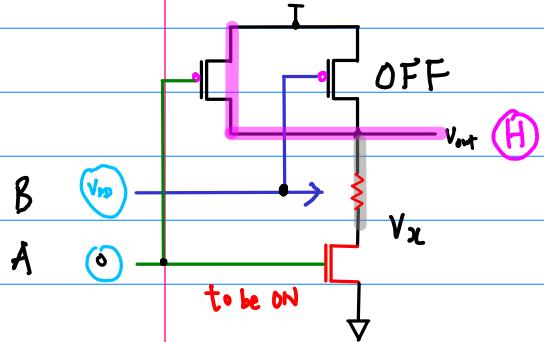



{ small R
 { large C (load)

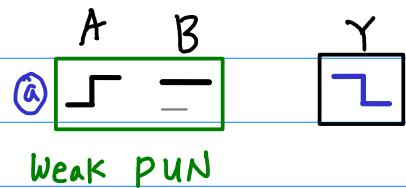


{ small voltage drop
 { slow change

nMB : Resistor
 nMA : ~~Body Effect~~

small effect on VTC

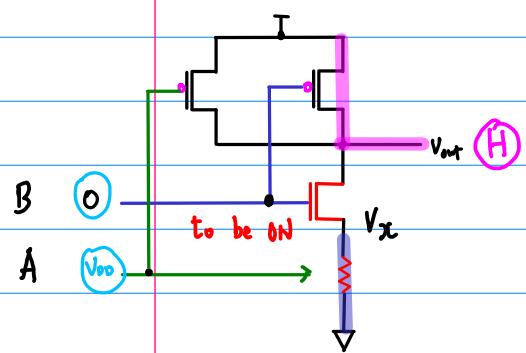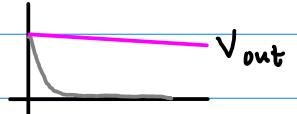


{ small R
 { small C (load)

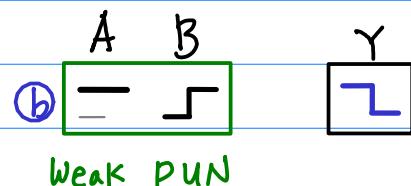

{ large voltage drop
 { immediate change




nMB: Body Effect
 nMA: resistor

increase V_T


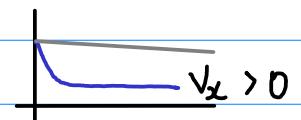


→ hard to turn ON nMB

→ VTC shifted to the right

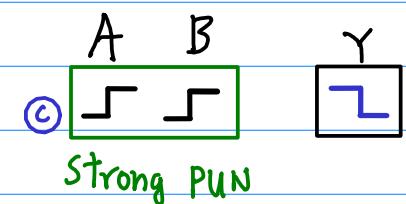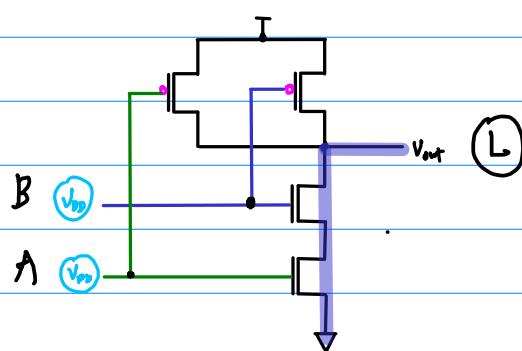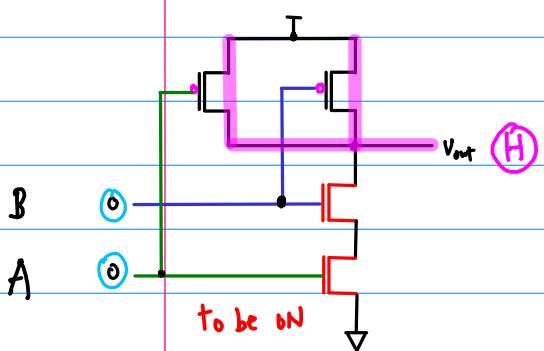


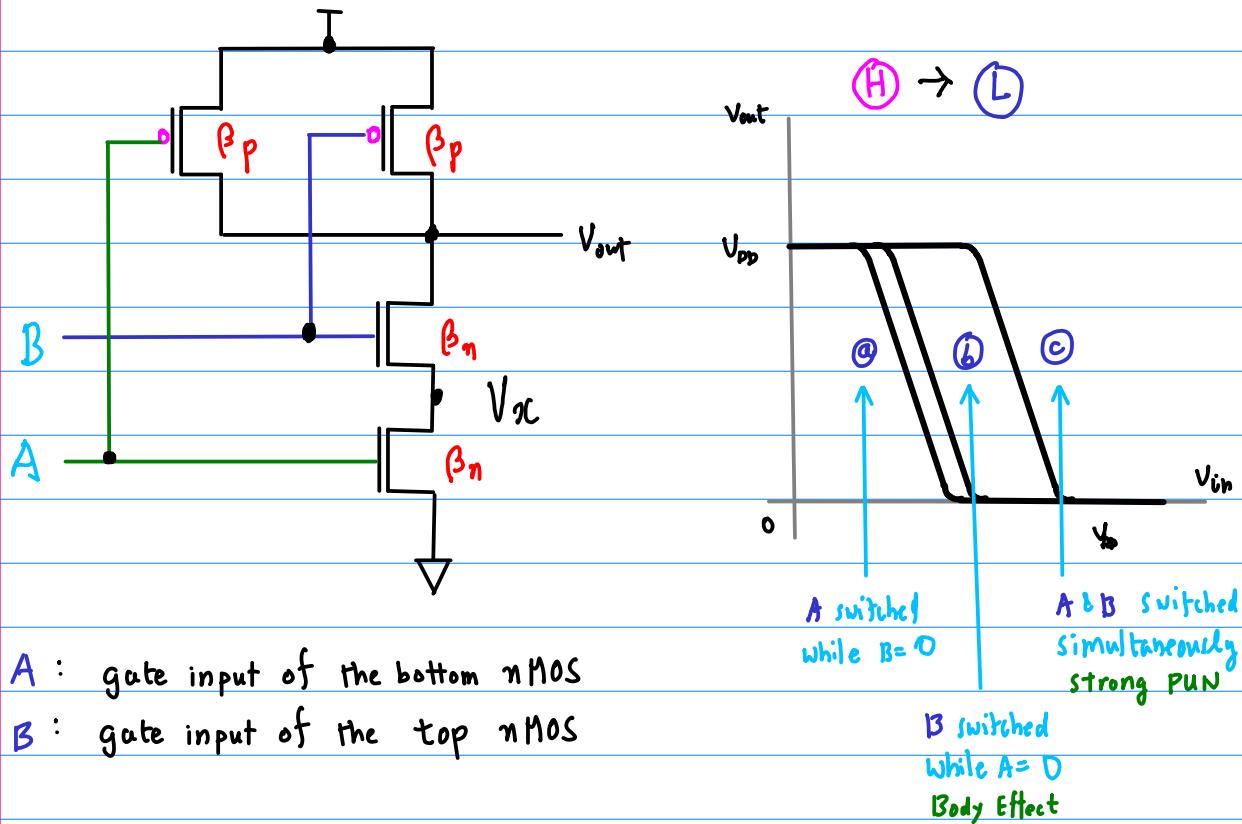
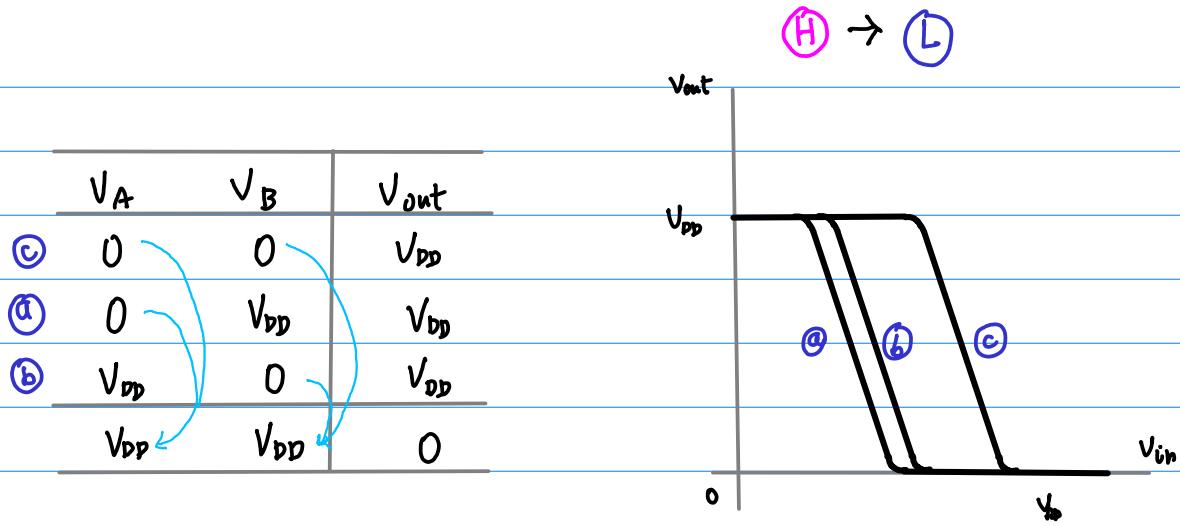
→ hard to turn ON nMA & nMB
 → VTC shifted to the right





Strong PUN
Body Effect } difficult to turn on nMOS


VTC shifted the right



	V_A	V_B	V_{out}		V_A	V_B	V_{out}
c	0	0	V_{DD}		0	0	0
a	0	V_{DD}	V_{DD}		0	—	—
b	V_{DD}	0	V_{DD}		—	0	—

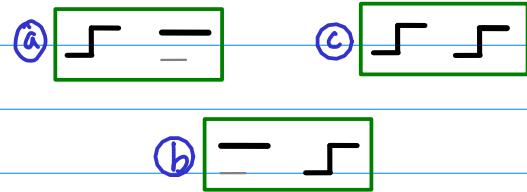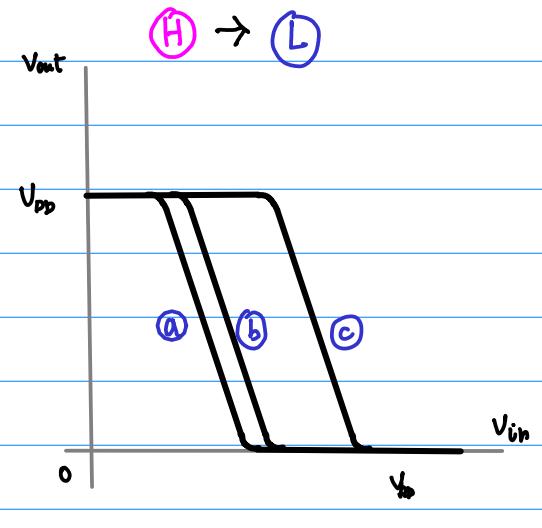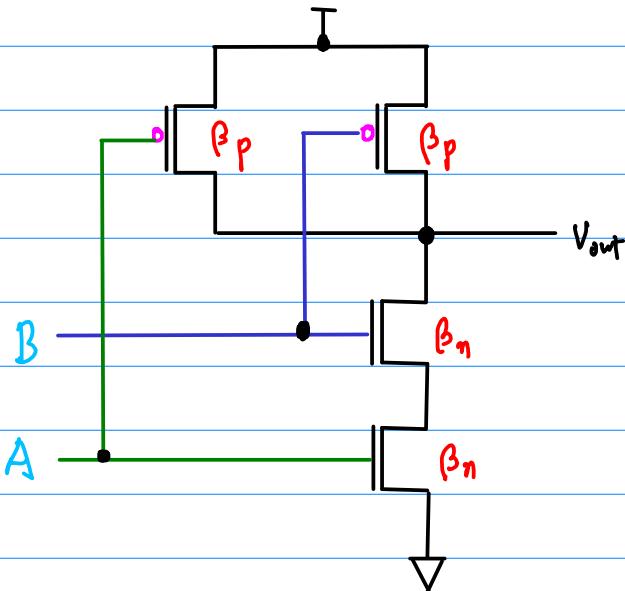

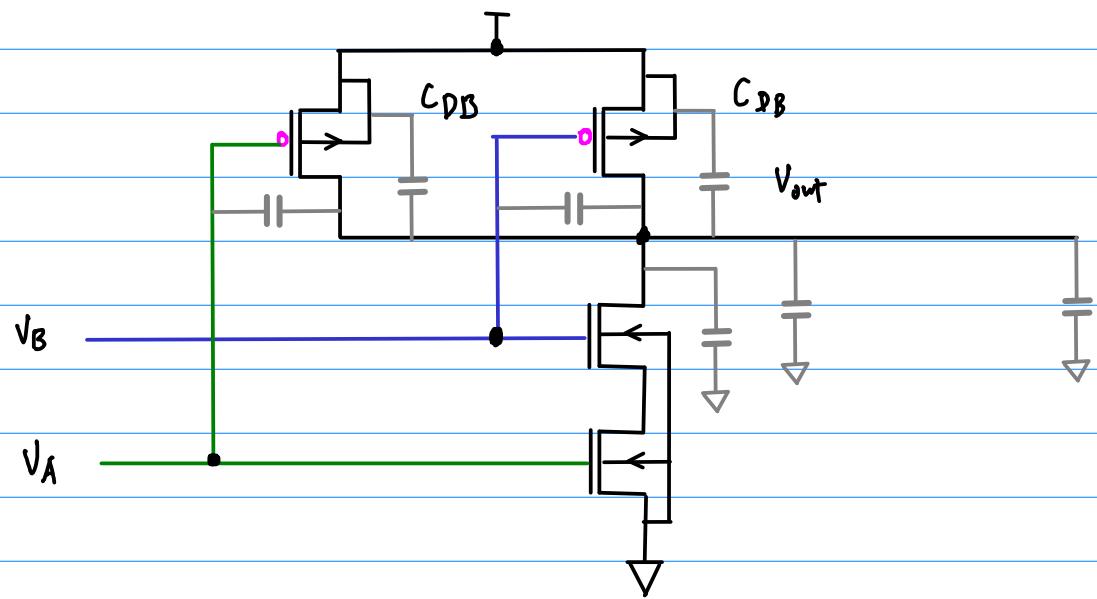

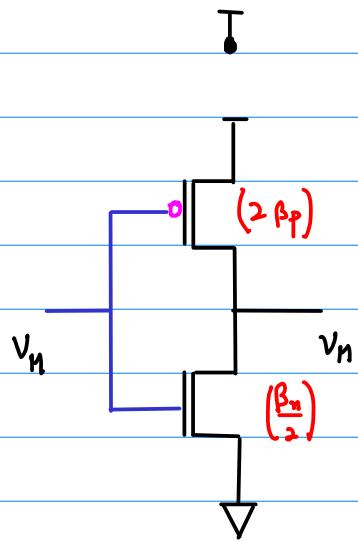

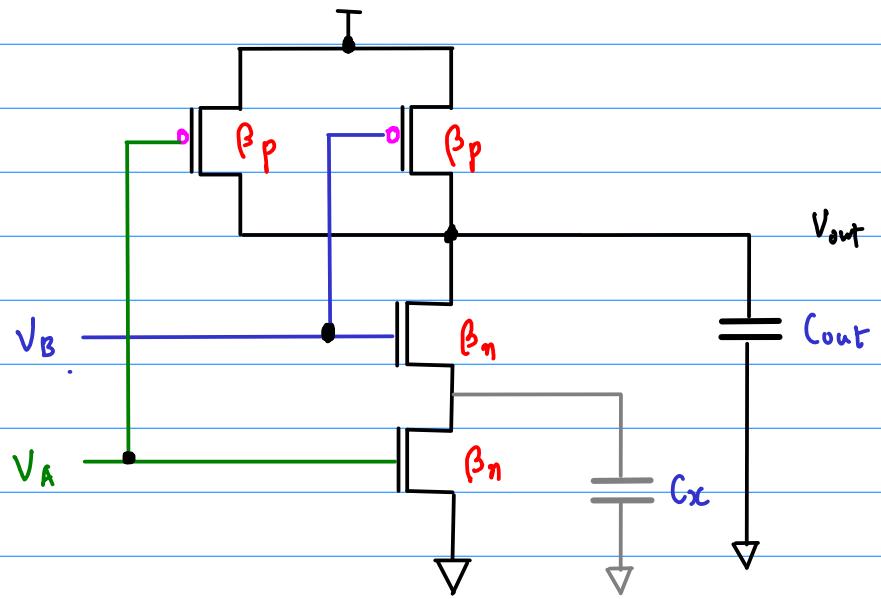


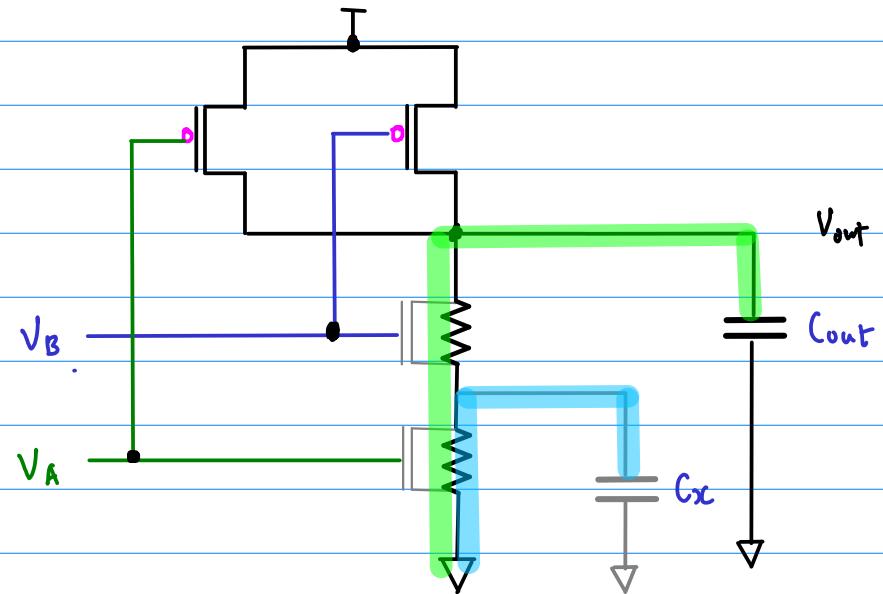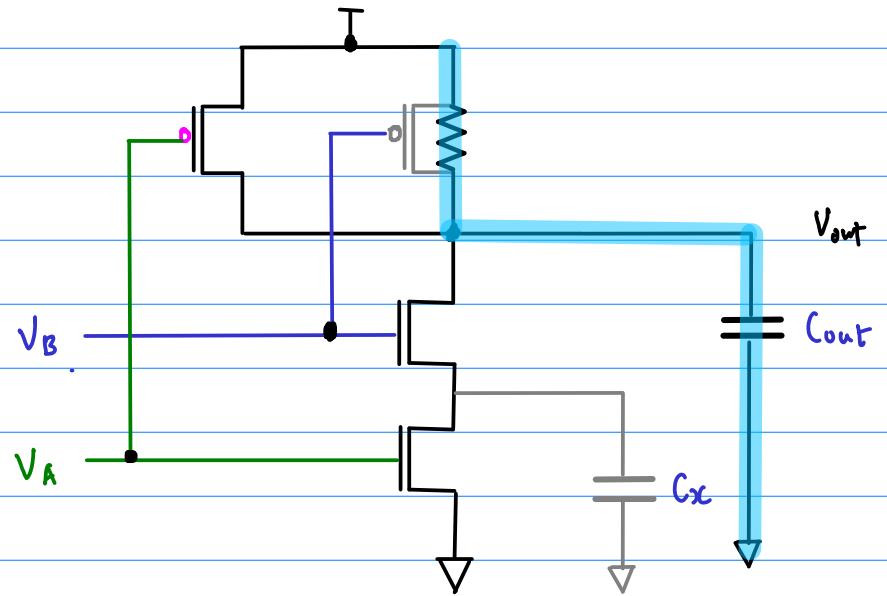


$$C_{out} = C_{FET} + C_L$$

$$C_{FET} = C_{Dn} + 2C_{Dp}$$

$$R_p = \frac{1}{\beta_p (V_{DD} - |V_{TP}|)} \quad R_n = \frac{1}{\beta_n (V_{DD} - V_{TN})}$$

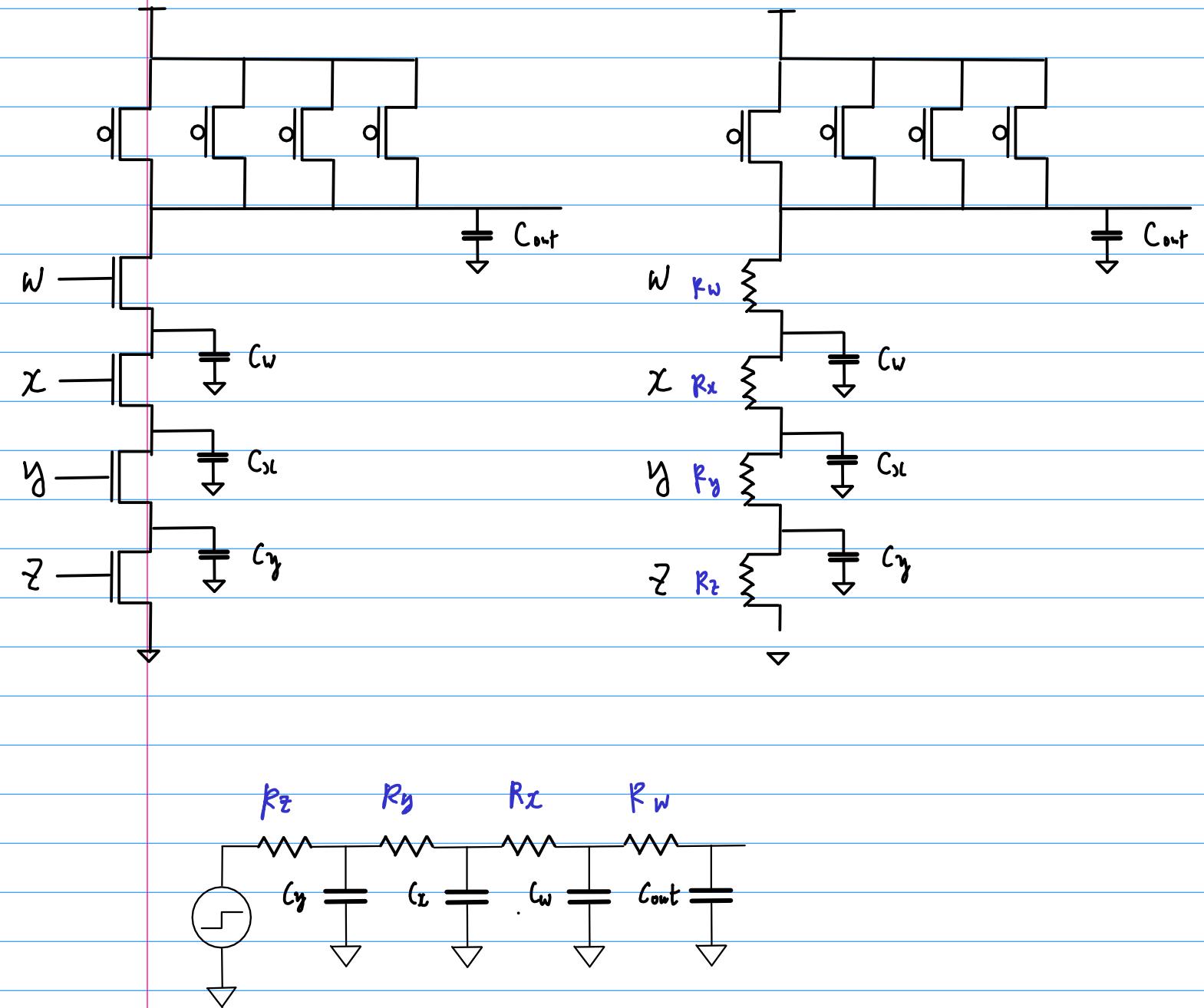


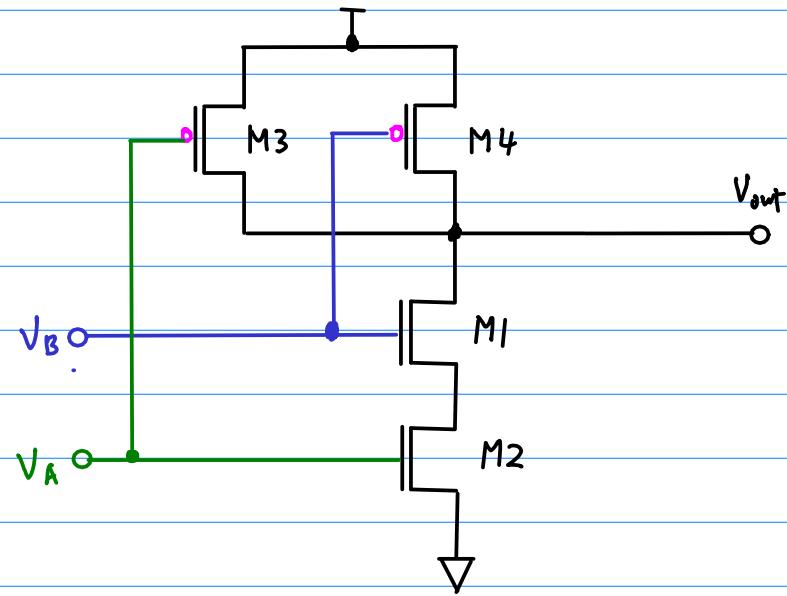
$$t_{pd} = C_y R_z + G_x (R_y + R_z) + C_w (R_x + R_y + R_z) + C_{out} (R_w + R_x + R_y + R_z)$$



V_A	V_B	V_{out}
0	0	V_{DD}
V_{DD}	0	V_{DD}
0	V_{DD}	V_{DD}

\Rightarrow

V_A	V_B	V_{out}
V_{th}	V_{th}	V_{th}
V_{DD}	V_{th}	V_{th}
V_{th}	V_{DD}	V_{th}

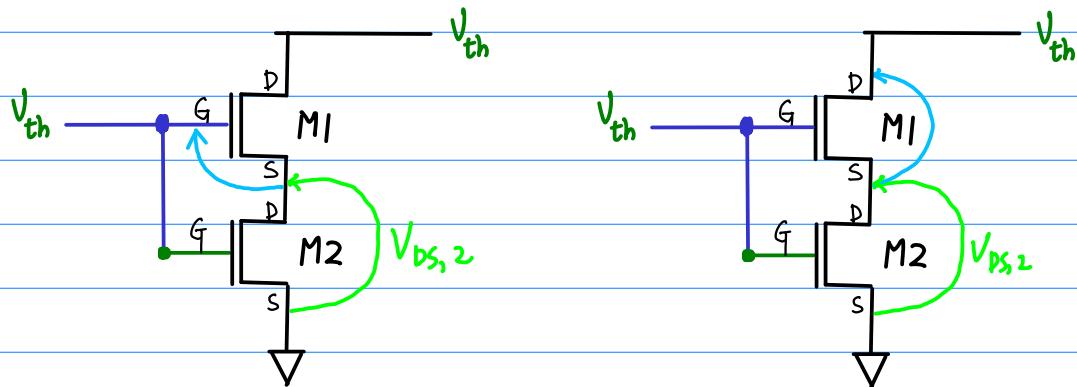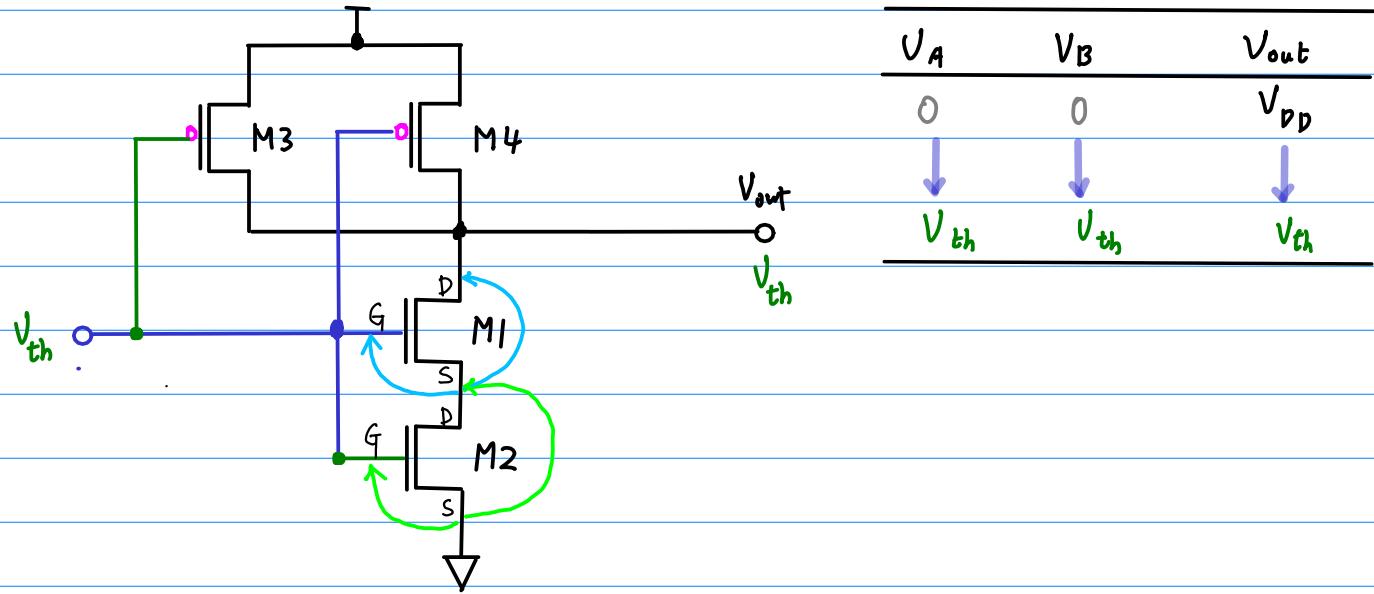

$$V_{GS,1} = V_{th} - V_{DS,2}$$


$$V_{th} = V_{DS,1} + V_{DS,2}$$

$$V_{th} - V_{DS,2} = V_{DS,1}$$

\therefore

$$V_{GS,1} = V_{DS,1}$$

M1 saturated.

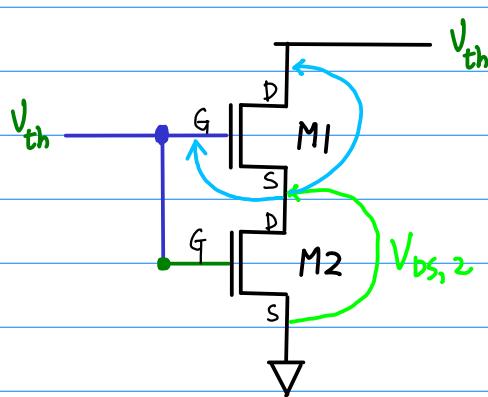

$$I_D = \frac{B_n}{2} (V_{GS,1} - V_{Ton})^2$$

$$V_{GS,1} = V_{th} - V_{DS,2}$$


$$I_D = \frac{B_n}{2} (V_{th} - V_{DS,2} - V_{Ton})^2$$

$$I_D = \frac{B_n}{2} (V_{th} - V_{Ton} - V_{DS,2})^2$$

\therefore

$$V_{GS,1} = V_{DS,1}$$

M1 saturated.

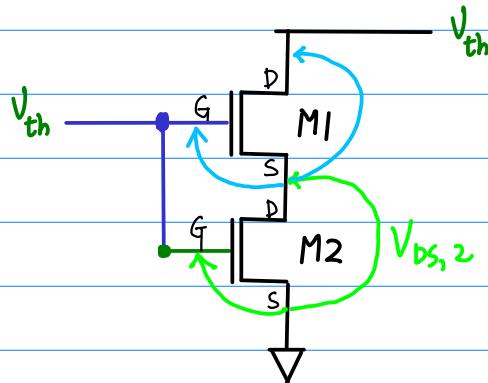

$$\begin{aligned} V_{th} &= V_{GS1} + V_{DS2} \\ &= V_{GS2} \end{aligned}$$

$$V_{GS1} < V_{GS2}$$



$$V_{GS2} - V_{DS2} = V_{GS1} > 0$$

$$V_{GS2} > V_{GS1}$$

Linear


$$I_{ds} = \begin{cases} 0 & V_{gs} < V_t \quad \text{cutoff} \\ \beta \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds} & V_{ds} < V_{dsat} \quad \text{linear} \\ \frac{\beta}{2} (V_{gs} - V_t)^2 & V_{ds} > V_{dsat} \quad \text{saturation} \end{cases}$$
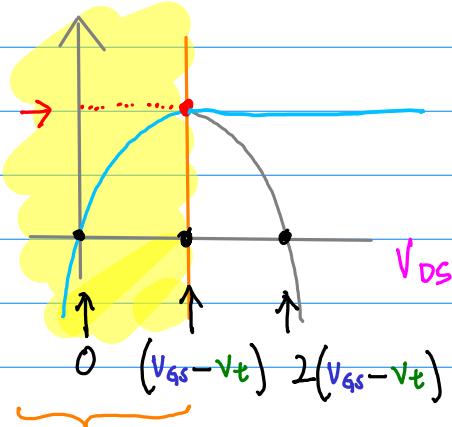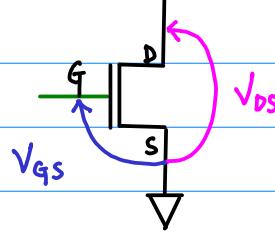
$$I_{ds} = f(V_{ds}) = \frac{\beta}{2} \left(2(V_{gs} - V_t) - V_{ds} \right) V_{ds}$$



$$V_{ds} \leq V_{gs} - V_t$$


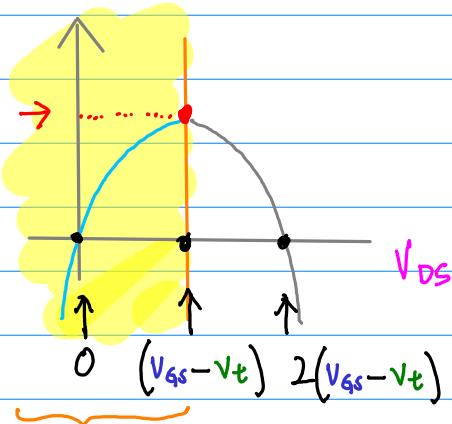
$$f(V_{DS}) = \frac{\theta}{2} \left(2(V_{GS} - V_t) - V_{DS} \right) V_{DS}$$



$$V_{DS} \leq V_{GS} - V_t$$

$$\begin{aligned} f(V_{GS} - V_t) &= \frac{\theta}{2} \left(2(V_{GS} - V_t) - (V_{GS} - V_t) \right) (V_{GS} - V_t) \\ &= \frac{\theta}{2} (V_{GS} - V_t)^2 \end{aligned}$$
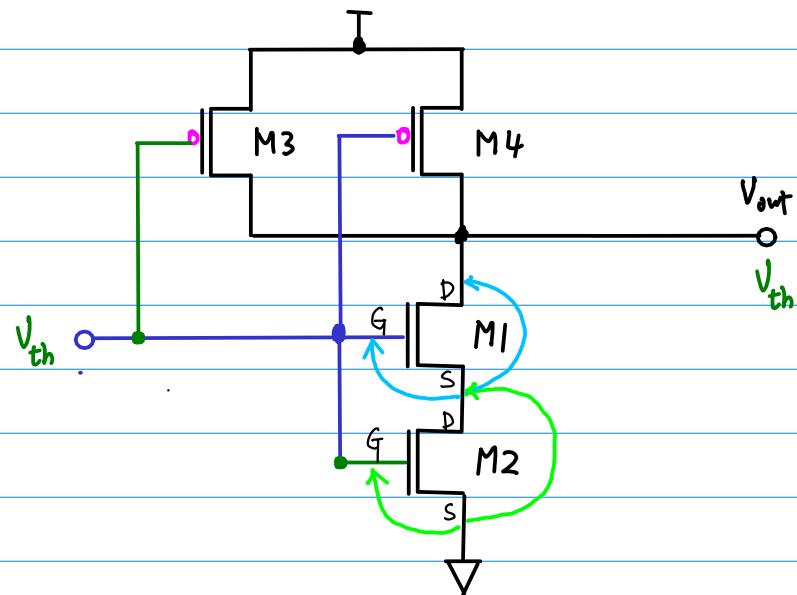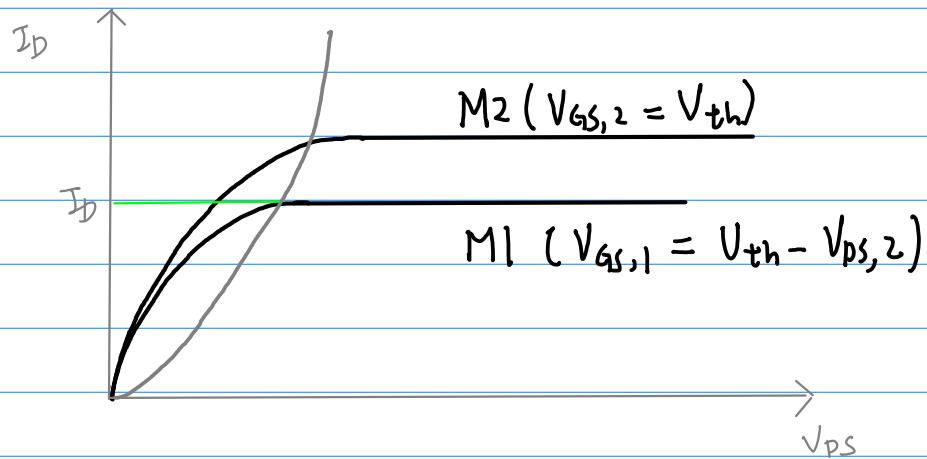
$$I_{DS} = \frac{\theta}{2} (V_{GS} - V_t)^2 \quad : \text{Saturated current}$$



$$M_1 \text{ SAT} \quad I_D = \frac{B_0}{2} (V_{th} - V_{Ton} - V_{DS,2})^2$$

$V_{GS,2} > V_{GS,1}$ Linear

$$I_D = \frac{B_0}{2} (2(V_{th} - V_{Ton})V_{DS,2} - V_{DS,2}^2)$$

Simultaneous switching

$$V_{GS,1} = V_{th} - V_{DS,2} \quad V_{GS,2} = V_{th}$$

$$V_{th} = V_{DS,1} - V_{DS,2}$$

$$V_{GS,1} = V_{DS,1}$$

$$I_D = \frac{\beta_n}{2} (V_{th} - V_{Ton} - V_{DS,2})^2$$

$$I_D = \frac{\beta_n}{2} (2(V_{th} - V_{Ton})V_{DS,2} - V_{DS,2}^2)$$

$$V_{DS,2} = (V_{th} - V_{Ton}) - \sqrt{\frac{2I_D}{\beta_n}}$$

$$V_{th} - V_{Ton} = (V_{DD} - V_{th})$$

$$V_{SG,3} = V_{SG,4} = (V_{DD} - V_{th})$$

$$V_{SD,3} = V_{SD,4} = (V_{DD} - V_{th})$$

$$I_D = I_{D,3} + I_{D,4} = \beta_p (V_{DD} - V_{th} - |V_{Top}|^2)$$

$$V_{th} = \frac{V_{Ton} + 2\sqrt{\frac{\beta_p}{\beta_n}} (V_{DD} - |V_{Top}|)}{1 + 2\sqrt{\frac{\beta_p}{\beta_n}}}$$

$$V_{th} = \frac{2V_{DD} - V_{Top}}{1 + 2\sqrt{\frac{\beta_p}{\beta_n}}}$$

Single Input Switching

$$V_{GS,1} = V_{th} - V_{DS,2} \quad V_{GS,2} = V_{DD}$$

$$\begin{aligned} I_D &= \frac{\beta_n}{2} (V_{th} - V_{T_{on}} - V_{DS,2})^2 \\ &= \frac{\beta_n}{2} [2(V_{DD} - V_{T_{on}}) V_{DS,2} - V_{DS,2}^2] \end{aligned}$$

$$V_{DS,2} = (V_{th} - V_{T_{on}}) - \sqrt{\frac{2I_D}{\beta_n}}$$

$$\frac{4I_D}{\beta_n} = 2(V_{DD} - V_{T_{on}})(V_{th} - V_{T_{on}}) + 2\sqrt{\frac{2I_D}{\beta_n}}(V_{th} - V_{DD}) - (V_{th} - V_{T_{on}})^2$$

$$\sqrt{\frac{2I_D}{\beta_n}} = \sqrt{\frac{\beta_p}{\beta_n}} (V_{DD} - |V_{T_{on}}| - V_{th})$$

$$\begin{aligned} &\left[1 + 2 \left(\sqrt{\frac{\beta_p}{\beta_n}} + \frac{\beta_p}{\beta_n} \right) \right] V_{th}^2 \\ &- \left\{ \left[4 \left(\frac{\beta_p}{\beta_n} \right) + 2 + 2 \sqrt{\frac{\beta_p}{\beta_n}} \right] (V_{DD} - V_{T_0}) + 2V_{T_0} + 2V_{DD}\sqrt{\frac{\beta_p}{\beta_n}} \right\} V_{th} \\ &+ 2 \left[2 \left(\frac{\beta_p}{\beta_n} \right) (V_{DD} - V_{T_0})^2 + 2 \left(V_{T_0} + \sqrt{\frac{\beta_p}{\beta_n}} \right) (V_{DD} - V_{T_0}) + V_{T_0}^2 \right] = 0 \end{aligned}$$

$$V_{th} = (V_{DD} - 0.6V_{T_0}) - \frac{1}{5} \sqrt{5V_{DD}^2 - 10V_{DD}V_{T_0} + 4V_{T_0}^2}$$