

Logic Circuit Design

NOR-1

20170829

Copyright (c) 2015 - 2016 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".



References



Some Figures from the following sites










[1] <http://pages.hmc.edu/harris/cmosvlsi/4e/index.html>
Weste & Harris Book Site

[2] Introduction to VLSI Circuits and Systems, Uyemura

[2] en.wikipedia.org

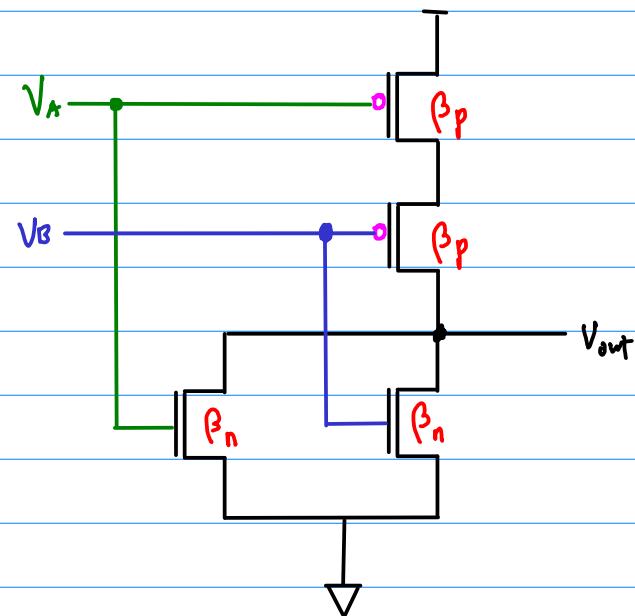
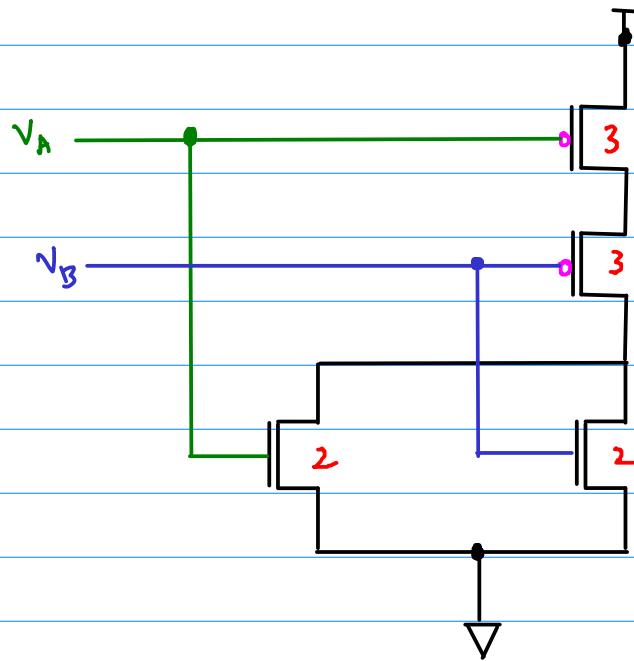


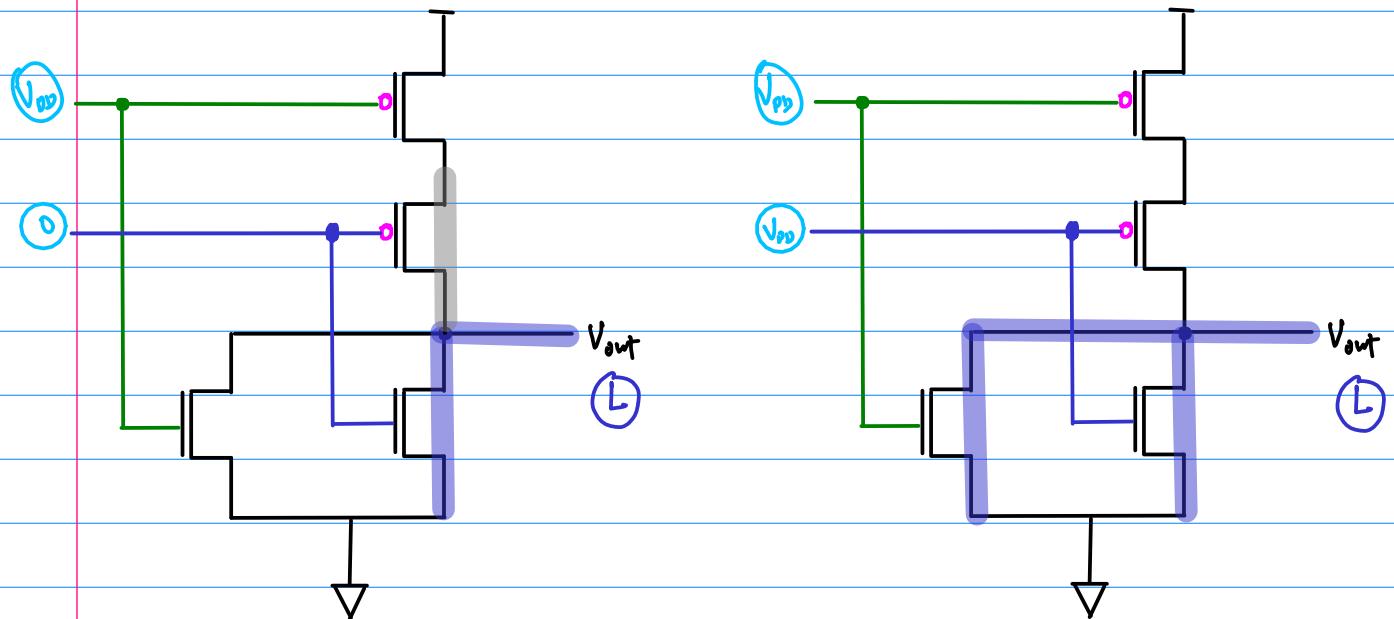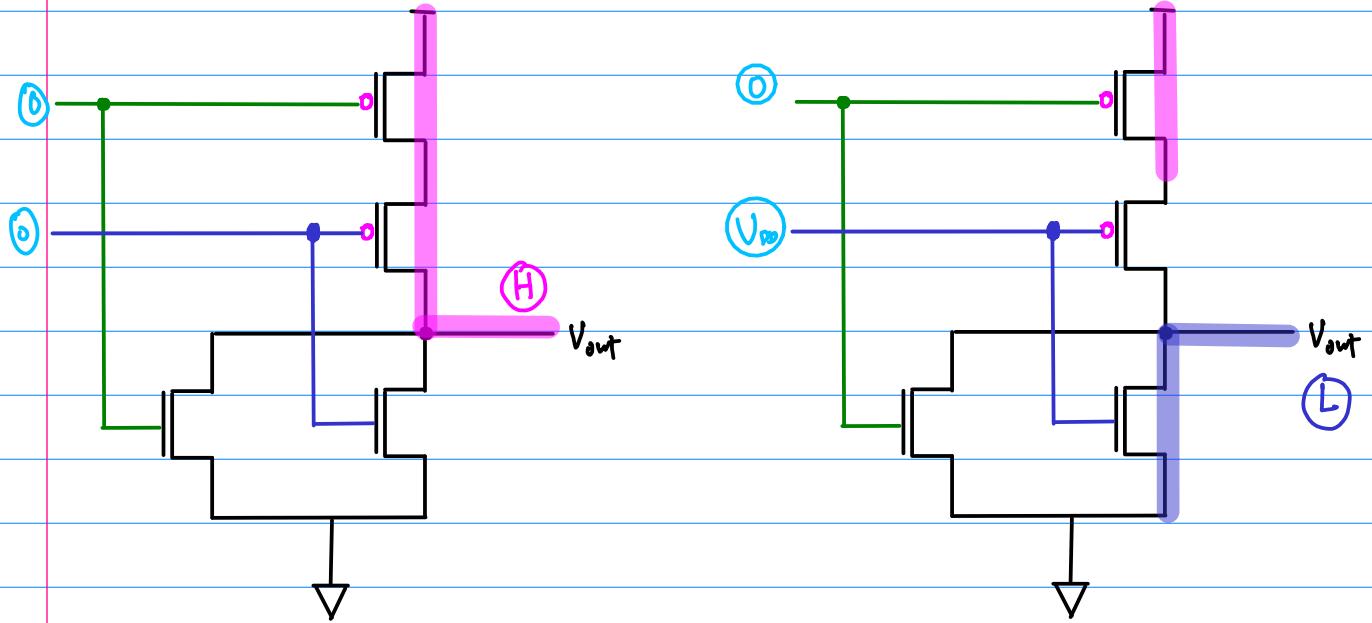

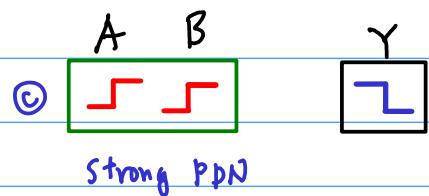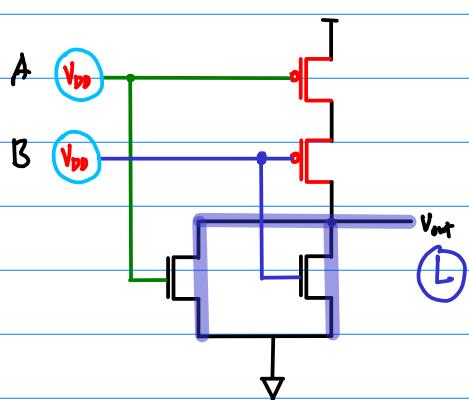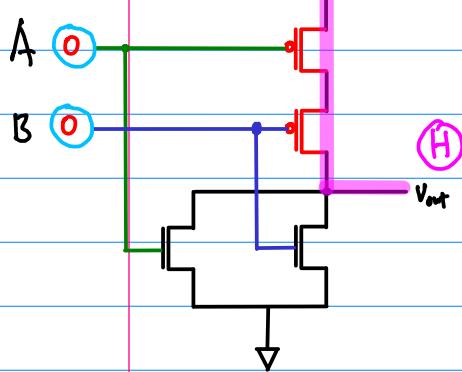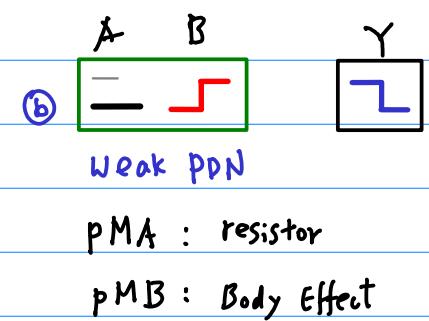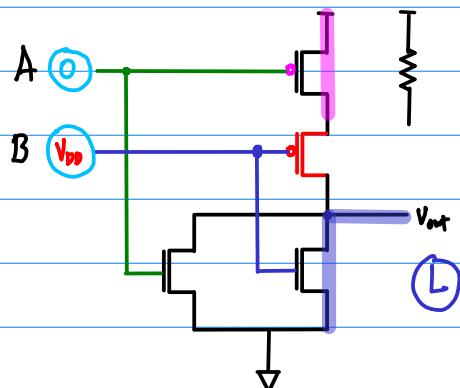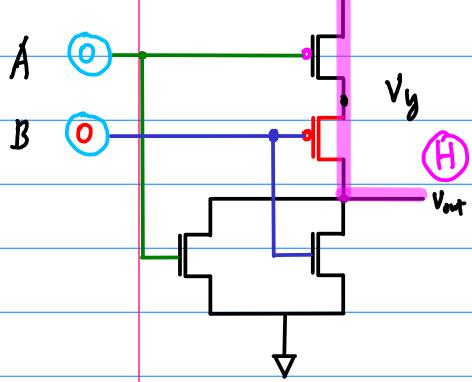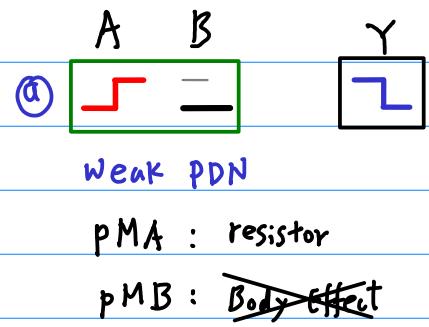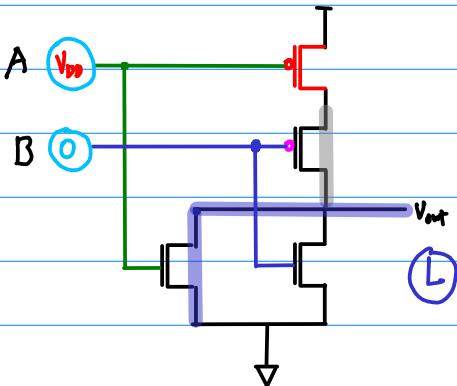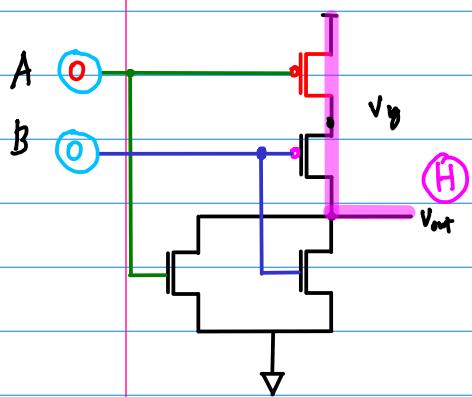

{ small R
 { large C (load)
 { small voltage drop
 { slow change





small effect on VTC

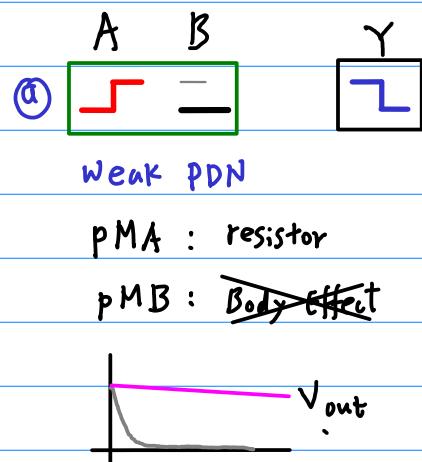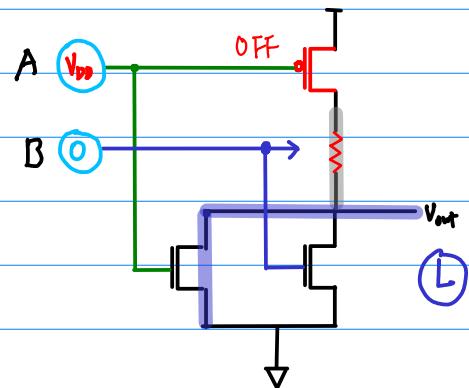




{ small R
 { small C (load)
 { large voltage drop
 { immediate change

increase V_T

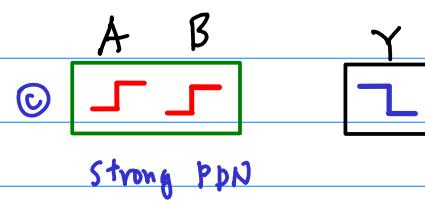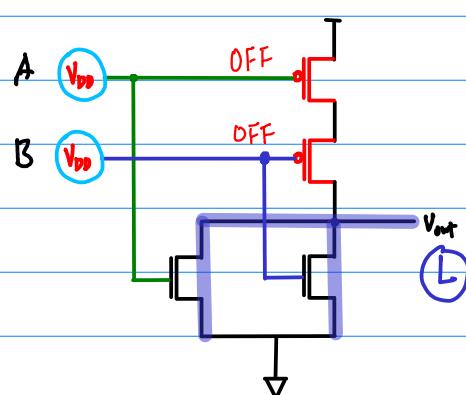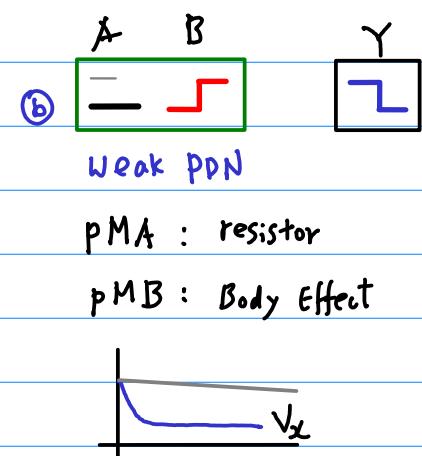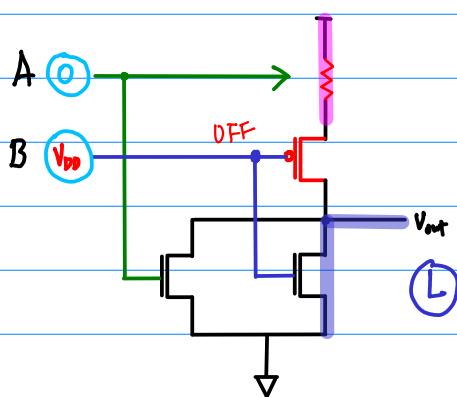- hard to turn on nMB
- VTC shifted to the right



V_A	V_B	V_{out}
0	0	V_{DD}
(b)	0	V_{DD}
(a)	V_{DD}	0
(c)	V_{DD}	0

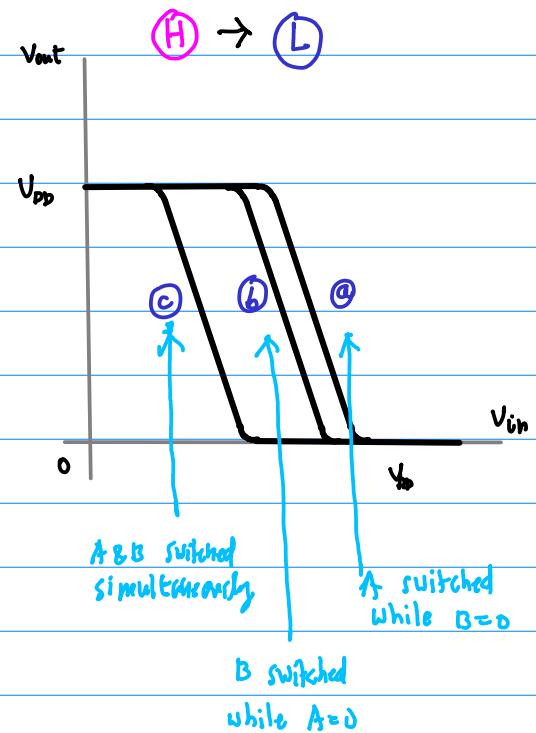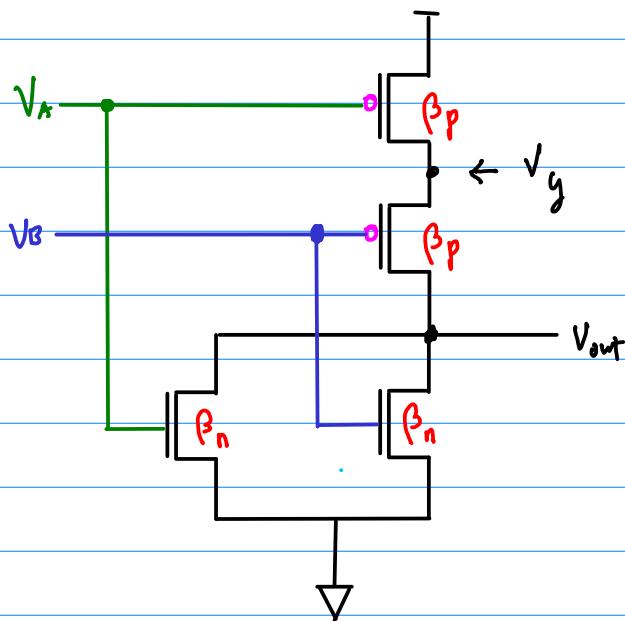
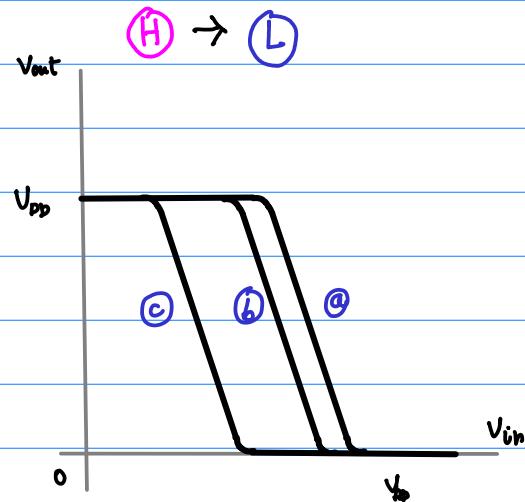



Body Effect


B is more difficult to be turned on
than A


V_A	V_B	V_{out}
0	0	V_{DD}
(b)	0	V_{DD}
(a)	V_{DD}	0
(c)	V_{DD}	V_{DD}


V_A	V_B	V_{out}
(a)	—	—
(b)	—	—
(c)	—	—

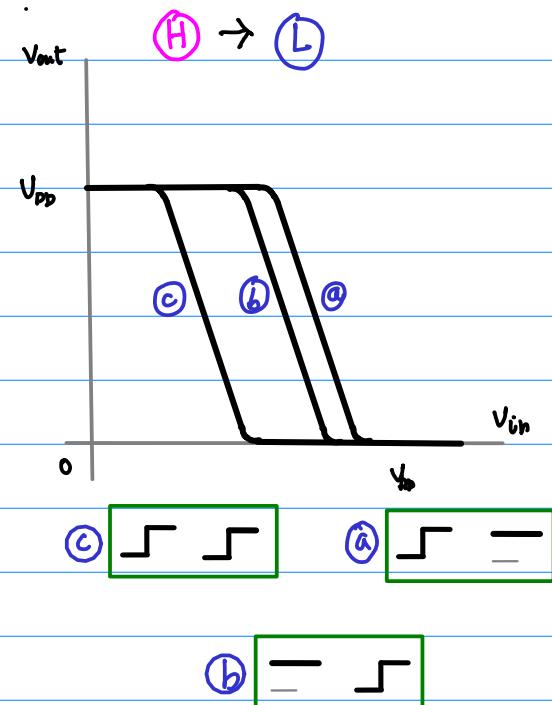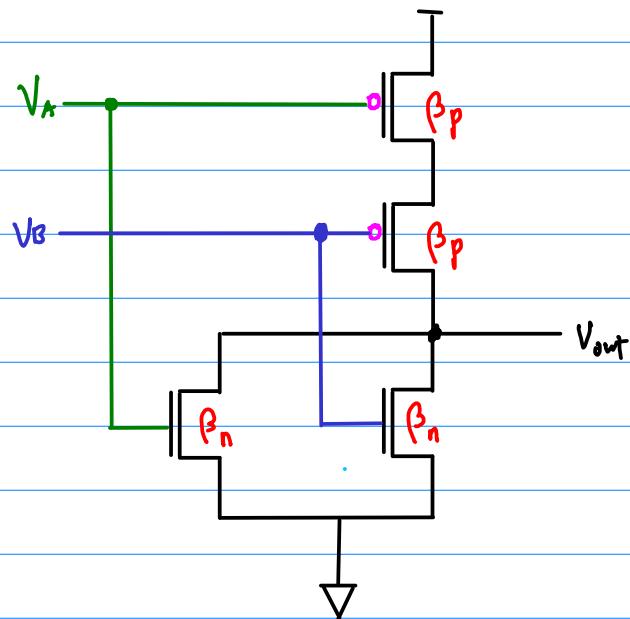


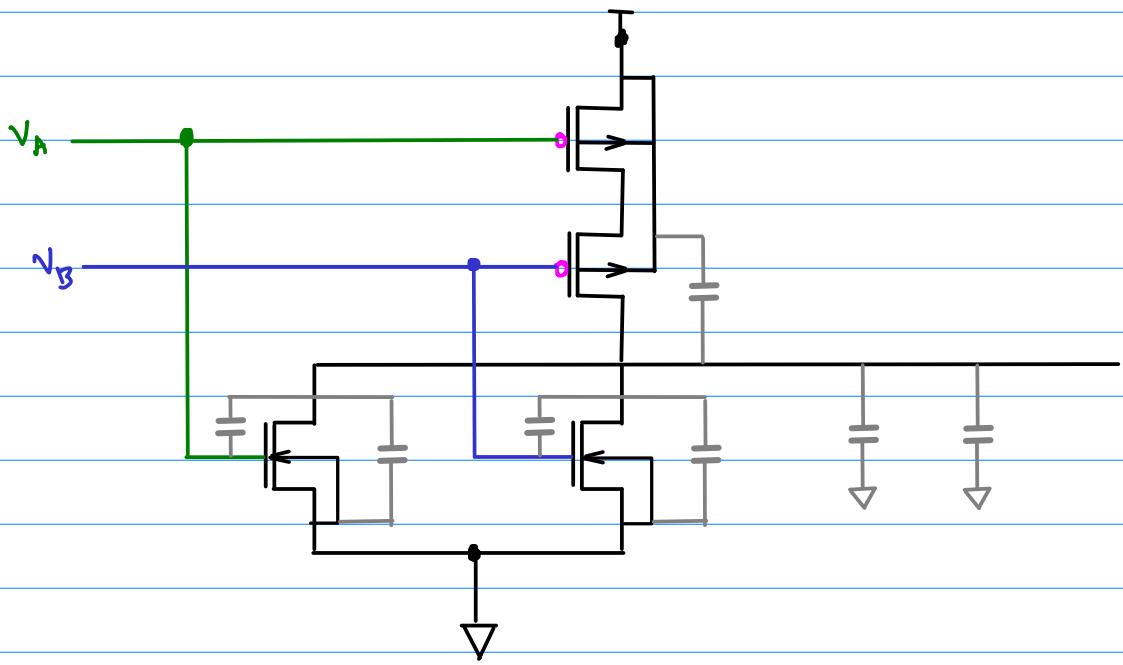

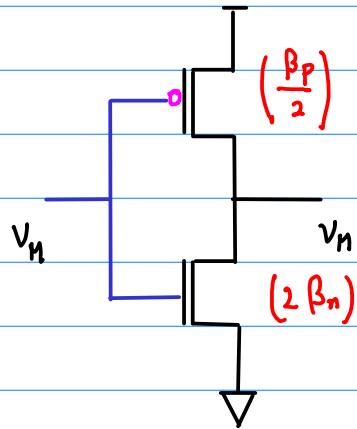

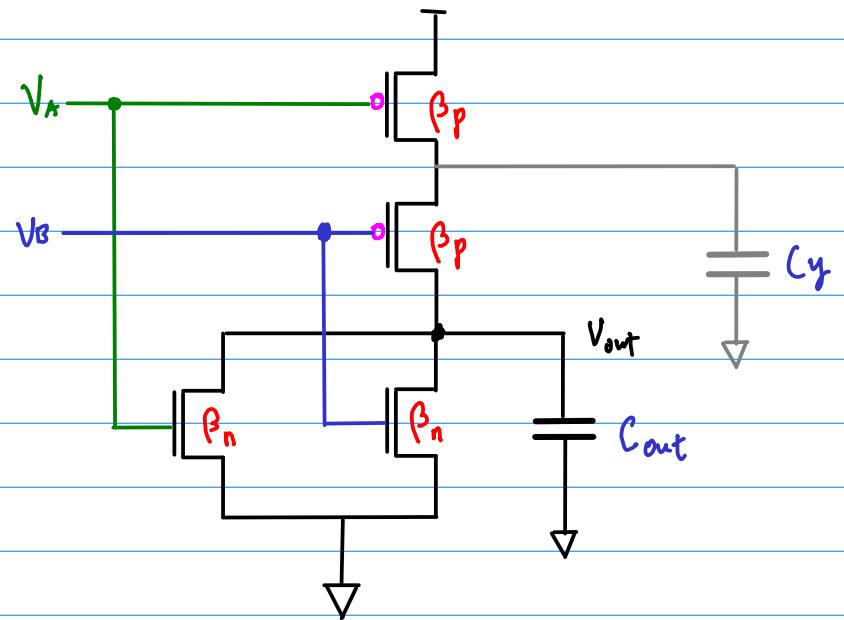

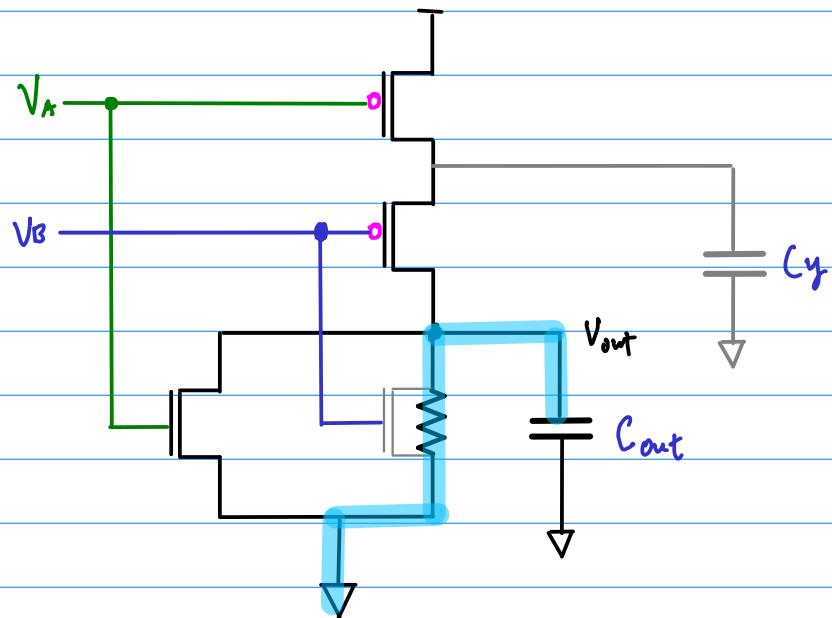

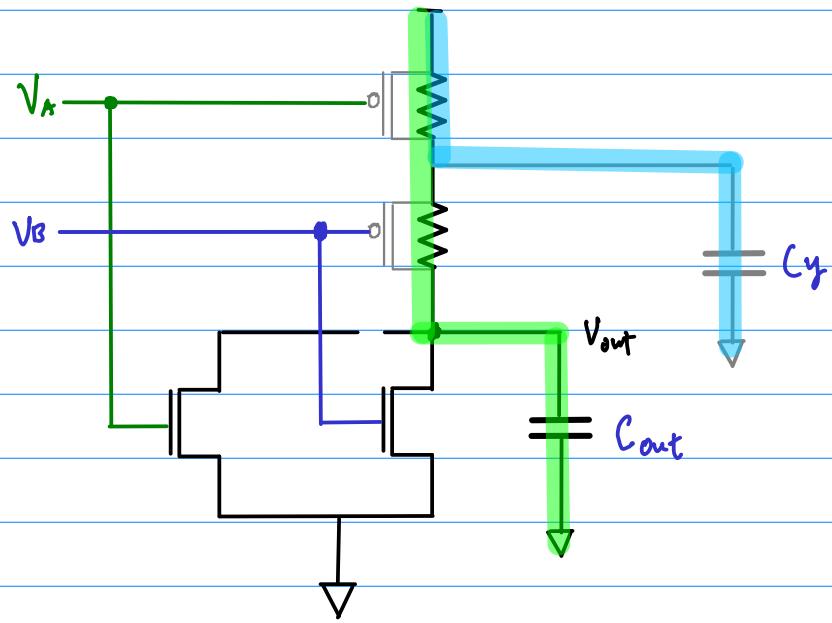

$$C_{out} = C_{FET} + C_L$$

$$C_{FET} = 2C_{Dn} + C_{Dp}$$

$$R_p = \frac{1}{\beta_p (V_{DD} - |V_{TP}|)} \quad R_n = \frac{1}{\beta_n (V_{DD} - V_{TN})}$$

Simultaneous Switching

$$V_{GS,1} = V_{GS,2} = V_{th} = V_{DS,1} = V_{DS,2}$$

$$\begin{aligned} I_D &= I_{D,1} + I_{D,2} \\ &= \beta_n (V_{th} - V_{Ton})^2 \end{aligned}$$

$$V_{th} - V_{Ton} = \sqrt{\frac{I_D}{\beta_n}}$$

$$V_{SG,3} = V_{DD} - V_{th}$$

$$V_{SG,4} = V_{DD} - V_{th} - V_{SD,3}$$

$$V_{DD} - V_{th} = V_{SD,3} + V_{SP,4}$$

$$I_D = \frac{\beta_p}{2} (2(V_{DD} - V_{th} - |V_{Ton}|) V_{SD,3} - V_{SD,3}^2)$$

$$= \frac{\beta_p}{2} (V_{DD} - V_{th} - |V_{Ton}| - V_{SD,3})^2$$

$$\sqrt{\frac{2I_D}{\beta_p}} = V_{DD} - V_{th} - |V_{Ton}|$$

$$V_{th} = \frac{V_{Ton} + \frac{1}{2}\sqrt{\frac{\beta_p}{\beta_n}} (V_{DD} - |V_{Ton}|)}{1 + \frac{1}{2}\sqrt{\frac{\beta_p}{\beta_n}}}$$

$$V_{th} = \frac{V_{DD} + V_{Ton}}{3}$$

Single Switching

$$I_D = I_{D,S} = \frac{\beta_n}{2} (V_{Th} - V_{TO,n})^2$$

$$V_{SD,3} = V_{DD}$$

$$V_{SD,4} = V_{DD} - V_{th} - V_{SD,3}$$

$$V_{DD} - V_{th} = V_{SD,3} + V_{SD,4}$$

$$I_D = \frac{\beta_p}{2} [2(V_{DD} - |V_{TO,p}|) V_{SD,3} - V_{SD,3}^2]$$

$$= \frac{\beta_p}{2} (V_{DD} - V_{th} - |V_{TO,p}| - V_{SD,3})^2$$

$$V_{SD,3} = (V_{DD} - |V_{TO,p}| - V_{th}) - \sqrt{\frac{2I_D}{\beta_p}}$$

$$2\left(\frac{2I_D}{\beta_p}\right) = (V_{DD} - |V_{TO,p}|)^2 - V_{th}^2 - 2\sqrt{\frac{2I_D}{\beta_p}} V_{th}$$

$$\begin{aligned} & \left[1 + 2\left(\frac{\beta_n}{\beta_p} + \sqrt{\frac{\beta_n}{\beta_p}}\right) \right] V_{th}^2 - 2V_{TO,n} \left[2\left(\frac{\beta_n}{\beta_p}\right) + \sqrt{\frac{\beta_n}{\beta_p}} \right] V_{th} \\ & - \left[(V_{DD} - |V_{TO,p}|)^2 - 2\left(\frac{\beta_n}{\beta_p}\right) V_{TO,n}^2 \right] = 0 \end{aligned}$$

$$V_{th} = 0.6 V_{TO} + 0.2 \sqrt{5V_{DD}^2 - 10V_{DD}V_{TO} + 4V_{TO}^2}$$