

Gate Level Design Example (2A)


Copyright (c) 2013 - 2016 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.

FSM Inputs and Outputs

 


Traffic Lights - Outputs

L_A L_B

Sensor - Inputs

T_A T_B

States

 

Moore FSM State Transition Table

S_1	S_0	T_A	T_B	S'_1	S'_0
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

S_1	S_0	T_A	T_B	S'_1
0	0	0	X	0
0	0	1	X	0
0	1	X	X	1
1	0	X	0	1
1	0	X	1	1
1	1	X	X	0

$$\bar{S}_1 S_0 \Rightarrow$$

$$S_1 \bar{S}_0 \bar{T}_B \Rightarrow$$

$$S_1 \bar{S}_0 T_B \Rightarrow$$

$$S'_1 = \bar{S}_1 S_0 + S_1 \bar{S}_0$$

$$= S_1 \oplus S_0$$

S_1	S_0	T_A	T_B	S'_0
0	0	0	X	1
0	0	1	X	0
0	1	X	X	0
1	0	X	0	1
1	0	X	1	0
1	1	X	X	0


$$\bar{S}_1 \bar{S}_0 \bar{T}_A \Rightarrow$$

$$S_1 \bar{S}_0 \bar{T}_B \Rightarrow$$

$$S'_0 = \bar{S}_1 \bar{S}_0 \bar{T}_A + S_1 \bar{S}_0 \bar{T}_B$$

States

S_1	S_0	L_{A1}	L_{A0}	L_{B1}	L_{B0}
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

 

- 00
- 01
- 10

S_1	S_0	L_{A1}
0	0	0
0	1	0
1	0	1
1	1	1

$$L_{A1} = S_1$$

S_1	S_0	L_{A0}
0	0	0
0	1	1
1	0	0
1	1	0

$$L_{A0} = \overline{S_1} S_0$$




S_1	S_0	L_{B1}
0	0	1
0	1	1
1	0	0
1	1	0

$$L_{B1} = \overline{S_1}$$

S_1	S_0	L_{B0}
0	0	0
0	1	0
1	0	0
1	1	1

$$L_{B0} = S_1 S_0$$


Moore FSM (1)

   

outputs (LA/LB)

00:	Green
01:	Yellow
10:	Red
11:	X

Moore FSM

 

Inputs

T_A T_B

Current State

S_1 S_0



Next States

$$S'_1 = S_1 \oplus S_0$$

$$S'_0 = \overline{S_1} \overline{S_0} \overline{T_A} + S_1 \overline{S_0} \overline{T_B}$$

Current State

S_1 S_0



Outputs

$$L_{A1} = S_1 \quad L_{B1} = \overline{S_1}$$

$$L_{A0} = \overline{S_1} S_0 \quad L_{B0} = S_1 S_0$$

Verilog Gate Level Design - testbench

```
`timescale 1ns/100ps

module traffic_controller_testbench;

    parameter cycle = 40;

    reg clock;

    always
    begin
        #(cycle/2) clock=~clock;
    end

    traffic_controller DUT (.clock(clock),
                           .reset(reset),
                           .TA(TA),
                           .TB(TB),
                           .LA(LA),
                           .LB(LB) );

    reg    reset;
    reg    TA, TB;
    wire [1:0] LA, LB;

    initial
    begin
        clock = 1;
        reset = 1;
        TA = 1;
        TB = 0;

        #1;
        #(cycle)  reset = 0;
        #(cycle)  TB = 1;
        #(cycle)  TA = 0;
        #(cycle*3) TA = 1;
                           TB = 0;
        #(cycle*3) TA = 0;
    end

    initial
    begin
        $dumpfile("traffic.vcd");
        $dumpvars(0, DUT);
        #(cycle * 10);
        $finish;
    end

endmodule
```

Verilog Gate Level Design - traffic_gate.v

```
module traffic_controller(clock, reset, TA, TB, LA, LB);
  input clock, reset;
  input TA, TB;
  output [1:0] LA, LB;

  reg [1:0] S;
  wire [1:0] NextS;

  always @(posedge clock)
    begin: SEQ
      if (reset)
        #8 S = 2'b00;
      else
        #8 S = NextS;
    end

  not #8 (S1b, S[1]);
  not #8 (S0b, S[0]);
  not #8 (TAb, TA);
  not #8 (TBb, TB);

  xor #8 (NextS[1], S[1], S[0]);
  or #8 (NextS[0], NS1, NS2);
  and #8 (NS1, S1b, S0b, TAb);
  and #8 (NS2, S[1], S0b, TBb);

  buf #8 (LA[1], S[1]);
  and #8 (LA[0], S1b, S[0]);
  not #8 (LB[1], S[1]);
  and #8 (LB[0], S[1], S[0]);


endmodule
```

traffic_controller - gate level design (1)

```
module traffic_controller  
  (clock, reset, TA, TB, LA, LB);
```

```
  input clock, reset;  
  input TA, TB;  
  output [1:0] LA, LB;
```
 
```
  wire S1, S0, NS1, NS0;  
  wire S1b, S0b;  
  wire TAb, TBb;  
  wire n1, n2;
```



```
endmodule
```

```
not U1 (S1b, S1);  
not U2 (S0b, S0);
```

```
not U3 (TAb, TA);  
not U4 (TBb, TB);
```

```
xor U5 (NS1, S1, S0);
```

```
and U6 (n1, S1b, S0b, TAb);  
and U7 (n2, S1, S0b, TBb);  
or U8 (NS0, n1, n2);
```

```
dff U9 (S0, NS0, clock, reset);  
dff U10 (S1, NS1, clock, reset);
```

```
buf U11 (LA[1], S1);  
and U12 (LA[0], S1b, S0);  
buf U13 (LB[1], S1b);  
and U14 (LB[0], S1, S0);
```

traffic_controller - gate level design (2)

```
primitive dff (q, d, clk, rst);
input d, clk, rst;
output q;
reg q;

initial q = 0;

table
// d clk rst : q: q+;
// Handle Rising Edge
0 (01) 0 : ? : 0;
1 (01) 0 : ? : 1;
1 (0?) 0 : 1 : 1;
0 (0?) 0 : 0 : 0;
// Ignore Falling Edge
? (?0) 0 : ? : -;
// Ignore data changes on Steady Clock
(??) ? 0 : ? : -;
// RESET Cases
? (??) 1 : ? : 0;
? ? 1 : ? : 0;
? ? (10): ? : -;
endtable

endprimitive
```

```
not U1 (S1b, S1);
not U2 (S0b, S0);

not U3 (TAb, TA);
not U4 (TBb, TB);


xor U5 (NS1, S1, S0);

and U6 (n1, S1b, S0b, TAb);
and U7 (n2, S1, S0b, TBb);
or U8 (NS0, n1, n2);


dff U9 (S0, NS0, clock, reset);
dff U10 (S1, NS1, clock, reset);

buf U11 (LA[1], S1);
and U12 (LA[0], S1b, S0);
buf U13 (LB[1], S1b);
and U14 (LB[0], S1, S0);
```


VCD Output with zero delay

 


VCD Output with gate delays

 

VCD Output with gate delays

 

Output Delay

 

References

- [1] <http://en.wikipedia.org/>
- [2] <http://www.allaboutcircuits.com/>
- [3] W. Wolf, "Modern VLSI Design : Systems on Silicon"
- [4] N. Weste, D. Harris, "CMOS VLSI Design: A Circuits and Systems Perspective"
- [5] J. P. Uyemura, "Introduction to VLSI Circuits and Systems"
- [6] https://en.wikiversity.org/wiki/The_necessities_in_SOC_Design
- [7] https://en.wikiversity.org/wiki/The_necessities_in_Digital_Design
- [8] https://en.wikiversity.org/wiki/The_necessities_in_Computer_Design
- [9] https://en.wikiversity.org/wiki/The_necessities_in_Computer_Architecture
- [10] https://en.wikiversity.org/wiki/The_necessities_in_Computer_Organization