

Logic Families Static-2 (H.2)

20151215

Copyright (c) 2015 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

References

Some Figures from the following sites

- [1] <http://pages.hmc.edu/harris/cmosvlsi/4e/index.html>
Weste & Harris Book Site
- [2] en.wikipedia.org
- [3] Digital Integrated Circuits : A Design Perspective,
Jan M. Rabaey,
(<http://bwrcs.eecs.berkeley.edu/Classes/IcBook/>)
- [4] Digital Electronics and Design with VHDL
Pedroni

Other MOS Architectures

Static MOS

Pseudo-nMOS Logic

Transmission-gate Logic

BiCMOS Logic

Dynamic MOS

Dynamic Logic


Domino Logic

C2MOS Logic

Weak / Strong pMOS

the same size
pMOS, nMOS

double size pMOS
minimum size nMOS

 


Weak pMOS


hard to turn off nMOS
hard to become "H"
decreased input V_{th}

V_{iL}

 to turn off nMOS
Vin have to be
closer to GND



a Unit Inverter

 


Strong pMOS

hard to turn off pMOS
hard to become "L"
increased input V_{th}

V_{iH}

 
to turn off nMOS
Vin have to be
closer to Vdd



Skewed Inverters


Low Skewed Inverter

fall delay : faster

 


Unskewed Inverter

Symmetric Inverter
Unit Inverter

 

High Skewed Inverter




rise delay : faster

 

$$\left(\frac{w}{L}\right)_p = 1 \left(\frac{w}{L}\right)_n$$


$$\left(\frac{w}{L}\right)_p = 2 \left(\frac{w}{L}\right)_n$$
   
$$\left(\frac{w}{L}\right)_p = 4 \left(\frac{w}{L}\right)_n$$




High Skewed Inverter

Unskewed Inverter


 


Unskewed Inverter
Unit Inverter

 


High Skewed Inverter

rise delay : faster

  


reduce
pMOS
size

reduce
nMOS
size

 

reduce
nMOS
size

 


Unskewed Inverter

Unskewed Inverter

High Skewed Inverter


Unskewed Inverter

 

$$C_{g0} = 1.5$$

γ_2

Unskewed Inverter Unit Inverter

 

$$C_{g0} = 3$$


γ_2

High Skewed Inverter

(rise delay : faster)


rise delay comparison

equal rise R

 


$$C_{g0} = 2,5$$

γ_2

 

equal fall R

 

fall delay comparison

Logic Effector : the same output current I
==> the same resistance


Unskewed Inverter

Unskewed Inverter

Unit Inverter

High Skewed Inverter


(rise delay : faster)

 

rise logical effort
 $G_u = 2.5/3 = 5/6 < 1$

reduced rise logical effort
—
 better rise delay

$\propto GH$

 

fall logical effort
 $G_d = 2.5 / 1.5 = 5/3 > 1$

increase fall logical effort
—
 worse fall delay


$\propto GH$

Unskewed Inverter Unit Inverter * 1/2

Unskewed Inverter Unit Inverter

High Skewed Inverter

(rise delay : faster)

 

$$\text{Gu} = 2.5/3 = 5/6 < 1$$

reduced rise logical effort
at the expense of increased fall logical effort

$$G_d = 2.5 / 1.5 = 5/3 > 1$$




suitable for rise delay critical application

i.e. when it is more important to reduce the rise delay than the fall delay


Low Skewed Inverter

fall delay : faster


 


Unskewed Inverter

Unit Inverter * 1/2

 
  
$$g_u = \frac{2}{1.5} = \frac{4}{3} > 1$$



$$g_d = \frac{2}{3} < 1$$

Low Skewed Inverter


Unskewed Inverter

Unit Inverter


suitable for fall delay
critical application

Ratioed Logic



resistive load

 

depletion load

 

pseudo-nMOS

  

weak
pMOS

$K_p \uparrow$



$L \rightarrow 0$ NM↑

Conflicting

$K_p \uparrow$


rise delay ↑

Cascade Connections of Ratioed Logic

  


Load Lines of Ratioed Logic




resistive load

 


depletion load

 


pseudo-nMOS

   


ideal model
current source

 

Charging Current Aspect

 


t_{PLH} : large


 


charging
current
drops
rapidly





t_{PLH} : small

 

takes shorter time

  

pseudo-nMOS

    


weak pMOS

$R_s \uparrow$ $L \rightarrow 0$ NM↑ Conflicting

$R_s \uparrow$ rise delay ↑


Low Skewed Inverter

fall delay : faster

 



Unskewed Inverter

Symmetric Inverter
Unit Inverter

 

2


I

  

competing


discharging current

Unskewed Inverter

 

$$g_u = \left(g_d \right) \times 3 = \frac{4}{9} \times 3 = \frac{4}{3} > 1$$

Unskewed Inverter

 

$$g_d = \frac{4}{3} / 3 = \frac{4}{9} < 1$$

