

SystemC - Overview (00A)

SystemC

Copyright (c) 2012 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.

Based on the following original work

- [1] Aleksandar Milenkovic, 2002
CPE 626 The SystemC Language – VHDL, Verilog Designer’s Guide
<http://www.ece.uah.edu/~milenka/ce626-02S/lectures/cpe626-SystemC-L2.ppt>
- [2] Alexander de Graaf, EEMCS/ME/CAS, 2010
SystemC: an overview ET 4351
ens.ewi.tudelft.nl/Education/courses/et4351/SystemC-2010v1.pdf
- [3] Joachim Gerlach, 2001
System-on-Chip Design with System of Computer Engineering
<http://www2.cs.uni-paderborn.de/cs/ag-hardt/Forschung/Data/SystemC-Tutorial.pdf>
- [4] Martino Ruggiero, 2008
SystemC
polimage.polito.it/~lavagno/codes/SystemC_Lezione.pdf
- [5] Deepak Kumar Tal, 1998-2012
SystemC Tutorial
<http://www.asic-world.com/systemc/index.html>

DFF (1) – VHDL & SystemC

```
library ieee;
use ieee.std_logic_1164.all;

entity dff is
    port(clock : in std_logic;
          din : in std_logic;
          dout : out std_logic);
end dff;

architecture rtl of dff is
begin
    process
        begin
            wait until clock'event and clock = '1';
            dout <= din;
        end process;
    end rtl;
```

```
// dff.h
#include "systemc.h"

SC_MODULE(dff)
{
    sc_in<bool> din;
    sc_in<bool> clock;
    sc_out<bool> dout;

    void doit();
};

SC_CTOR(dff)
{
    SC_METHOD(doit);
    sensitive_pos << clock;
};
```

DFF (2) – VHDL & SystemC

```
library ieee;
use ieee.std_logic_1164.all;
entity dffa is
  port( clock : in std_logic;
        reset : in std_logic;
        din : in std_logic;
        dout : out std_logic);
end dffa;

architecture rtl of dffa is
begin
  process(reset, clock)
  begin
    if reset = '1' then
      dout <= '0';
    elsif clock'event and clock = '1' then
      dout <= din;
    end if;
  end process;
end rtl;
```

```
// dffa.h
#include "systemc.h"
SC_MODULE(dffa)
{
  sc_in<bool> clock;
  sc_in<bool> reset;
  sc_in<bool> din;
  sc_out<bool> dout;

  void do_ffa()  {
    if (reset) {
      dout = false;
    } else if (clock.event()) {
      dout = din;
    }
  };

  SC_CTOR(dffa) {
    SC_METHOD(do_ffa);
      sensitive(reset);
      sensitive_pos(clock);
  }
};
```

Shifter - VHDL

```
library ieee;
use ieee.std_logic_1164.all;

entity shift is
  port( din : in std_logic_vector(7 downto 0);
        clk : in std_logic;
        load : in std_logic;
        LR : in std_logic;
        dout : out std_logic_vector(7 downto 0));
end shift;

architecture rtl of shift is
  signal shiftval : std_logic_vector(7 downto 0);
begin
  nxt: process(load, LR, din, dout)
  begin
    end process;
  end rtl;
```

```
if load = '1' then
  shiftval <= din;
elsif LR = '0' then
  shiftval(6 downto 0)
  <= dout(7 downto 1);
  shiftval(7) <= '0';
elsif LR = '1' then
  shiftval(7 downto 1)
  <= dout(6 downto 0);
  shiftval(0) <= '0';
end if;
```



Shifter - SystemC

```
// shift.h
#include "systemc.h"
SC_MODULE(shift)
{
    sc_in<sc_bv<8> > din;
    sc_in<bool> clk;
    sc_in<bool> load;
    sc_in<bool> LR;
    sc_out<sc_bv<8> > dout;
    sc_bv<8> shiftval;

    void shifty();
}

SC_CTOR(shift)
{
    SC_METHOD(shifty);
    sensitive_pos (clk);
}
};
```

```
// shift.cc
#include "shift.h"
void shift::shifty()
{
    if (load) {
        shiftval = din;
    } else if (!LR) {
        shiftval.range(6,0) = shiftval.range(7,1);
        shiftval[7] = '0';
    } else if (LR) {
        shiftval.range(7,1) = shiftval.range(6,0);
        shiftval[0] = '0';
    }
    dout = shiftval;
```

Counter – VHDL

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
entity counter is
    port( clock : in std_logic;
          load : in std_logic;
          clear : in std_logic;
          din : in std_logic_vector(7 downto 0);
          dout : inout std_logic_vector(7 downto 0));
end counter;
```

```
architecture rtl of counter is
    signal countval : std_logic_vector(7 downto 0);
begin
    process
    begin
        wait until clock'event and clock = '1';
        dout <= countval;
    end process;
end rtl;
```



```
process(load, clear, din, dout)
begin
    if clear = '1' then
        countval <= "00000000";
    elsif load = '1' then
        countval <= din;
    else
        countval <= dout + "00000001";
    end if;
end process;
```

Counter – SystemC

```
#include "systemc.h"
SC_MODULE(counter)
{
    sc_in<bool> clock;
    sc_in<bool> load;
    sc_in<bool> clear;
    sc_in<sc_int<8>> din;
    sc_out<sc_int<8>> dout;
    int countval;

    void onetwothree();
}

SC_CTOR(counter)
{
    SC_METHOD(onetwothree);
        sensitive_pos (clock);
}
};
```

```
// counter.cc
#include "counter.h"

void counter::onetwothree()
{
    if (clear) {
        countval = 0;
    } else if (load) {
        countval = din.read(); // use read when a
        // type conversion is happening
        // from an input port
    } else {
        countval++;
    }
    dout = countval;
}
```

State Machine – VHDL (1)

```
package vm_pack is
    type t_vm_state is (main_st, review_st, repeat_st, save_st, erase_st, send_st,
                         address_st, record_st, begin_rec_st, message_st);
    type t_key is ('0', '1', '2', '3', '4', '5', '6', '7', '8', '9', '*', '#');
end vm_pack;

use work.vm_pack.all;
library ieee;
use ieee.std_logic_1164.all;
entity stmach is
    port(    clk : in std_logic;
             key : in t_key;
             play, recrd, erase, save, address : out std_logic);
end stmach;
```

State Machine – VHDL (2)

```
architecture rtl of stmach is
signal next_state, current_state : t_vm_state;
begin

process(current_state, key)
begin
  play <= '0';  save <= '0';
  erase <= '0';  recrd <= '0';
  address <= '0';
  case current_state is
    when main_st =>
    when review_st =>
    when repeat_st =>
    when save_st =>
    when erase_st =>
    when send_st =>
    when address_st =>
    when record_st =>
    when begin_rec_st =>
    when message_st =>
  end case;
end process;
```

```
process
begin
  wait until clk'event and clk = '1';
  current_state <= next_state;
end process;

end rtl;
```

State Machine – VHDL (3)

```
when main_st =>
    if key = '1' then
        next_state <= review_st;
    elsif key = '2' then
        next_state <= send_st;
    else
        next_state <= main_st;
    end if;
when review_st =>
    if key = '1' then
        next_state <= repeat_st;
    elsif key = '2' then
        next_state <= save_st;
    elsif key = '3' then
        next_state <= erase_st;
    elsif key = '#' then
        next_state <= main_st;
    else
        next_state <= review_st;
    end if;
when repeat_st =>
    play <= '1';
    next_state <= review_st;
when save_st =>
    save <= '1';
    next_state <= review_st;
when erase_st =>
    erase <= '1';
    next_state <= review_st;
```

```
when send_st =>
    next_state <= address_st;
when address_st =>
    address <= '1';
    if key = '#' then
        next_state <= record_st;
    else
        next_state <= address_st;
    end if;
when record_st =>
    if key = '5' then
        next_state <= begin_rec_st;
    else
        next_state <= record_st;
    end if;
when begin_rec_st =>
    recrd <= '1';
    next_state <= message_st;
when message_st =>
    recrd <= '1';
    if key = '#' then
        next_state <= send_st;
    else
        next_state <= message_st;
    end if;
```

State Machine – SystemC (1)

```
// stmach.h
#include "systemc.h"
enum vm_state {
    main_st, review_st, repeat_st,
    save_st, erase_st, send_st,
    address_st, record_st,
    begin_rec_st, message_st
};

SC_MODULE(stmach)
{
    sc_in<bool> clk;
    sc_in<char> key;
    sc_out<sc_logic> play;
    sc_out<sc_logic> recrd;
    sc_out<sc_logic> erase;
    sc_out<sc_logic> save;
    sc_out<sc_logic> address;
    sc_signal<vm_state> next_state;
    sc_signal<vm_state> current_state;
```

```
void getnextst();
void setstate();
```

```
SC_CTOR(stmach)
{
    SC_METHOD(getnextst);
        sensitive << key << current_state;
    SC_METHOD(setstate);
        sensitive_pos (clk);
}
```

State Machine – SystemC (2)

```
// stmach.cc
#include "stmach.h"
void stmach::getnextst()
{
    play = sc_logic_0;
    recrd = sc_logic_0;
    erase = sc_logic_0;
    save = sc_logic_0;
    address = sc_logic_0;
    switch (current_state) {
        case main_st:
            if (key == '1') {
                next_state = review_st;
            } else {
                if (key == '2') {
                    next_state = send_st;
                } else {
                    next_state = main_st;
                }
            }
        }
    case review_st:
        if (key == '1') {
            next_state = repeat_st;
        } else {
            if (key == '2') {
                next_state = save_st;
            } else {
                if (key == '3') {
                    next_state = erase_st;
                } else {
                    if (key == '#') {
                        next_state = main_st;
                    } else {
                        next_state = review_st;
                    }
                }
            }
        }
    }
}
```

State Machine – SystemC (3)

```
case repeat_st:  
    play = sc_logic_1;  
    next_state = review_st;  
  
case save_st:  
    save = sc_logic_1;  
    next_state = review_st;  
  
case erase_st:  
    erase = sc_logic_1;  
    next_state = review_st;  
  
case send_st:  
    next_state = address_st;  
  
case address_st:  
    address = sc_logic_1;  
    if (key == '#') {  
        next_state = record_st;  
    } else {  
        next_state = address_st;  
    }  
  
case record_st:  
    if (key == '5') {  
        next_state = begin_rec_st;  
    } else {  
        next_state = record_st;  
    }  
  
case begin_rec_st:  
    recrd = sc_logic_1;  
    next_state = message_st;  
  
case message_st:  
    recrd = sc_logic_1;  
    if (key == '#') {  
        next_state = send_st;  
    } else {  
        next_state = message_st;  
    }  
} // end switch  
} // end method  
  
void stmach::setstate()  
{  
    current_state = next_state;  
}
```

Memory – VHDL (1)

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity ram is
    port (enable : in std_logic;
          readwr : in std_logic;
          addr : in std_logic_vector(7 downto 0);
          data : inout std_logic_vector(15 downto 0)
    );
end ram;
```

DFF (2) – VHDL & SystemC

```
architecture rtl of ram is
begin
  process(addr, enable, readwr)
    subtype data16 is std_logic_vector(15 downto 0);
    type ramtype is array(0 to 255) of data16;
    variable ramdata : ramtype;
begin
  if (enable = '1') then
    if readwr = '0' then
      data <= ramdata(conv_integer(addr));
    elsif readwr = '1' then
      ramdata(conv_integer(addr)) := data;
    end if;
  else
    data <= "ZZZZZZZZZZZZZZZZ";
  end if;
end process;
end rtl;
```

Memory – SystemC (1)

```
// ram.h
#include "systemc.h"
SC_MODULE(ram)
{
    sc_in<sc_int<8> > addr;
    sc_in<bool> enable;
    sc_in<bool> readwr;
    sc_inout_rv<16> data;

    void read_data();
    void write_data();
    sc_lv<16> ram_data[256];

SC_CTOR(ram)
{
    SC_METHOD(read_data);
        sensitive << addr << enable << readwr;
    SC_METHOD(write_data);
        sensitive << addr << enable << readwr << data;
}
};
```

Memory – SystemC (2)

```
// ram.cc
#include "ram.h"
void ram::read_data()
{
    if (enable && ! readwr ) {
        data = ram_data[addr.read()];
    } else {
        data = "ZZZZZZZZZZZZZZZZ";
    }
}

void ram::write_data()
{
    if (enable && readwr) {
        ram_data[addr.read()] = data;
    }
}
```

1-Bit Adder

```
// Adder.h
#include "systemc.h"

SC_MODULE(Adder){
    sc_out<sc_logic> sum, Cout;
    sc_in<sc_logic> A, B, Cin;

    void add(){
        sc_logic tempC, tempD, tempE;
        tempC = A.read() & B.read();
        tempD = A.read() ^ B.read();
        tempE = Cin.read() & tempD.read();
        sum.write(tempD ^ Cin.read());
        cout.write(tempC | tempE);
    }

    SC_CTOR(Adder){
        SC_METHOD(add);
        sensitive << A << B << Cin;
    }
};
```

1-Bit Adder Testbench

```
//Testbench.h
#include "systemc.h"

SC_MODULE(Testbench){
    sc_out<sc_logic> TA, TB, TCin;

    void testprocess()
    {
        TA.write(SC_LOGIC_0);
        TB.write(SC_LOGIC_0);
        TCin.write(SC_LOGIC_0);
        wait(5, SC_NS);
        TA.write(SC_LOGIC_1);
        TB.write(SC_LOGIC_1);
        TCin.write(SC_LOGIC_0);
        wait(10, SC_NS);
        sc_stop(); //Stop simulation
    }

    SC_CTOR(Testbench){
        SC_THREAD(testprocess);
    }
};
```

1-Bit Adder TOP

```
//AdderMain.cpp

#include "Adder.h"
#include "Testbench.h"
int main(int argc, char *argv[]){
    sc_signal<sc_logic> A, B, Cin;
    sc_signal<sc_logic> sum, Cout;

    Adder adder1bit("BitAdder");
    Testbench tb("Testbench");

    adder1bit.A(A);
    adder1bit.B(B);
    adder1bit.Cin(Cin);
    adder1bit.sum(sum);
    adder1bit.Cout(Cout);

    tb.TA(A);
    tb.TB(B);
    tb.TCin(Cin);

    //Start the simulation for 200ns
    sc_start(200, SC_NS);
    return 0;
}
```

2-Bit Adder

```
#include "Adder.h"
SC_MODULE(Adder2Bits) {
    sc_in<sc_logic> A0, B0, A1, B1, Cin;
    sc_out<sc_logic> sum0, sum1, Cout;
    sc_signal<sc_logic> CoutConnection;

    Adder adder1bit0, adder1bit1;

    SC_CTOR(Adder2Bits):
        adder1bit0("Adder0"),
        adder1bit1("Adder1")
    {
        adder1bit0.A(A0);
        adder1bit0.B(B0);
        adder1bit0.Cin(Cin);
        adder1bit0.sum(sum0);
        adder1bit0.Cout(CoutConnection);

        adder1bit1.A(A1);
        adder1bit1.B(B1);
        adder1bit1.Cin(CoutConnection);
        adder1bit1.sum(sum1);

        adder1bit1.Cout(Cout);
    }
};
```

FIFO Memory (1)

```
#include "systemc.h"

SC_MODULE(FIFOMemory) {
    sc_in<bool> RD; // ReadNotWrite
    sc_inout<int> data;
    sc_in_clk clock;
    sc_out<bool> status; // 0:NOERROR, 1:ERROR

    sc_fifo<int> buffer;
    const int size;

    void memory_process() {
        * * *
    }

    SC_HAS_PROCESS(FIFOMemory);

    FIFOMemory(sc_module_name name_, int size_=10):
        module(name_), size(size_), buffer(size_)
    {
        SC_THREAD(memory_process);
        sensitive << clock.pos();
    }
};
```

```
void memory_process() {
    int temp;
    while(true) {
        wait();
        if (RD.read() == true) {
            if(buffer.nb_read(temp)) {
                status.write(0);
                data.write(temp);
            } else {
                status.write(1);
            }
        } else {
            temp = data.read();
            if(buffer.nb_write(temp)) {
                status.write(0);
            } else {
                status.write(1);
            }
        }
    }
}
```

FIFO Memory (2)

```
#include "systemc.h"
SC_MODULE(Testbench){
    sc_in_clk clock; sc_inout<int> data;
    sc_out<bool> RD; sc_in<bool> status;

    void testprocess(){
        * * *
    }

    SC_CTOR(Testbench){
        SC_THREAD(testprocess);
        sensitive << clock.pos();
    }
};

void testprocess(){
    wait();
    data.write(0x010);
    RD.write(0);
    wait();
    cout << "@: " << sc_time_stamp() << ": WR " <<
    data.read() << ": STATUS: " <<
    status.read() << endl;

    data.write(0x020);
    RD.write(0);
    wait();
    cout << "@: " << sc_time_stamp() << ": WR " <<
    data.read() << ": STATUS: " <<
    status.read() << endl;
    // write 0x030, 0x040, 0x050, 0x060not shown

    RD.write(1);
    wait();
    cout << "@: " << sc_time_stamp() << ": RD " <<
    data.read() << ": STATUS: " <<
    status.read() << endl;

    //also read four more times
}
```

FIFO Memory (3)

```
#include "FIFOMemory.h"
#include "Testbench.h"
int sc_main(int argc, char *argv[]){
    sc_signal<int> data;
    sc_signal<bool> RD, status;

    sc_clock sysclock("clock1", 20, SC_NS);
    FIFOMemory memory1("Memory1");
    Testbench test1("Test1");

    memory1.clock(sysclock);

    memory1.data(data);
    memory1.RD(RD);
    memory1.status(status);
    test1.clock(sysclock);
    test1.data(data);
    test1.RD(RD);
    test1.status(status);
}
```


References

- [1] Aleksandar Milenkovic, 2002
CPE 626 The SystemC Language – VHDL, Verilog Designer's Guide
<http://www.ece.uah.edu/~milenka/ce626-02S/lectures/cpe626-SystemC-L2.ppt>
- [2] Alexander de Graaf, EEMCS/ME/CAS, 2010
SystemC: an overview ET 4351
ens.ewi.tudelft.nl/Education/courses/et4351/SystemC-2010v1.pdf
- [3] Joachim Gerlach, 2001
System-on-Chip Design with Systent of Computer Engineering
<http://www2.cs.uni-paderborn.de/cs/ag-hardt/Forschung/Data/SystemC-Tutorial.pdf>
- [4] Martino Ruggiero, 2008
SystemC
polimage.polito.it/~lavagno/codes/SystemC_Lezione.pdf
- [5] Deepak Kumar Tal, 1998-2012
SystemC Tutorial
<http://www.asic-world.com/systemc/index.html>