

# Thevenin & Norton Equivalent Circuits (H.1)


20170517

Copyright (c) 2015 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

# Thevenin & Norton Theorem


## Thevenin's Theorem

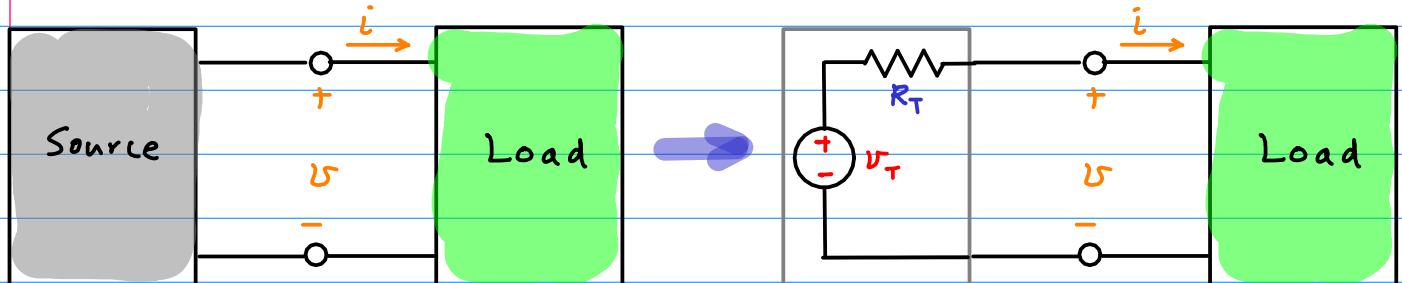

$$v_T = v_{oc} \text{ when } i=0 \quad \boxed{\text{max } v}$$

$$R_T = R_N$$

## Norton's Theorem

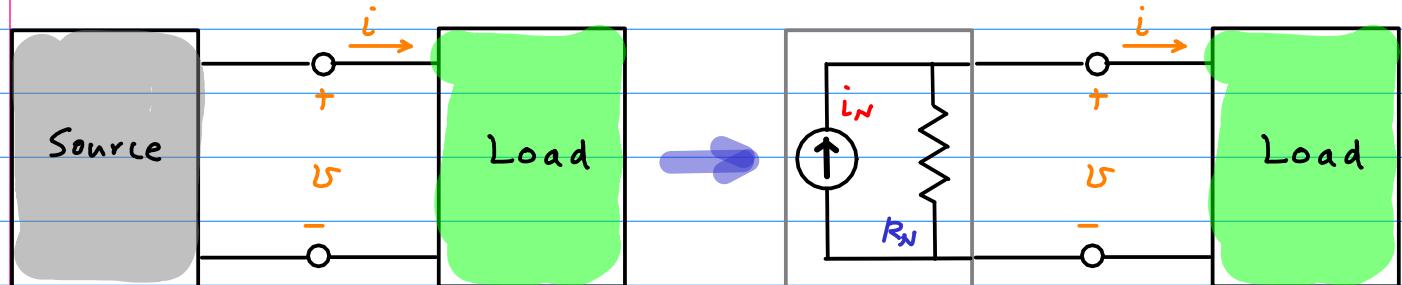


$$i_N = i_{sc} \text{ when } v=0 \quad \boxed{\text{max } i}$$


$$R_N = R_T$$

# Max $V$ and Max $I$ conditions

## Thevenin's Theorem

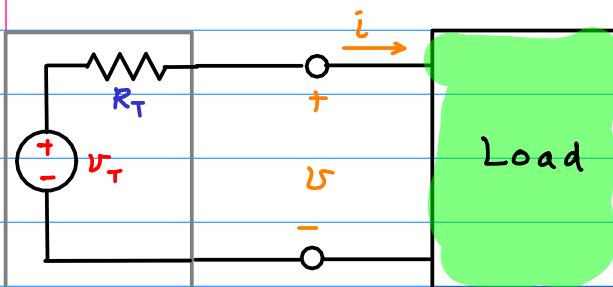

no voltage drop

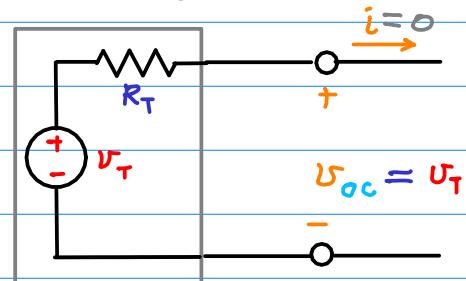



$V_T = V_{oc}$  when  $i = 0$

max  $V$

max  $V$  when O.C. ( $R_L = \infty$ )

$$R_T = R_N$$

## Norton's Theorem

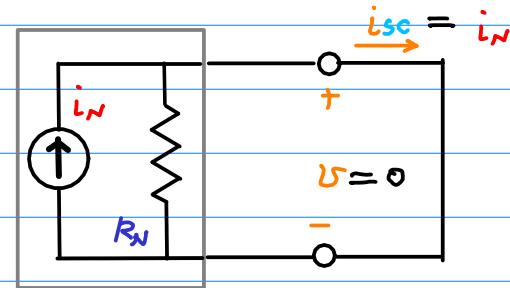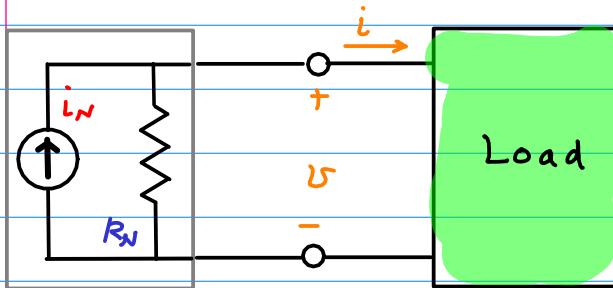


$i_N = i_{sc}$  when  $V = 0$

max  $i$

max  $i$  when S.C. ( $R_L = 0$ )

$$R_N = R_T$$

## Voltage divider

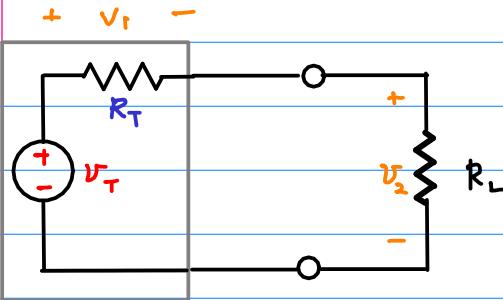


$$V_1 = \frac{R_T}{R_T + R_L} V_T$$

$$V_2 = \frac{R_L}{R_T + R_L} V_T$$

$$\lim_{R_L \rightarrow \infty} V_2 = V_T$$

## current divider

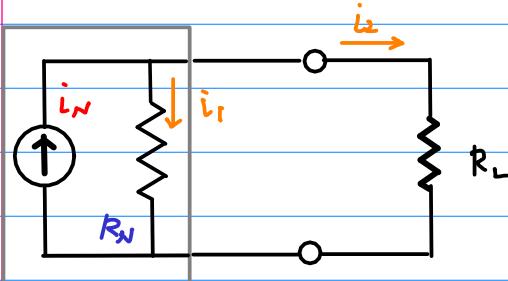


$$i_1 = \frac{R_N}{R_N + R_L} i_N$$

$$i_2 = \frac{R_L}{R_N + R_L} i_N$$


$$\lim_{R_L \rightarrow 0} i_2 = i_N$$

# Superposition

$$I = i_1 + i_2$$

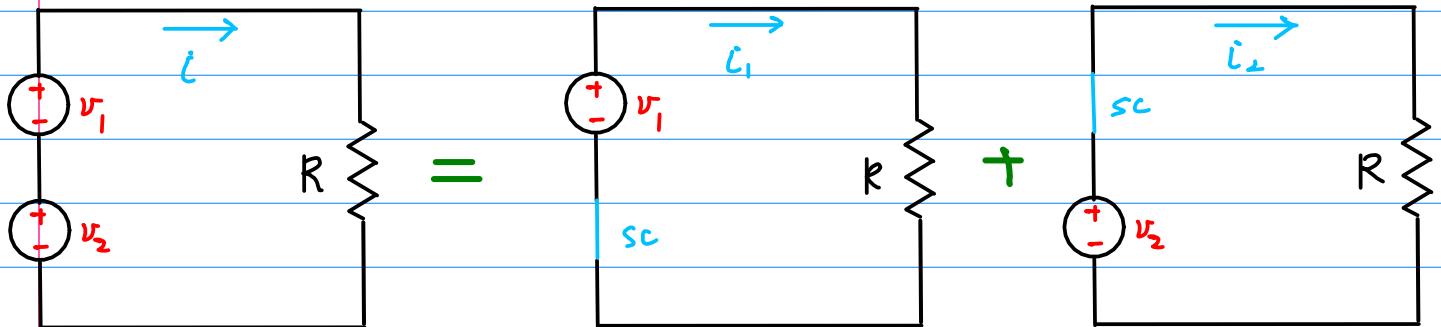


$$V = V_1 + V_2$$

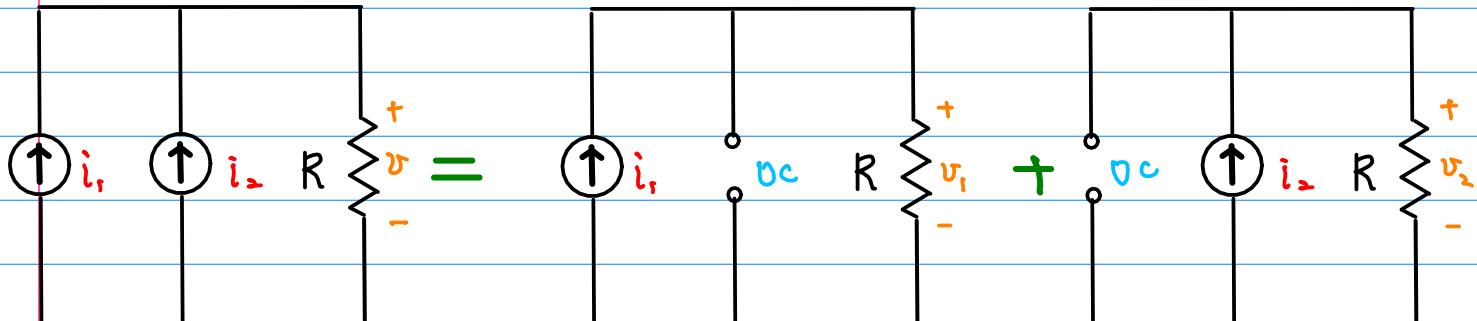


	$\rightarrow$	SC (short circuit)
	$\rightarrow$	OC (open circuit)

# Equivalent Resistance $R_T = R_N$


① remove  $R_L$


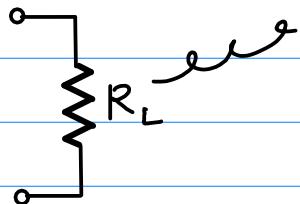


②

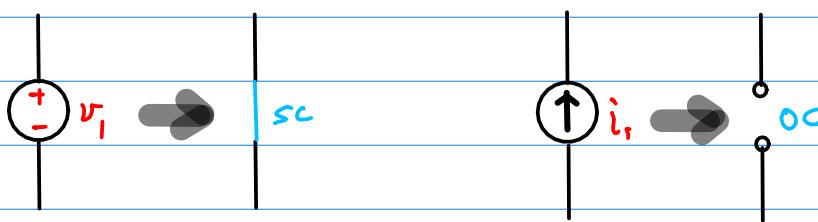


③ resistance seen from the  $R_L$  side

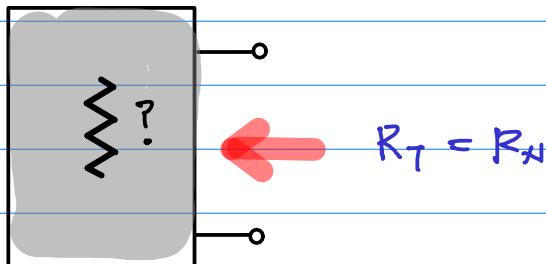


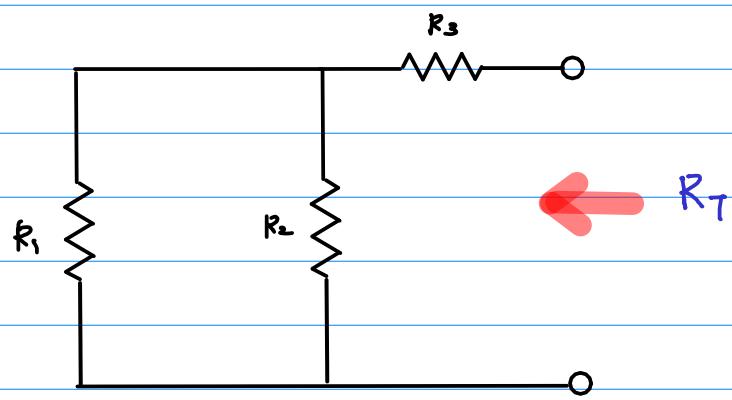
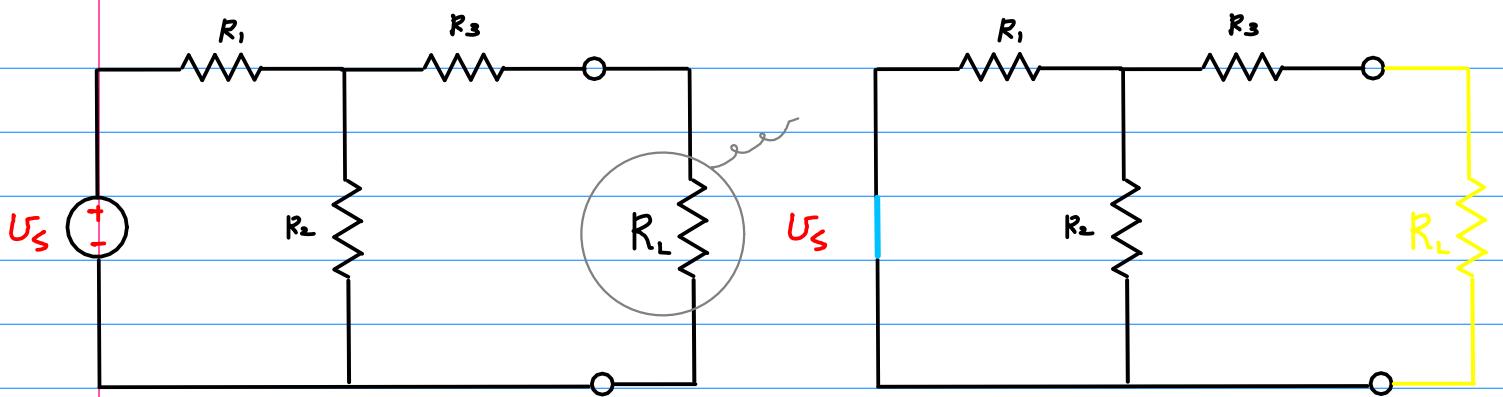


$$R_T = R_1 \parallel R_2 + R_3$$

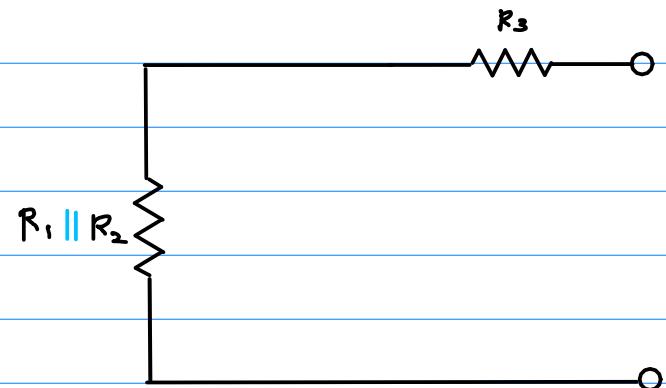




# Thevenin Voltage $U_T$


max  $U$

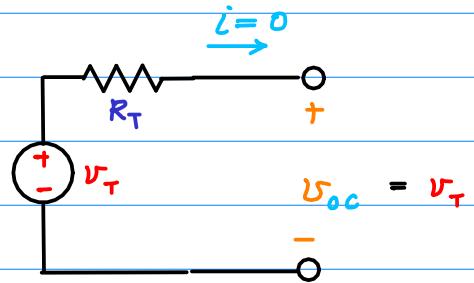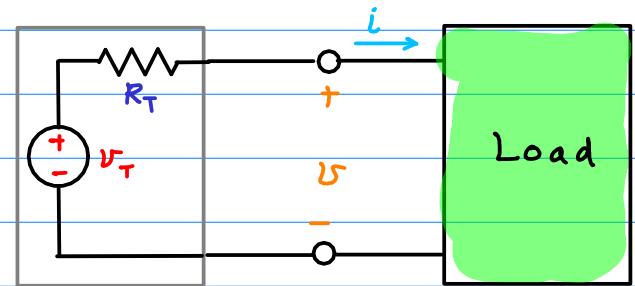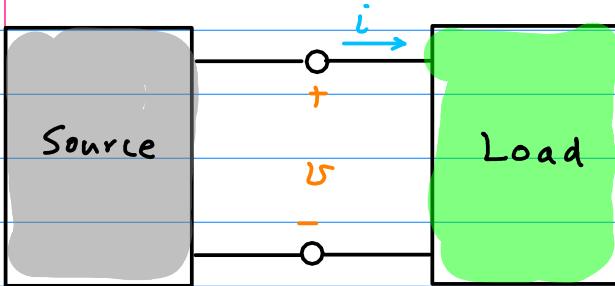

① Remove  $R_L \rightarrow OC$


②  $U_{oc}$

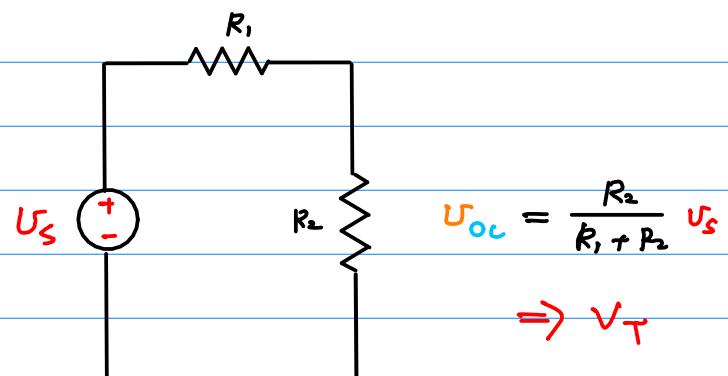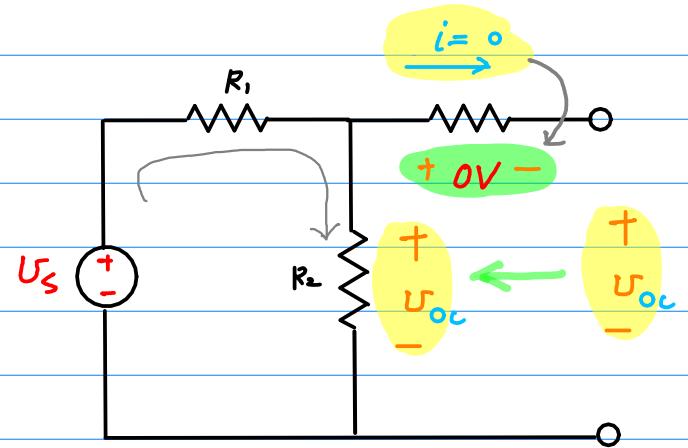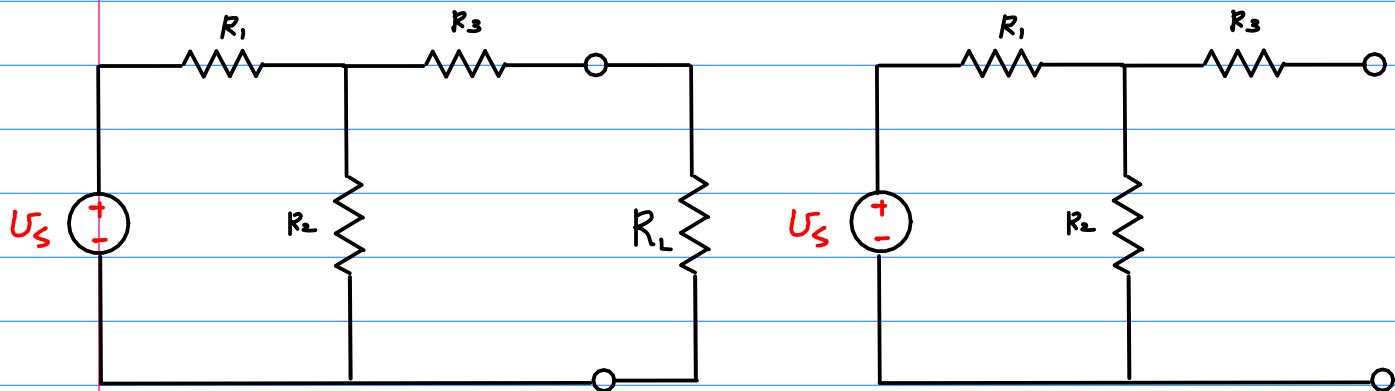

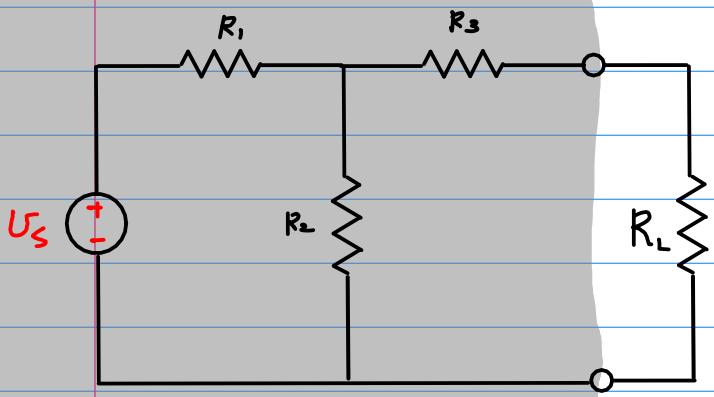




$$R_T = R_1 \parallel R_2 + R_3$$




$$U_T = \frac{R_2}{R_1 + R_2} U_S$$

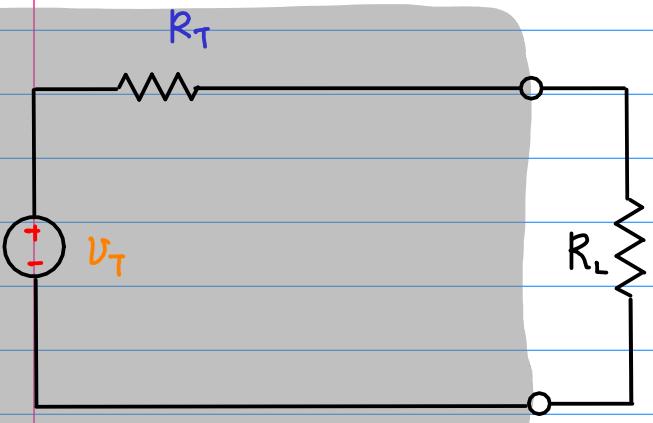

# Norton Current $i_T$

max  $i$

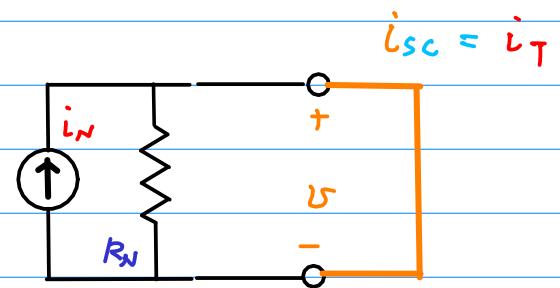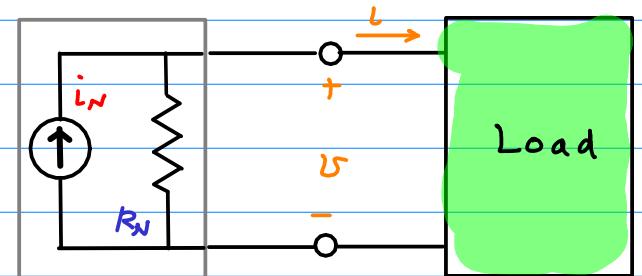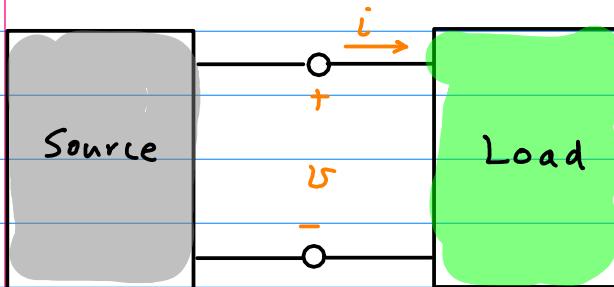

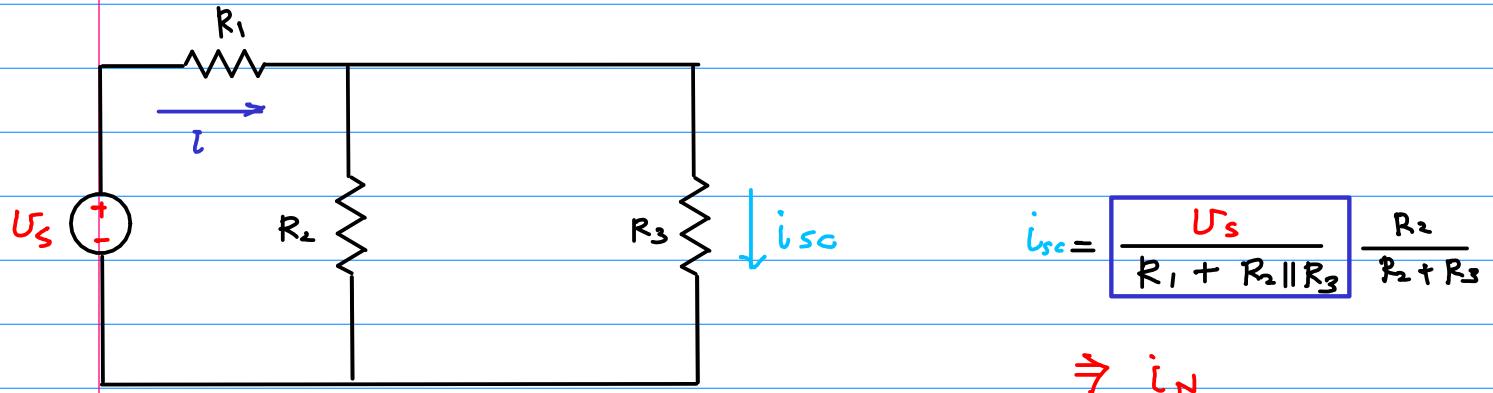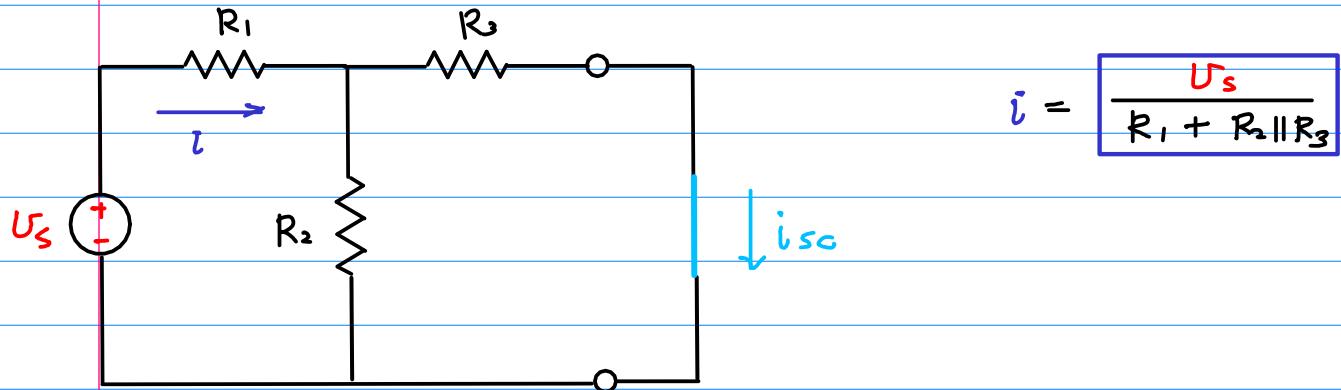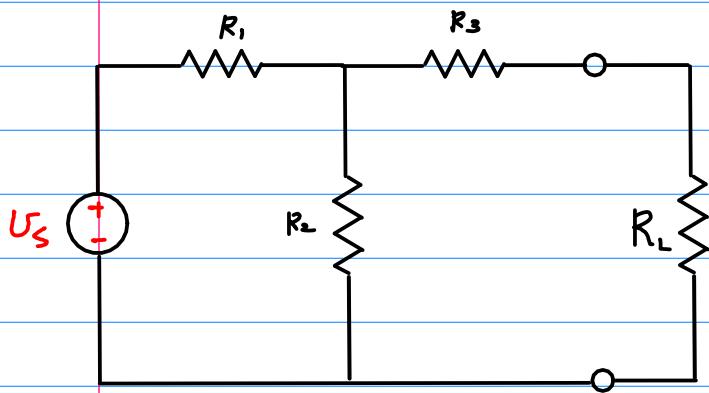

$$i = \frac{U_s}{R_1 + R_2 \parallel R_3}$$

$$i_{sc} = \frac{U_s}{R_1 + R_2 \parallel R_3} \cdot \frac{R_2}{R_2 + R_3}$$


$$\Rightarrow i_N$$

$$R_2 \parallel R_3 = \frac{1}{\frac{1}{R_2} + \frac{1}{R_3}} = \frac{R_2 R_3}{R_2 + R_3}$$


$$(R_1 + R_2 \parallel R_3)(R_2 + R_3) = R_1(R_2 + R_3) + R_2 R_3$$

$$\frac{R_2}{(R_1 + R_2 \parallel R_3)(R_2 + R_3)} = \frac{R_2}{(R_1 + R_3)R_2 + R_1 R_3}$$
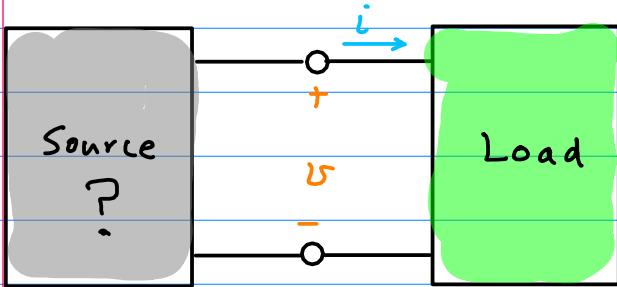
$$i_N = \frac{R_2}{(R_1 + R_3)R_2 + R_1 R_3} U_s$$



Thévenin Voltage  $v_T$

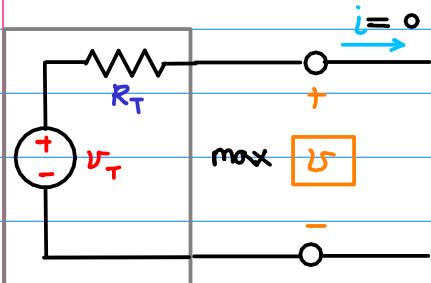


$$U_T = U_{oc} \text{ when } i = 0$$

$$R_T = R_N$$

**max  $U$**

Norton Current  $i_N$

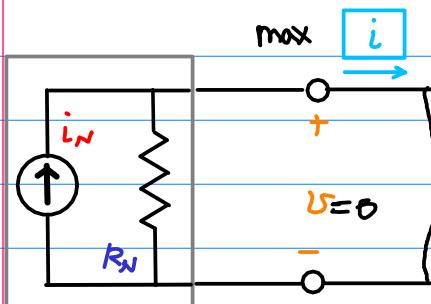


$$i_N = i_{sc} \text{ when } U = 0$$

$$R_N = R_T$$


**max  $i$**

$$U_T = R_T i_N$$

## Thévenin Equivalent Circuit



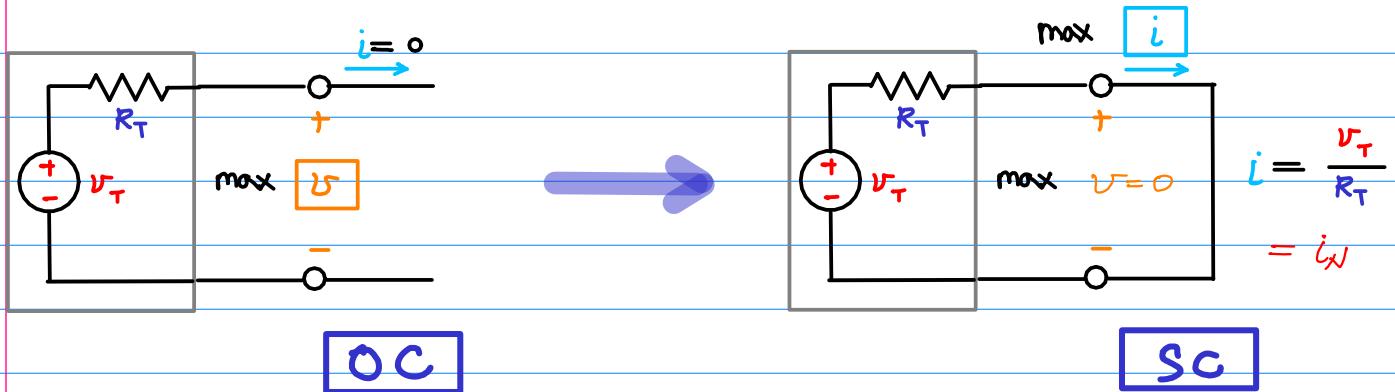


## Norton Equivalent Circuit

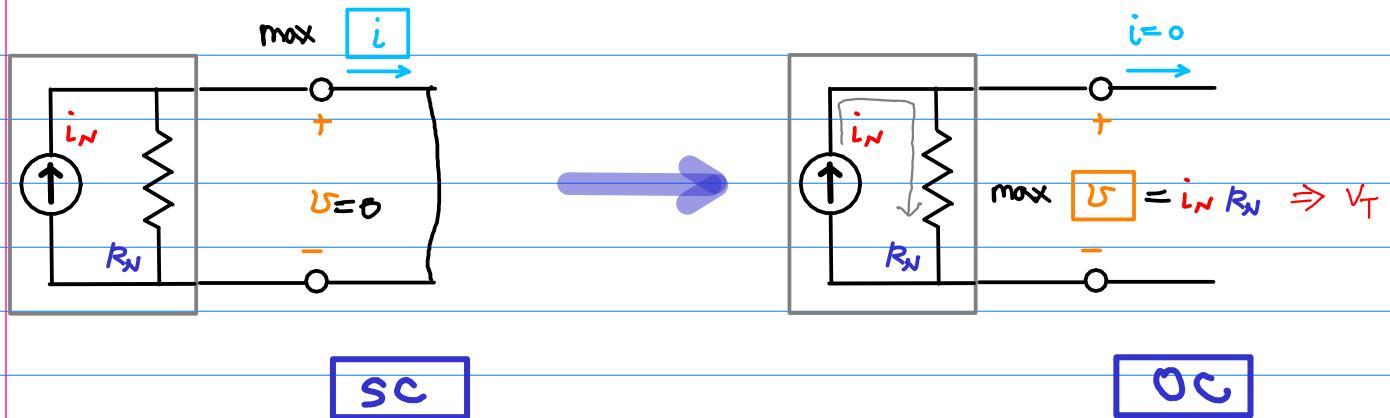

$$V_T = R_T i_N$$


# Source Transformation

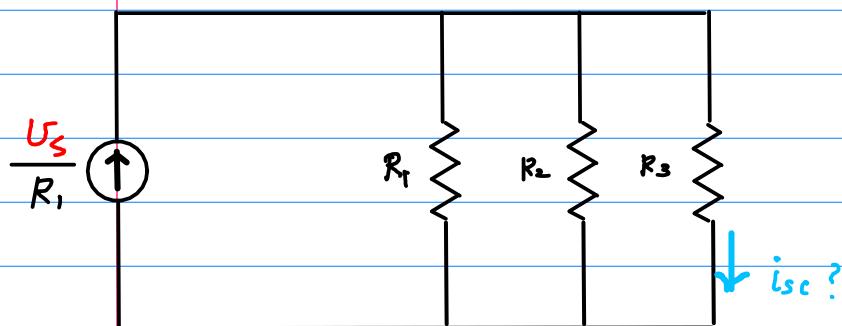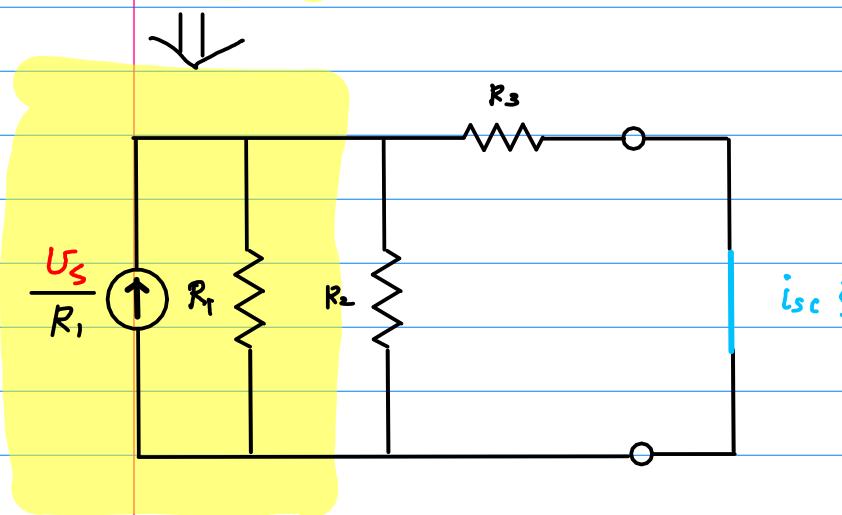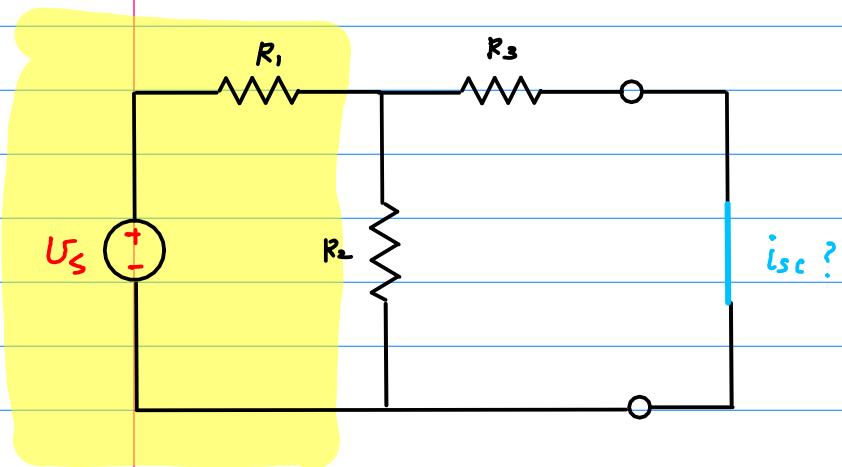


$$\begin{aligned}
 i_{sc} &= \frac{\frac{1}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \frac{U_S}{R_1} \\
 &= \frac{\cancel{R_1 R_2}}{R_2 R_3 + R_1 R_3 + R_1 R_2} \frac{1}{\cancel{R_1}} U_S \\
 &= \frac{R_2 U_S}{R_2 R_3 + R_1 R_3 + R_1 R_2}
 \end{aligned}$$

# Source Side Equation $R_T$

$$\max v \leftarrow R_L = \infty$$

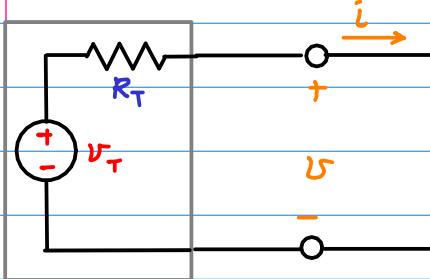



$$\max i \leftarrow R_L = 0$$

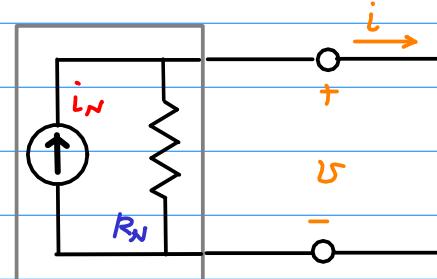

$$i < i_N$$


$$v < v_T$$

$$0 < R_L < \infty$$

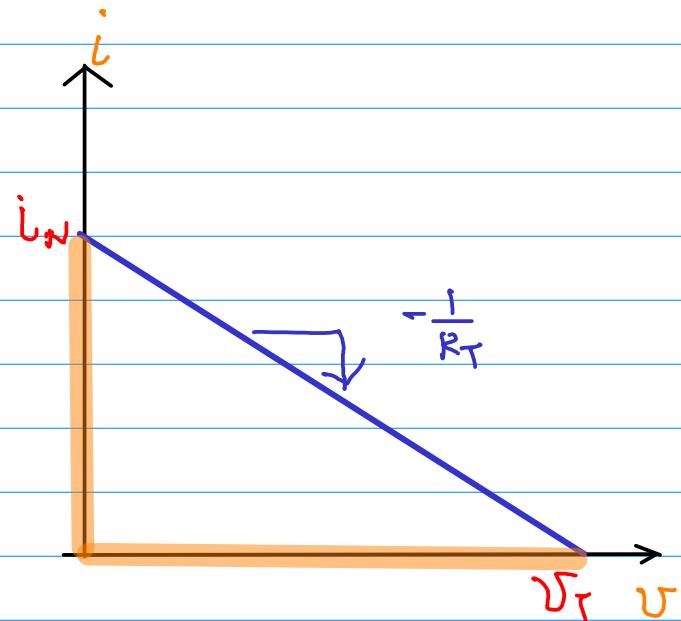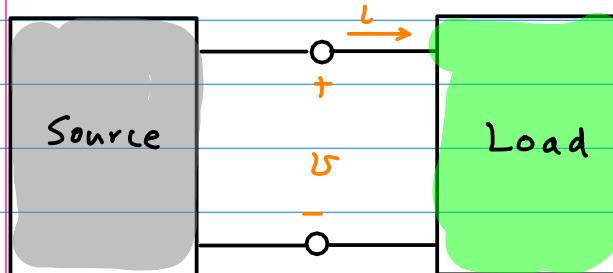

$$i = \frac{1}{R_T} (v_T - v)$$

# Load Line

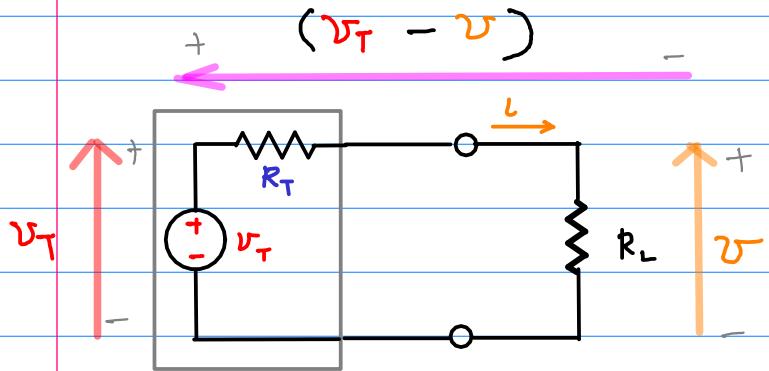


$$(v_T - v) = R_T \cdot i$$

$$i = \frac{1}{R_T} (v_T - v)$$


$$R_T = R_N$$

$$i = -\frac{1}{R_T} v + \frac{1}{R_T} v_T$$

$$y = -\alpha x + b$$

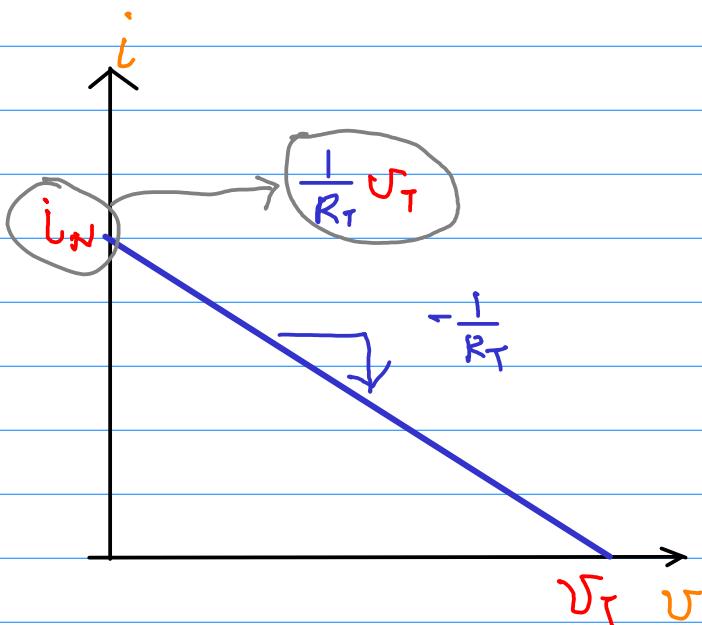


# Load side Equation

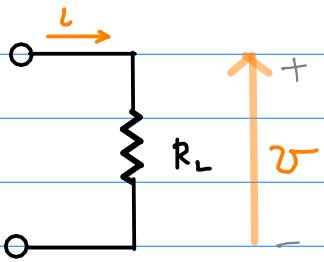


$$V = I R_L$$


$$I = \frac{1}{R_L} V$$

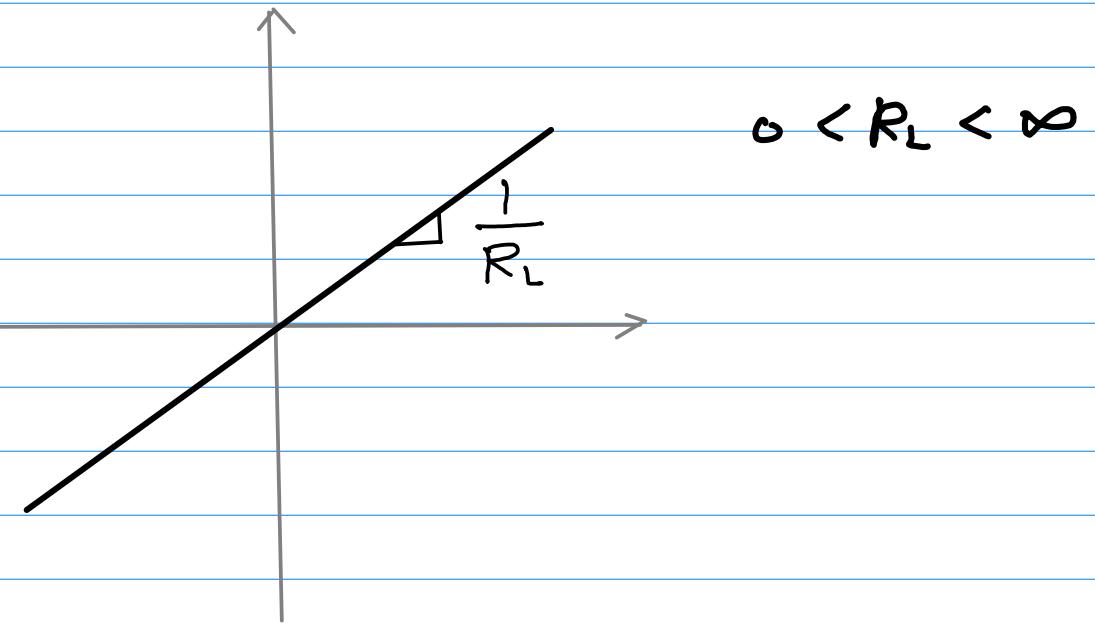




$$0 < R_L < \infty$$

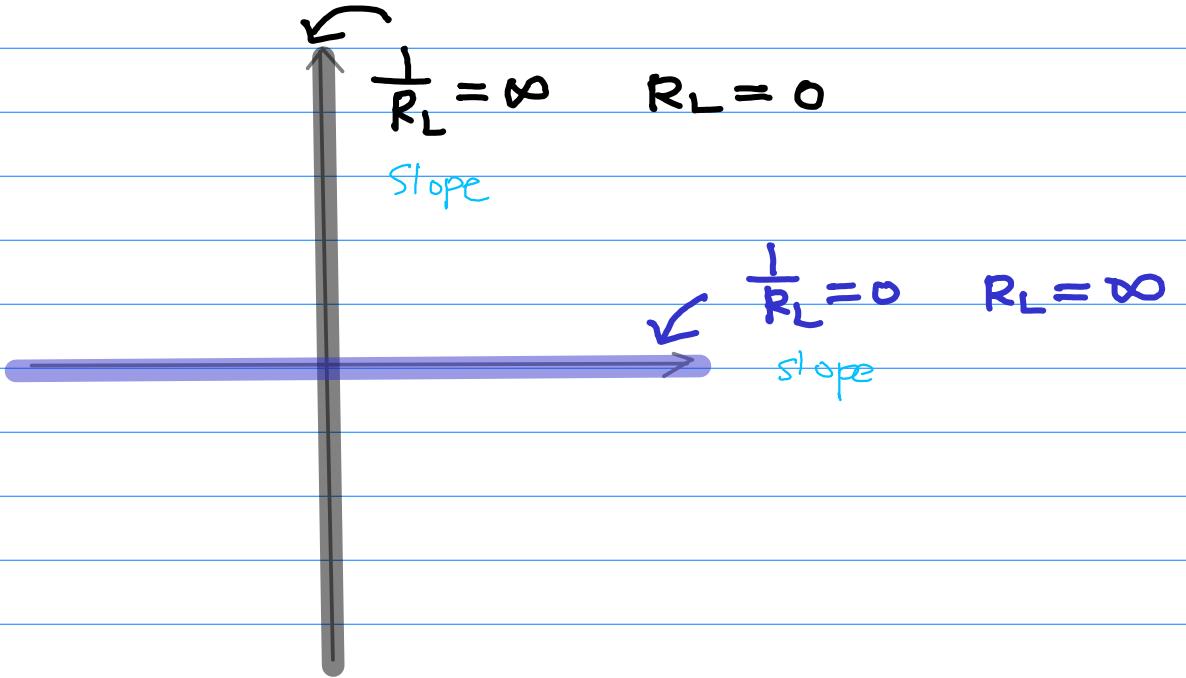




source side equation

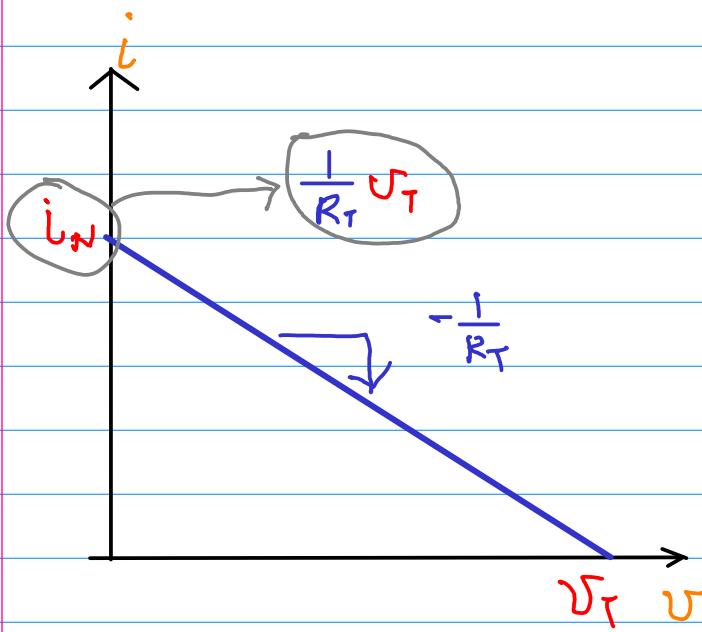

load side equation

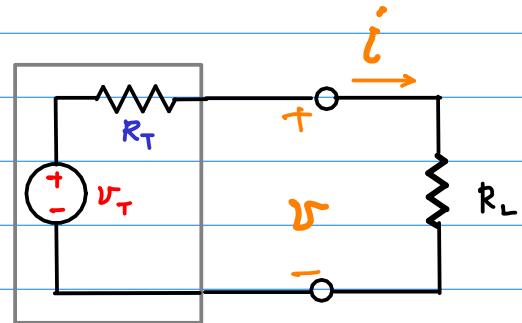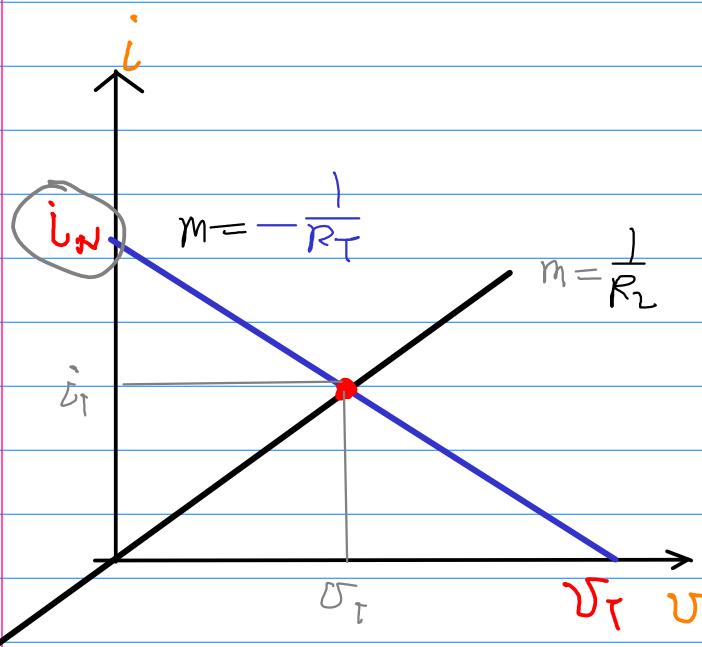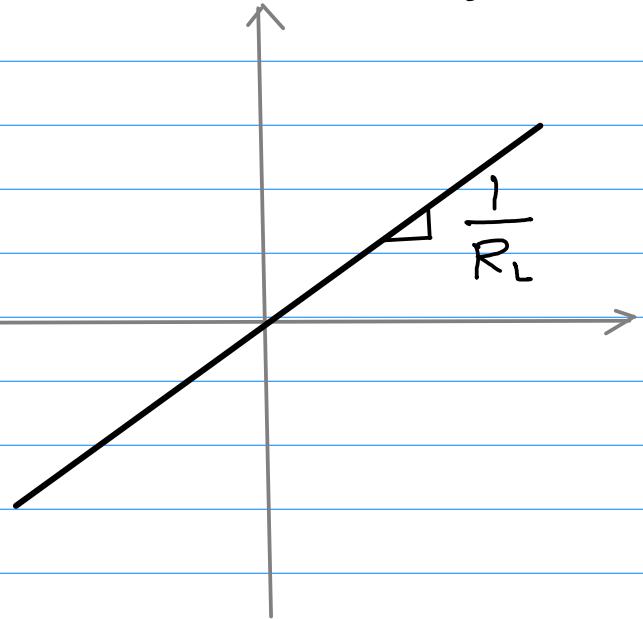

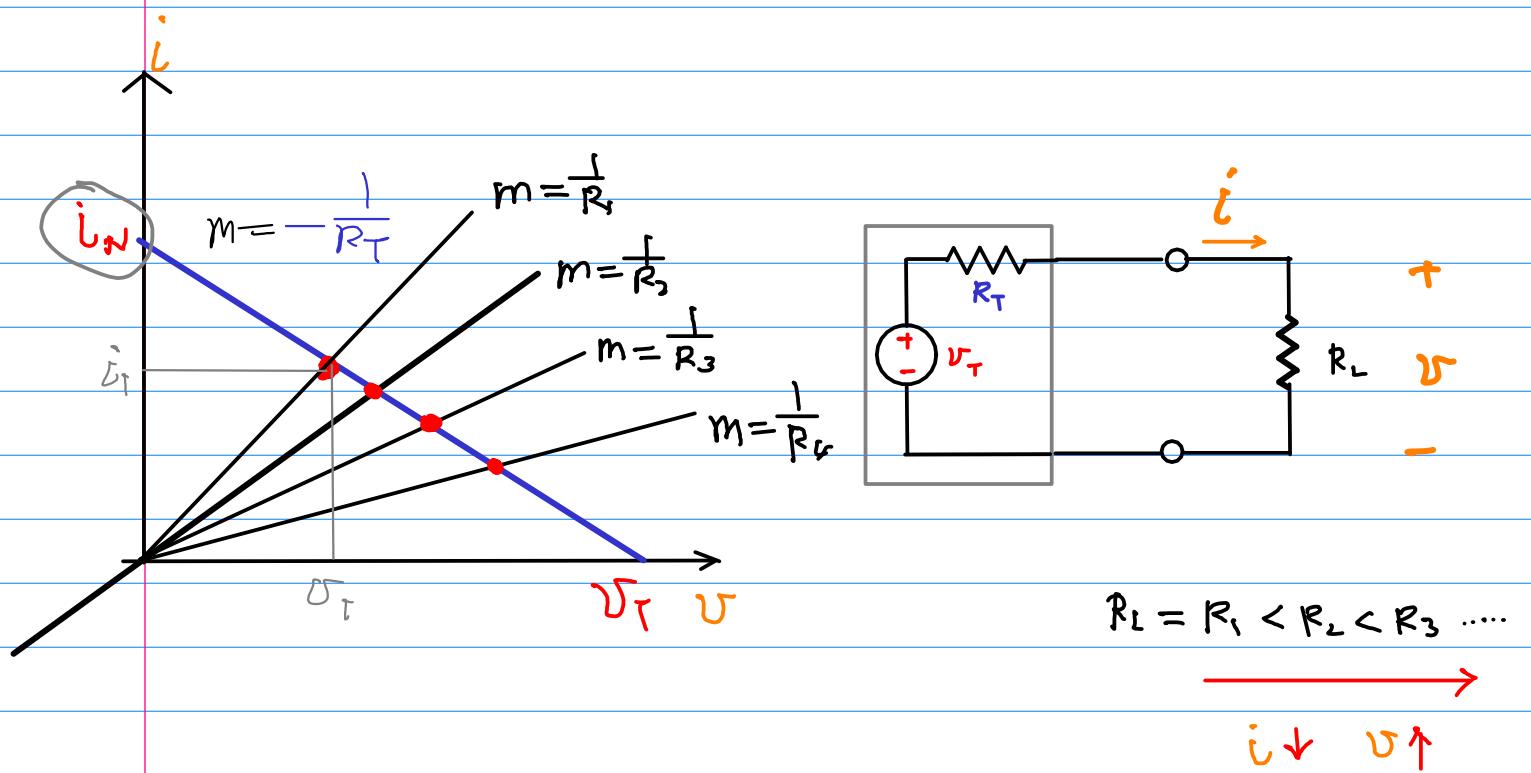

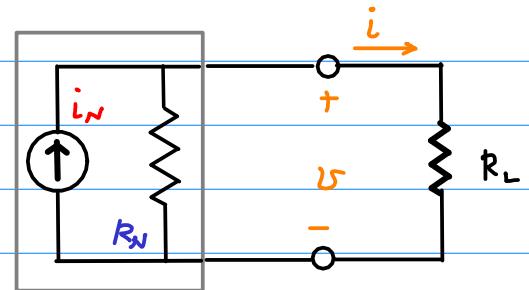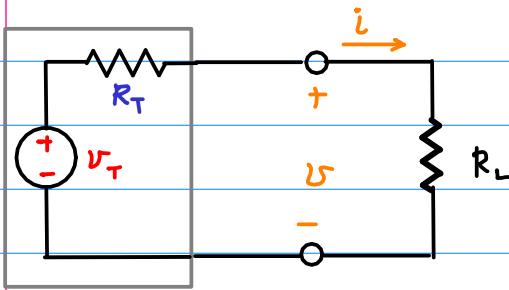

$$v = \frac{R_L}{R_T + R_L} v_T$$

$$i = \frac{R_N}{R_N + R_L} i_N$$

$$v = \frac{R_N}{R_N + R_L} i_N R_L$$

$$U_T = i_N R_N$$

$$R_N = R_T$$

$$\begin{aligned} &= \frac{R_L}{R_N + R_L} i_N R_N \\ &= \frac{R_L}{R_T + R_L} v_T \end{aligned}$$

$$v = (R_N \parallel R_L) i_N$$

$$= \frac{R_N R_L}{R_N + R_L} i_N$$