

BJT Topologies - DC Characteristics

Copyright (c) 2012 – 2017 Young W. Lim.


Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.

This document was produced by using OpenOffice and Octave.


Active and Saturation Regions (1)

Common Base

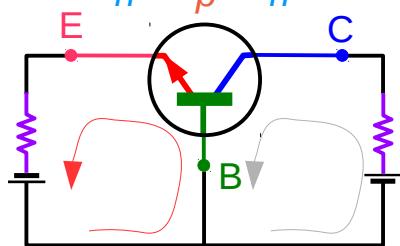


active

Common Emitter

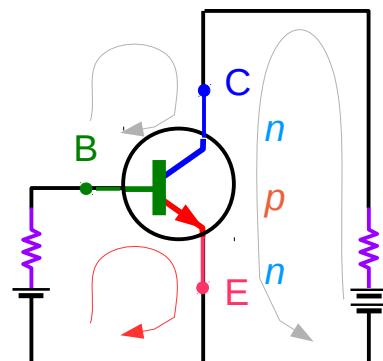


active

Common Collector

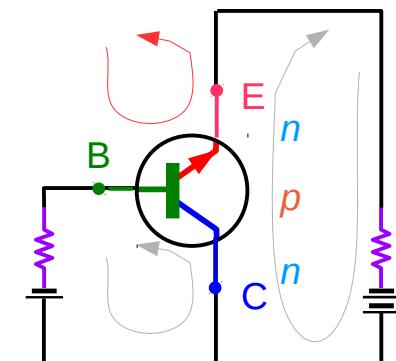


active

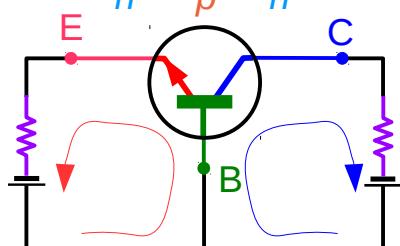


Large V_{BB} , Small V_{CE}

saturation

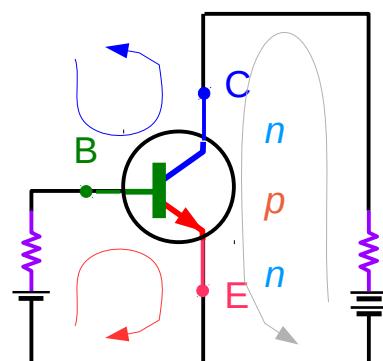

Large V_{BB} , Small V_{CE}

saturation

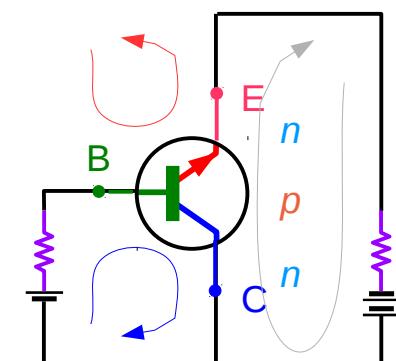


Large V_{BB} , Small V_{CE}


saturation

Active and Saturation Regions (2)


Common Base

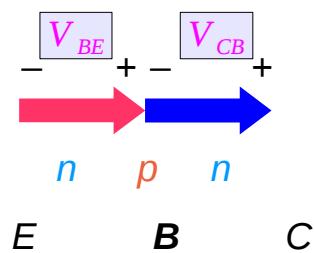


Common Emitter

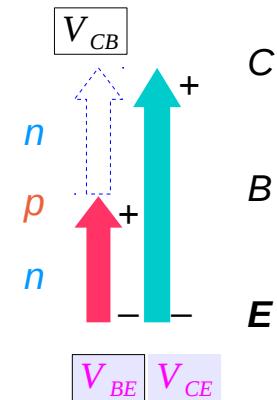


Common Collector

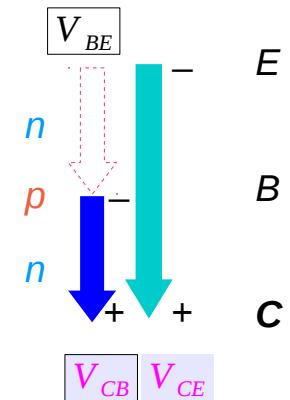


active

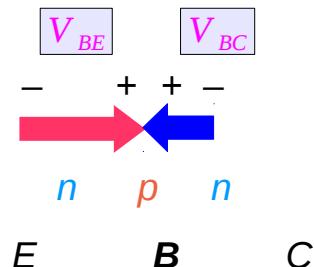

active

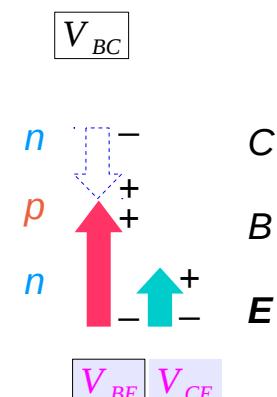

active

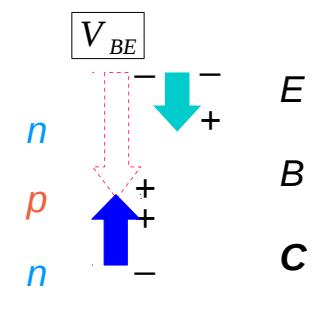


saturation

saturation


saturation

Active and Saturation Regions (3)

Common Emitter

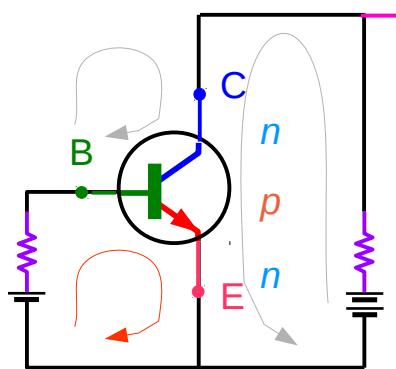


active

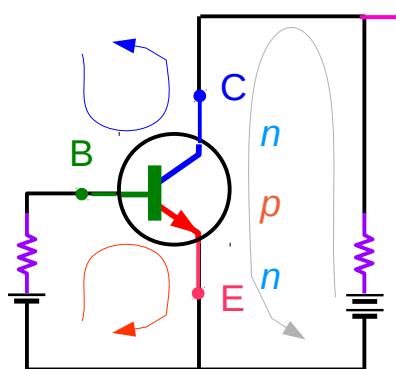


saturation

Common Collector 2

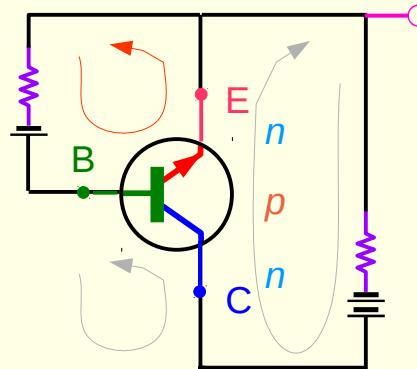


active

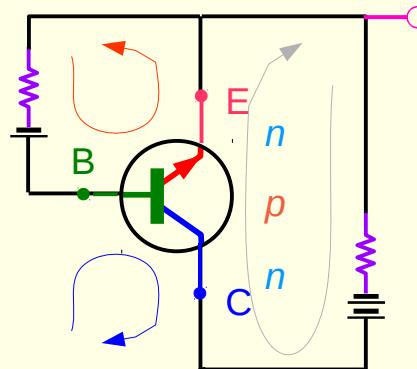


saturation

Common Collector

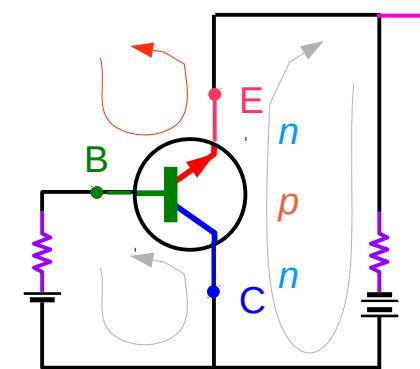


active

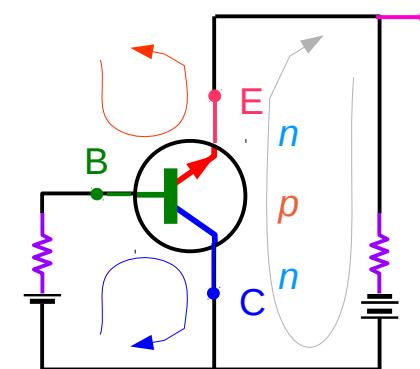


saturation

Active and Saturation Regions (4)


Common Emitter

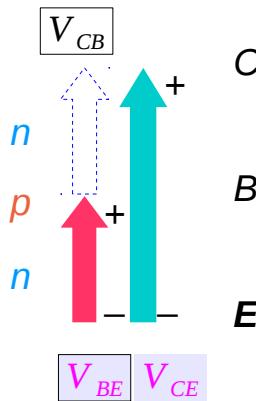

Common Collector 2

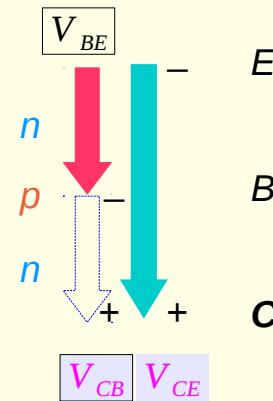


Common Collector

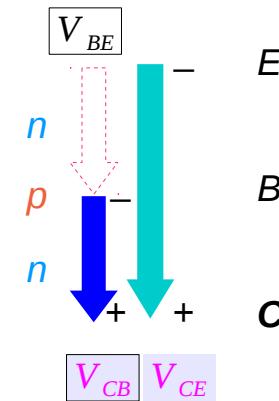


CC & CB from CE


Common Emitter

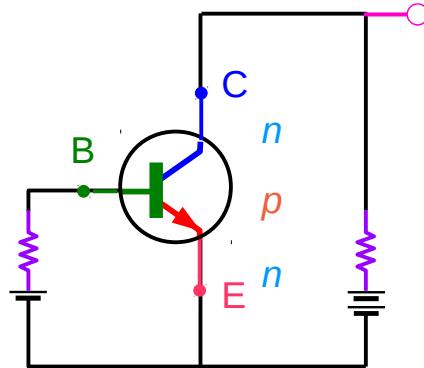

Common Collector 3

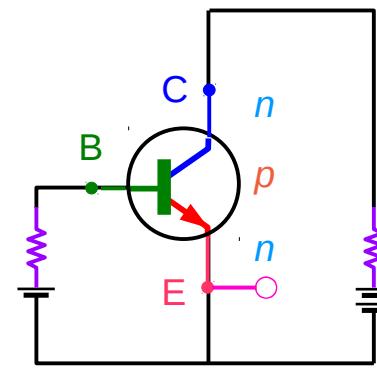


Common Base

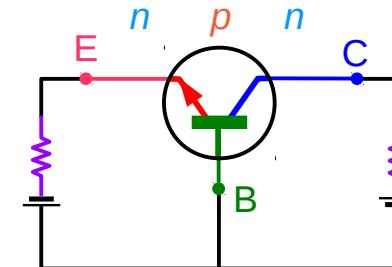


1. DC Characteristics of CE Amplifiers


Common Emitter

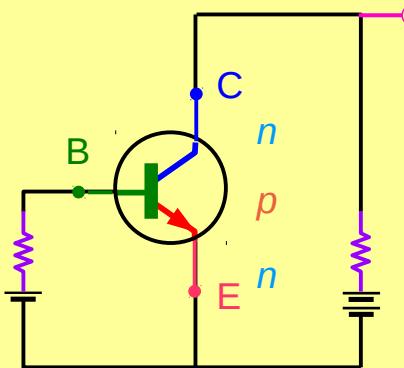

Common Collector 3

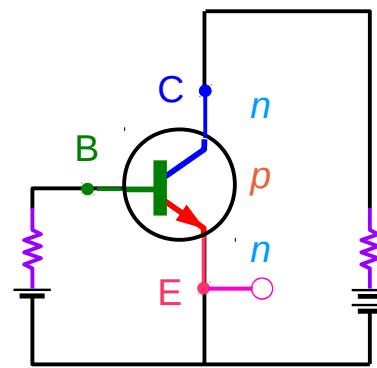


Common Base


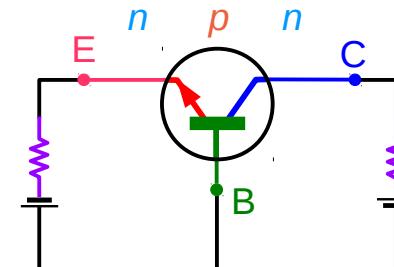


CE Amplifier : Voltage drops across resistors

Common Emitter

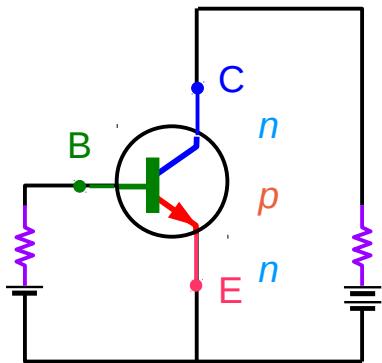


Active region

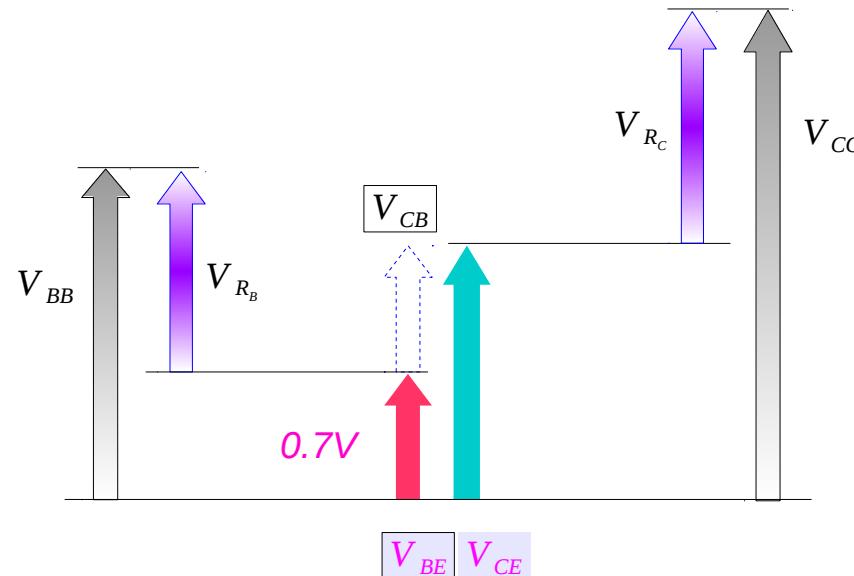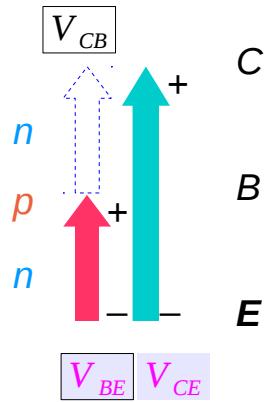


CE Amplifier : Load lines


Common Emitter

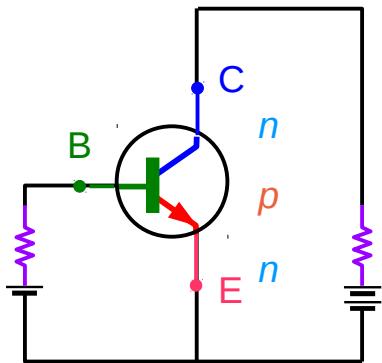



Input Characteristics

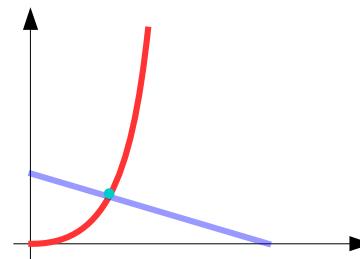

Output Characteristics

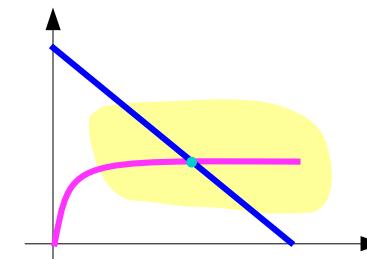


Active region

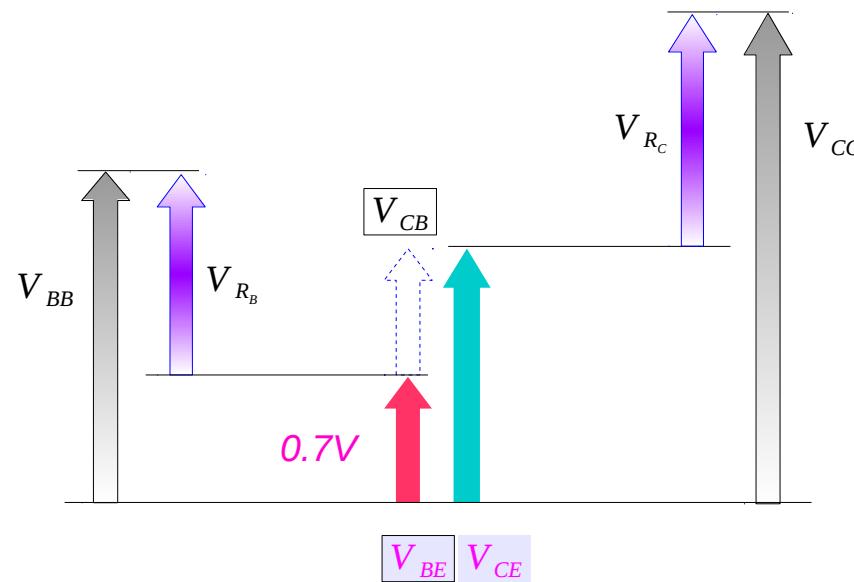
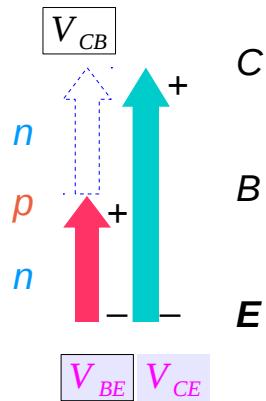


CE Amplifier : increasing V_{BB} \rightarrow increasing V_R

Common Emitter

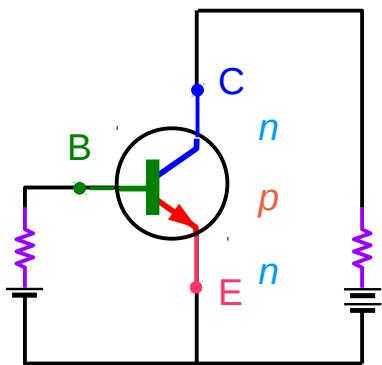


Active region

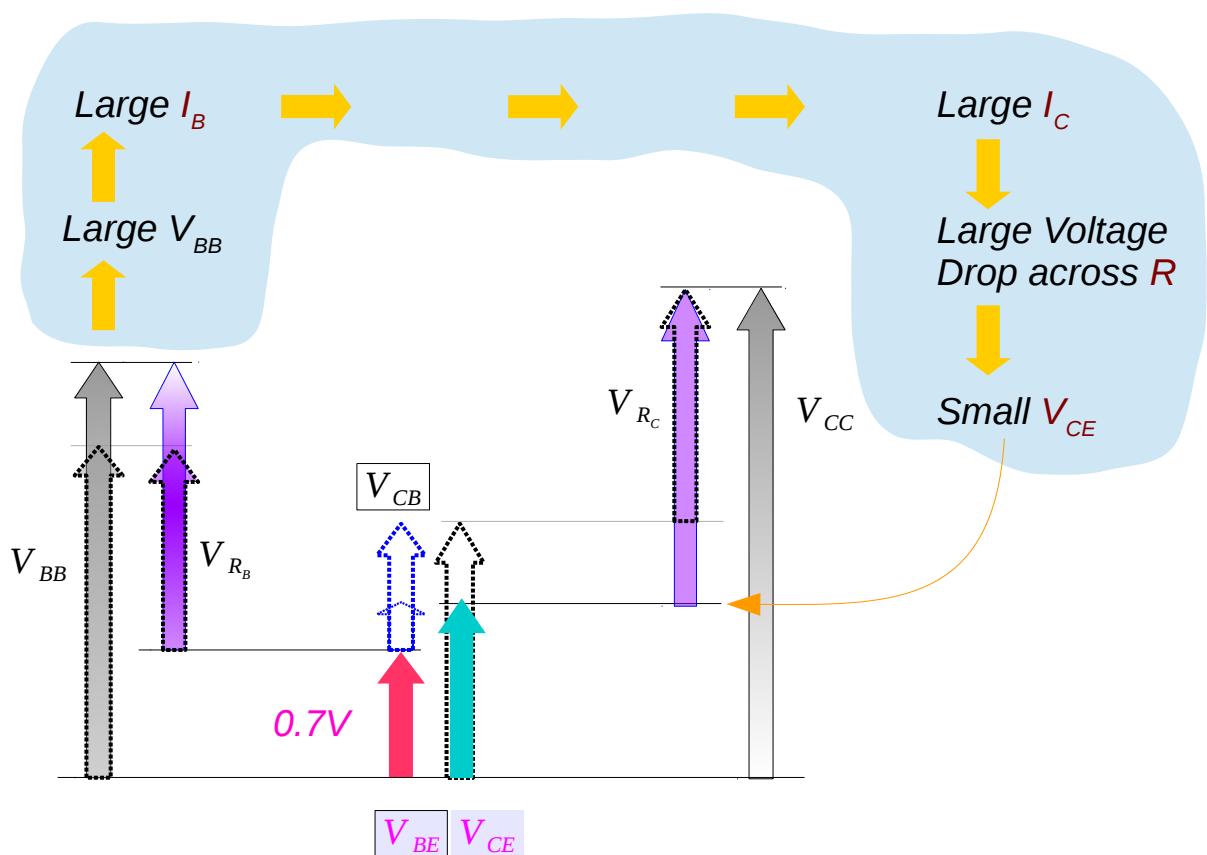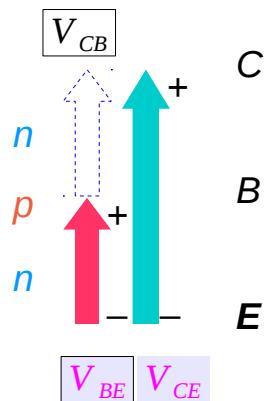


CE Amplifier : increasing $I_B \rightarrow$ decreasing V_{CE}


Common Emitter

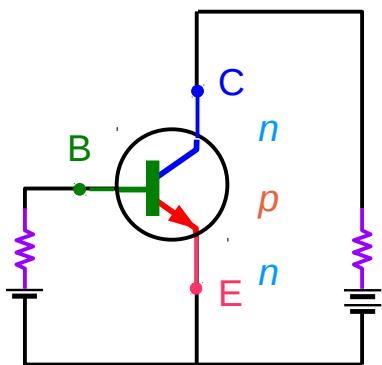



Input Characteristics

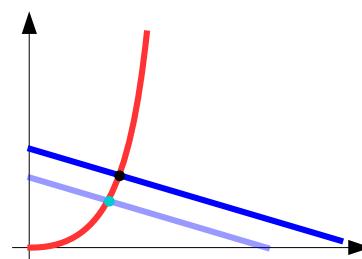

Output Characteristics



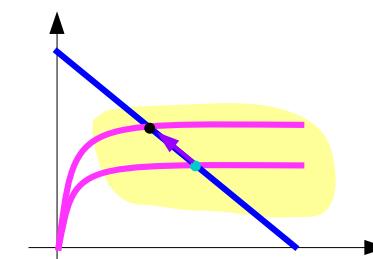


Active region

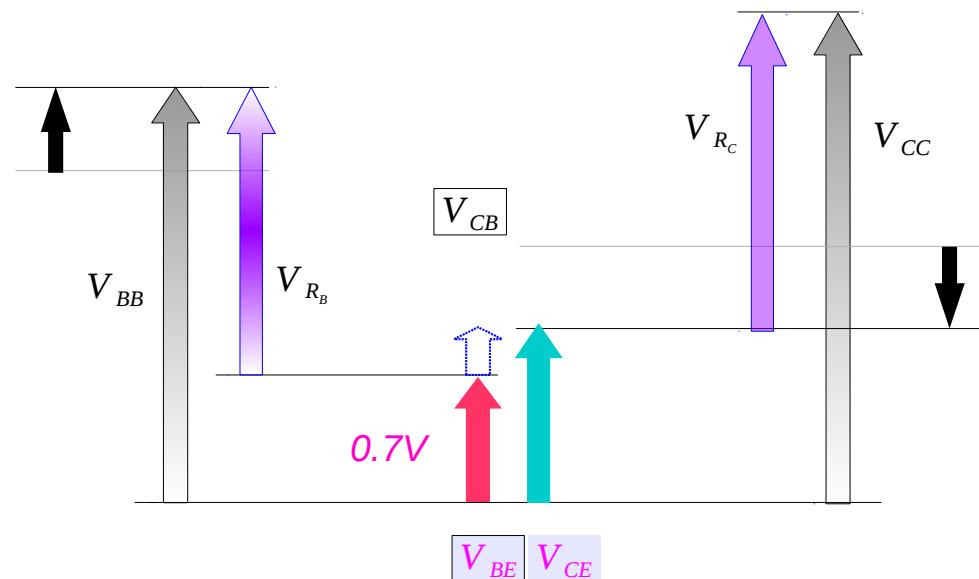
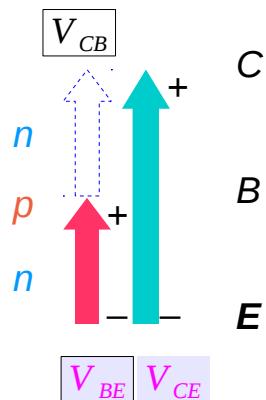


CE Amplifier : Saturation when $V_{RC} \approx V_{CC}$

Common Emitter

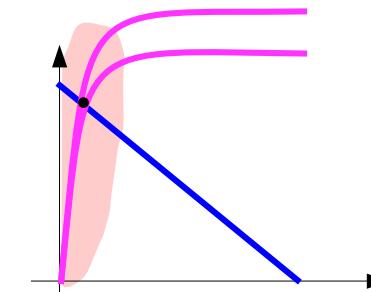
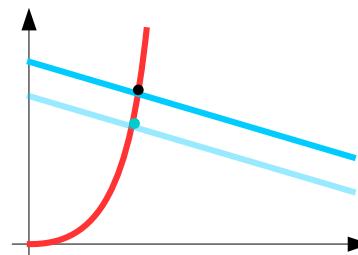
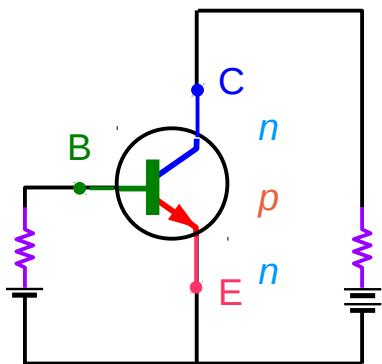


saturation

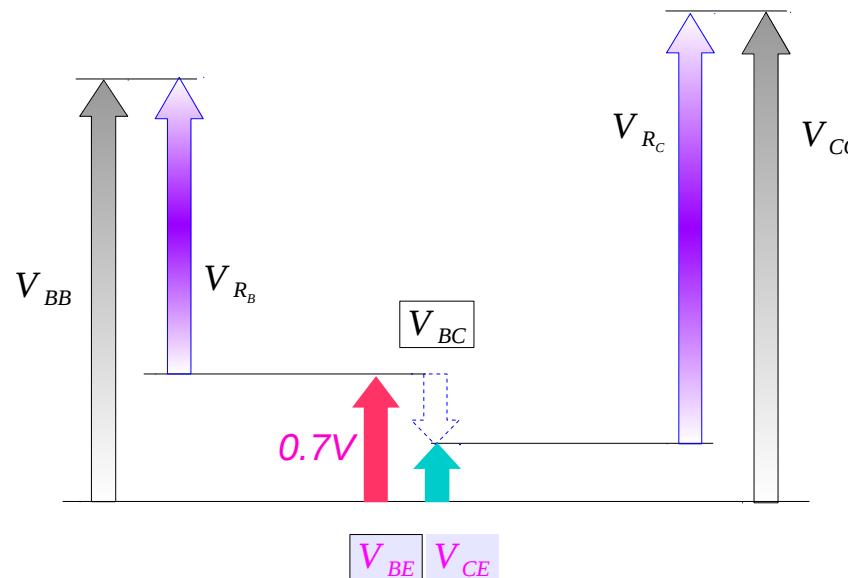
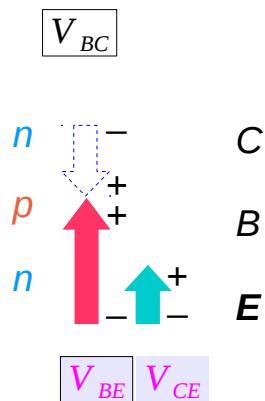


CE Amplifier : increasing I_B \nrightarrow decreasing V_{CE} : Saturation

Common Emitter

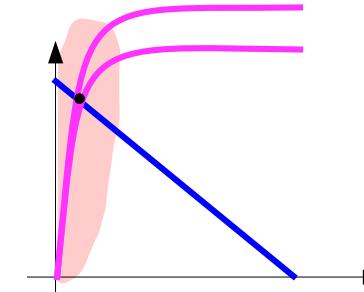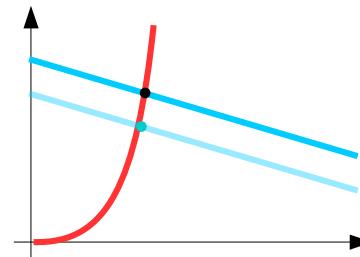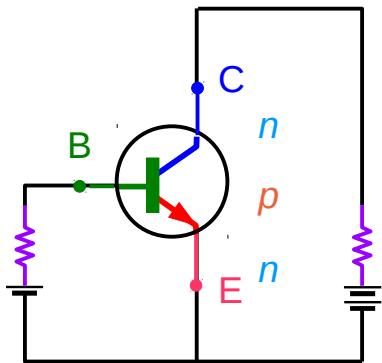


saturation

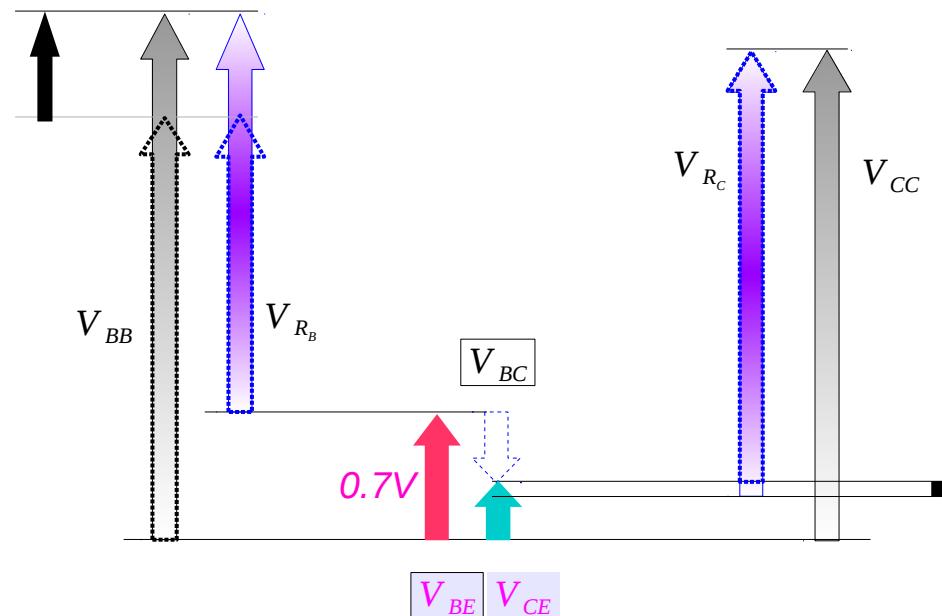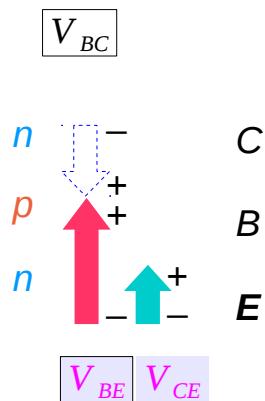


AC Equivalent Circuits

2. DC Characteristics of CC Amplifiers


Common Emitter

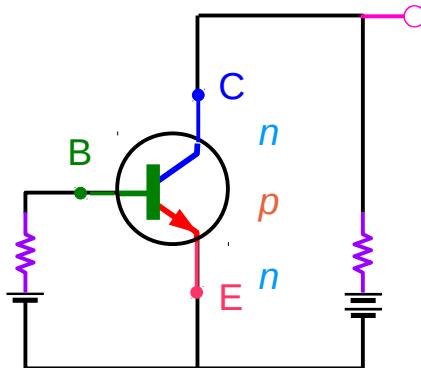

Common Collector 3

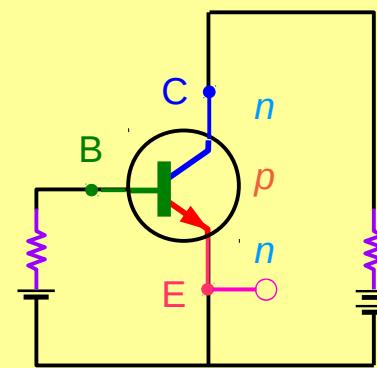


Common Base

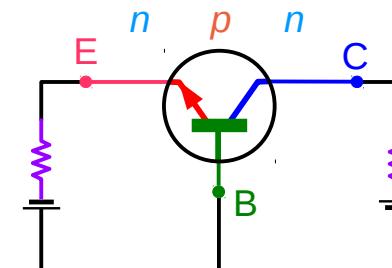


CE & CC Comparison



Common Emitter

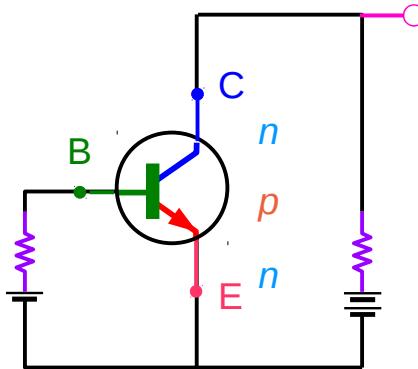


Common Collector 2

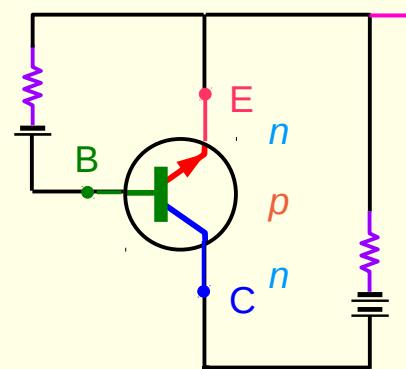


Common Collector

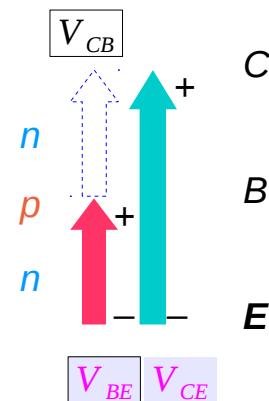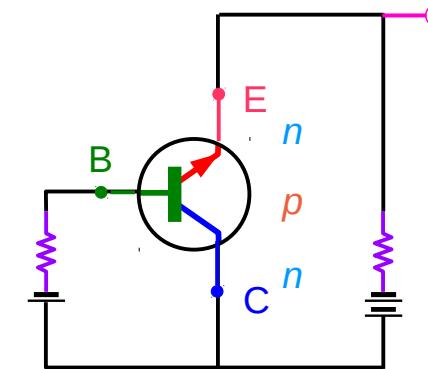

Active region

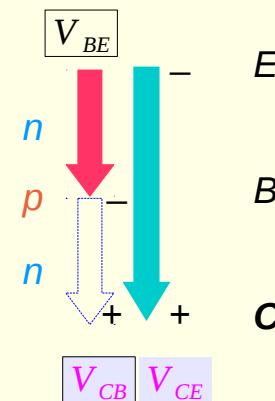


Active region

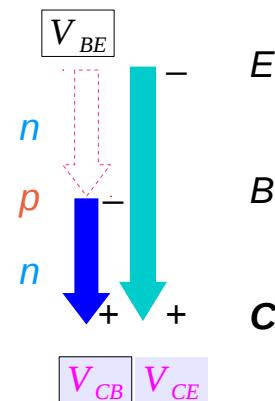


Active region

CE & CC Comparison



Common Emitter

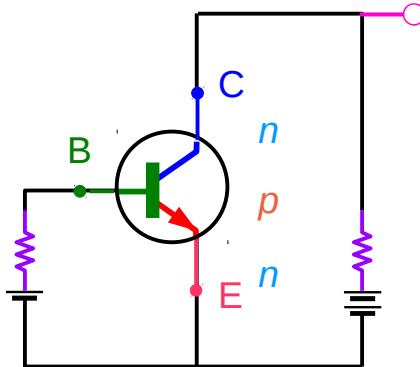


Common Collector 2

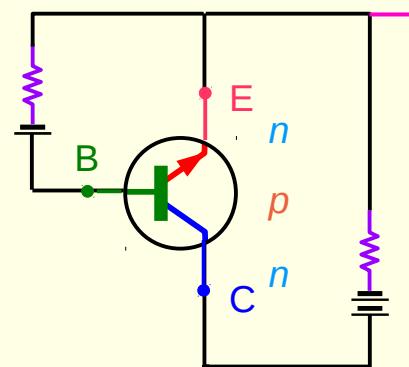


Common Collector 3

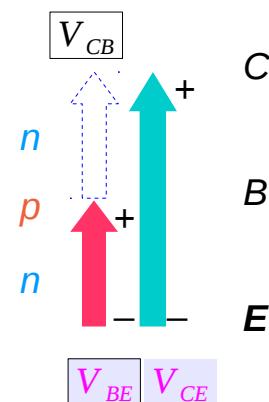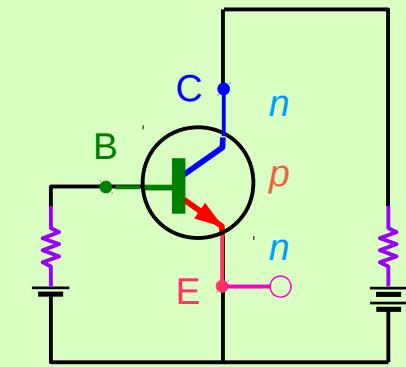

Active region

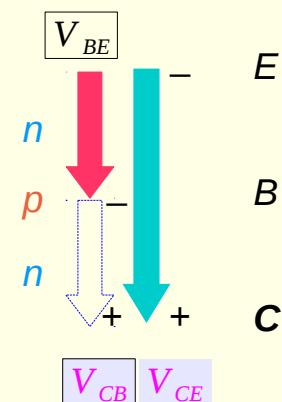



Active region

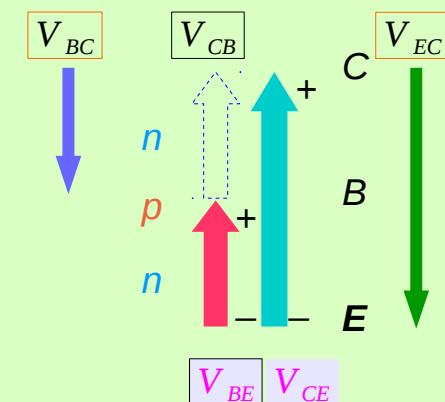


Active region

CC Amplifier : Voltage drops across resistors

Common Collector 3

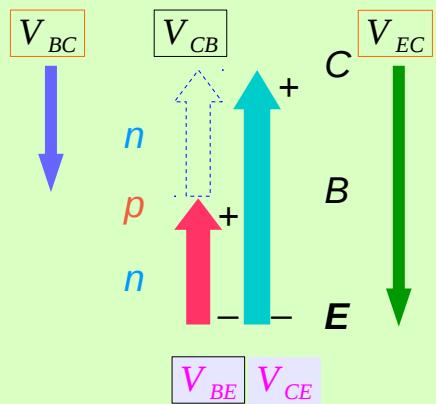
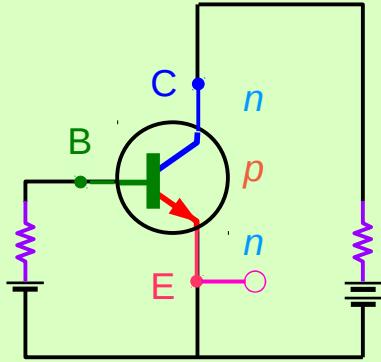


Active region

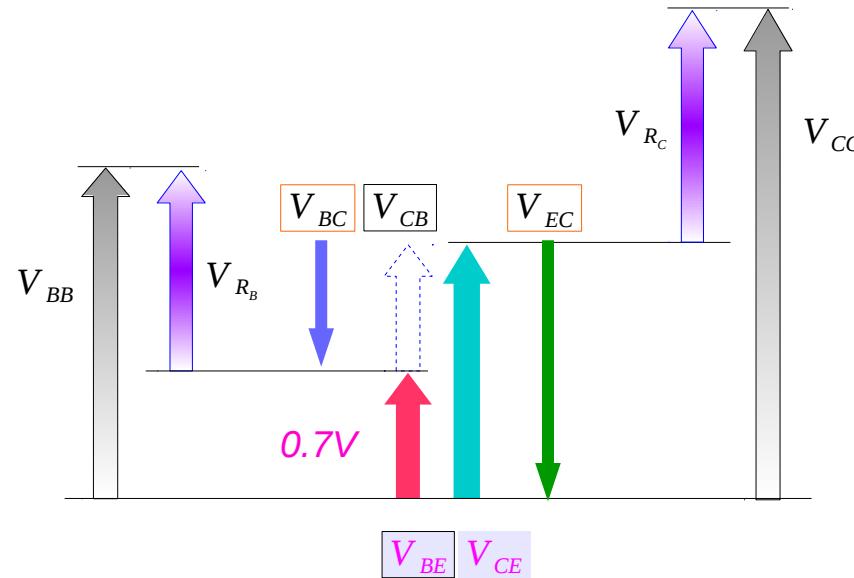


CC Amplifier : Load lines

Common Collector 3

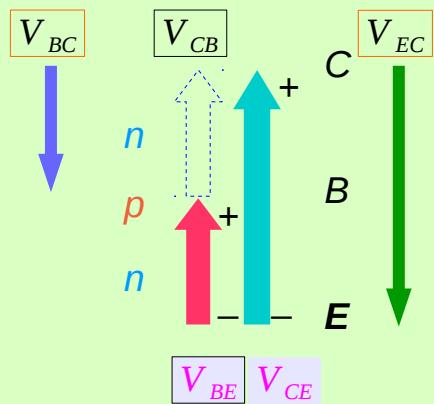
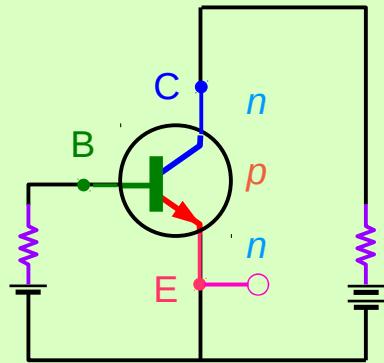


Active region

Input Characteristics


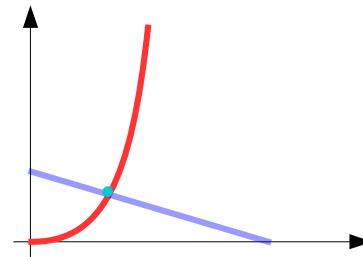


Output Characteristics

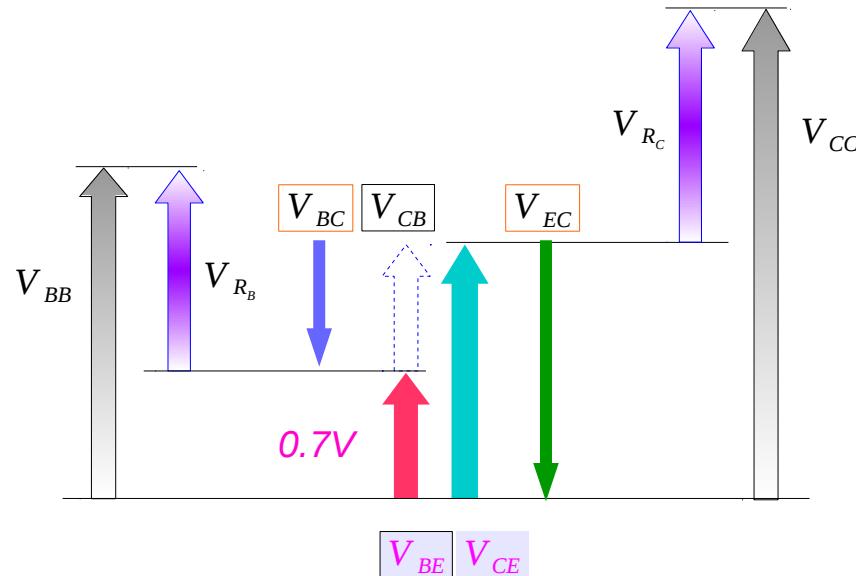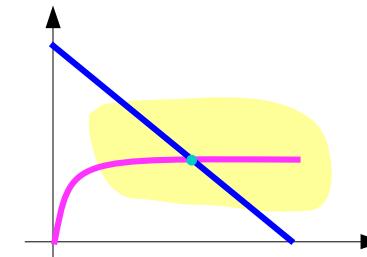


CC Amplifier : increasing V_{BB} \rightarrow increasing V_R

Common Collector 3

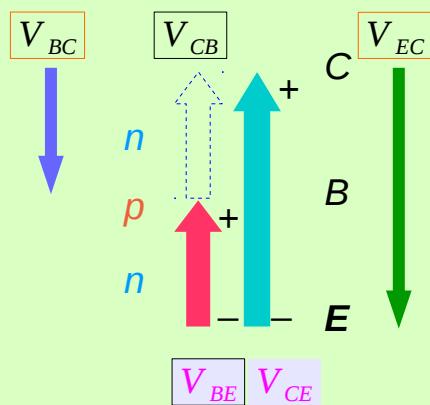
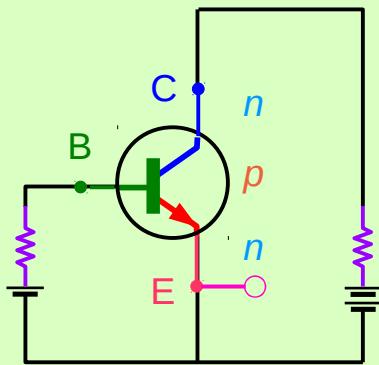


Active region

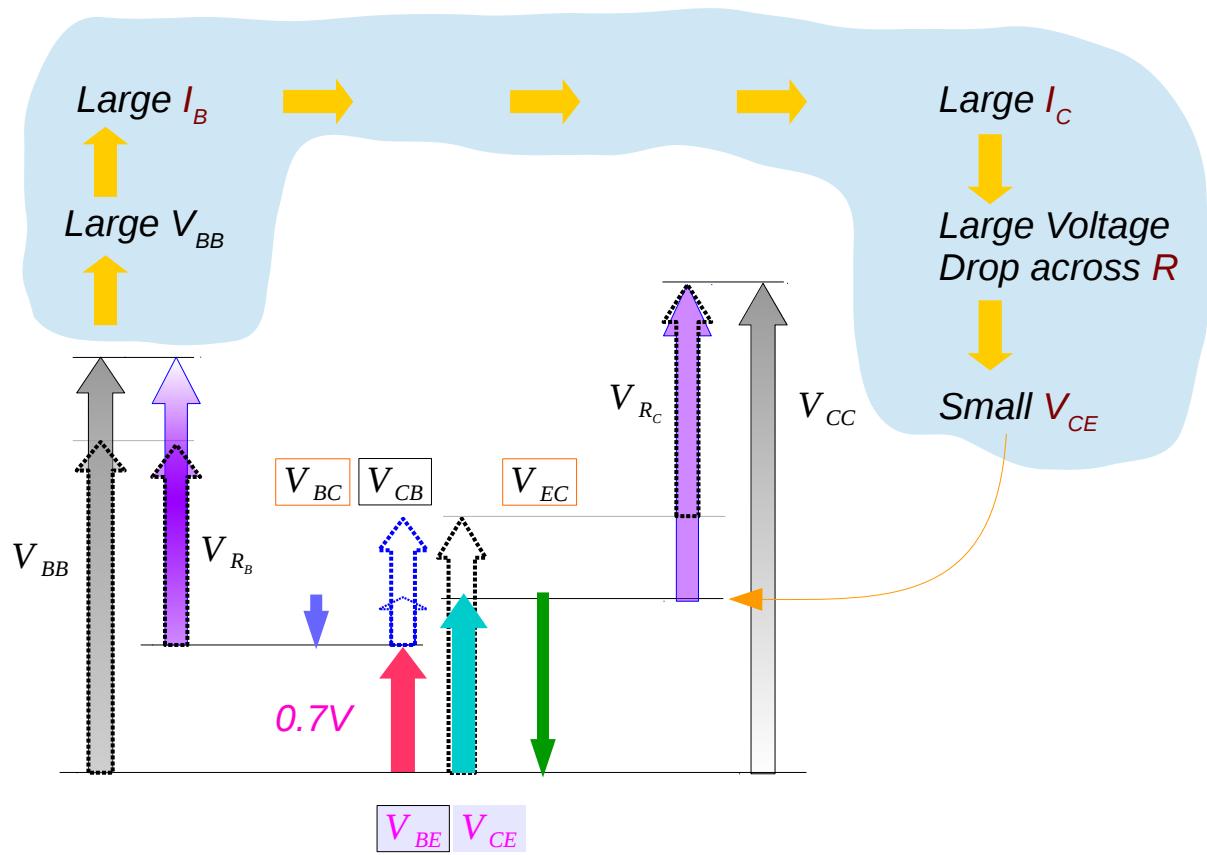


CC Amplifier : increasing $I_B \rightarrow$ decreasing $-V_{EC}$

Common Collector 3

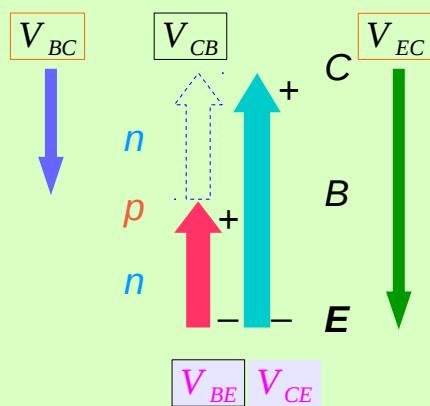
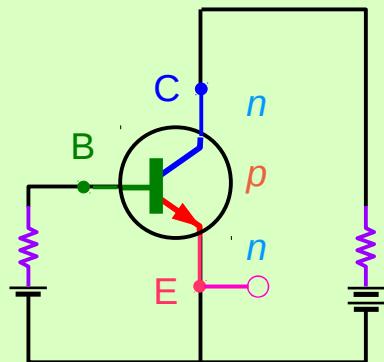


Active region

Input Characteristics

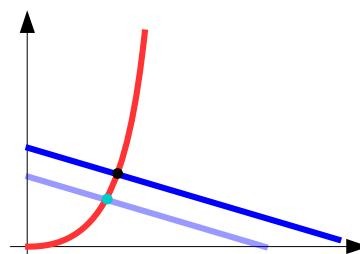


Output Characteristics


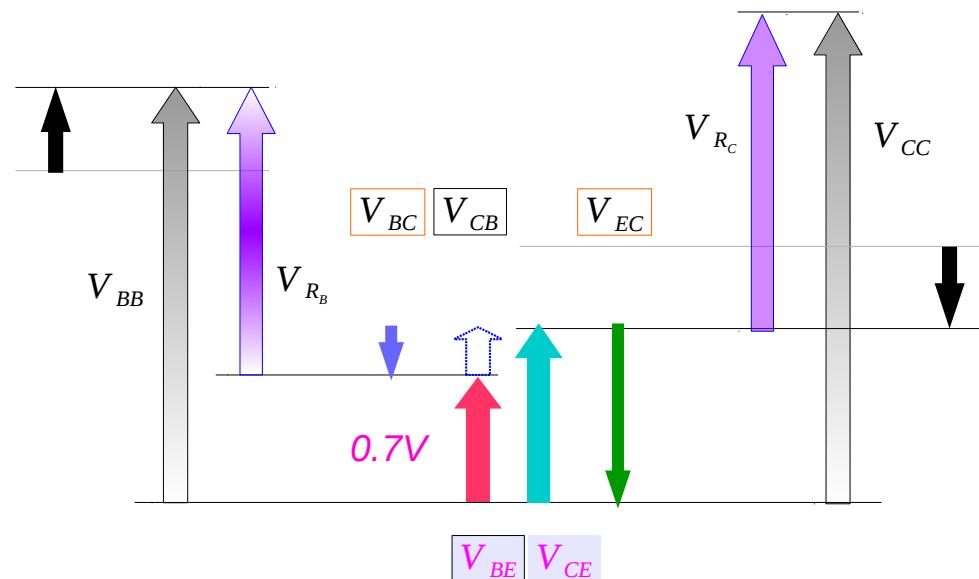
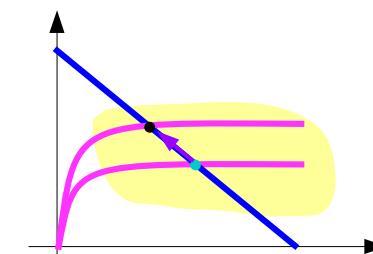


CC Amplifier : Saturation when $V_{RC} \approx V_{CC}$

Common Collector 3

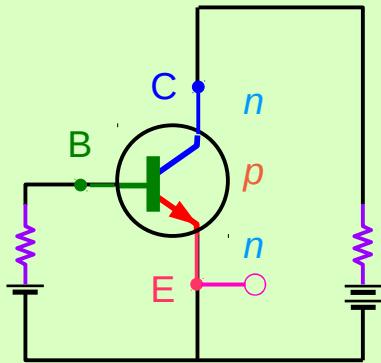


saturation

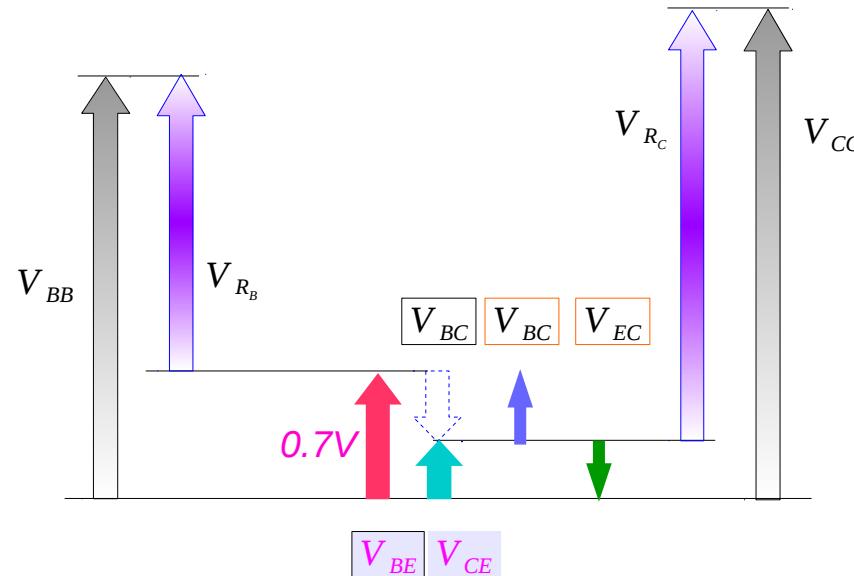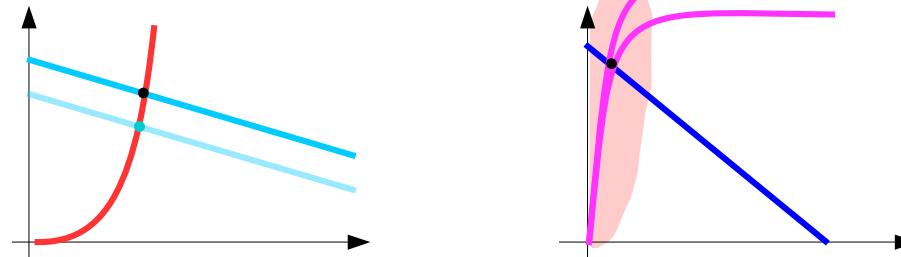
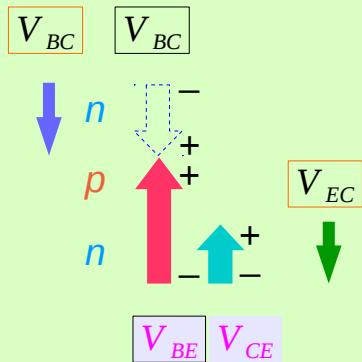


CC Amplifier : increasing I_B \rightarrow decreasing $-V_{EC}$: Saturation

Common Collector 3


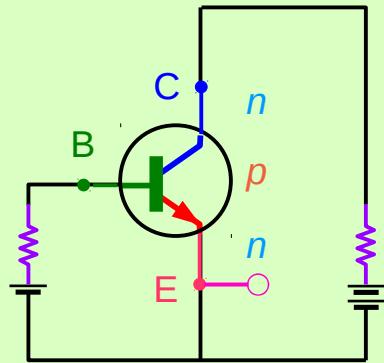


saturation

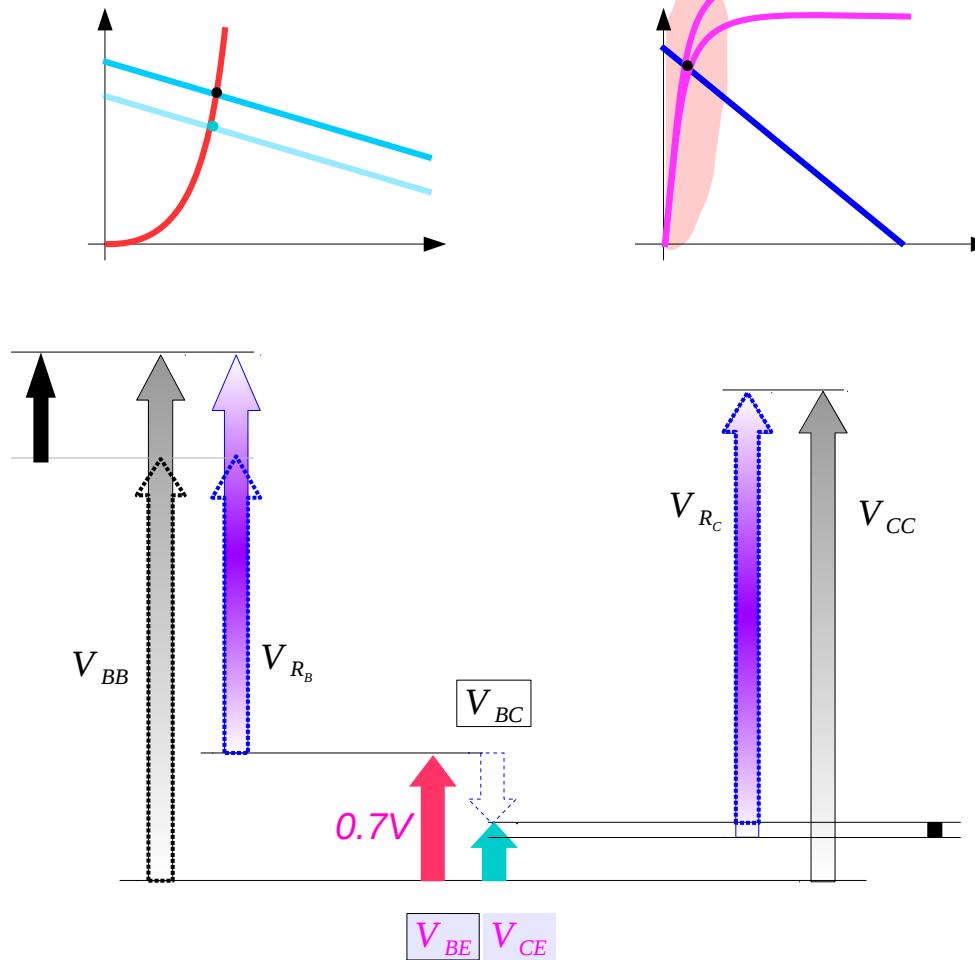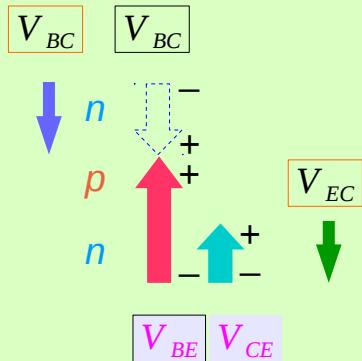


CC Amplifier : Load lines

Common Collector 3


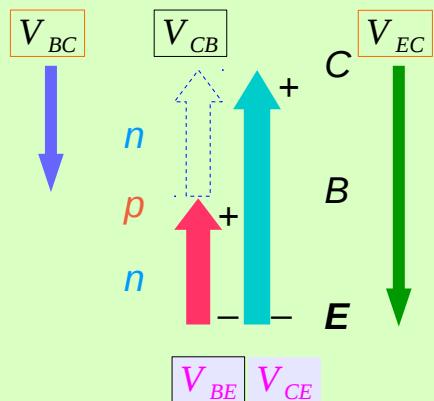
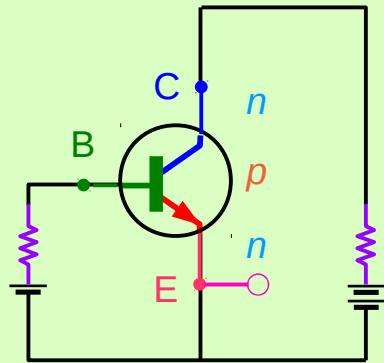


Active region

Input Characteristics

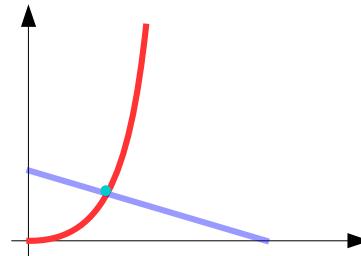


Output Characteristics

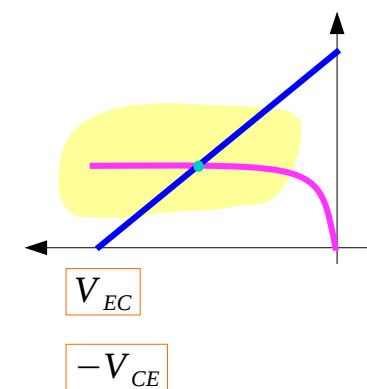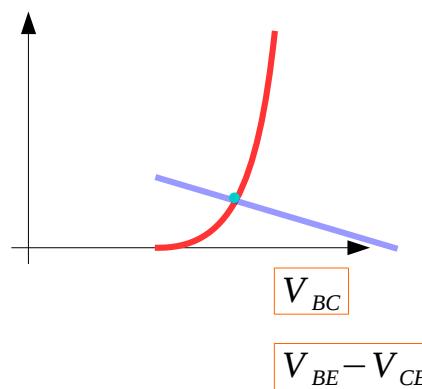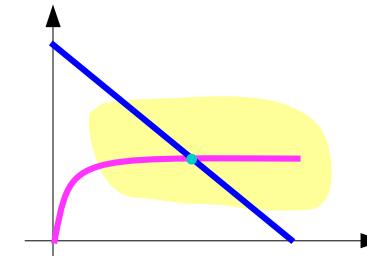


AC Equivalent Circuits

3. DC Characteristics of CB Amplifiers


Common Emitter

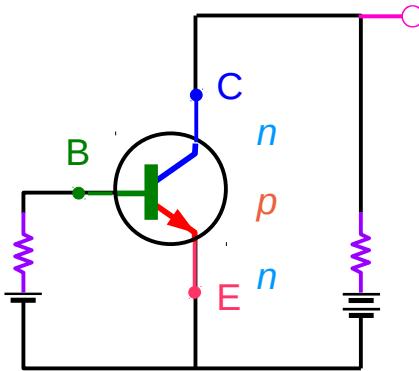

Common Collector 3


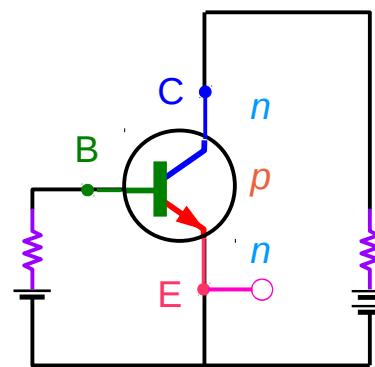


Common Base

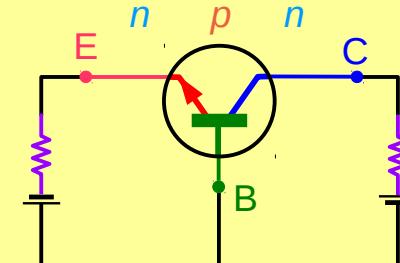


CB Amplifier : Voltage drops across resistors

Common Base

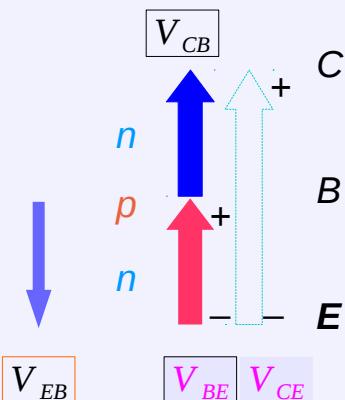
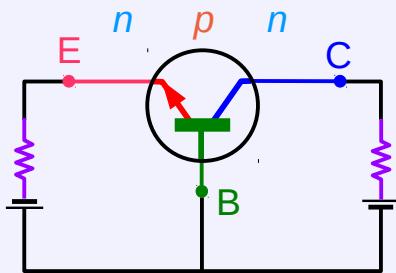


Active region

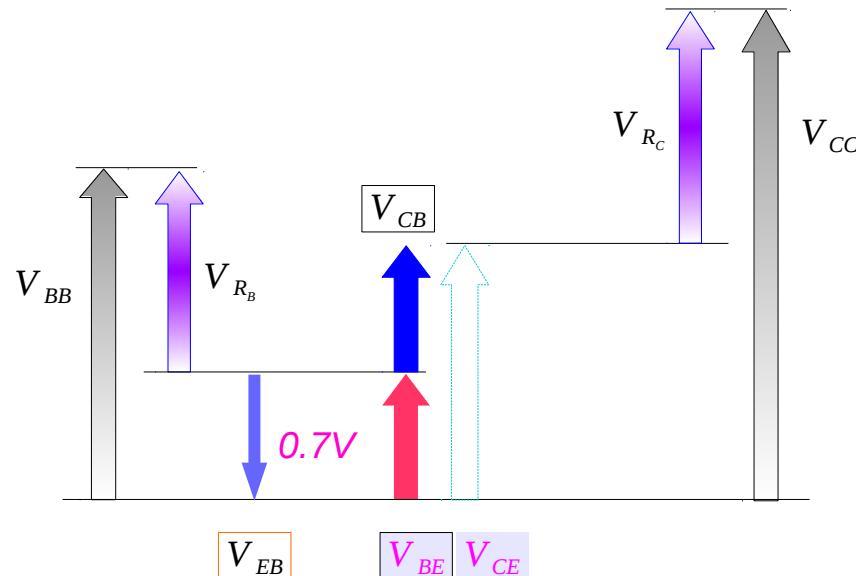


CB Amplifier : Load lines

Common Base

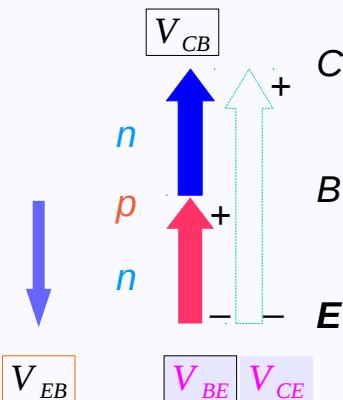
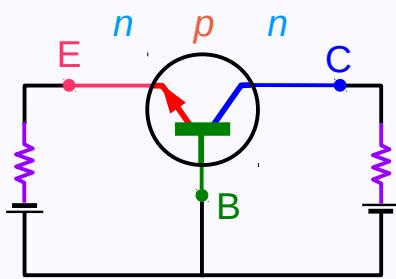


Active region

Input Characteristics


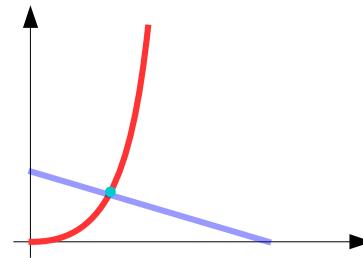


Output Characteristics

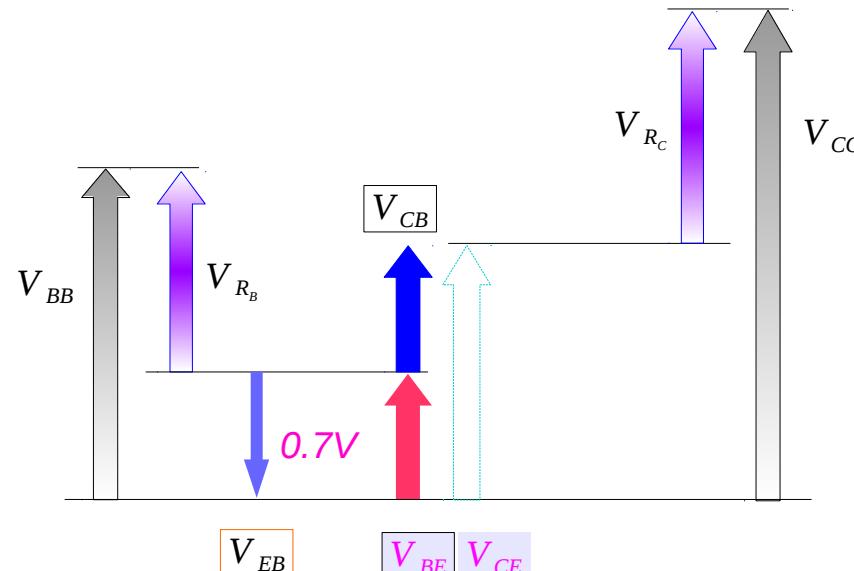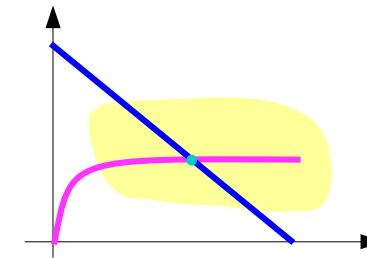


CB Amplifier : increasing V_{BB} \rightarrow increasing V_R

Common Base

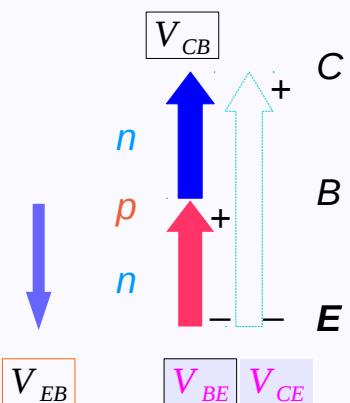
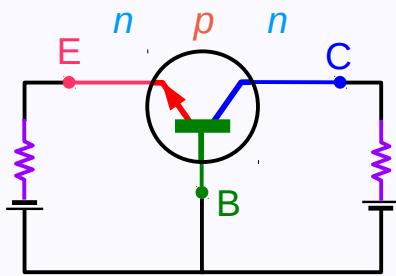


Active region

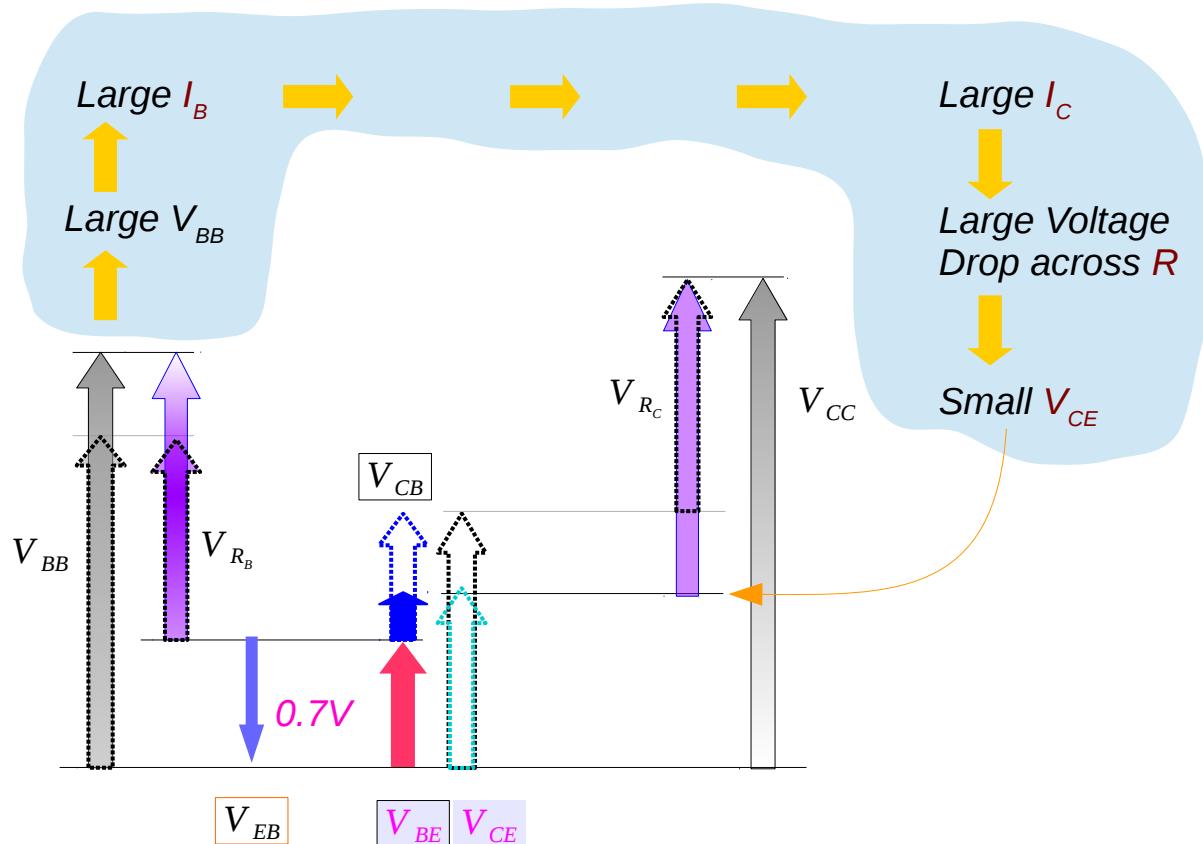


CB Amplifier : increasing I_B \rightarrow decreasing V_{CE}

Common Base

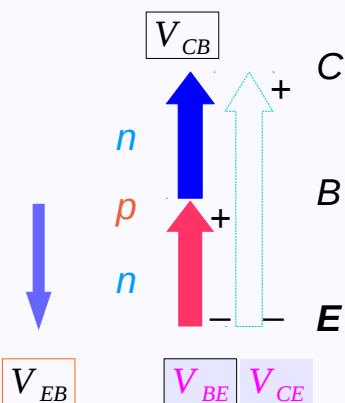
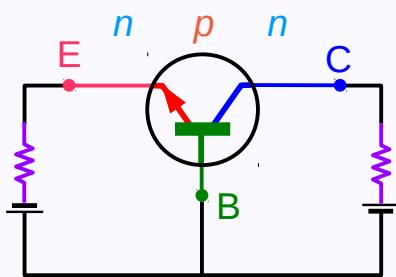


Active region

Input Characteristics



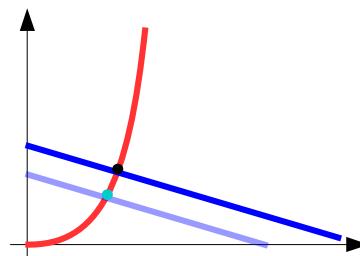


Output Characteristics

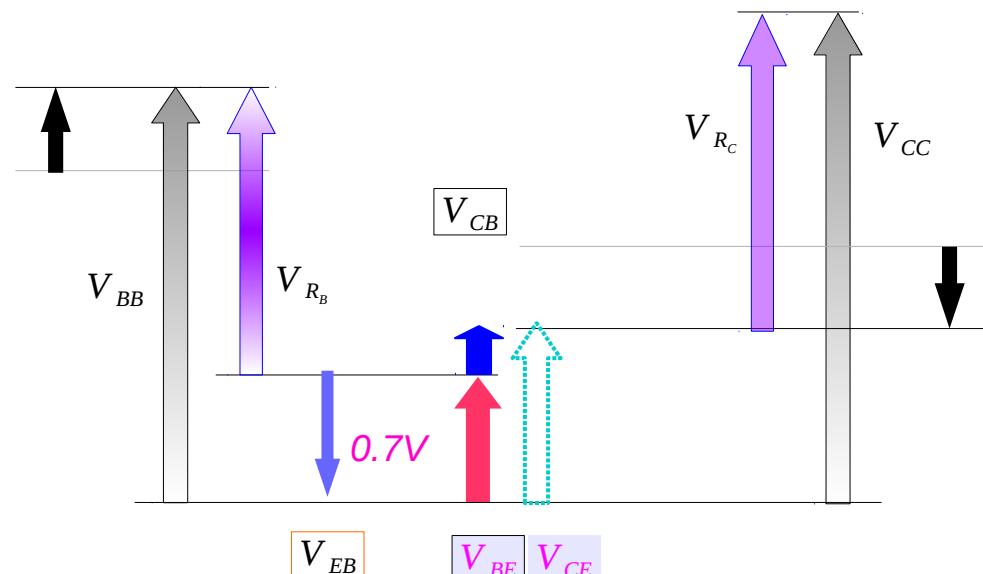
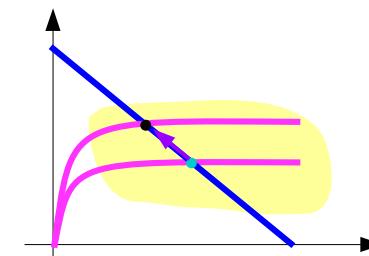


CB Amplifier : Saturation when $V_{RC} \approx V_{CC}$

Common Base

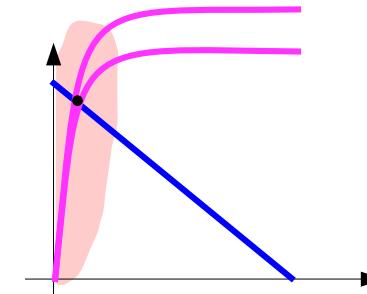
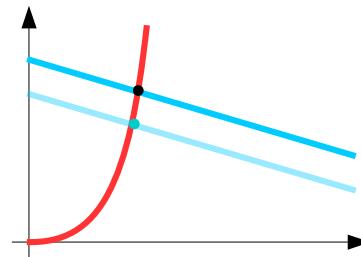
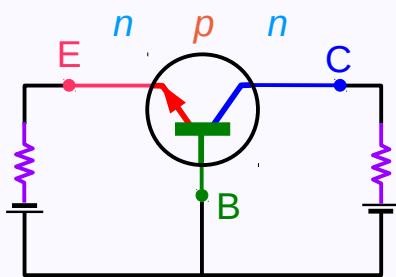


saturation

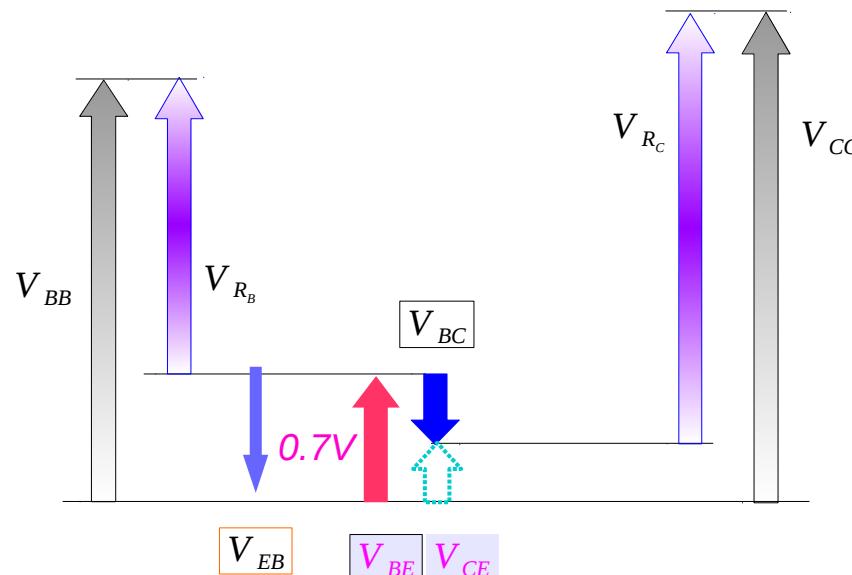
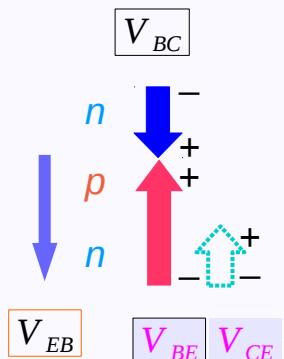


CB Amplifier : increasing I_B \nrightarrow decreasing V_{CE} : Saturation

Common Base

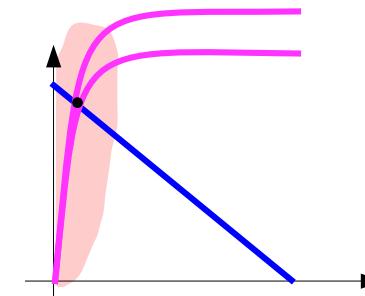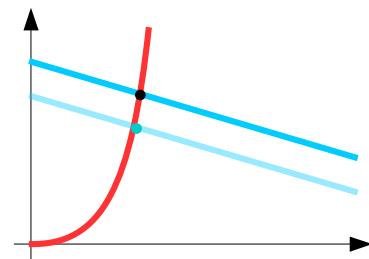
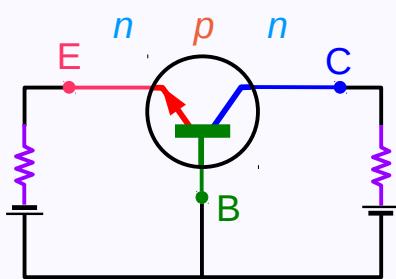


saturation

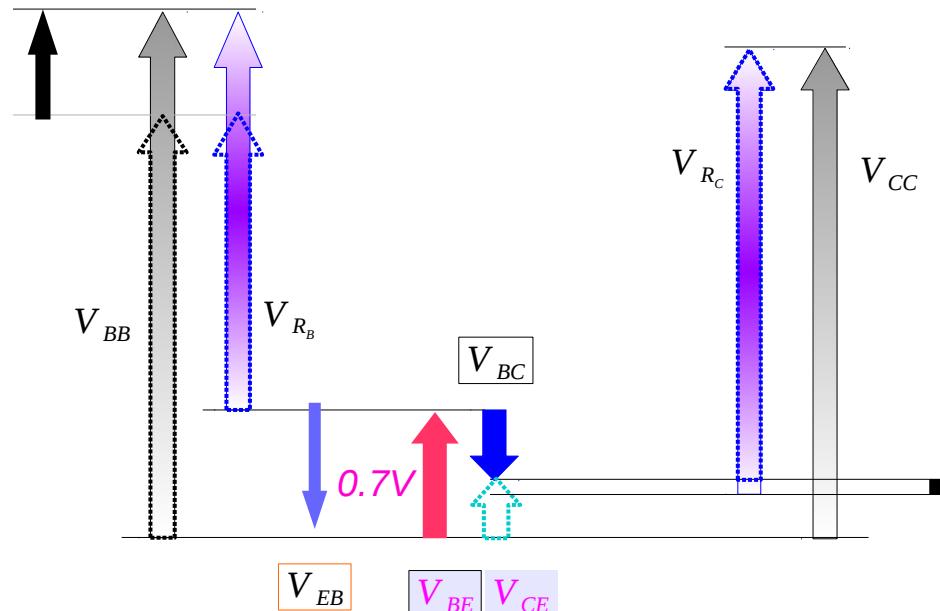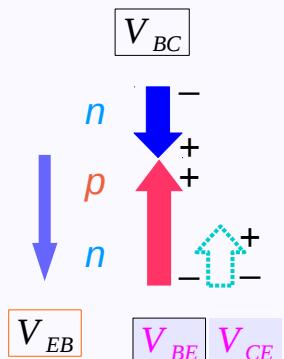


CB Amplifier : Load lines

Common Base


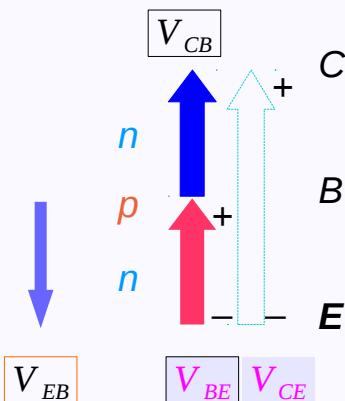
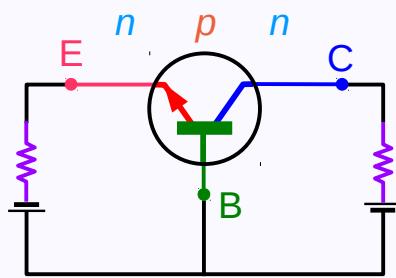


Active region

Input Characteristics

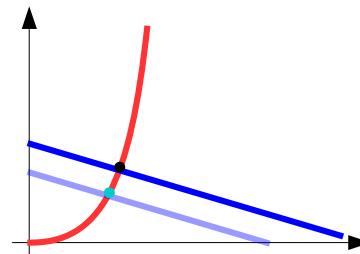

Output Characteristics

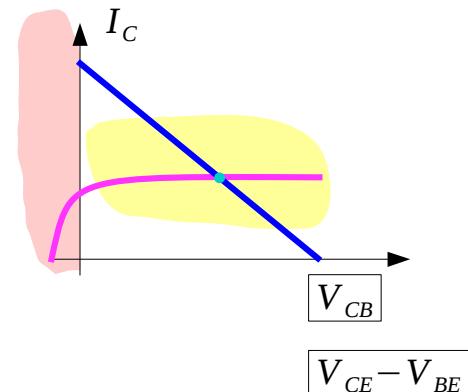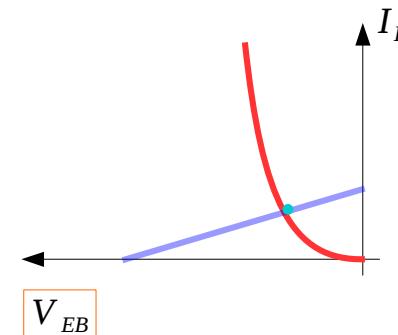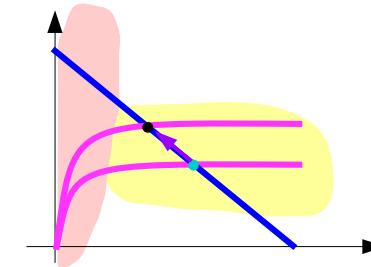

References

- [1] <http://en.wikipedia.org/>
- [2] J.H. McClellan, et al., Signal Processing First, Pearson Prentice Hall, 2003