

BJT Topologies - AC Characteristics

Copyright (c) 2012 – 2017 Young W. Lim.

Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.2 or any later version published by the Free Software Foundation; with no Invariant Sections, no Front-Cover Texts, and no Back-Cover Texts. A copy of the license is included in the section entitled "GNU Free Documentation License".

Please send corrections (or suggestions) to youngwlim@hotmail.com.


This document was produced by using OpenOffice and Octave.

Input Characteristic Curves


Output Characteristic Curves

CE Amplifier : Linear Region


Common Emitter

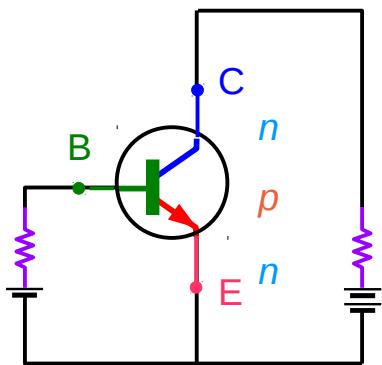



Input Characteristics

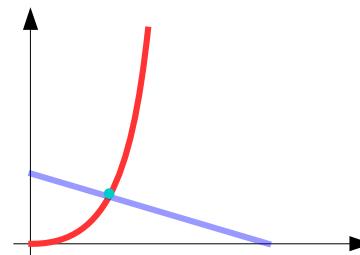

Output Characteristics



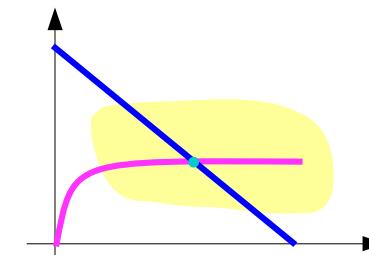


Active region

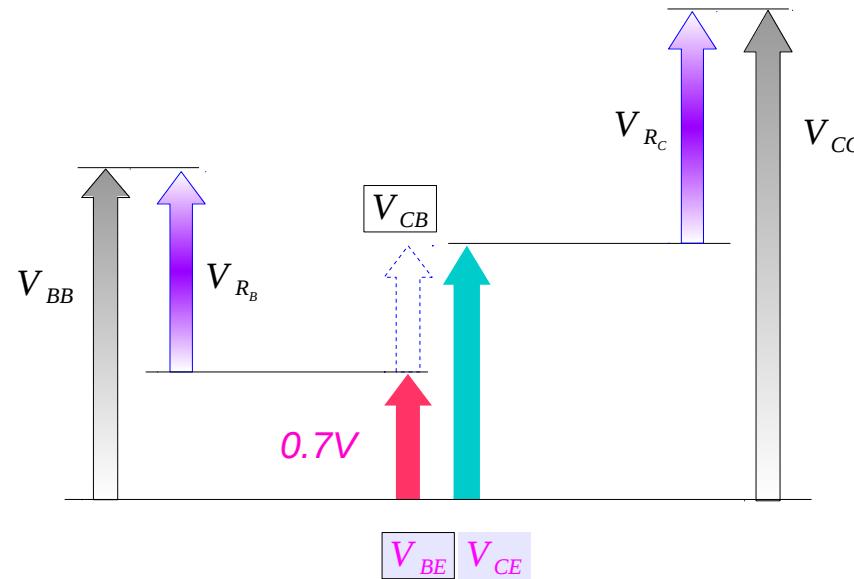
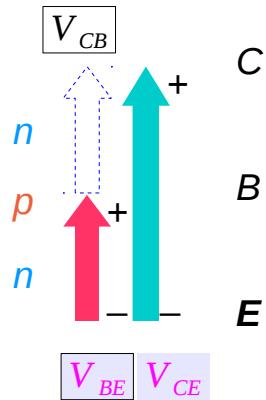


CE Amplifier : Saturation Region

Common Emitter

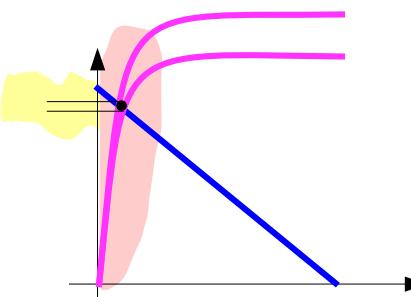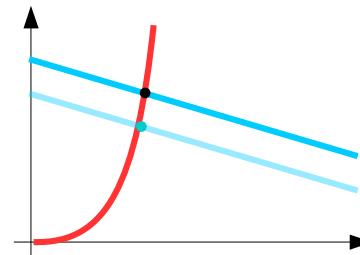
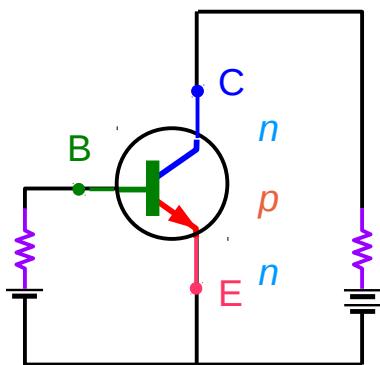


saturation

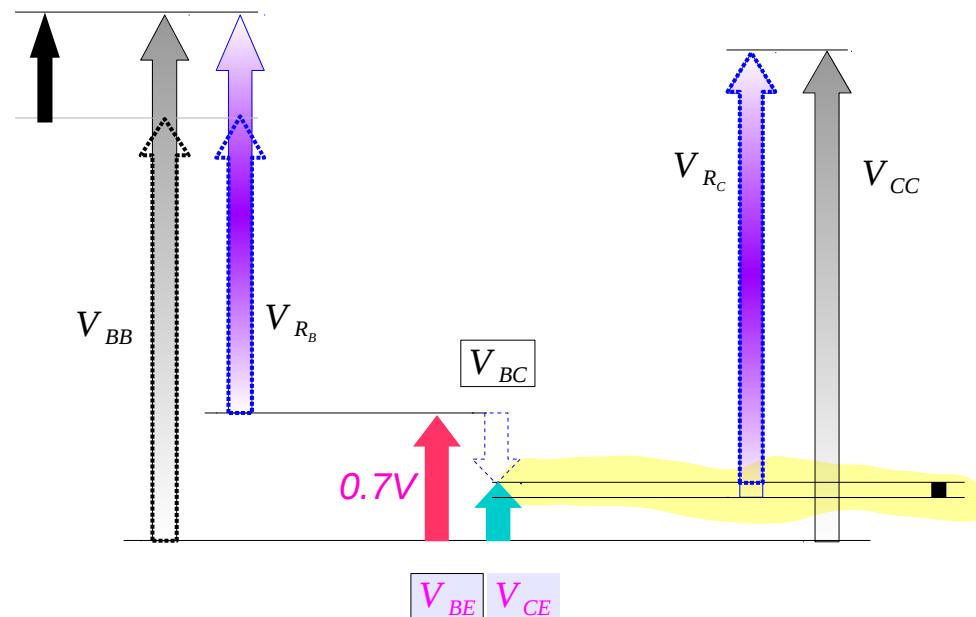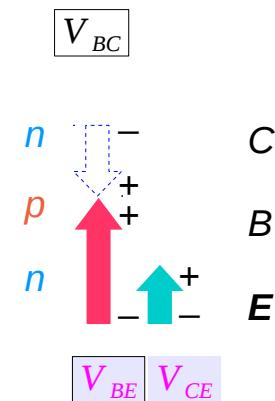


CC Amplifier : Characteristic Curves


Common Collector 3

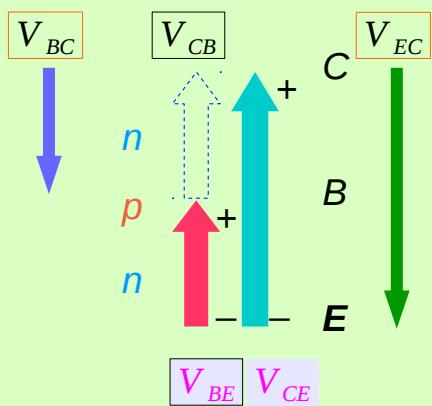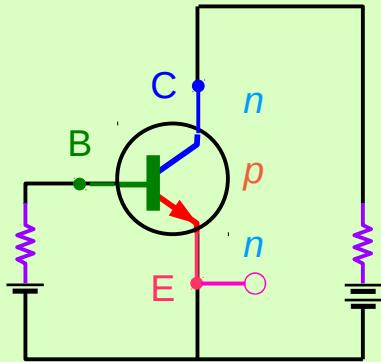


Active region

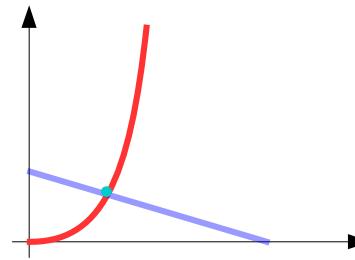

Input Characteristics

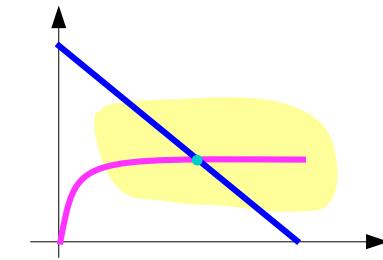


Output Characteristics

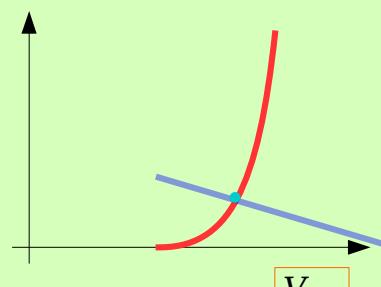

V_{BC}

$V_{BE} - V_{CE}$



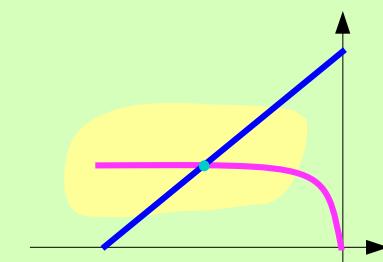


V_{EC}


$-V_{CE}$

CB Amplifier : Characteristic Curves


Common Base

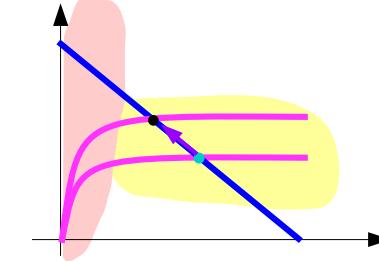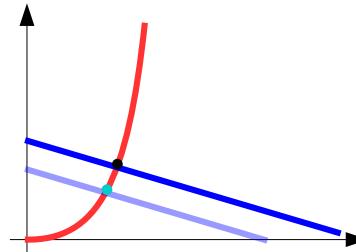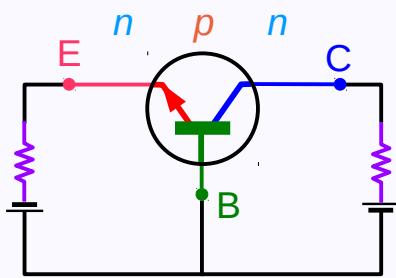


Input Characteristics

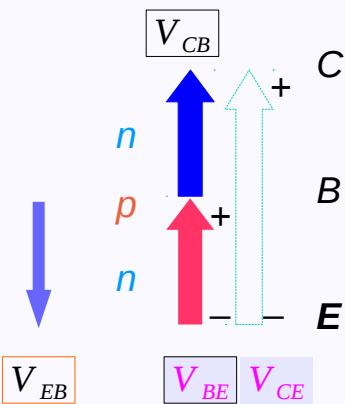

Active region

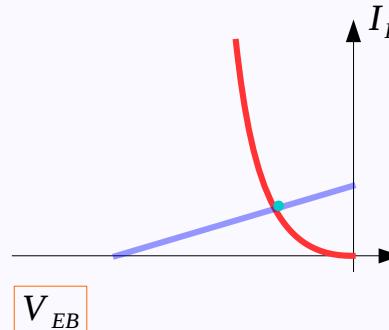


Output Characteristics

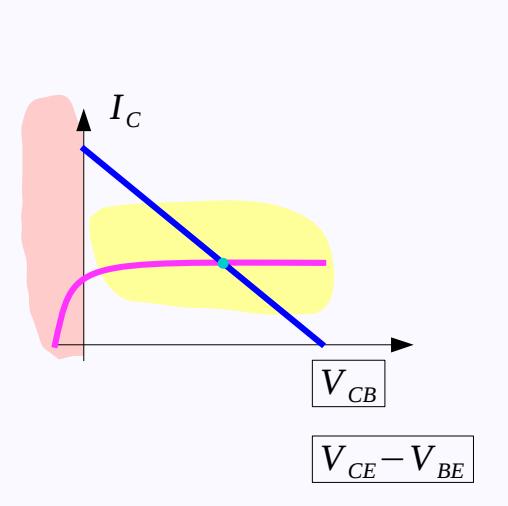


V_{in} & V_{out} Phase Relationship

Notations

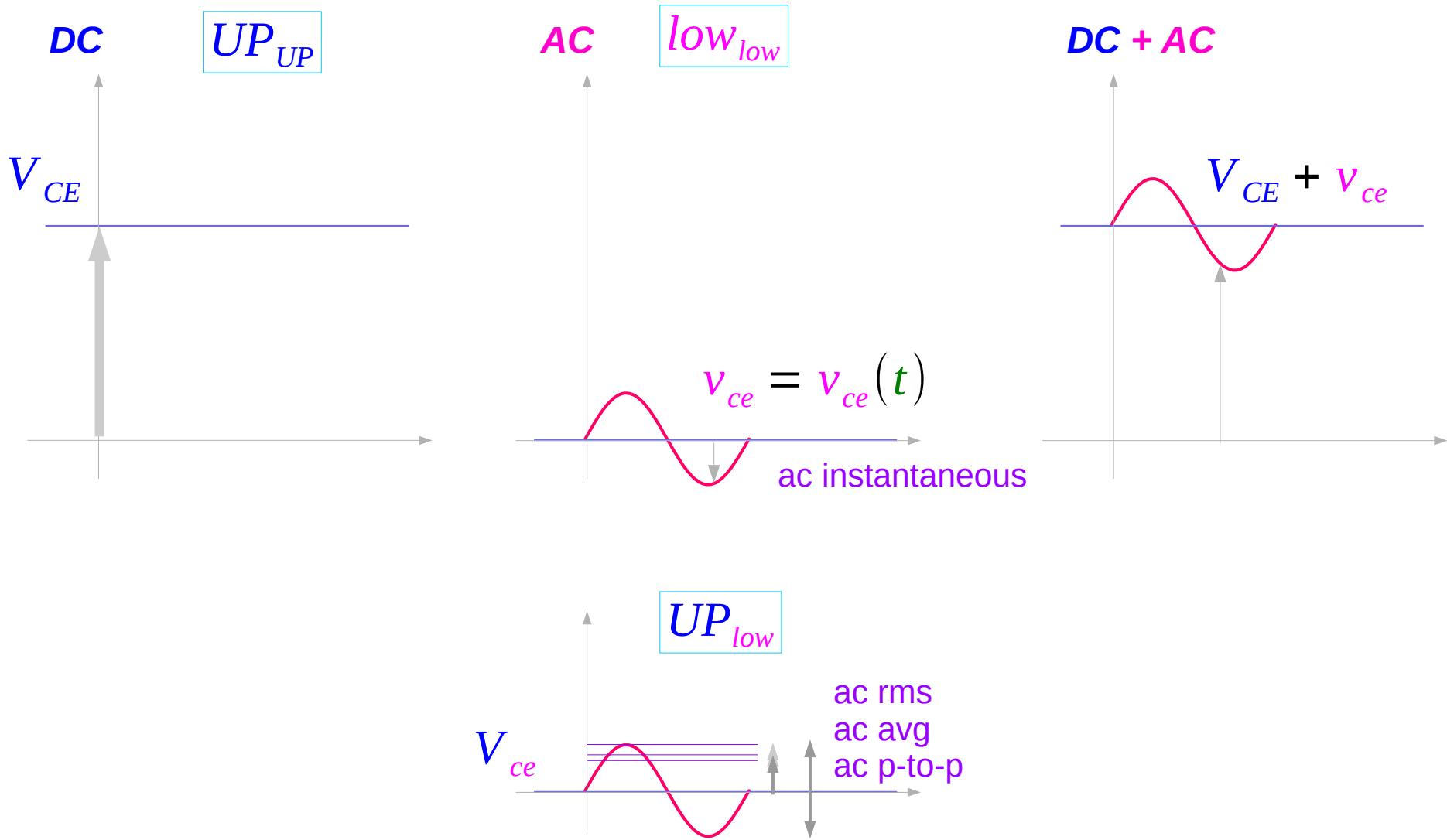

CE Amplifier : Phase Relationship






Common Emitter

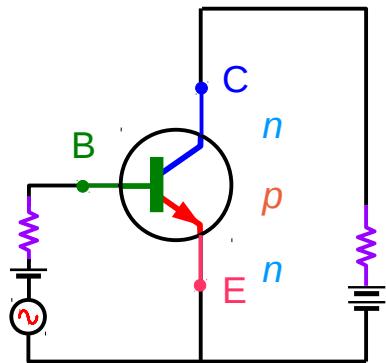

Input Characteristics



$$inc I_B + I_b \rightarrow inc I_C + I_c, I_E + I_e$$
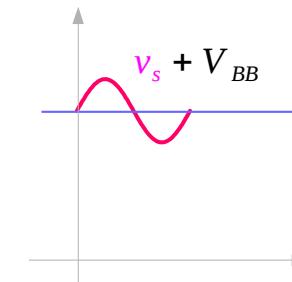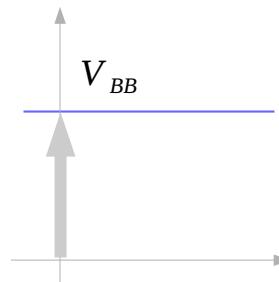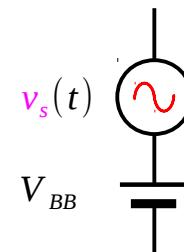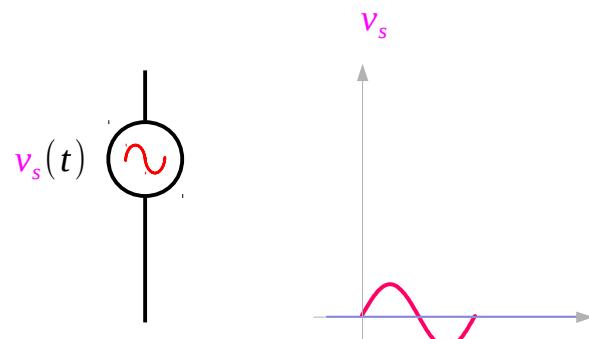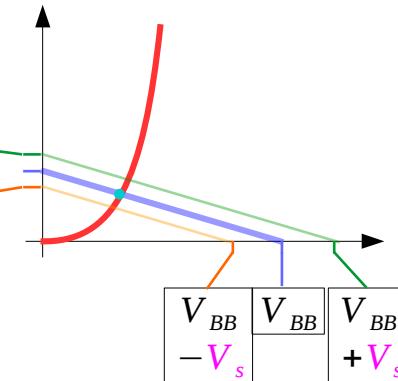
$$dec I_B - I_b \rightarrow dec I_C - I_c, I_E - I_e$$




CE Amplifier : Phase Relationship

Common Emitter

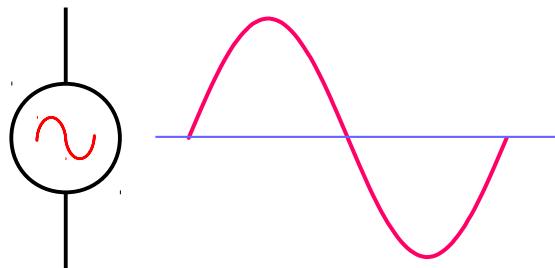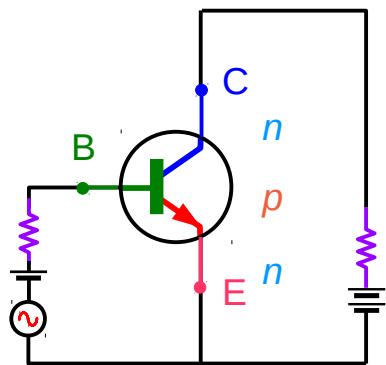


Input Characteristics

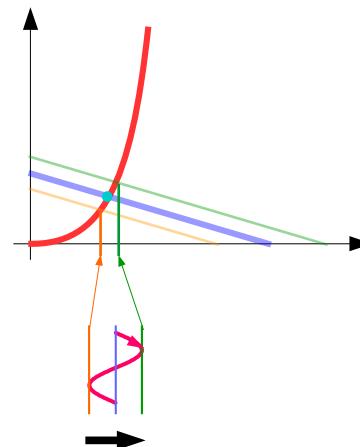

increasing v_i direction

Output Characteristics


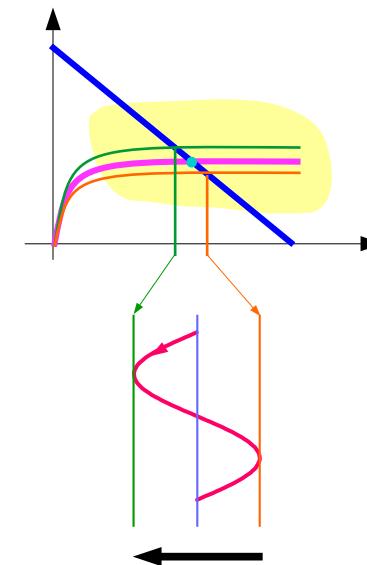


decreasing v_o direction

Active region


CC Amplifier : Phase Relationship

Common Collector 3

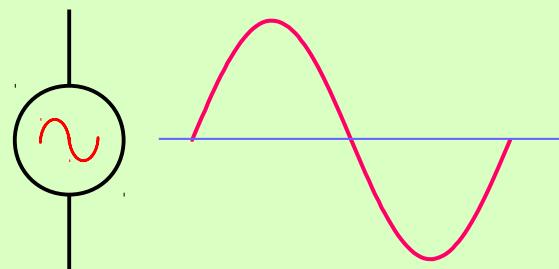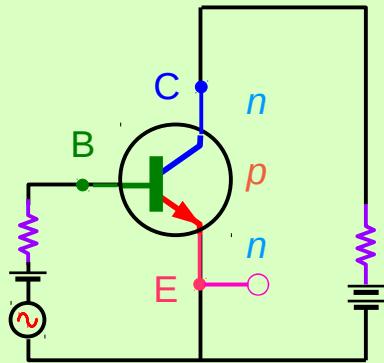


Active region

Input Characteristics


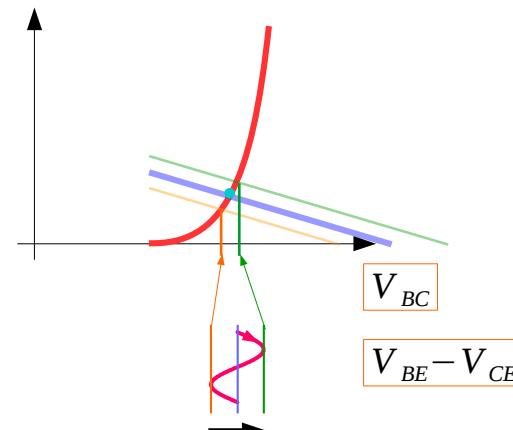


Output Characteristics

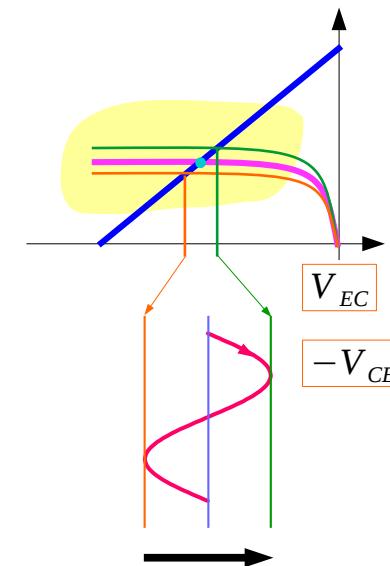


CB Amplifier : Phase Relationship

Common Base

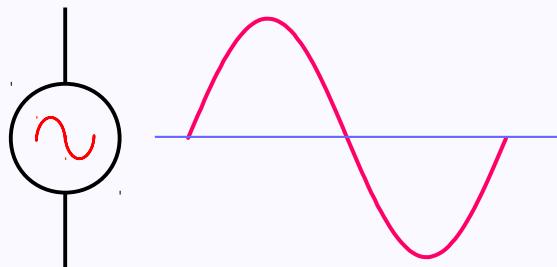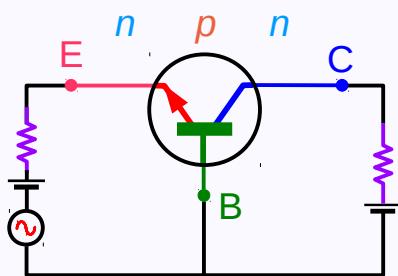


Active region

Input Characteristics

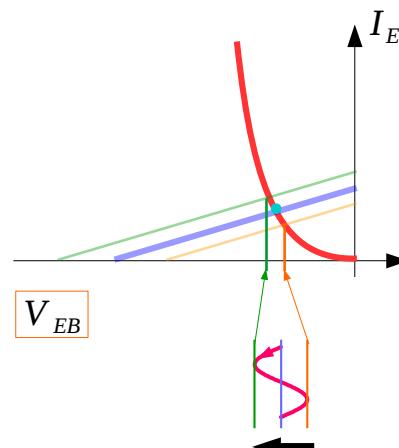

increasing v_i direction







Output Characteristics

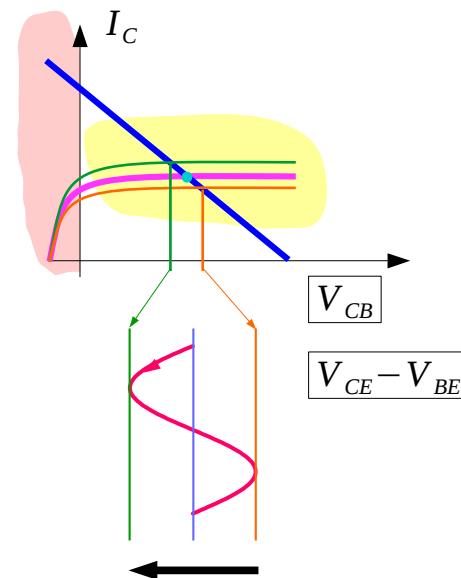


increasing v_o direction

DC bias only circuits
DC + small AC
AC only circuits


BJT Amplifier Configurations

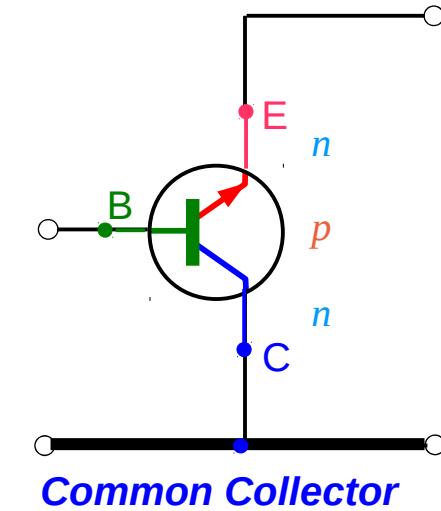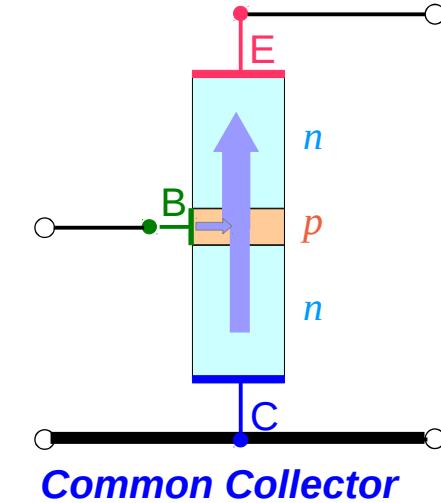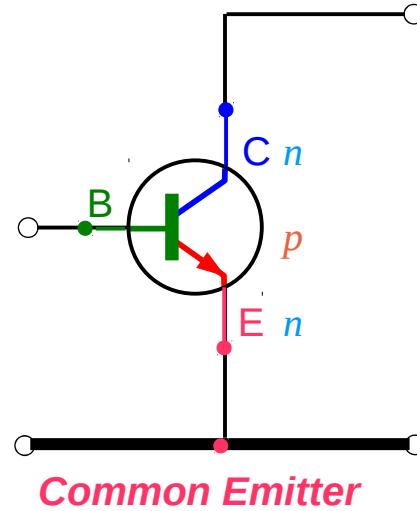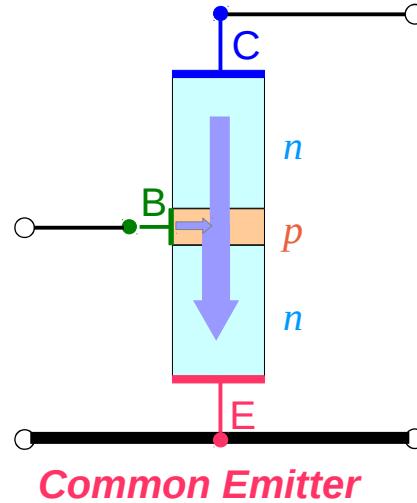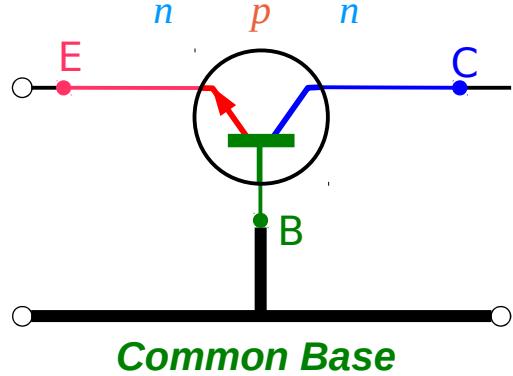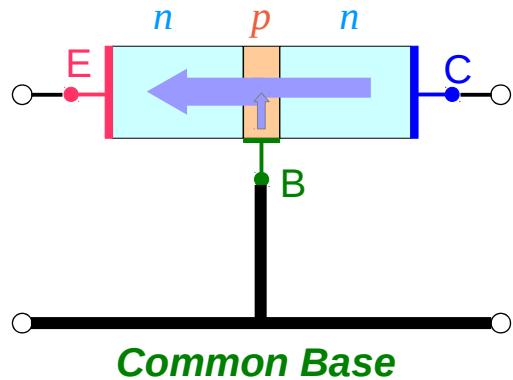


Basic BJT Configuration Circuits

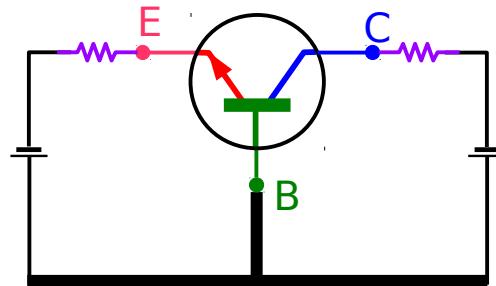




Common Base

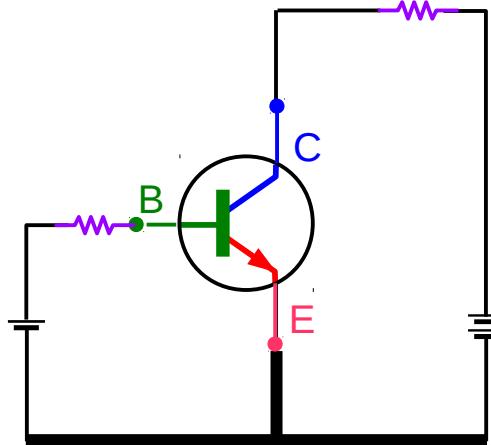


Common Emitter

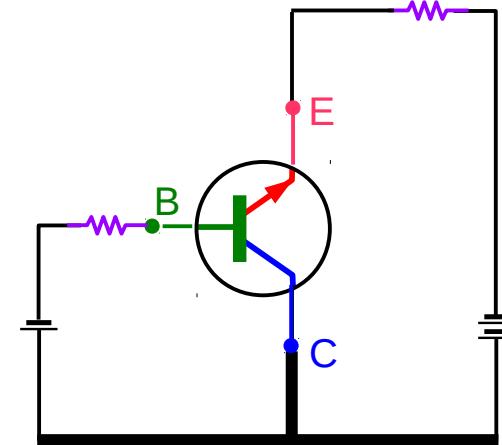


Common Collector

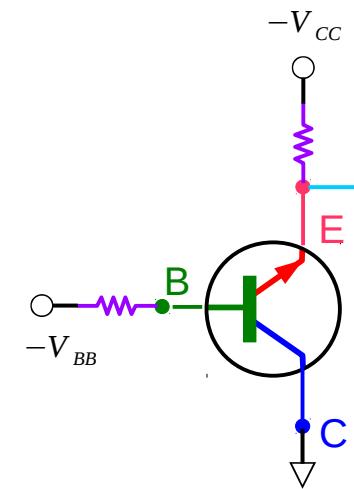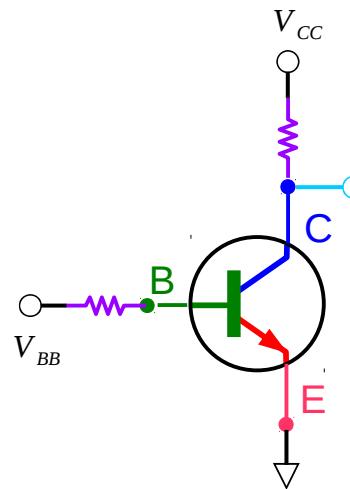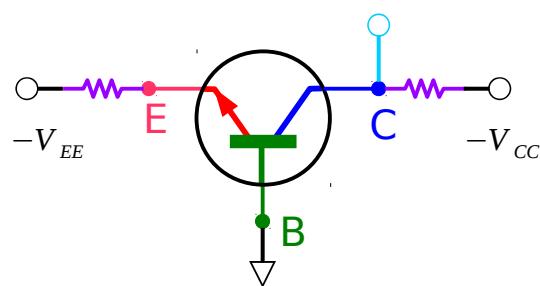


DC Bias

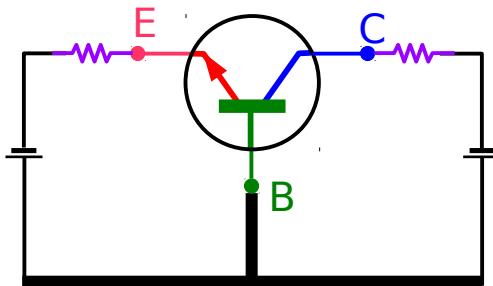

Common Base

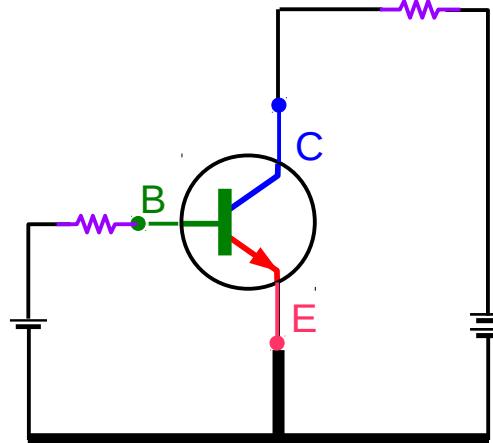


Common Emitter

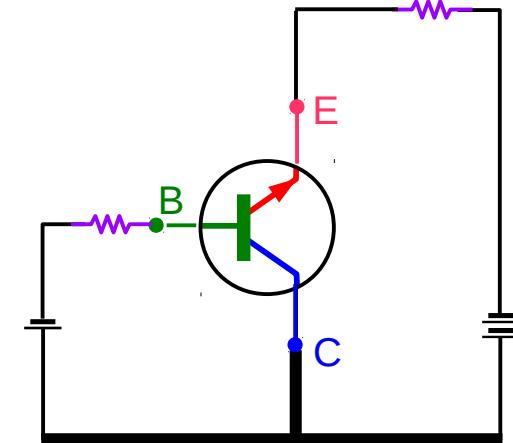


Common Collector


DC Bias + AC Small Signal

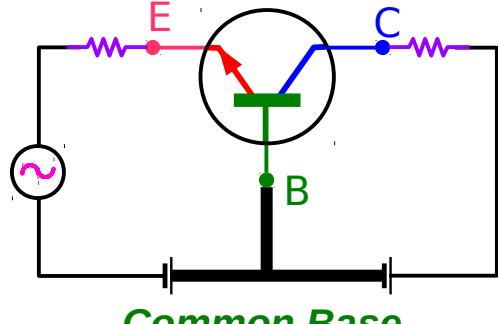

Common Base

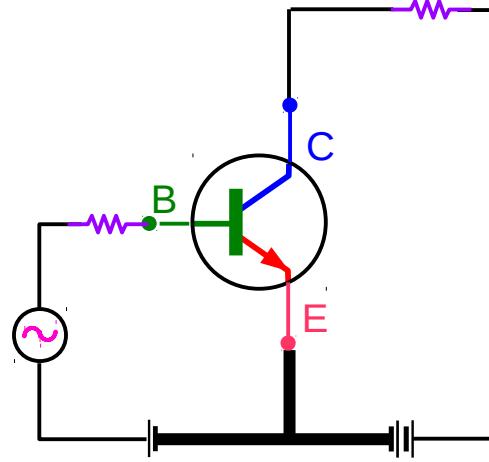


Common Emitter

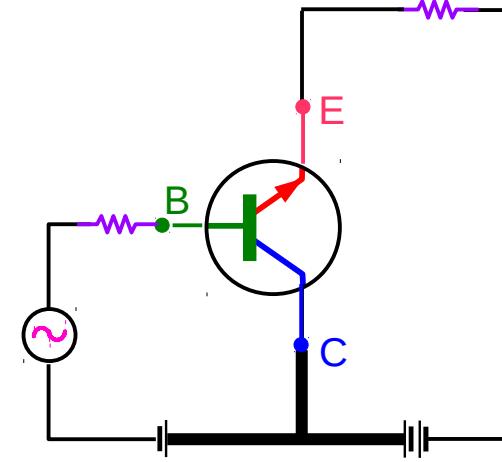


Common Collector


AC Equivalent Circuits

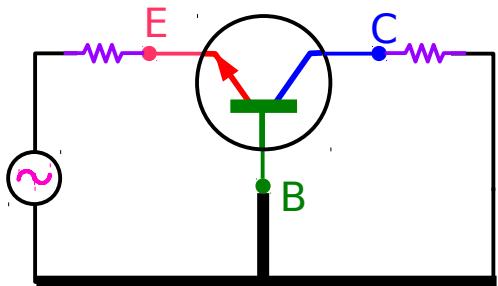




Common Base

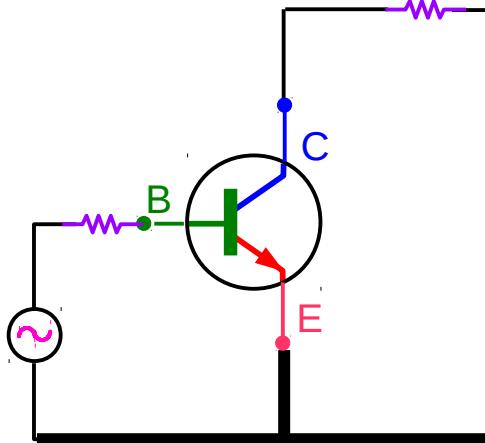

Common Emitter

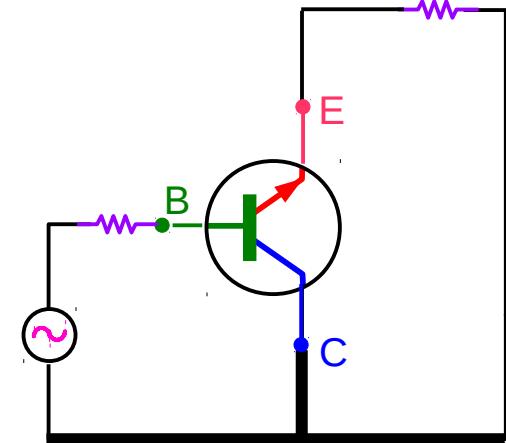


Common Collector

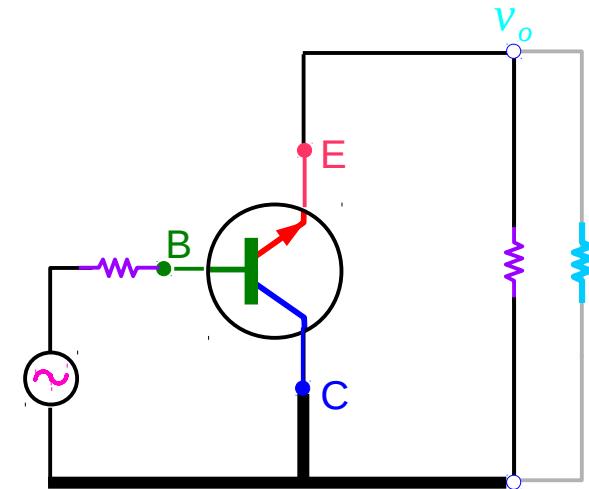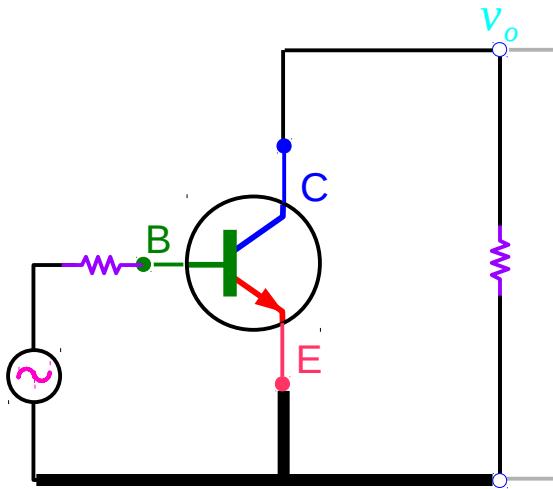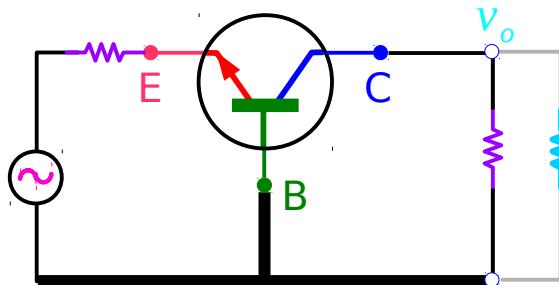


CB Amplifiers – DC Bias, AC Signal, Output Load
CE Amplifiers – DC Bias, AC Signal, Output Load
CC Amplifiers – DC Bias, AC Signal, Output Load


Common Base

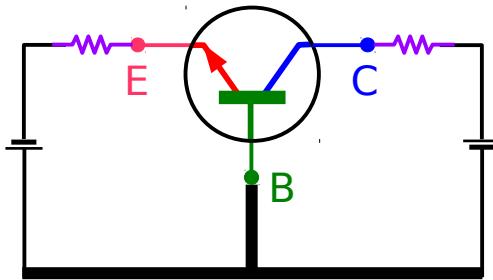


DC Bias

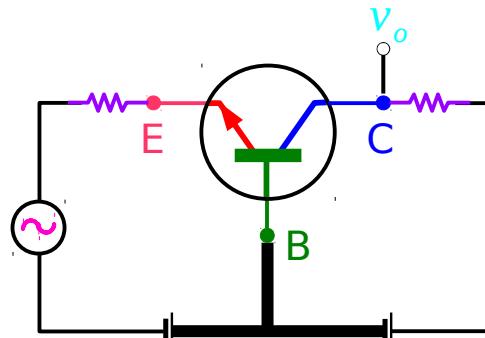


DC Bias + AC Signal

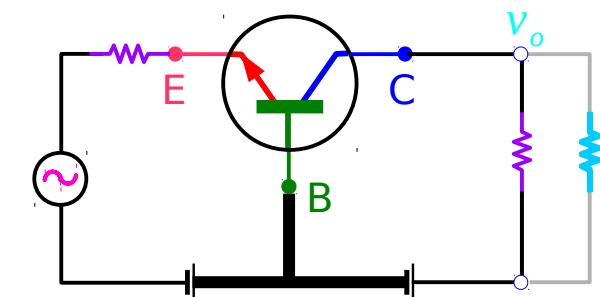

DC Bias + AC Signal + Load

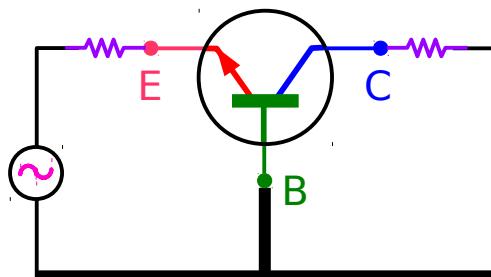


AC Signal

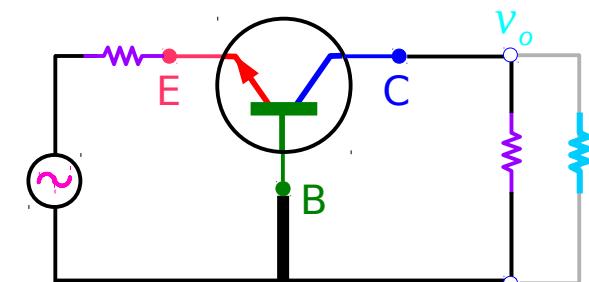


AC Signal + Load


Common Emitter

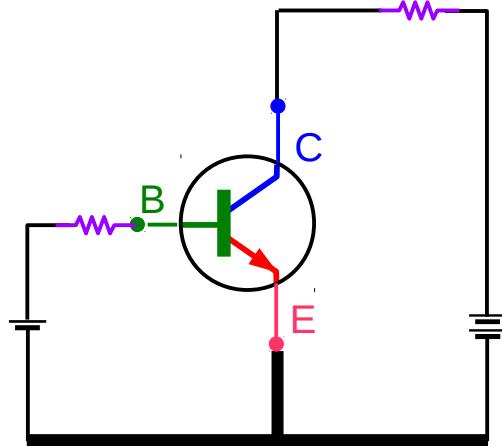


DC Bias

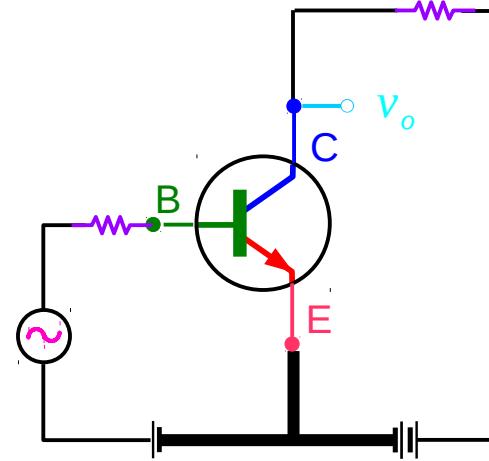


DC Bias + AC Signal

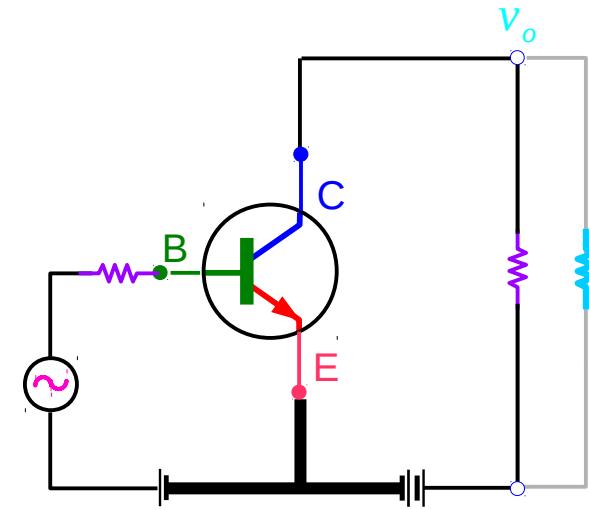

DC Bias + AC Signal + Load

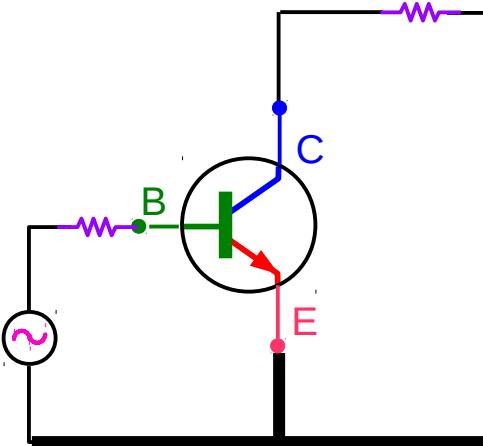


AC Signal

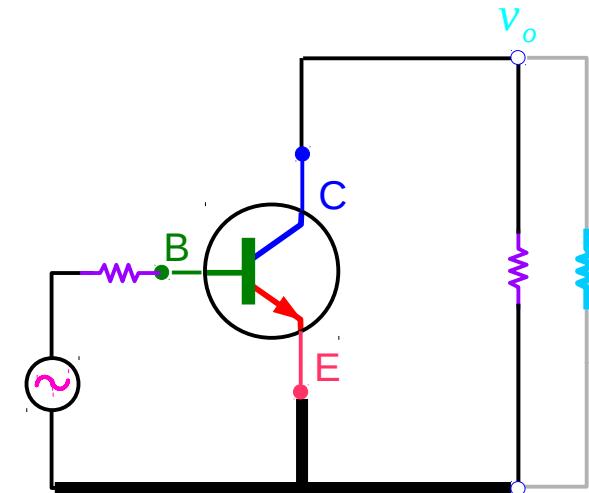


AC Signal + Load


Common Collector

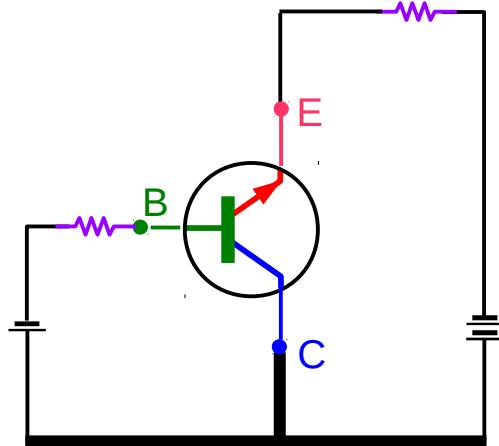


DC Bias

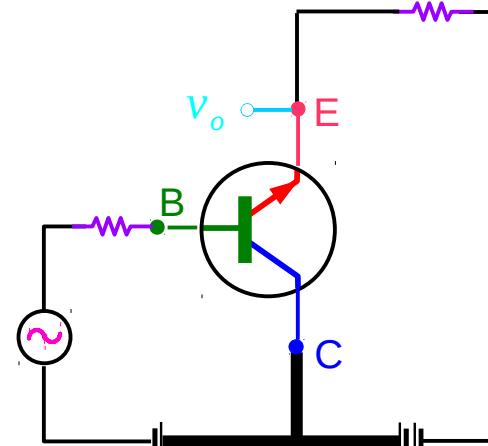


DC Bias + AC Signal

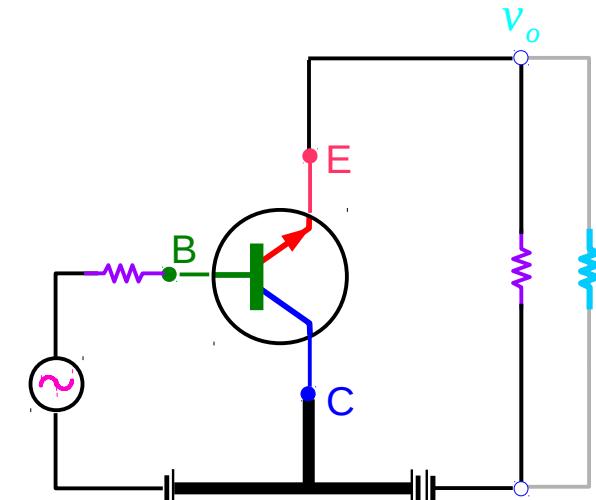

DC Bias + AC Signal + Load

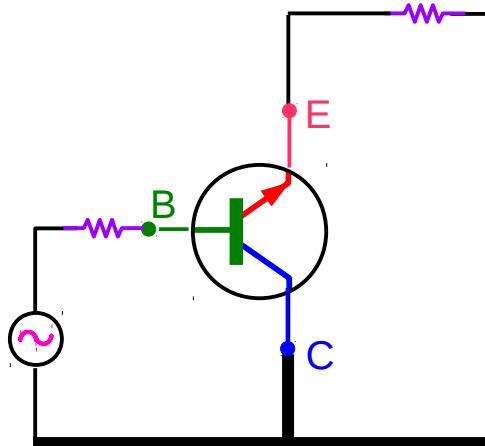

AC Signal

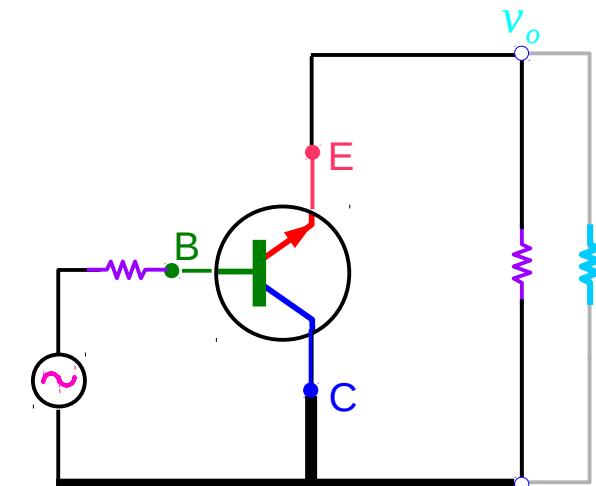

AC Signal + Load

AC Equivalent Model

T-model

Pi-model


Input Impedance

Output Impedance


Voltage Gain

Current Gain


AC t & pi models

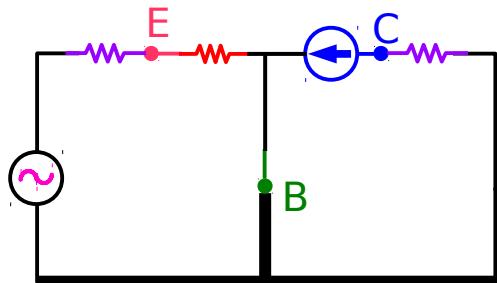


Common Base

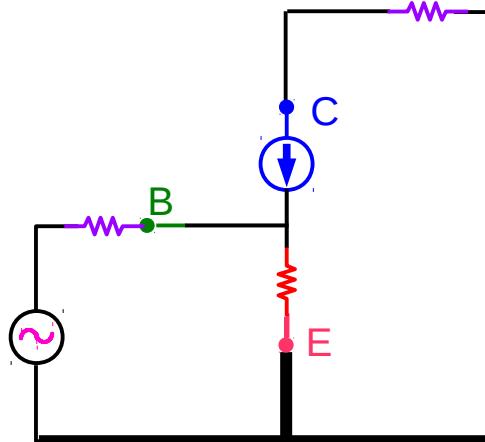


Common Emitter

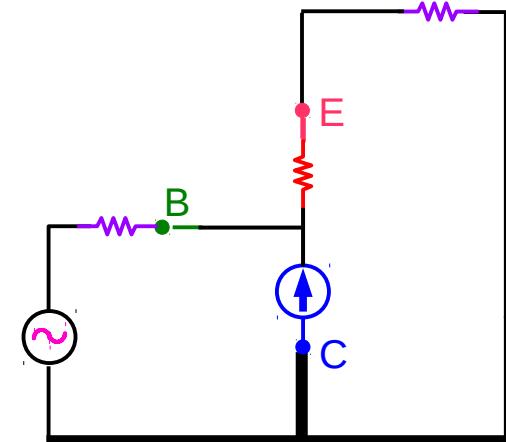


Common Collector

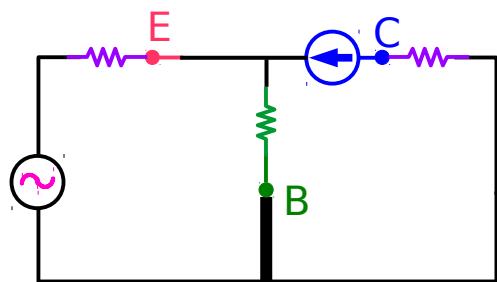

Common Base



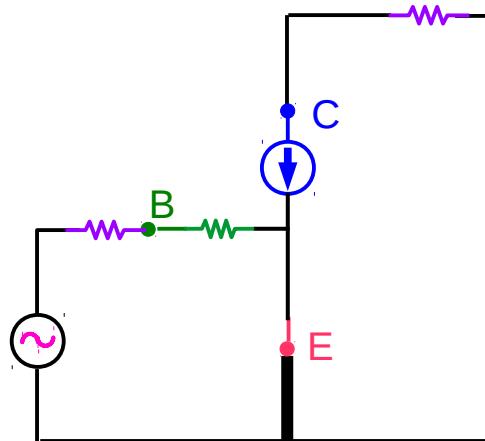


Common Emitter

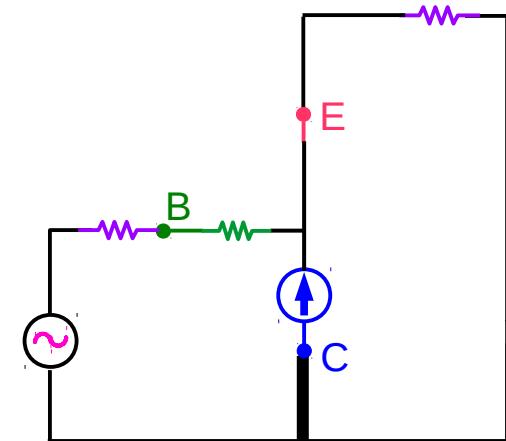


Common Collector

Input Impedance Z_{in}

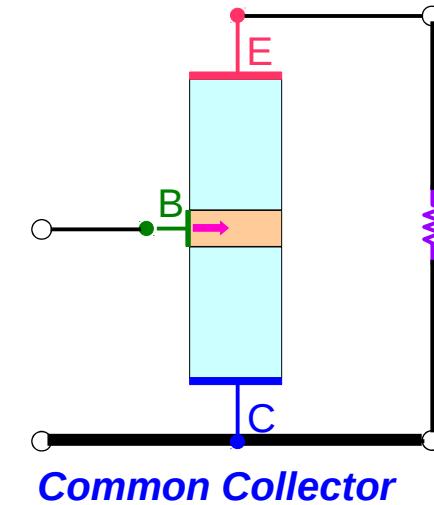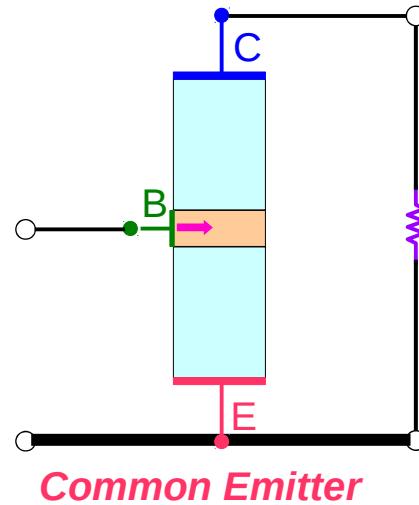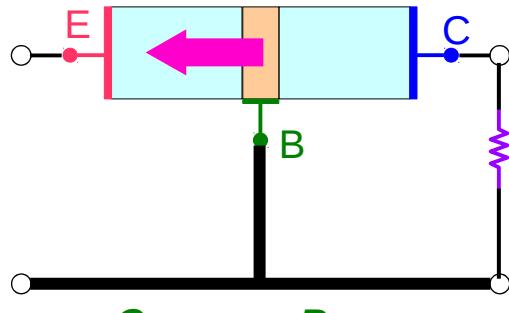

Z_{in} : low r_e'

I_e : Large

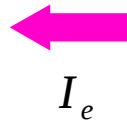

Z_{in} : high $\beta r_e'$

I_b : Small




Z_{in} : high $\beta(r_e' + R_E)$


I_b : Small




Output Impedance Z_{in}

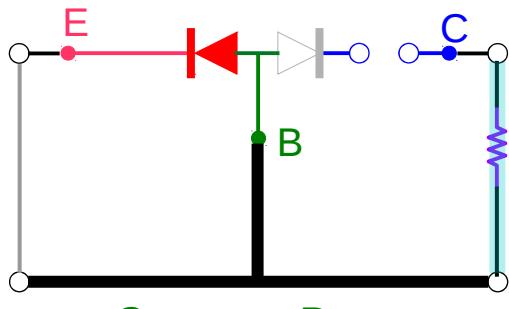

Common Base

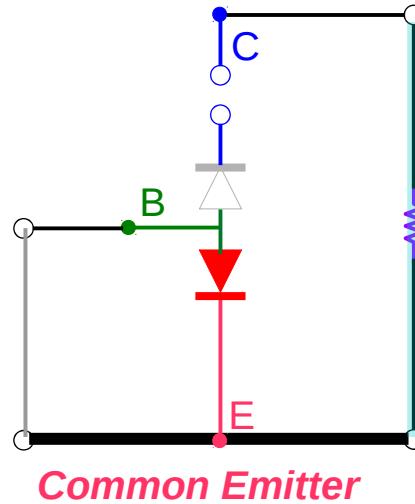

Common Emitter

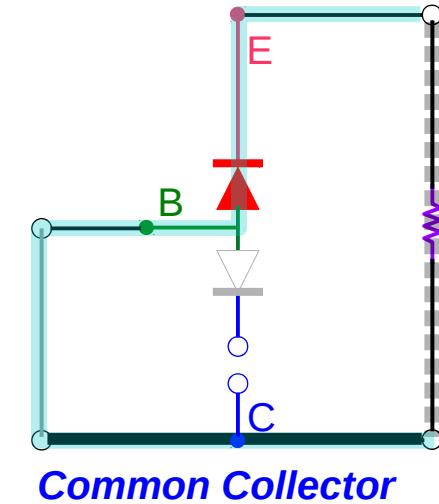

Common Collector

$Z_{out} : \text{high } R_C$

Thevenin R


$Z_{out} : \text{high } R_C$

Thevenin R


$Z_{out} : \text{low } r_e'$

Thevenin R


Voltage Gain A_v

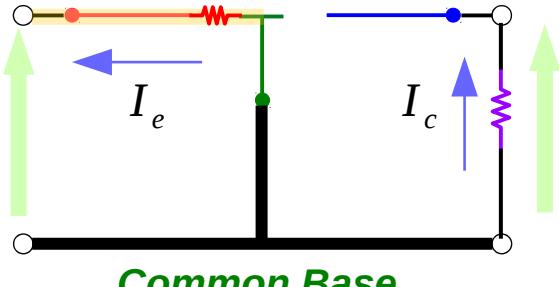

Common Base

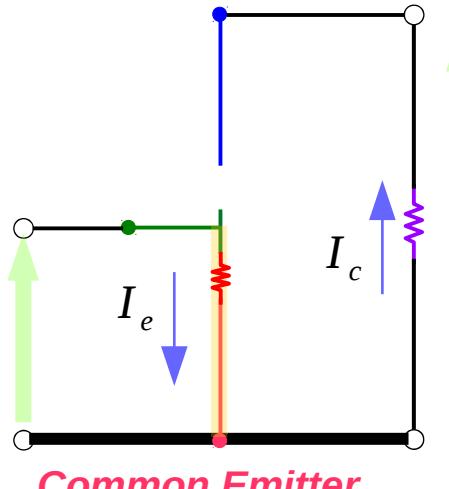

Common Emitter



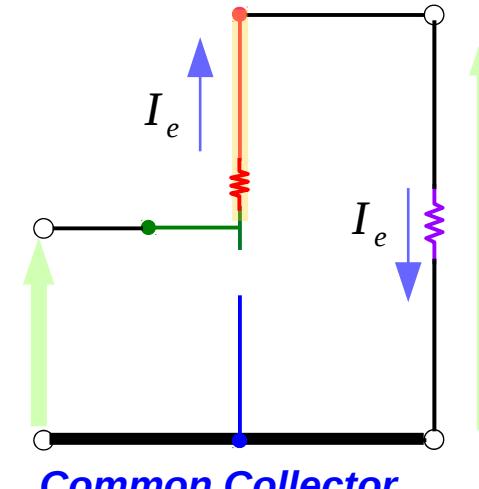


Common Collector


$A_v : \text{high}$ R_C/r_e'

$A_v : \text{high}$ R_C/r_e'

$A_v : \text{unity}$ 1

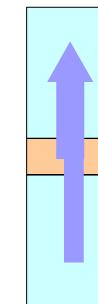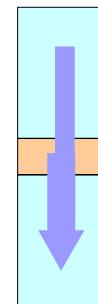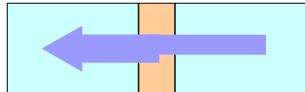


Current Gain A_i

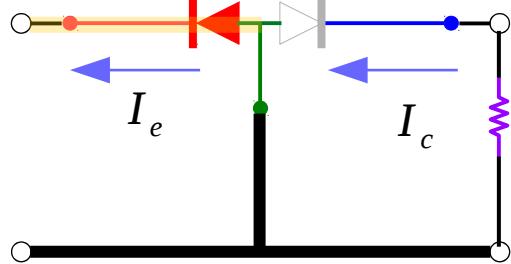


Common Base

A_i : unity 1

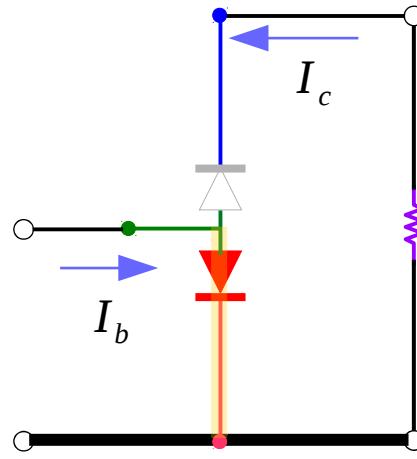

Common Emitter

A_i : high β

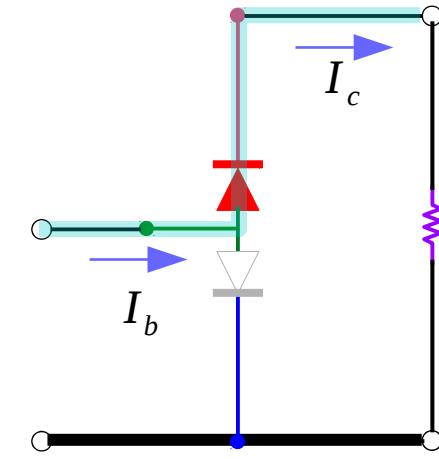


Common Collector

A_i : high β


BJT Configuration Properties

BJT Configuration Properties (1)


Low Z_{in}

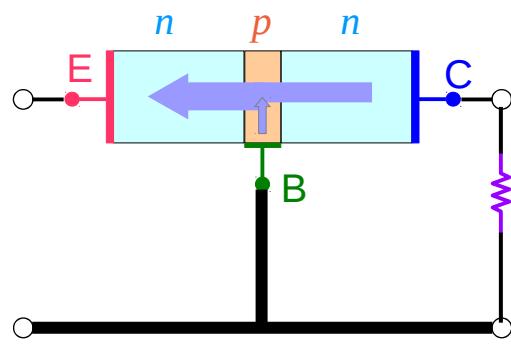

Common Base

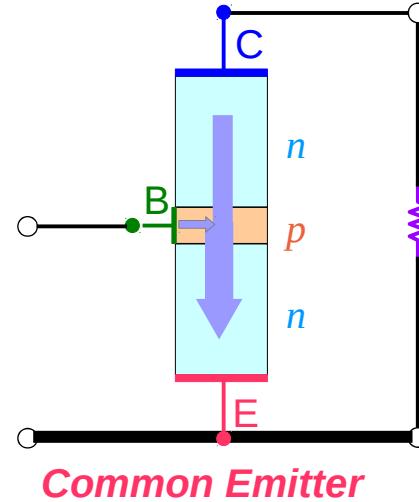

Common Emitter

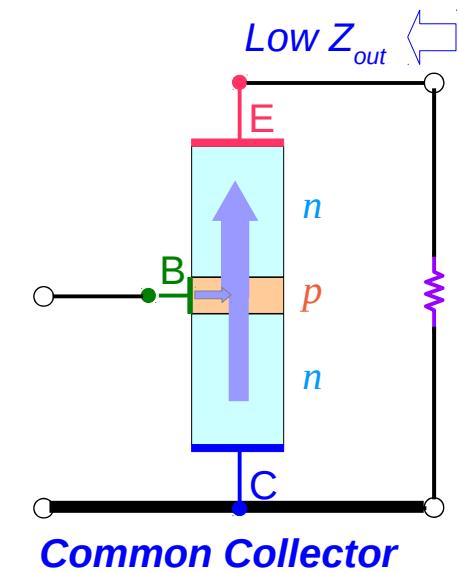

Common Collector

input Z : low
output Z : high
voltage gain : high
current gain : unity

RF Applications

EB
 CB

input Z : high
output Z : high
voltage gain : high
current gain : high

Widely used




BE
 CE

input Z : high
output Z : low
voltage gain : unity
current gain : high

Emitter Follower
Buffer to
Low Impedance Load

BC
 EC

BJT Configuration Properties (2)

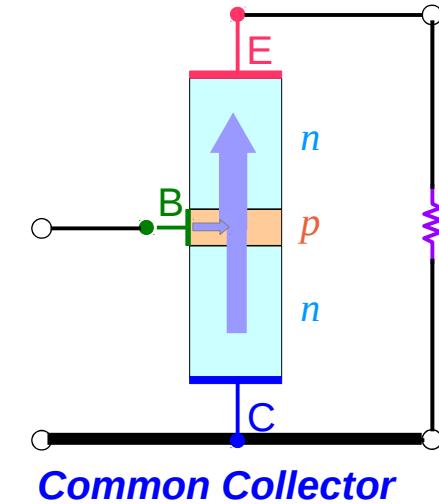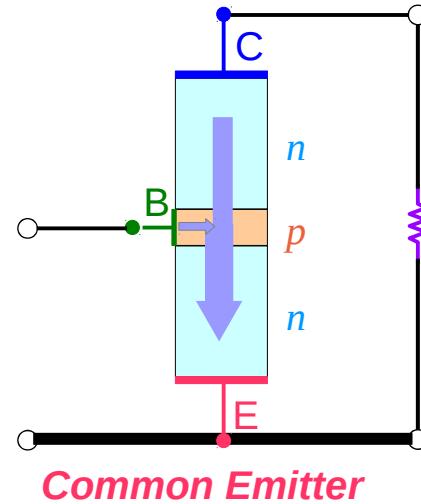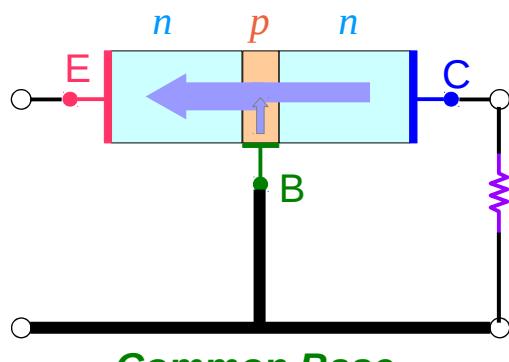

Z_{in} : low r_e'

Z_{out} : high R_C

A_v : high R_C/r_e'

A_i : unity 1

Z_{in} : high $\beta r_e'$

Z_{out} : high R_C

A_v : high R_C/r_e'

A_i : high β

Z_{in} : high $\beta(r_e' + R_E)$


Z_{out} : low r_e'

A_v : unity 1

A_i : high β

BJT Configuration Properties

	<i>Common Base</i>	<i>Common Emitter</i>	<i>Common Collector</i>
Z_{in}	CB : low r_e'	CE : high $\beta r_e'$	CC : high $\beta(r_e' + r_E)$
Z_{out}	CB : high R_C	CE : high R_C	CC : low r_e'
A_v	CB : high R_C/r_e'	CE : high R_C/r_e'	CC : unity 1
A_i	CB : unity 1	CE : high β	CC : high β

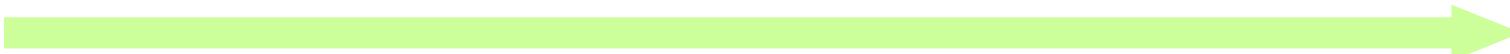

	<i>CB : low</i>	<i>r_e'</i>	<i>CE : high</i>	<i>$\beta r_e'$</i>	<i>CC : high</i>	<i>$\beta(r_e' + R_E)$</i>
Z_{in}	CB : low r_e'	CE : high $\beta r_e'$	CC : high $\beta(r_e' + R_E)$			
Z_{out}	CC : low r_e'	CE : high R_C	CB : high R_C			
A_v	CC : unity 1	CE : high R_C/r_e'	CB : high R_C/r_e'			
A_i	CB : unity 1	CE : high β	CC : high β			

BJT Configuration Properties

	Common Base		Common Emitter		Common Collector
Z_{in}	CB : low	r_e'	CE : high	$\beta r_e'$	CC : high $\beta(r_e' + r_E)$
Z_{out}	CB : high	R_C	CE : high	R_C	CC : low r_e'
A_v	CB : high	R_C/r_e'	CE : high	R_C/r_e'	CC : unity 1
A_i	CB : unity	1	CE : high	β	CC : high β

	Common Base		Common Emitter		Common Collector
Z_{in}	CB : low	r_e	CE : med $r_\pi = (\beta+1)r_e$		CC : high $(\beta+1)[r_e + (r_o R_L)]$
Z_{out}	CB : high	R_C	CE : med $R_C r_o$		CC : low $r_o [r_e + \frac{R_s}{(\beta+1)}]$
A_v	CB : high	$\frac{\alpha R_C}{(R_s + r_e)}$	CE : med $\frac{\beta(R_C r_o)}{(R_s + r_\pi)}$		CC : unity $\frac{(\beta+1)(R_L r_o)}{R_s + (\beta+1)[r_e + (R_L r_o)]}$
A_i	CB : unity	α	CE : med $\frac{\beta r_o}{(R_c + r_o)}$		CC : high $\frac{(\beta+1)r_o}{r_o + R_L}$

r_o, R_s, R_E are used

BJT Configuration Properties

	Common Base	Common Emitter	Common Collector
Z_{in}	CB : low r_e'	CE : high $\beta r_e'$	CC : high $\beta(r_e' + r_E)$
Z_{out}	CB : high R_C	CE : high R_C	CC : low r_e'
A_v	CB : high R_C/r_e'	CE : high R_C/r_e'	CC : unity 1
A_i	CB : unity 1	CE : high β	CC : high β

	Common Base	Common Emitter	Common Collector
Z_{in}	CB : low $r_e \parallel R_E \approx r_e$	CE : med $R_1 \parallel R_2 \parallel \beta r_e$	CC : high $R_1 \parallel R_2 \parallel \beta(r_e + R_E)$
Z_{out}	CB : high R_C	CE : med R_C	CC : low $(r_e + \frac{R_s}{\beta}) \parallel R_E = \frac{R_s}{\beta} \parallel R_E$
A_v	CB : high $\frac{R_C}{r_e}, \frac{R_C \parallel R_L}{r_e}$	CE : med $\frac{R_C}{r_e}, \frac{R_C \parallel R_L}{r_e}$	CC : unity $\frac{R_E}{(r_e + R_E)} \approx 1$
A_i	CB : unity	CE : med	CC : high


VDB

AC Equivalent Circuits

Input Characteristic Curves

Output Characteristic Curves

Storing Magnetic Energy

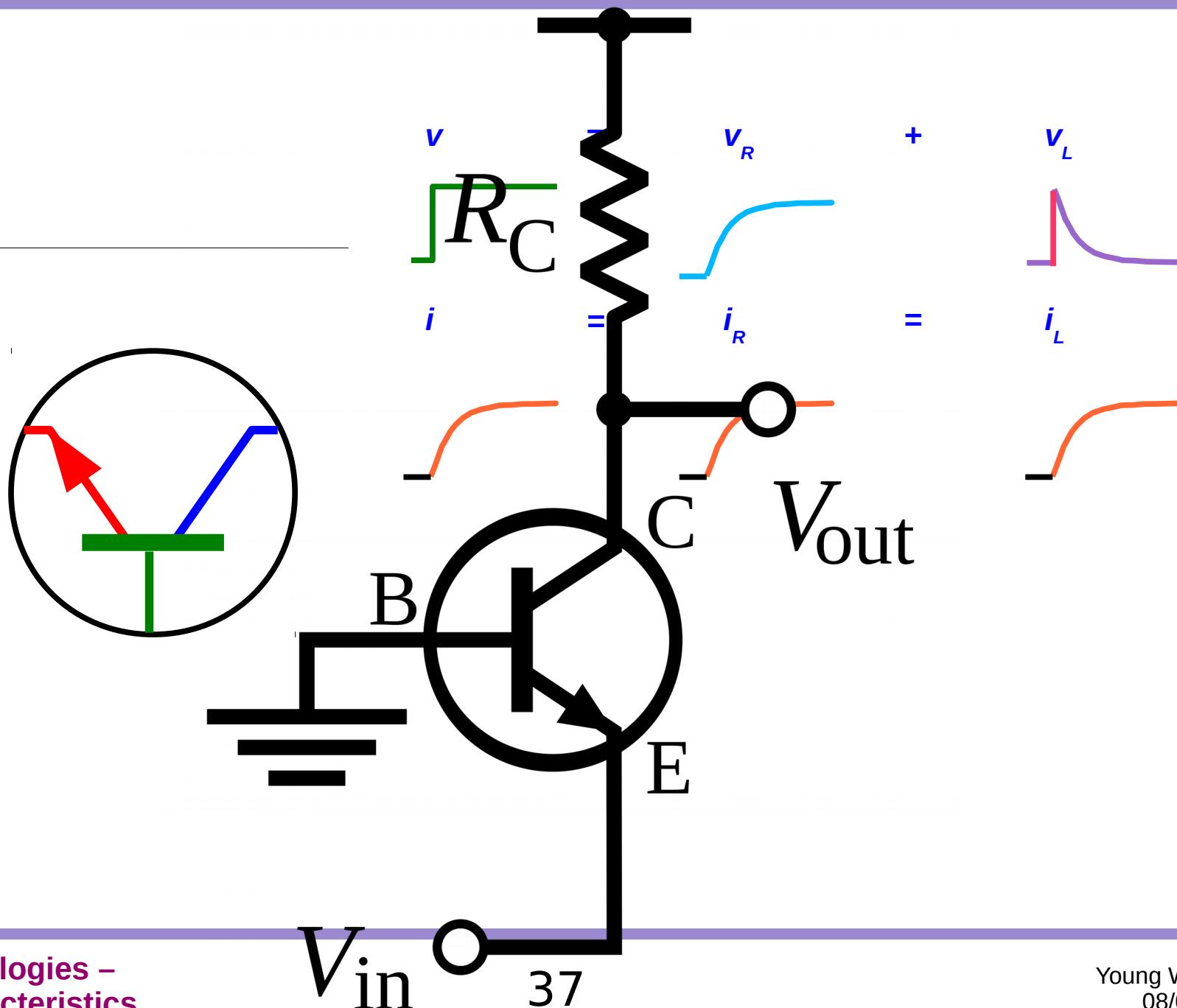

References

- [1] <http://en.wikipedia.org/>
- [2] J.H. McClellan, et al., Signal Processing First, Pearson Prentice Hall, 2003